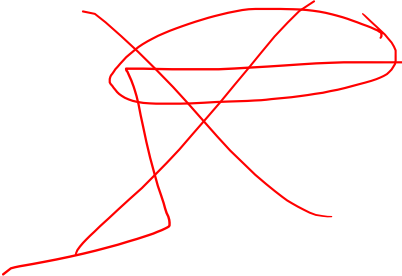
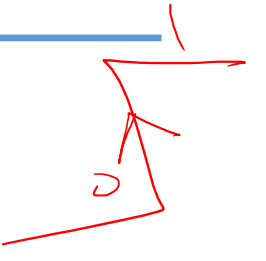
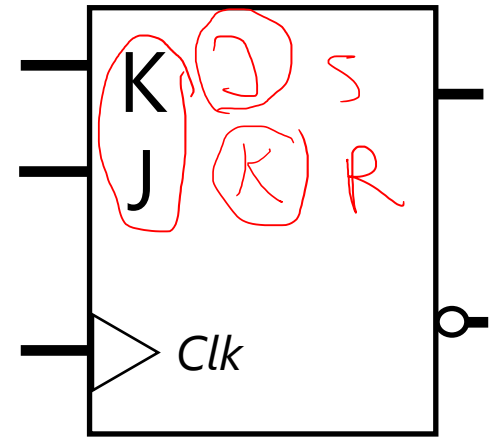
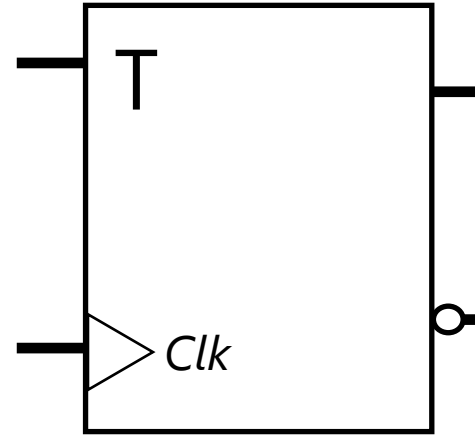
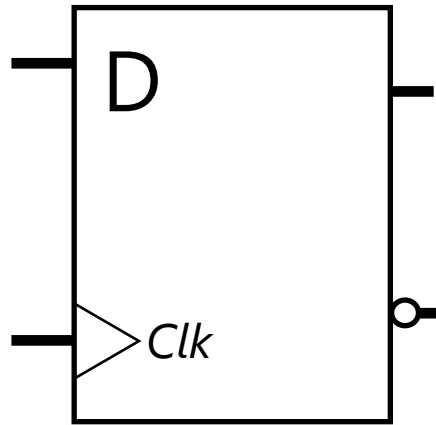
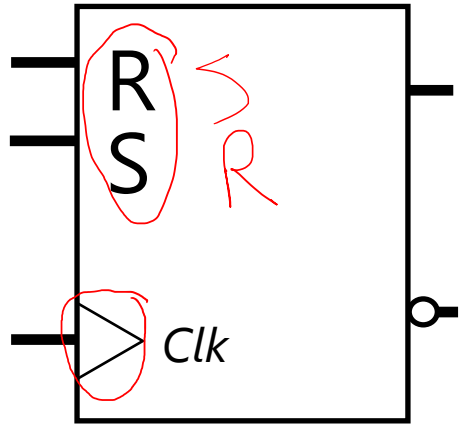

Flip-Flop

A *single edge* triggered latch

level  edge 




S	R	Q
0	0	Q_t
0	1	0
1	0	1
1	1	X

D	Q
0	0
1	1

T	Q
0	Q_t
1	Q_t'

J	K	Q
0	0	Q_t
0	1	0
1	0	1
1	1	Q_t'

Single Edge *Positive*

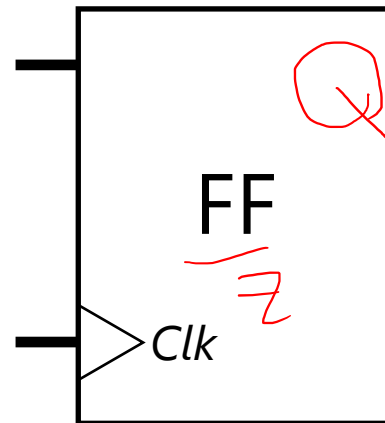


$Q_z(T) =$

$Q'_z(T) =$

A red arrow points from the top output 'Q' to the first equation.


Analysis: Given a sequential circuit, show the behavior
vs.

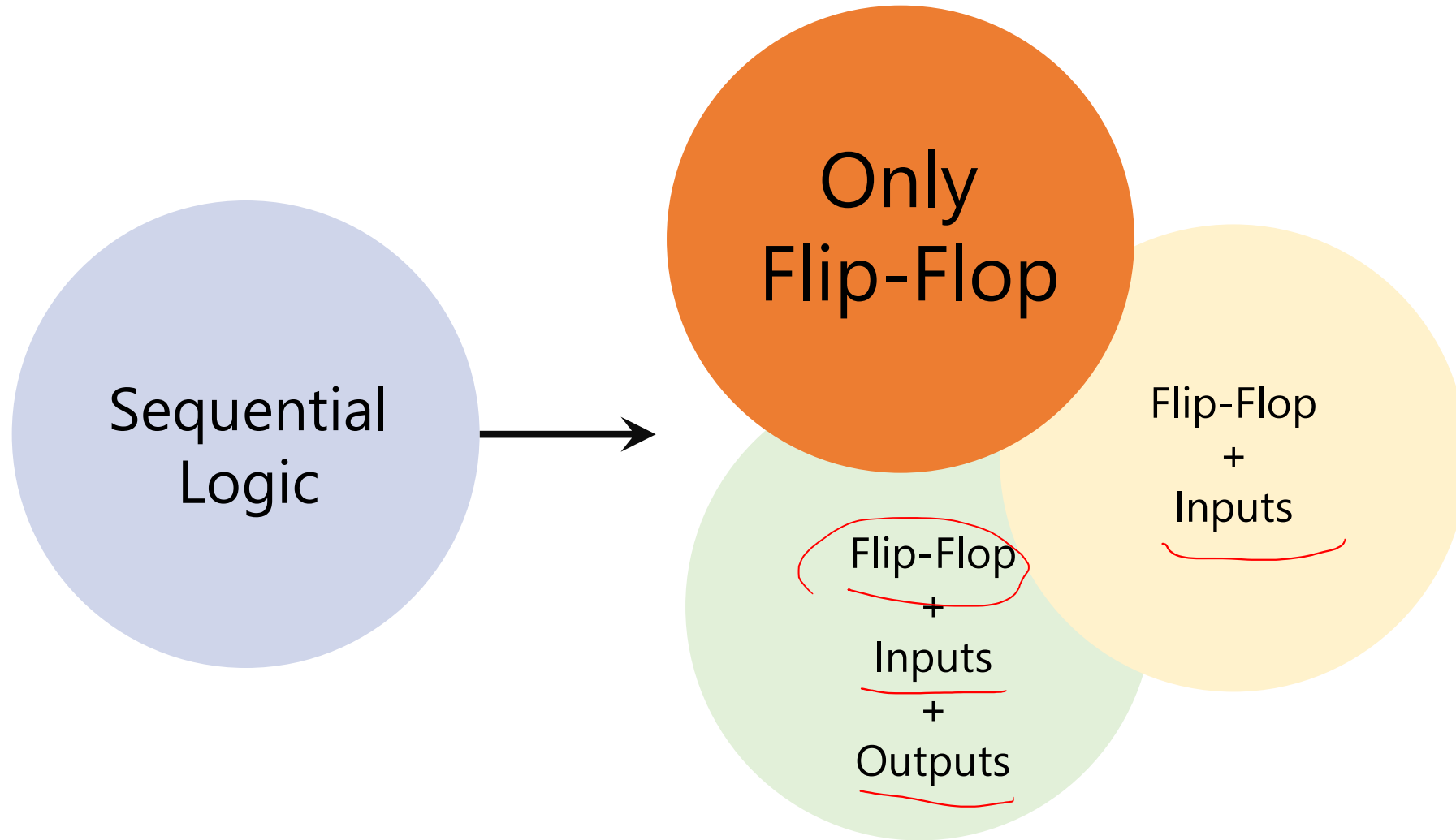Design: Given a behavior, build the sequential circuit




Analysis (Recap)

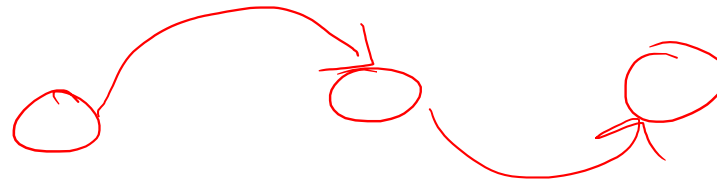0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
2. What are the state combinations? $2^{\#FF}$
3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: $2^{\#FF}$
4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs \Rightarrow action
5. Form State Transition Diagram ←
6. (Optional) Analyze paths and states in state transition diagram



Analysis by an example

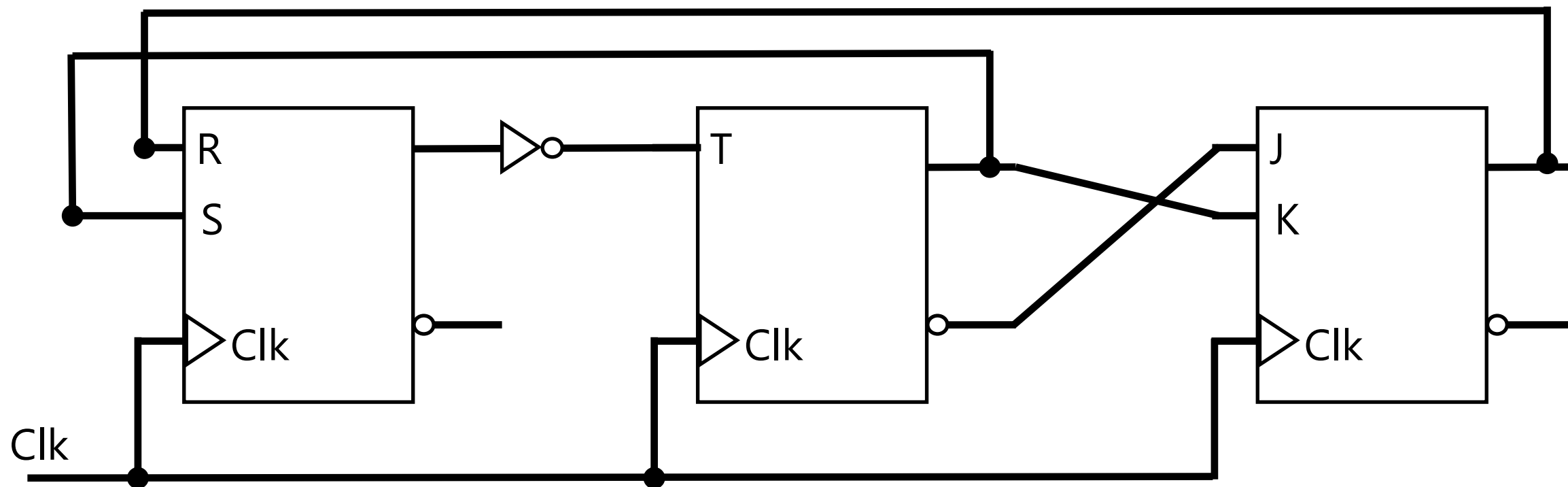


Analysis

0) Is it sequential circuit?

At least one FF \rightarrow Yes

At least one feedback \rightarrow Yes

Otherwise \rightarrow No

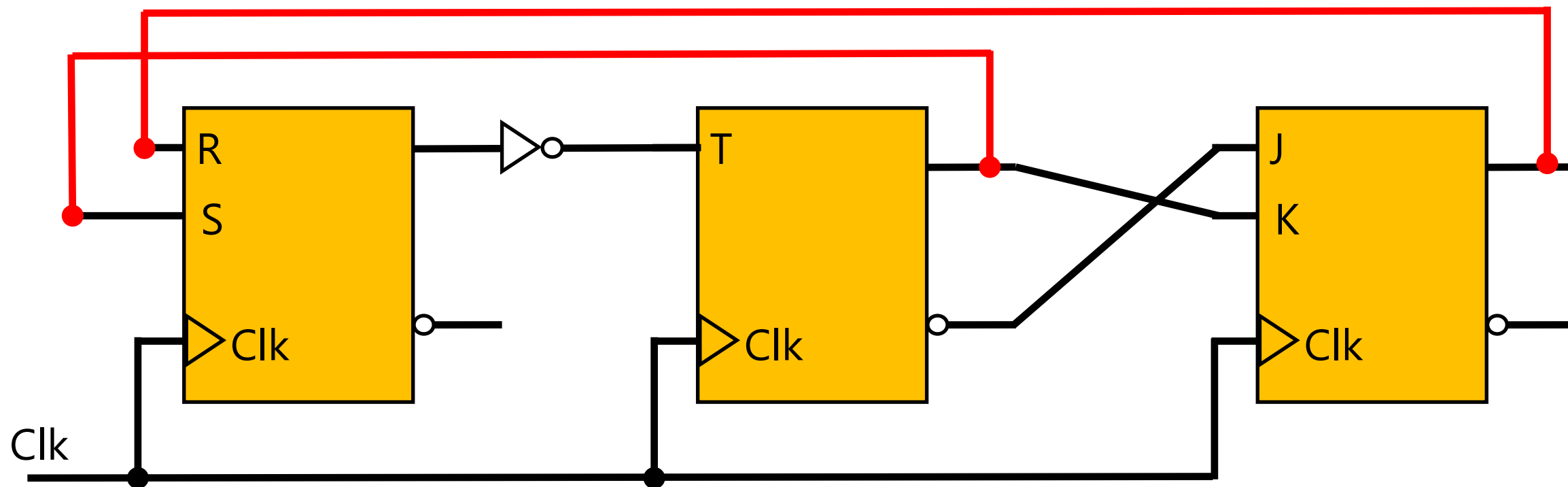


Analysis

1) What are the FFs?

1.1. We pick a name for each FF

1.2. We note the type of FF

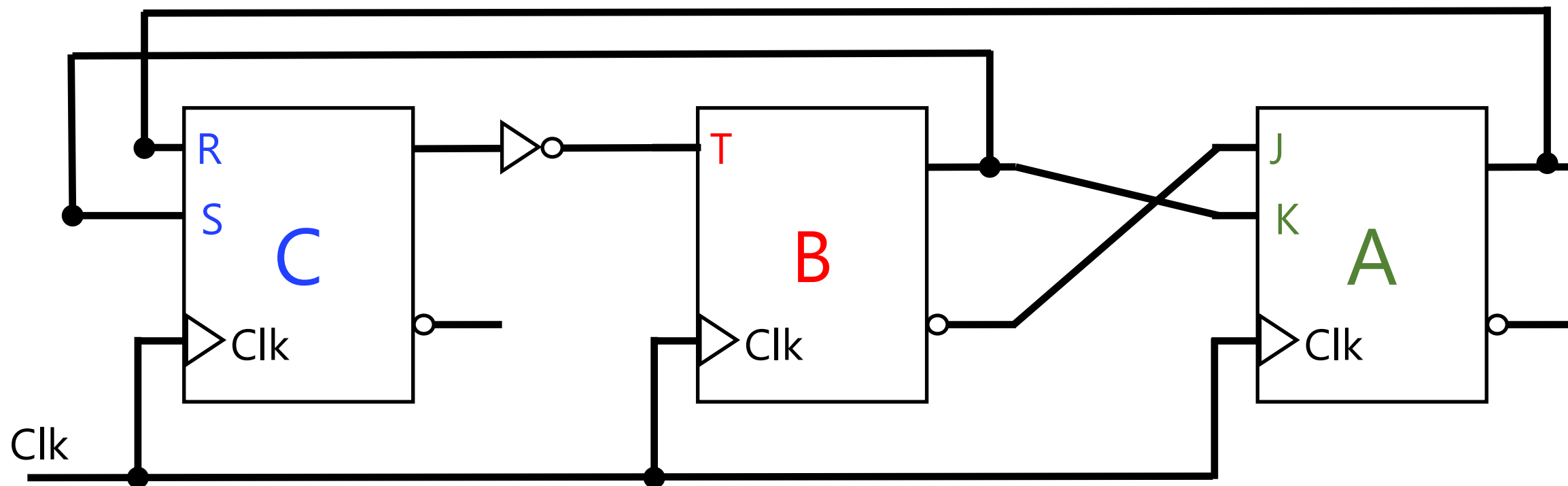


Analysis

2) What are the state combinations
(possibilities)?

Each FF can have $\{0,1\}$ states

In total, $2^{\#FFs}$

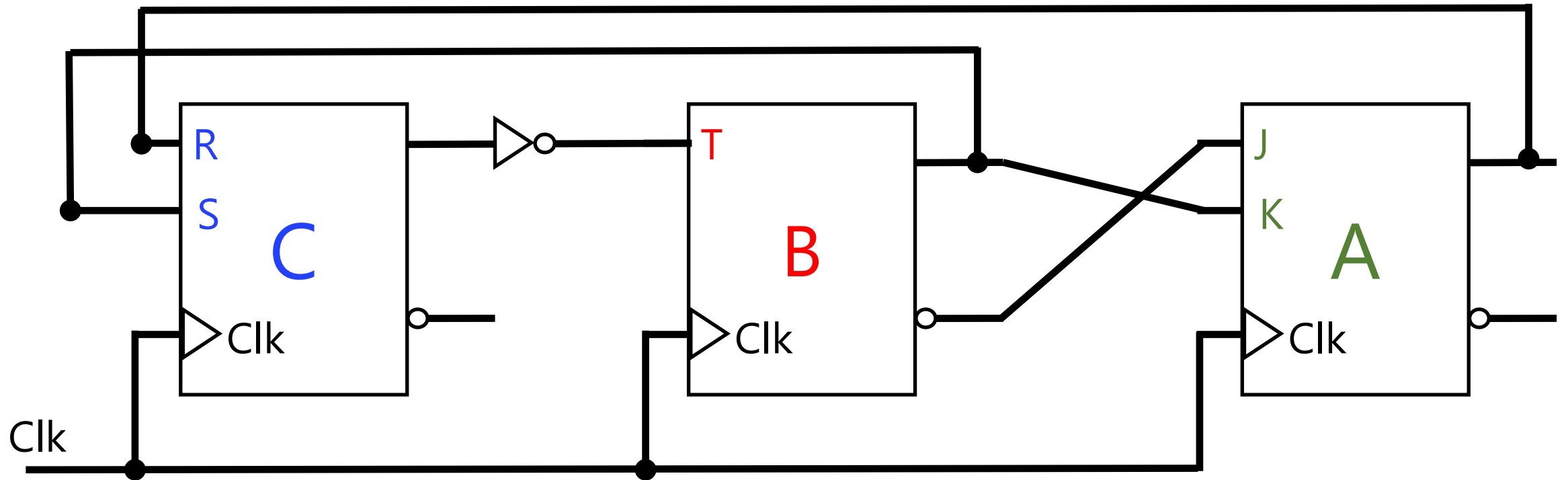


#FFs = 3 $\rightarrow 2^3 = 8$ combinations

Analysis

3) Form a 'State' Table

- 3.1. For each FF, one column for **current** state
- 3.2. For each FF, one column for **next** state
- 3.3. For each combination of current state one row

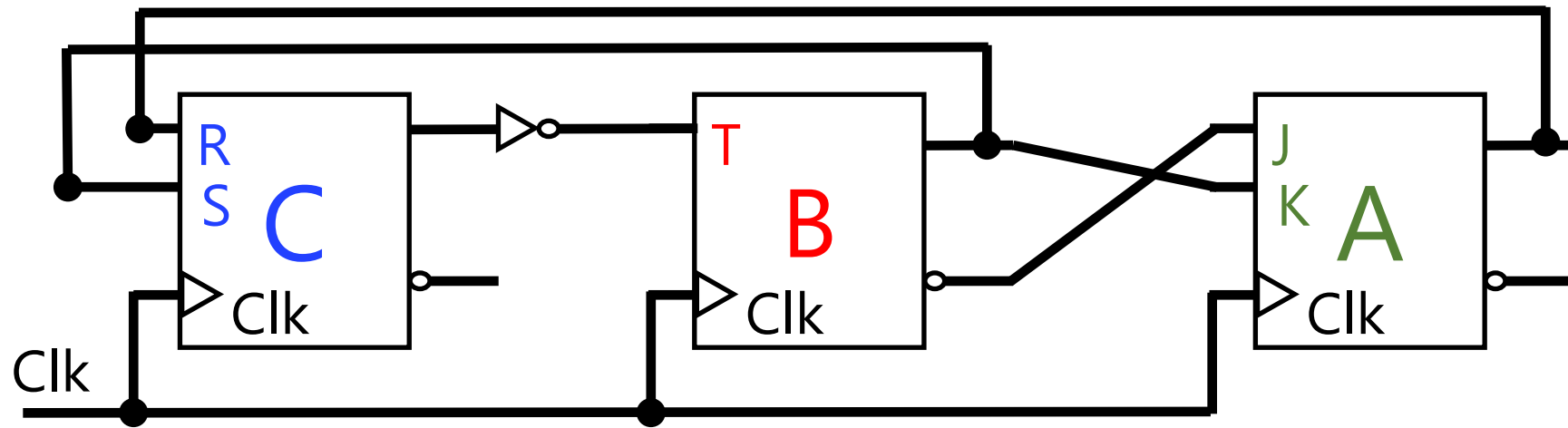[illegible]


Analysis

4) Fill the 'State' table


For each FF, we determine the **next** state based on

I) current state

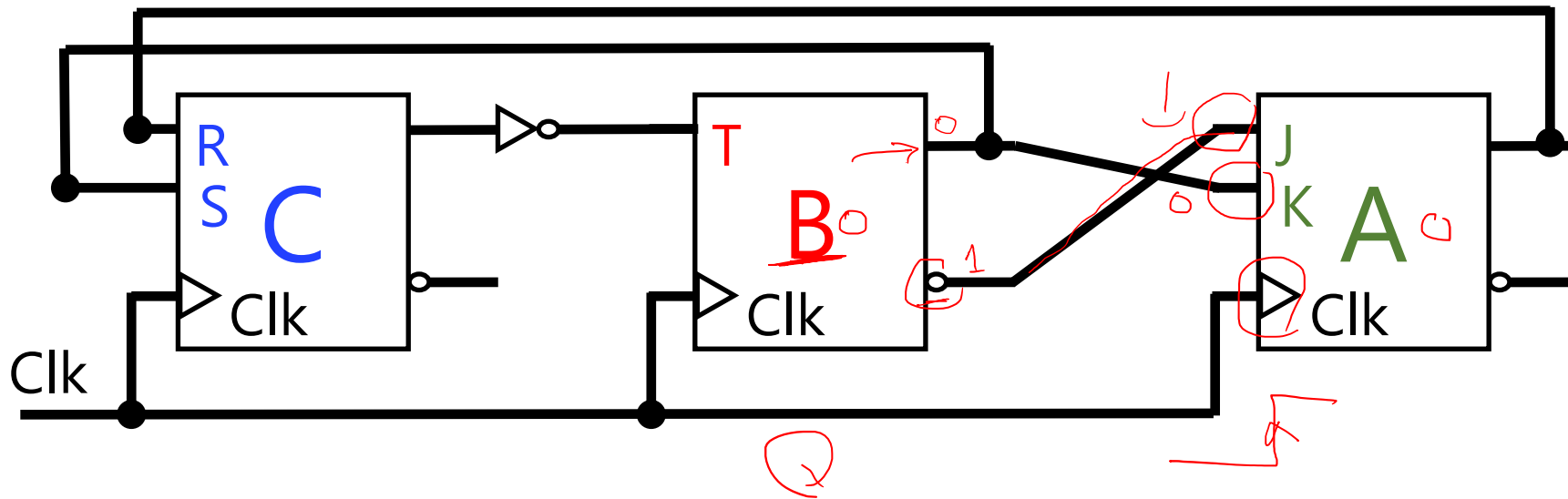
II) the current value of inputs to the FF



Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0			$Q_A(T)=0$ $J_A=Q'_B(T)=1$ $K_A=Q_B(T)=0$ <hr/> Set Action: 1
0	0	1			
0	1	0			
0	1	1			
1	0	0			

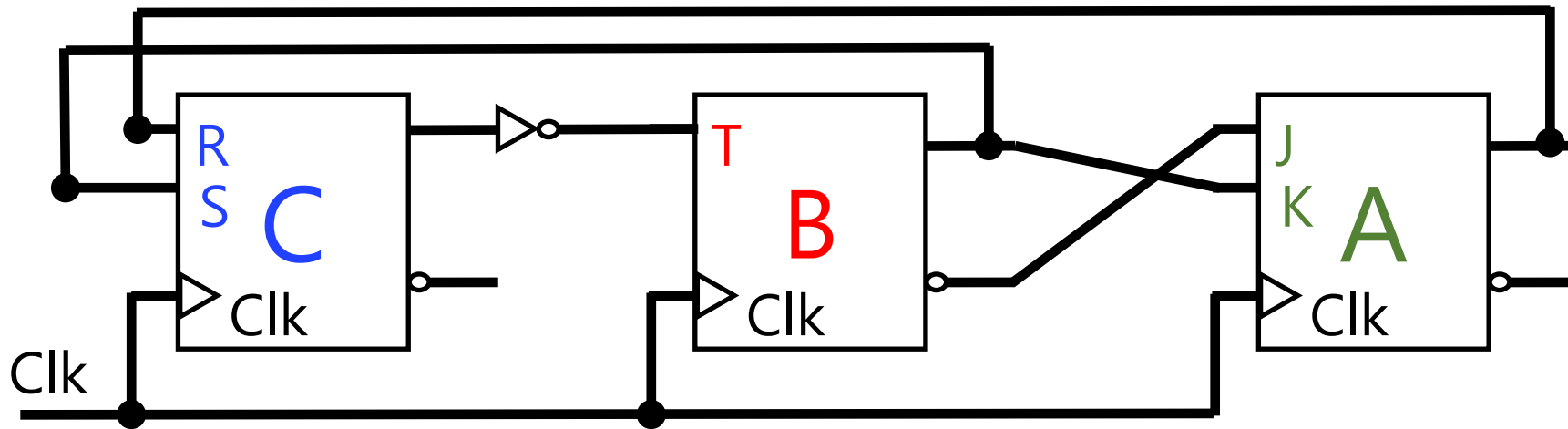

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0		$Q_B(T)=0$ $T_B=Q'_C(T)=1$ ----- $\text{Comp. } (Q_B(T)) = 1$	1
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

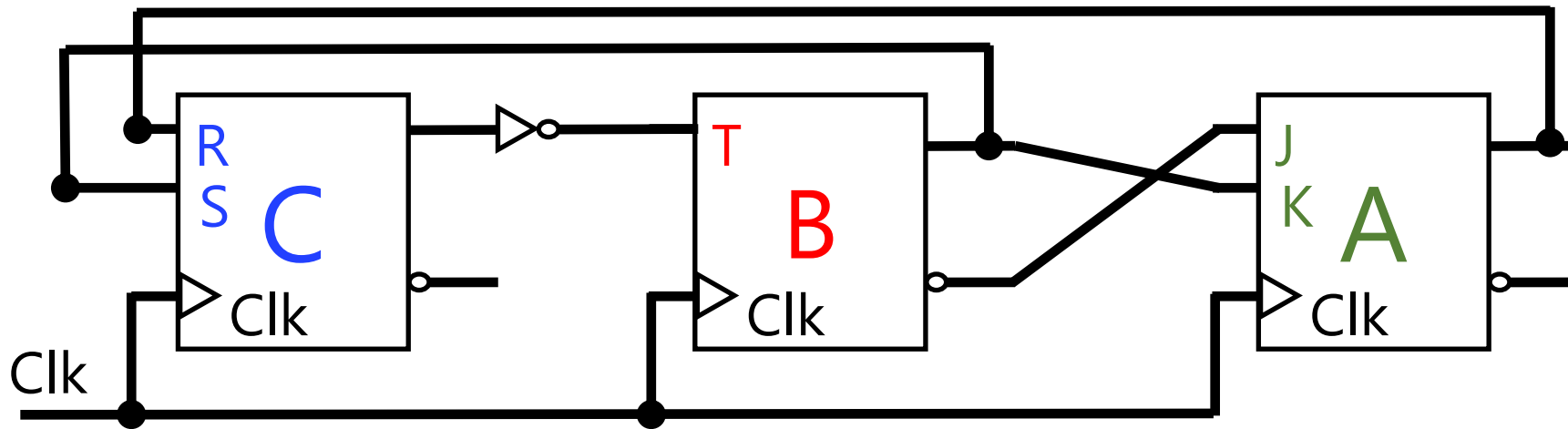

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	$Q_C(T)=0$ $R_C=Q_A(T)=0$ $S_C=Q_B(T)=0$ ----- Store $Q_C(T) = 0$	1	1
0	0	1			
0	1	0			
0	1	1			
1	0	0			

Analysis


$$Q_A(T) = A, Q_{A'}(T) = A'$$


For simplicity, the **current status** of a FF can be assume to be as a **binary variable**

Analysis

5) State Transition Diagram

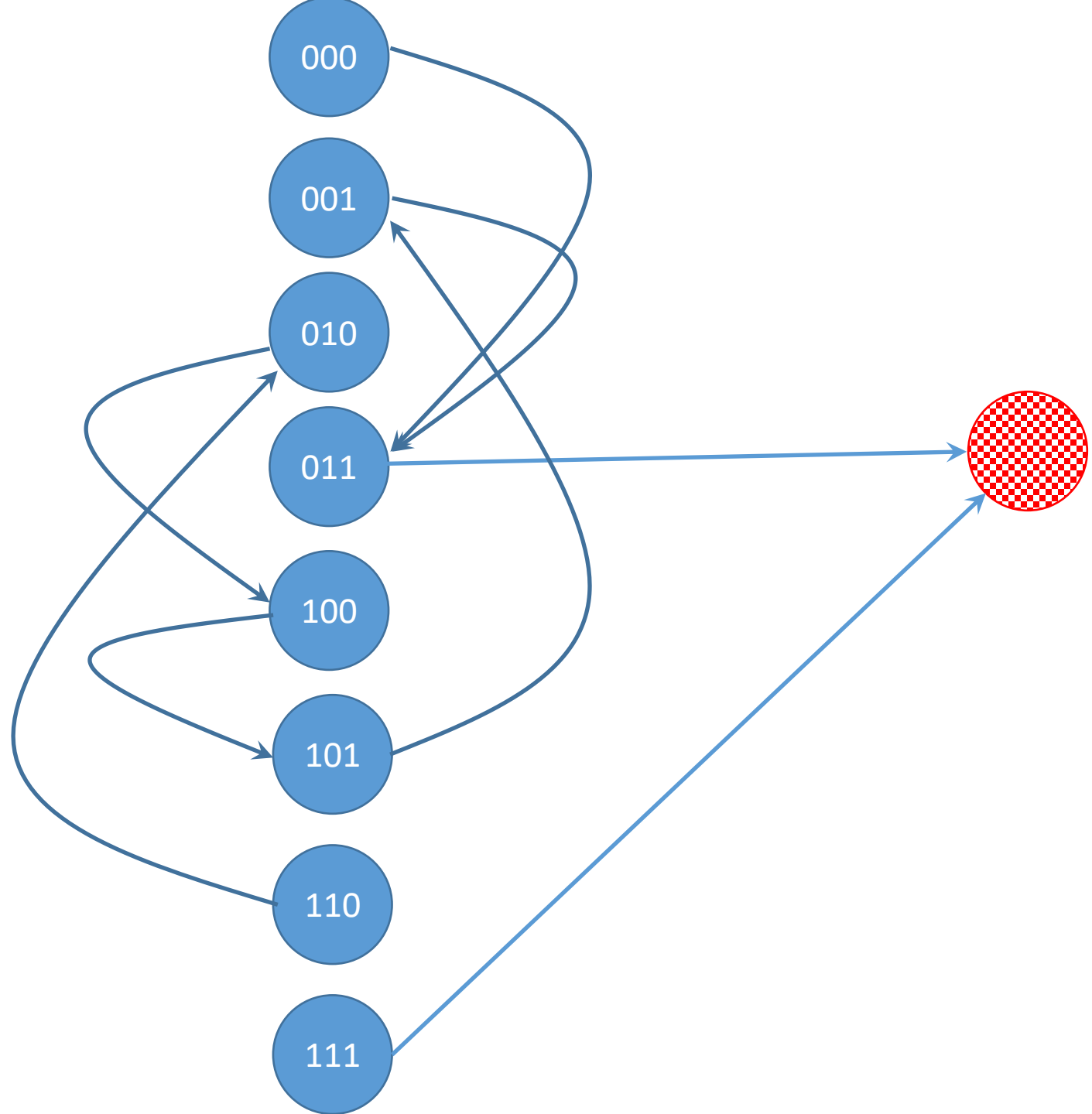- 5.1. for each state combination (each row), a node
- 5.2. from one state (node) to another state, a directed edge



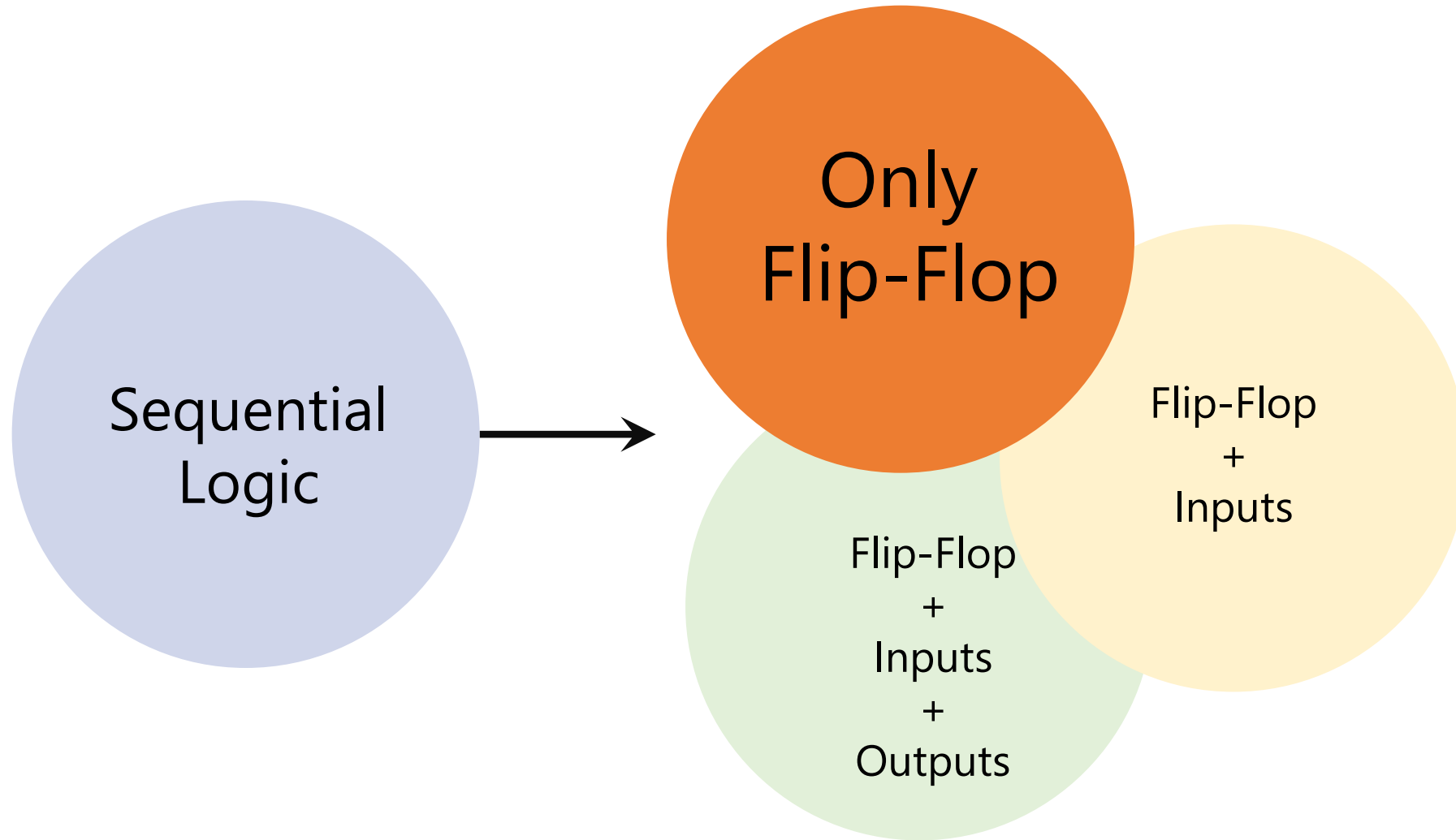

Design by an example

Counter

Count from 0 to N


Design

0. Do we need combinational logic or
→ sequential logic?

Do we need memory?

Counter

Count from 0 to N

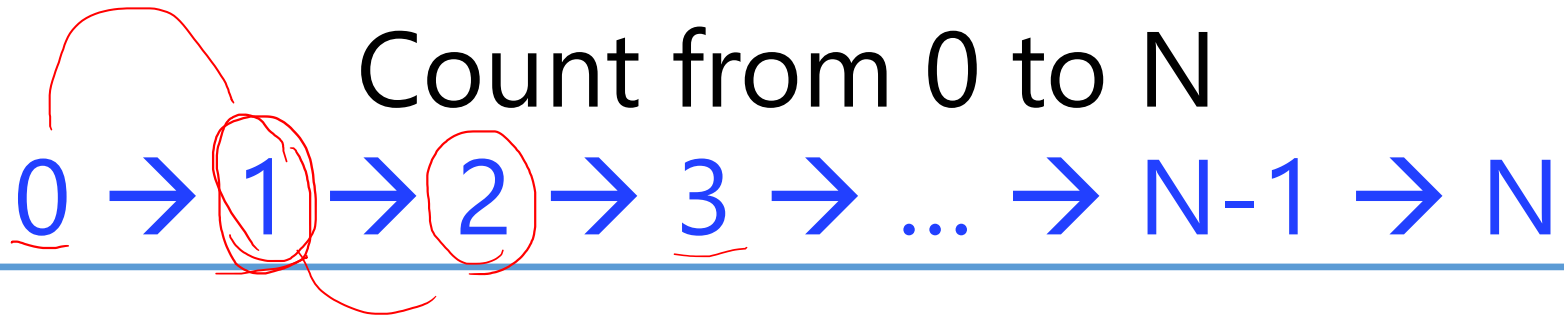

Counter

Count from 0 to N

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow \dots \rightarrow N-1 \rightarrow N$

At each step, we have to see at number we are and then move to next number: $i \rightarrow i+1$

Counter

Count from 0 to N

We need a storage to store current number.

We need a sequential circuit!

Design

1. How many storage (flip-flops)?

Depends on the storage you need to store
the current state in binary system!

Counter

Count from 0 to N

N = 7

0 → 1 → 2 → 3 → 4 → 5 → 6 → 7

000 → 001 → 010 → 011 → 100 → 101 → 110 → 111


For each intermediate state, we need 3 bits → 3 flip-flops


Design

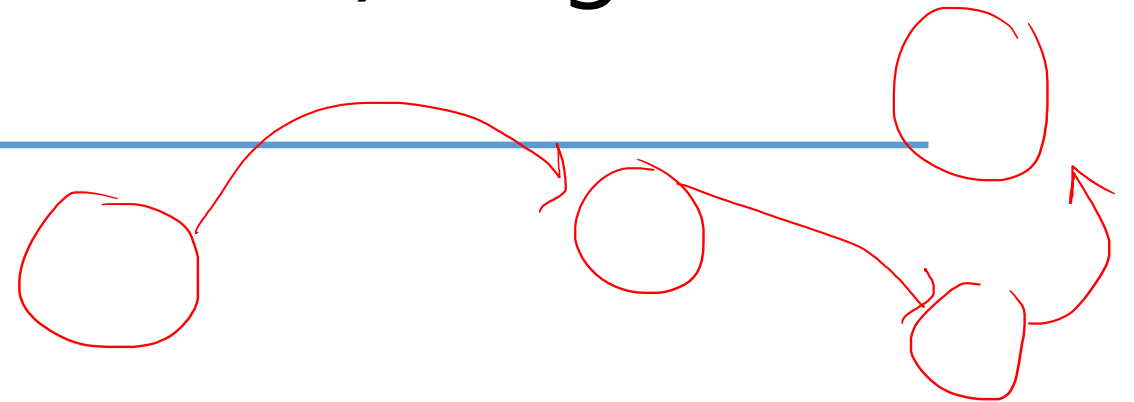
2. Form the state (transition) diagram

Same as analysis,


- For each state → one node
- For each state transition to next state → a directed edge



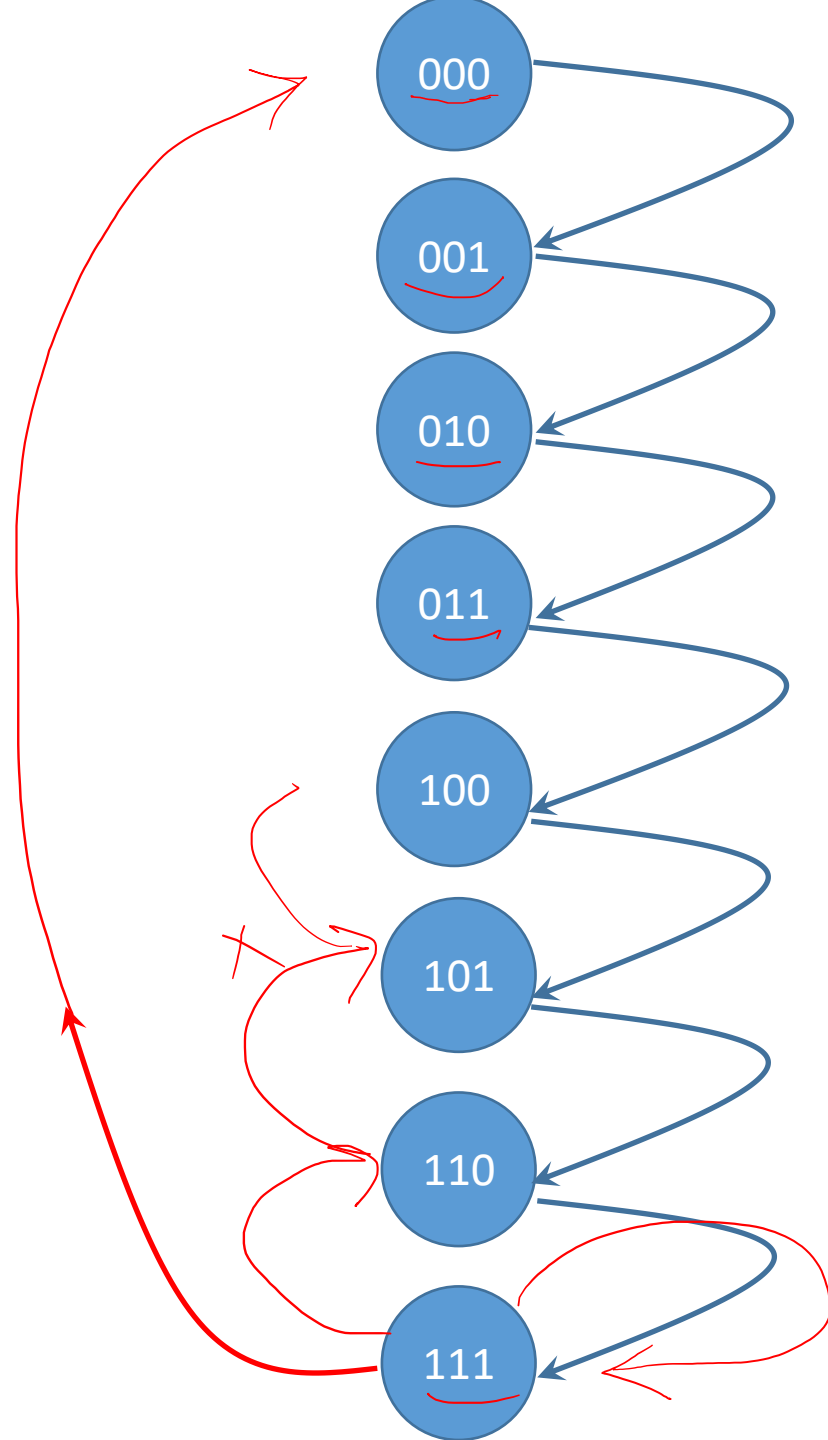

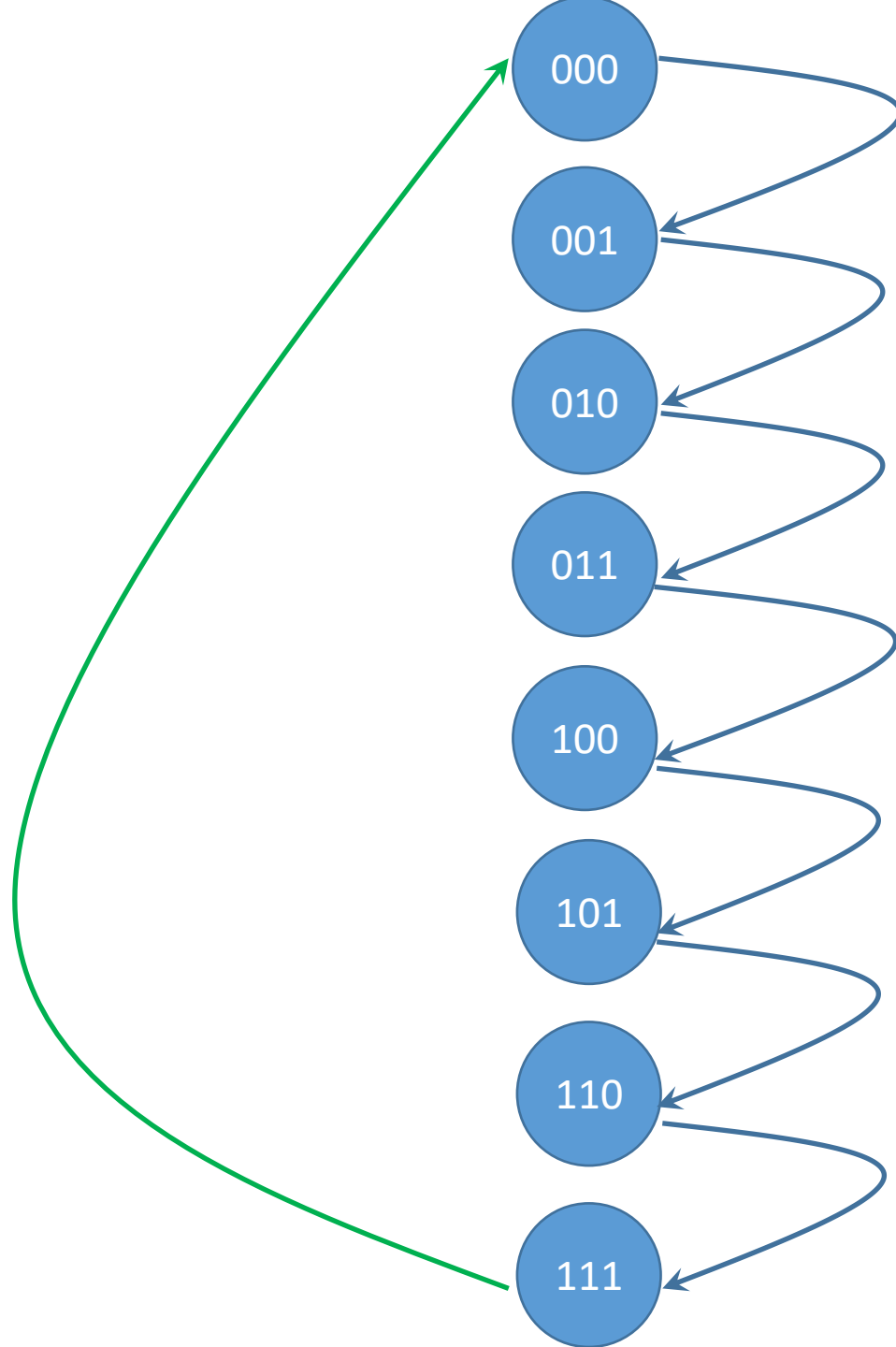

Loop to the
beginning!

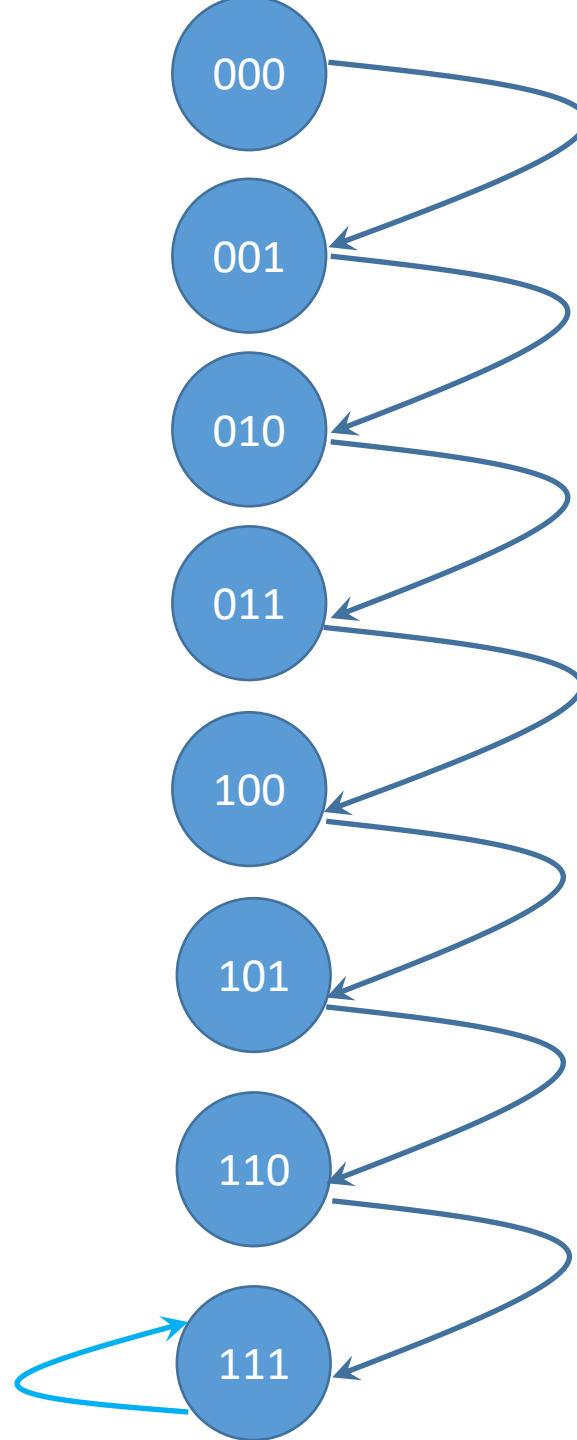

Stuck in 7
Just one time counter!

Design

3. Form the state table


Same as analysis, **two columns** for **each flip-flop** (storage unit)

- a) One for current state $Q(T)$
- b) One for next state $Q(\underline{T+1})$


Design

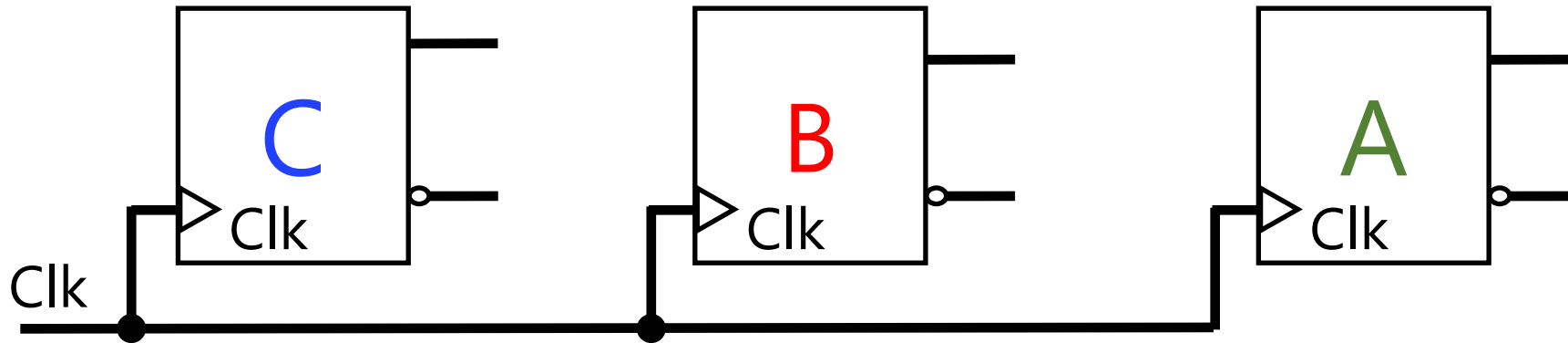4. Fill the state table


Unlike analysis, here we already know what is going to be the next state $Q(T+1)$ based on current state $Q(T)$




Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

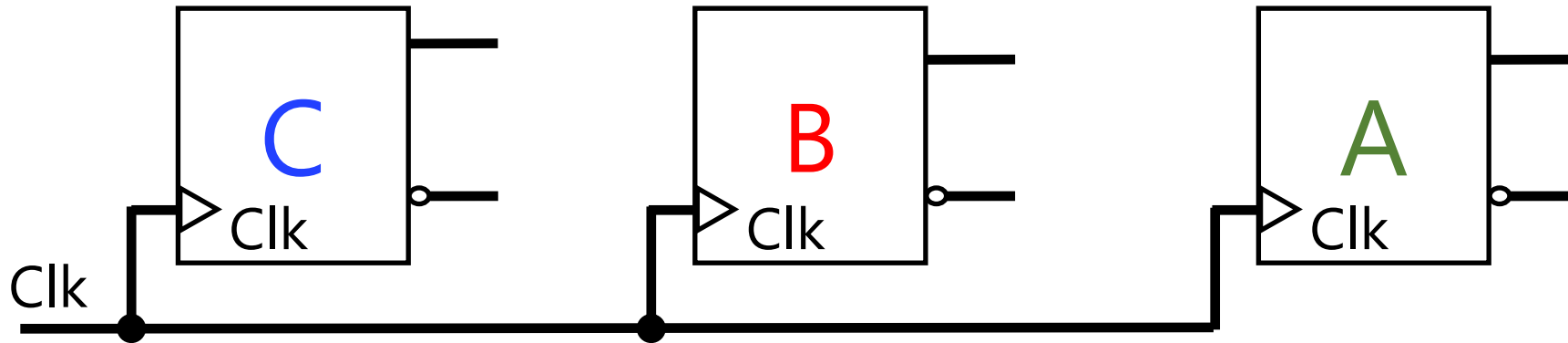


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

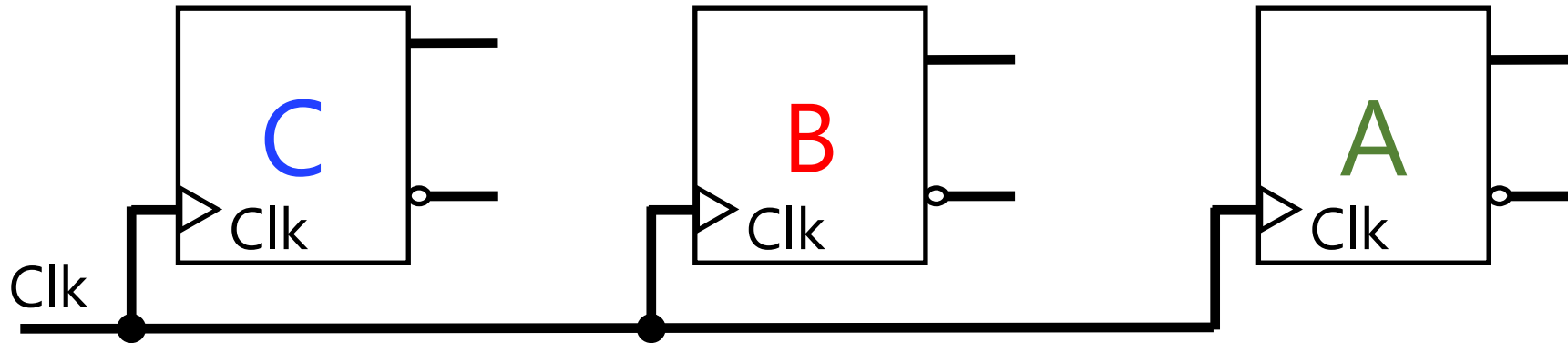


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

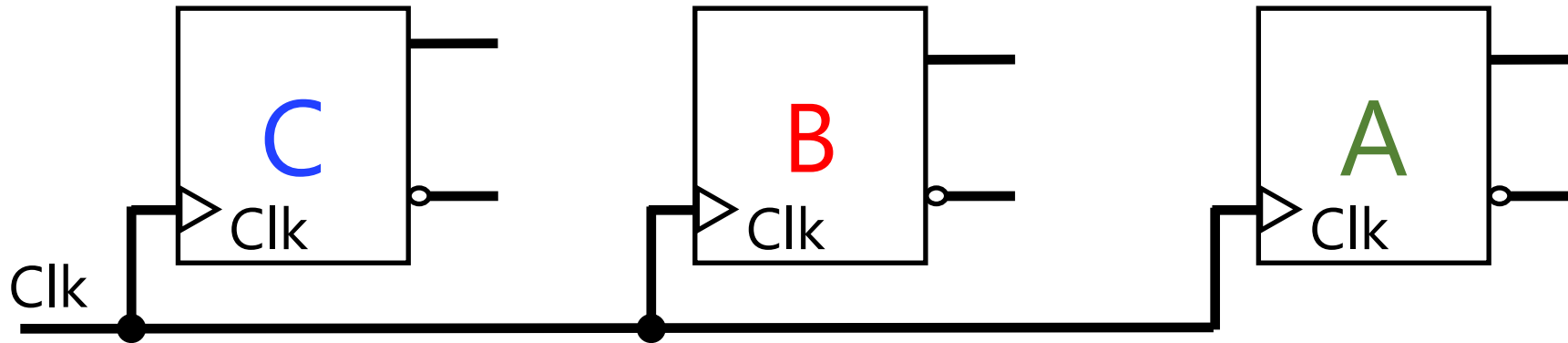


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0			
1	0	1			
1	1	0			
1	1	1			

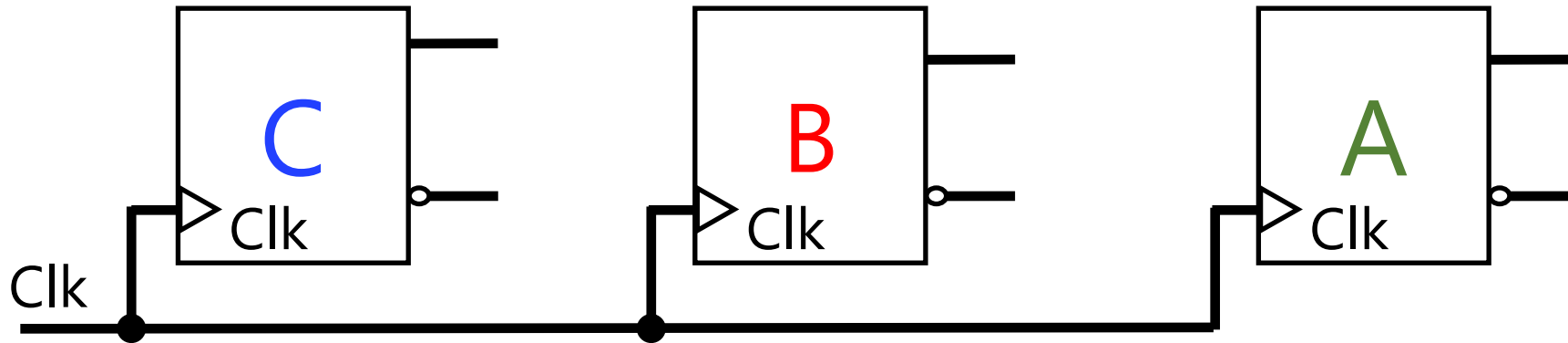


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1			
1	1	0			
1	1	1			

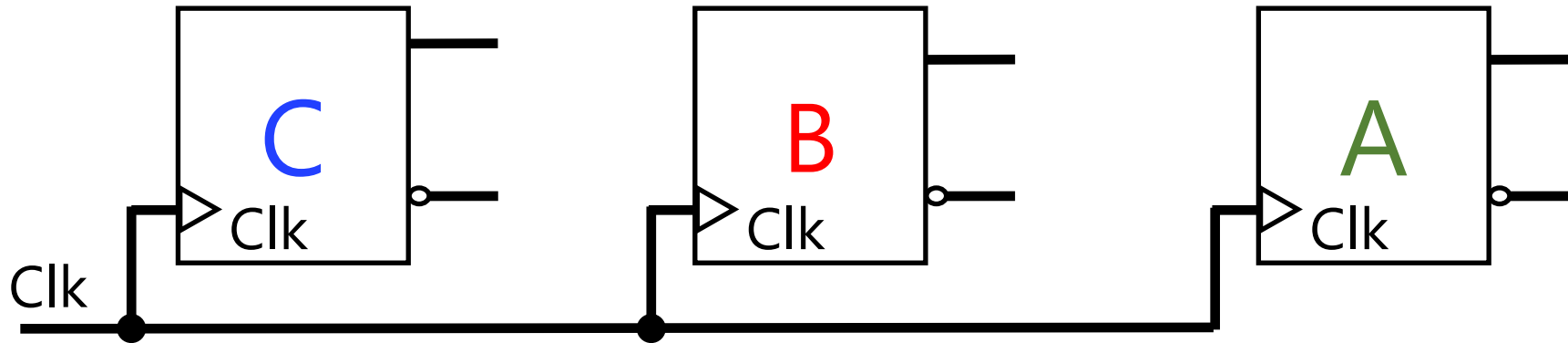


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0			
1	1	1			

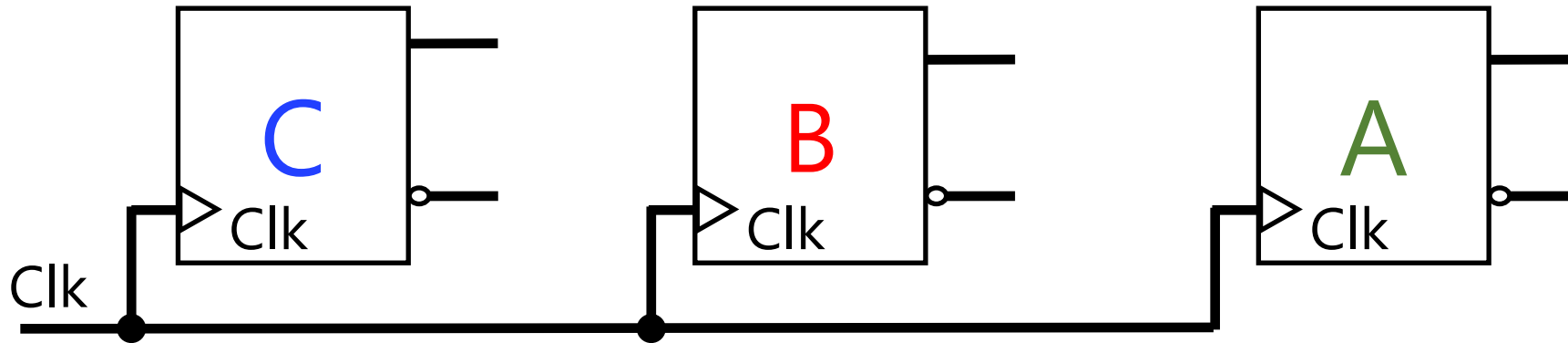


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1			

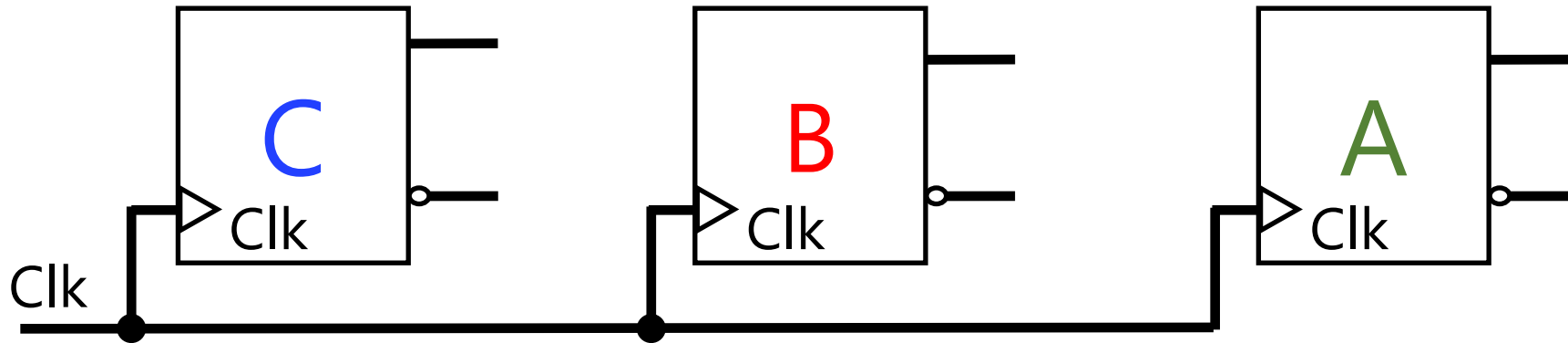


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	?	?	?

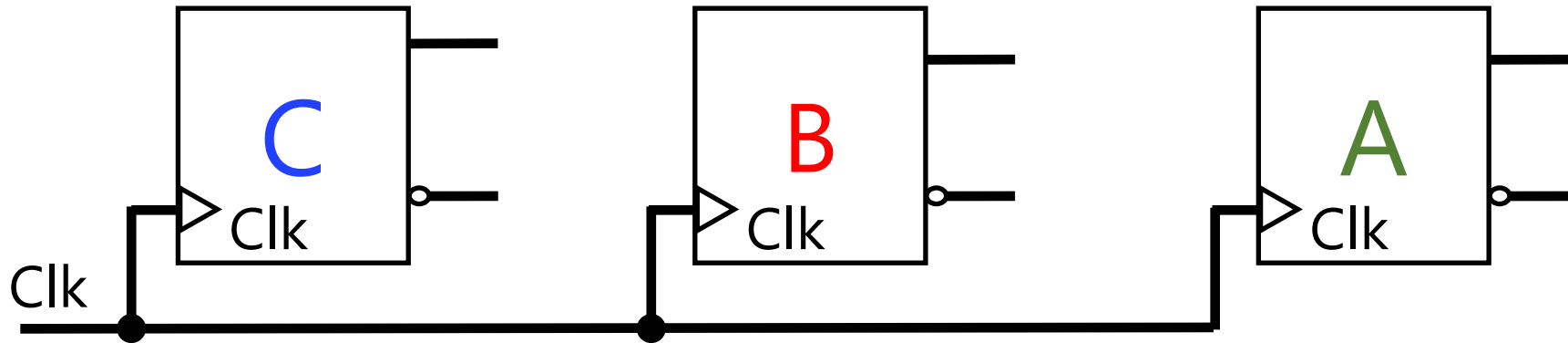

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	Loop to the beginning!	1
1	0	1	1		0
1	1	0	1		1
1	1	1	0	0	0

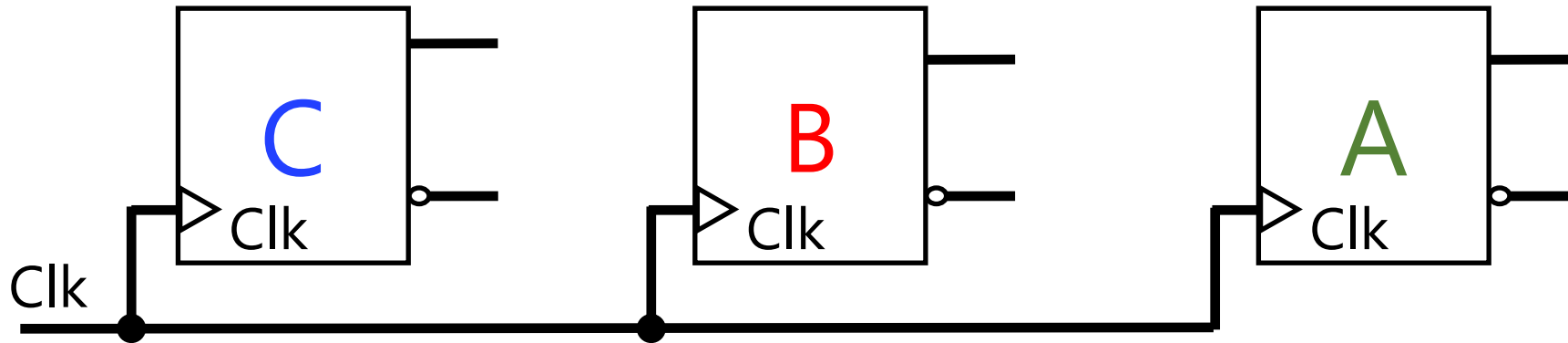

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	Stuck in 7 Just one time counter!	1
1	0	1	1		0
1	1	0	1		1
1	1	1	1		1

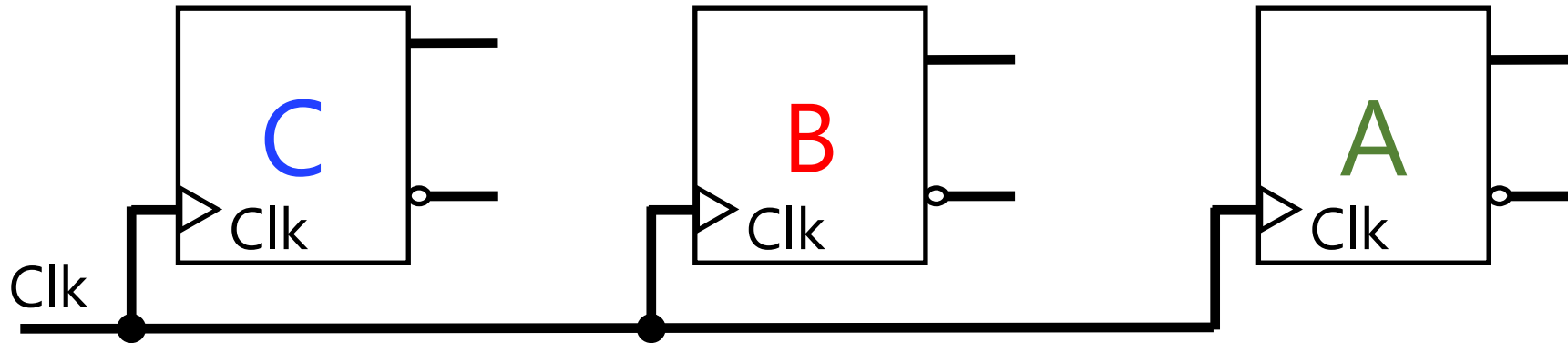

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Our Design Choice!

Design

5. What type of storage (flip-flop)?

RS, D, T, JK, or Mixed

Design

5. What type of storage (flip-flop)?

RS, D, T, JK, or Mixed



In terms of design, does not matter.

In terms of efficiency, matters!

Counter

Count from 0 to $N=7$

Let's select **JK**, the complete FF.

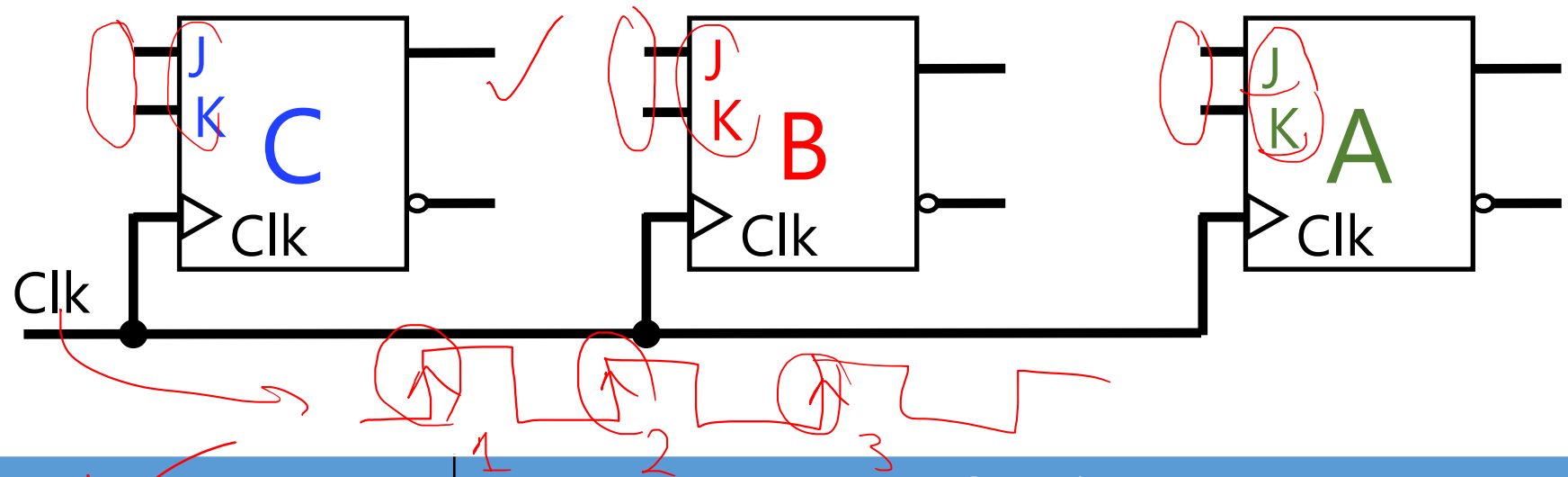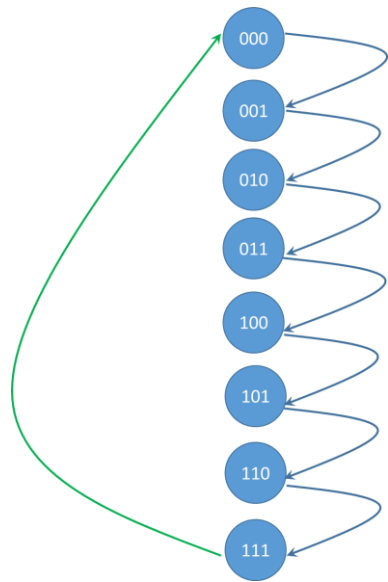


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Design

6. Boolean expression for the flip-flops' input?
input equations, aka, *excitation* equations

T_A
 T_B
 T_C

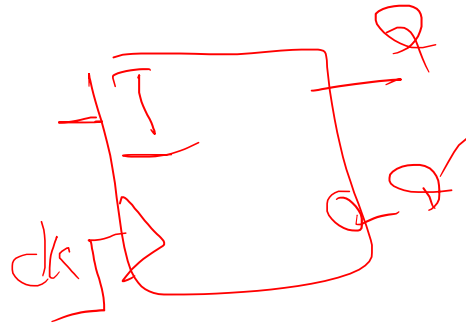

D_A
 D_B
 D_C

R_A
 S_A
 R_B
 S_B
 R_C
 S_C

Counter


Count from 0 to $N=7$

A	$J_A =$	$K_A =$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$


Counter

Count from 0 to $N=7$


A	$J_A =$	$K_A =$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

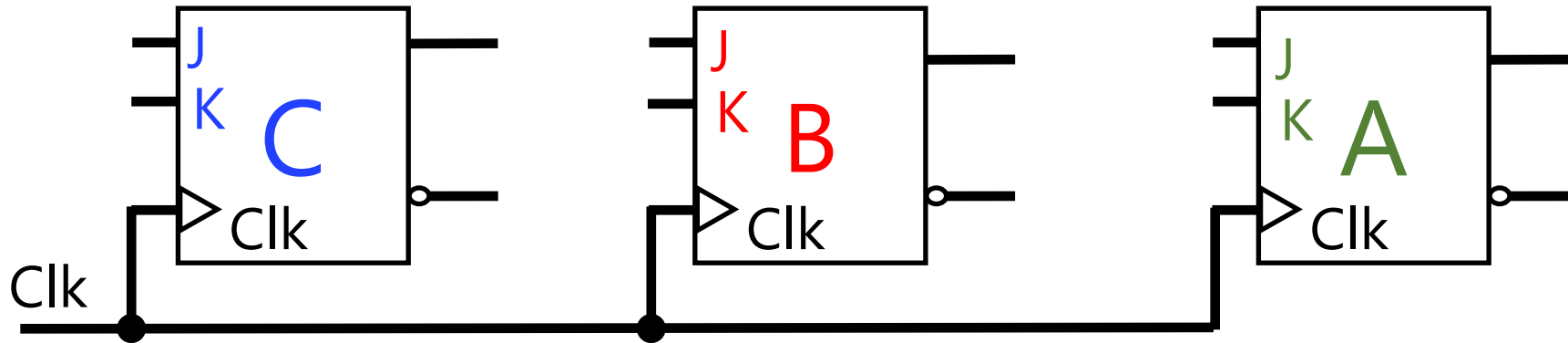

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

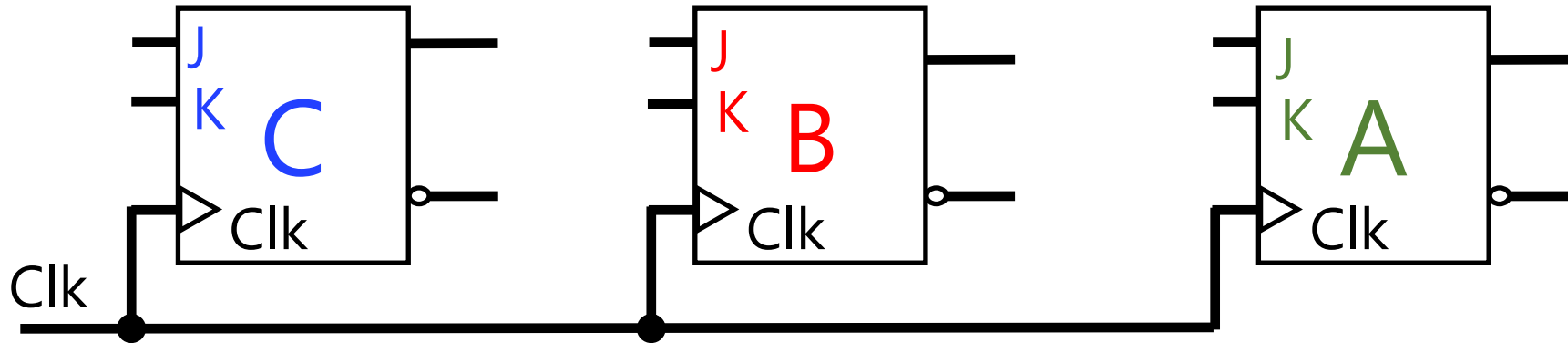


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1			
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

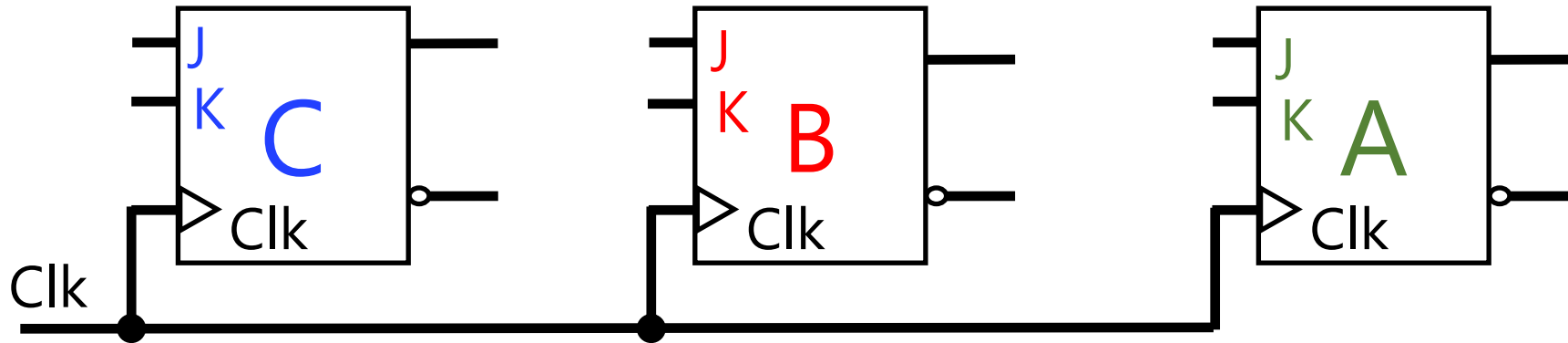


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	<u>Set</u>	<u>1</u>	<u>0</u>
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			


OR

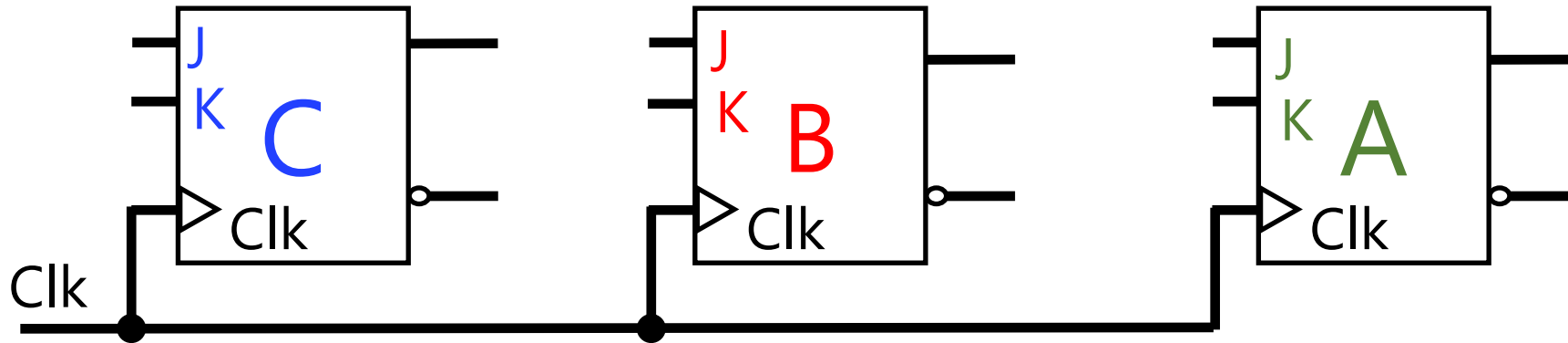

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	<u>Comp</u>	<u>1</u>	<u>1</u>
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

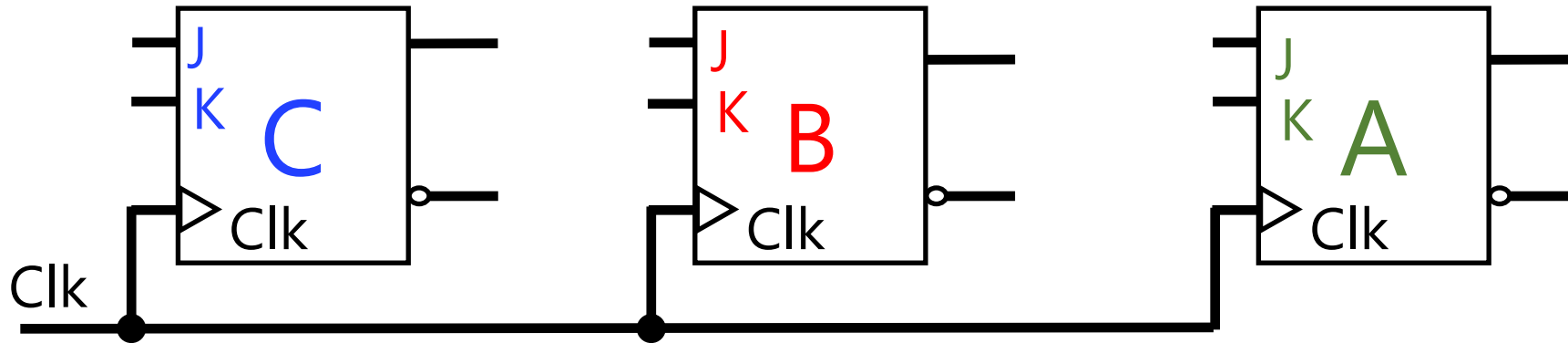


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	0/1 → x
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

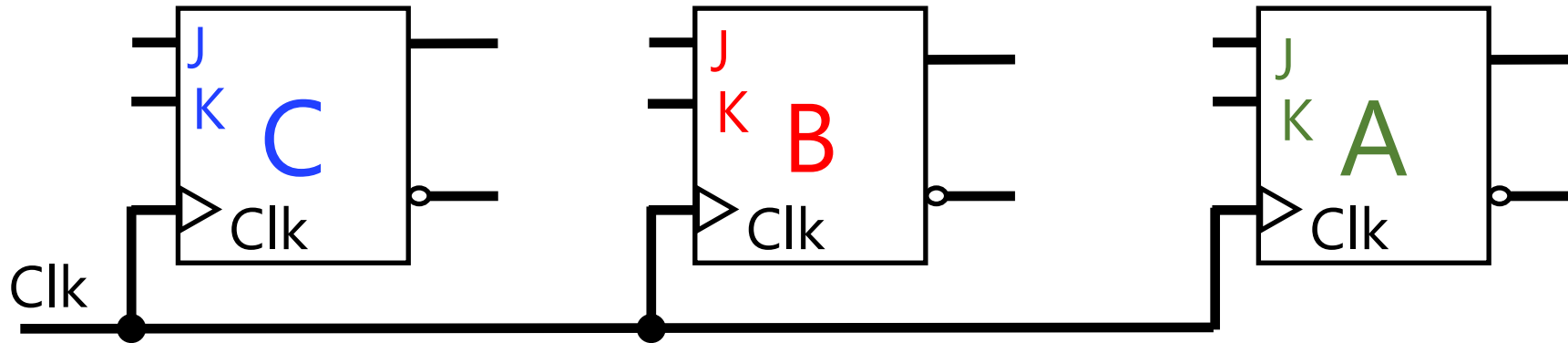


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	×
0	0	1	0	1	0	<u>Reset</u>	<u>0</u>	<u>1</u>
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			


OR

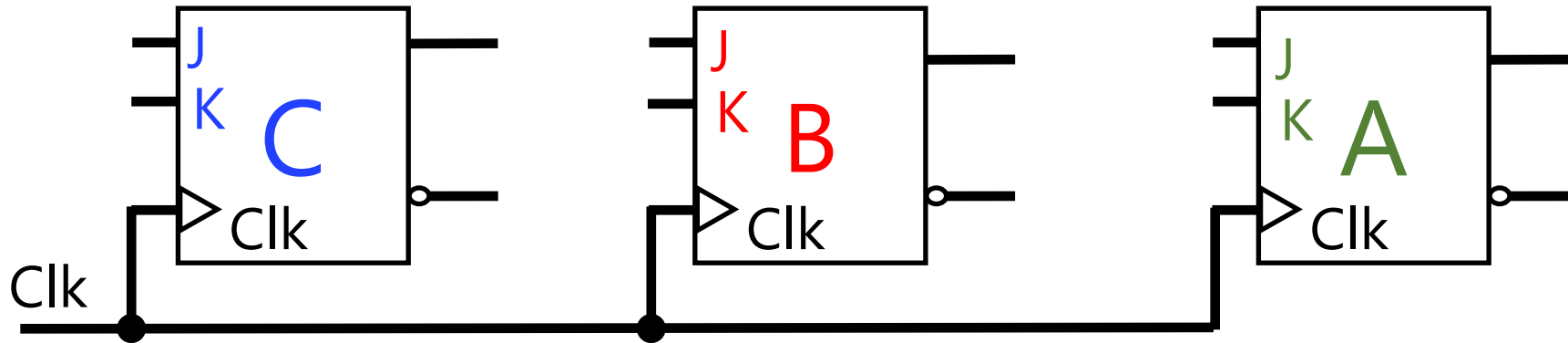


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	×
0	0	1	0	1	0	<u>Comp.</u>	1	1
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

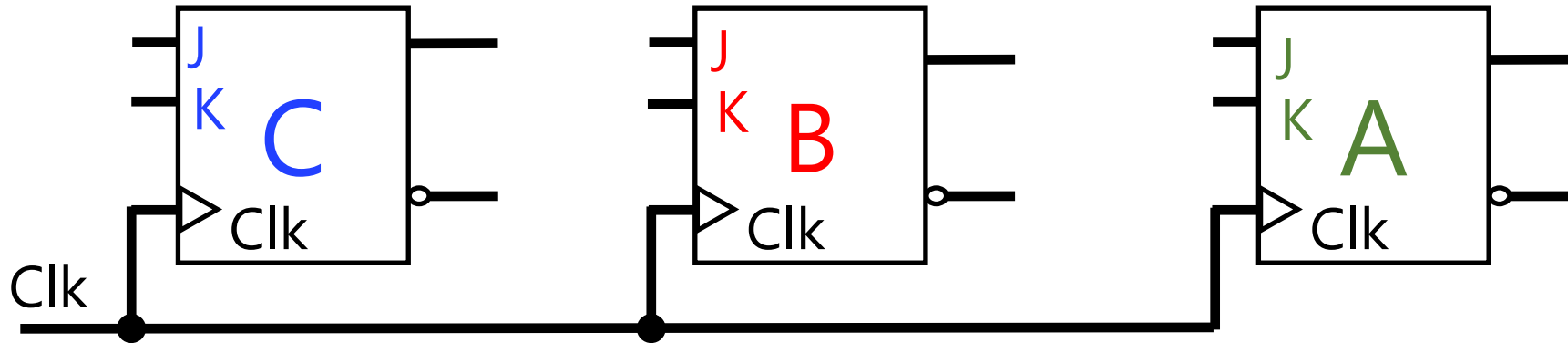


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset/Comp	\times	1
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

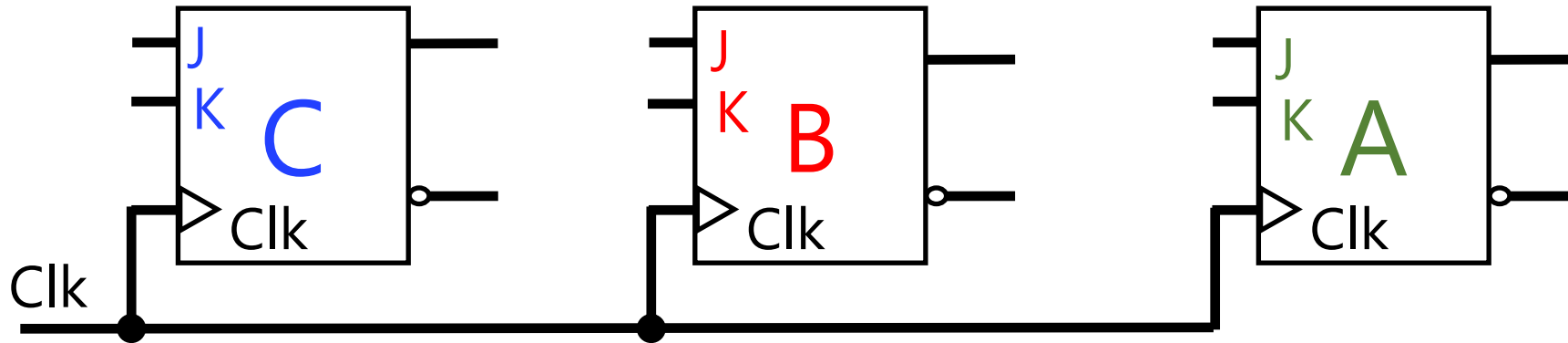

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset/Comp	\times	1
0	1	0	0	1	1	Set/Comp	1	\times
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

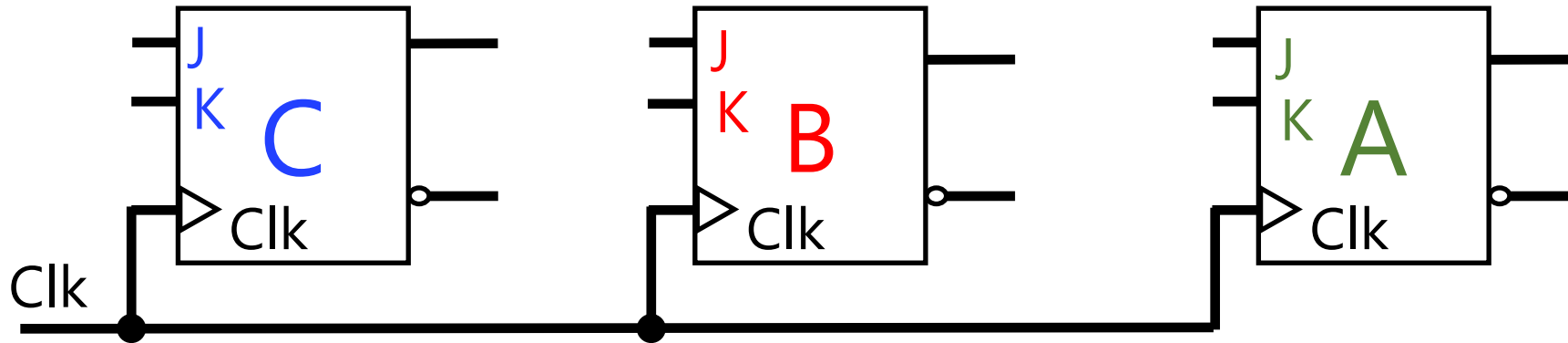

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset/Comp	\times	1
0	1	0	0	1	1	Set/Comp	1	\times
0	1	1	1	0	0	Reset/Comp	\times	1
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

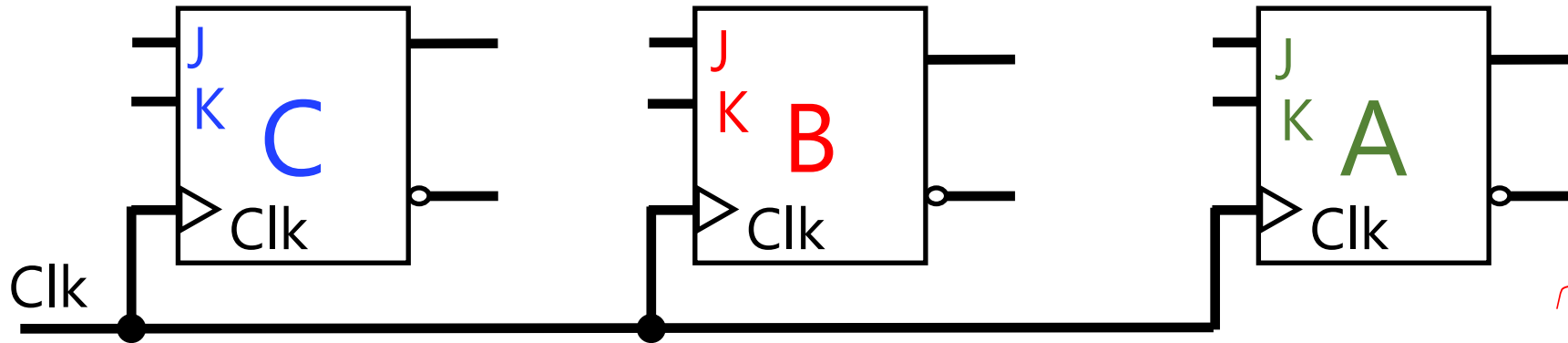


$$J_A = \sum m(0,3)$$

<i>m₀</i> Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	×
0	0	1	0	1	0	Reset/Comp	×	1
0	1	0	0	1	1	Set/Comp	1	×
0	1	1	1	0	0	Reset/Comp	×	1
1	0	0	1	0	1	Set/Comp	1	×
1	0	1	1	1	0	Reset/Comp	×	1
1	1	0	1	1	1	Set/Comp	1	×
1	1	1	0	0	0	Reset/Comp	×	1

Counter

Count from 0 to N=7

Flip-Flops

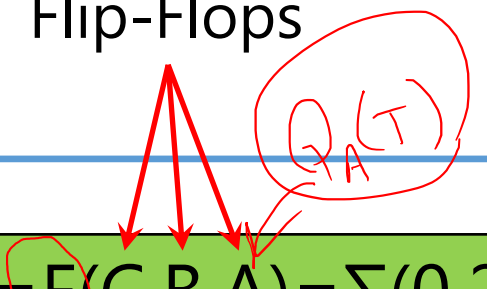


A	$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$	$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

Counter


Count from 0 to N=7

A	$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$	$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

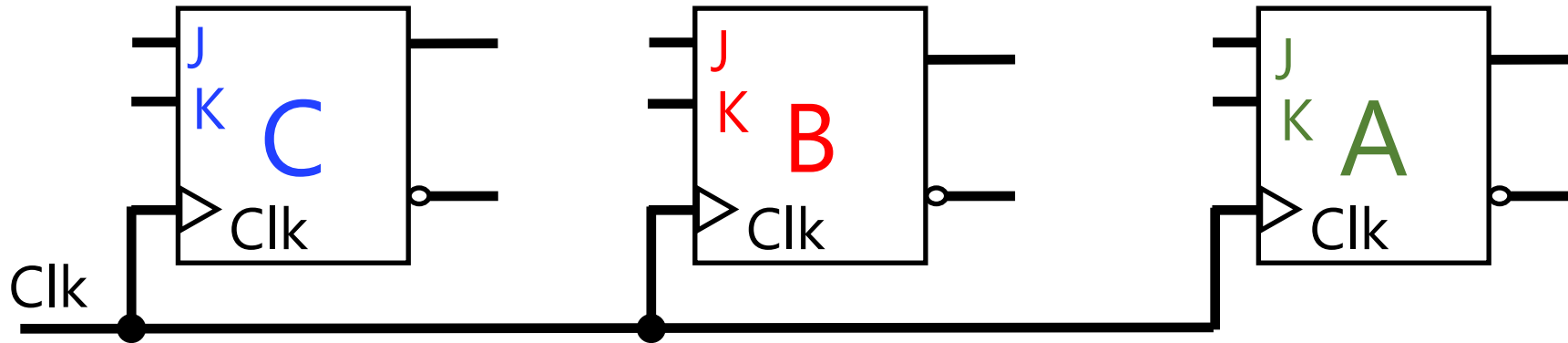


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_B	K_B
0	0	0	0	0	1	Store	0	0
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

OR

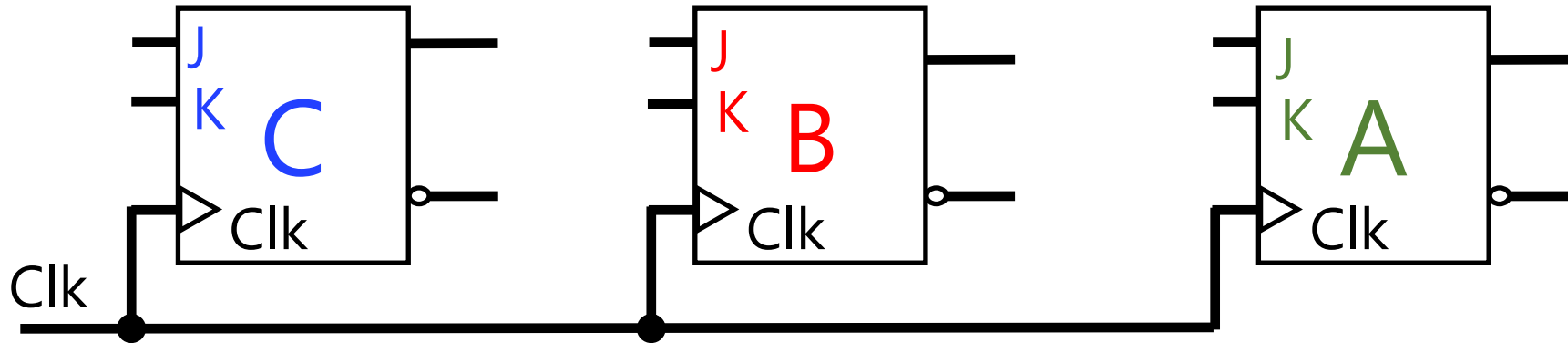

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _B	K _B
0	0	0	0	1	1	Reset	0	1
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

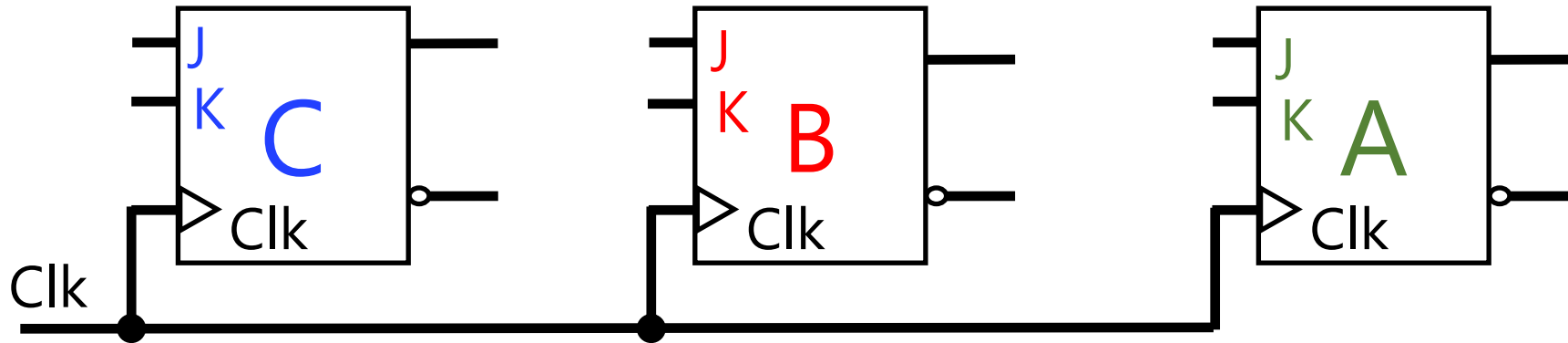

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _B	K _B
0	0	0	0	0	1	Store/Reset	0	×
0	0	1	0	1	0	Set/Comp	1	×
0	1	0	0	1	1	Store/Set	×	0
0	1	1	1	0	0	Reset/Comp	×	1
1	0	0	1	0	1	Store/Reset	0	×
1	0	1	1	1	0	Set/Comp	1	×
1	1	0	1	1	1	Store/Set	×	0
1	1	1	0	0	0	Reset/Comp	×	1

Counter


Count from 0 to N=7

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C =$	$K_C =$

Counter

Count from 0 to N=7

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C =$	$K_C =$

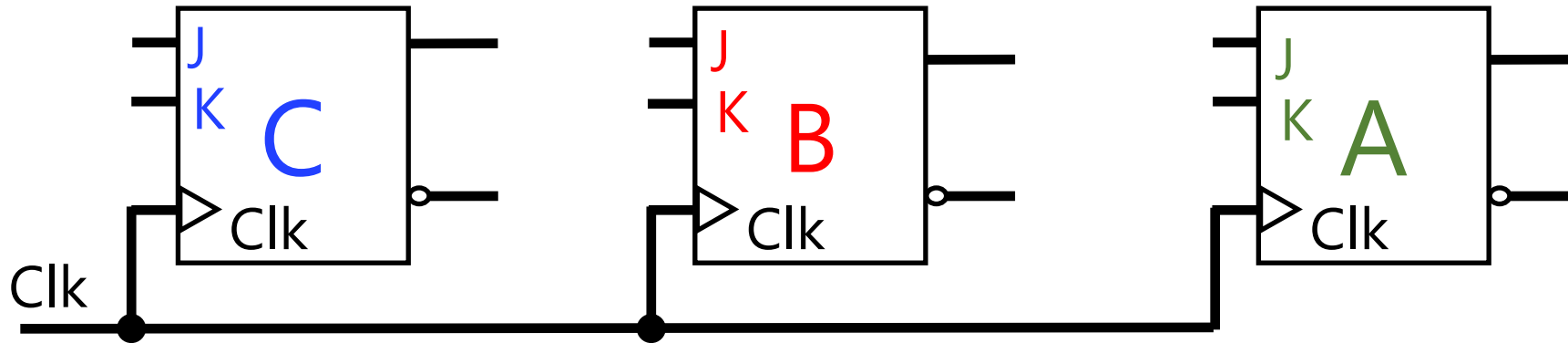

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_C	K_C
0	0	0	0	0	1	Store/Reset	0	x
0	0	1	0	1	0	Store/Reset	0	x
0	1	0	0	1	1	Store/Reset	0	x
0	1	1	1	0	0	Comp/Set	1	x
1	0	0	1	0	1	Store/Set	x	0
1	0	1	1	1	0	Store/Set	x	0
1	1	0	1	1	1	Store/Set	x	0
1	1	1	0	0	0	Comp/Reset	x	1

3-variable
6x ↑

Counter

Count from 0 to N=7

A	$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$	$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$
B	$J_B = F(C, B, A) = \sum(1, 5) + d(2, 3, 6, 7)$	$K_B = F(C, B, A) = \sum(3, 7) + d(0, 1, 4, 5)$
C	$J_C = F(C, B, A) = \sum(3) + d(4, 5, 6, 7)$	$K_C = F(C, B, A) = \sum(7) + d(0, 1, 2, 3)$

Design

7. Minimization of input (*excitation*) equations

Counter

Count from 0 to N=7

3-Variable K-Map

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C = F(C,B,A) = \sum(3) + d(4,5,6,7)$	$K_C = F(C,B,A) = \sum(7) + d(0,1,2,3)$

		BA			
		00	01	11	10
C	0	0 m_0	0 m_1	1 m_3	0 m_2
	1	X m_4	X m_5	X m_7	X m_6

$$J_C = F(C, B, A) = \sum(3) + d(4, 5, 6, 7)$$

$$J_C = \underline{BA}$$

		BA			
		00	01	11	10
C	0	X m_0	X m_1	X m_3	X m_2
	1	0 m_4	0 m_5	1 m_7	0 m_6

$$K_C = F(C, B, A) = \sum(7) + d(0, 1, 2, 3)$$

$$K_C = \underline{BA}$$

		BA			
		00	01	11	10
C	0	0 m_0	1 m_1	X m_3	X m_2
	1	0 m_4	1 m_5	X m_7	X m_6

$$J_B = F(C, B, A) = \sum(1, 5) + d(2, 3, 6, 7)$$

$$J_B = \underline{A}$$

		BA			
		00	01	11	10
C	0	X m_0	X m_1	0 m_3	1 m_2
	1	X m_4	X m_5	0 m_7	1 m_6

$$K_B = F(C, B, A) = \sum(3, 7) + d(0, 1, 4, 5)$$

$$K_B = \underline{A}$$

		BA			
		00	01	11	10
C	0	1 m_0	X m_1	X m_3	1 m_2
	1	1 m_4	X m_5	X m_7	1 m_6

$$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$$

$$J_A = \underline{1}$$


		BA			
		00	01	11	10
C	0	X m_0	1 m_1	1 m_3	X m_2
	1	X m_4	1 m_5	1 m_7	X m_6


$$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$$

$$K_A = \underline{1}$$

Design


8. Draw/Sketch Logic Circuit

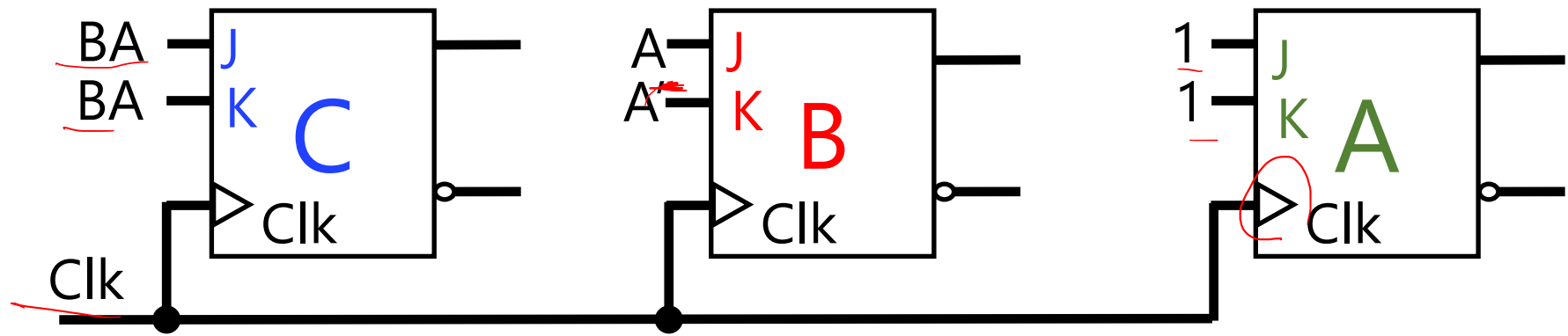

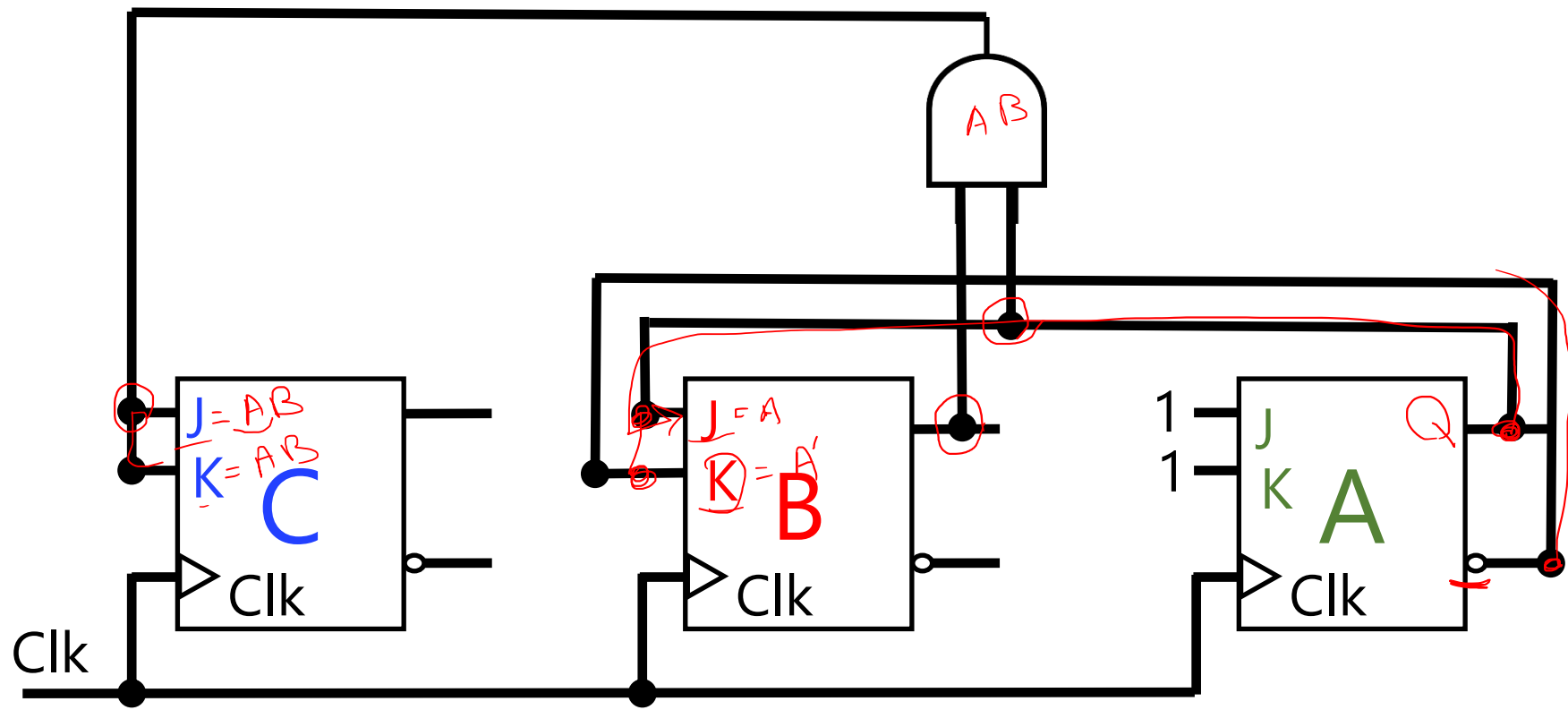


Design


9. (Optional) Test

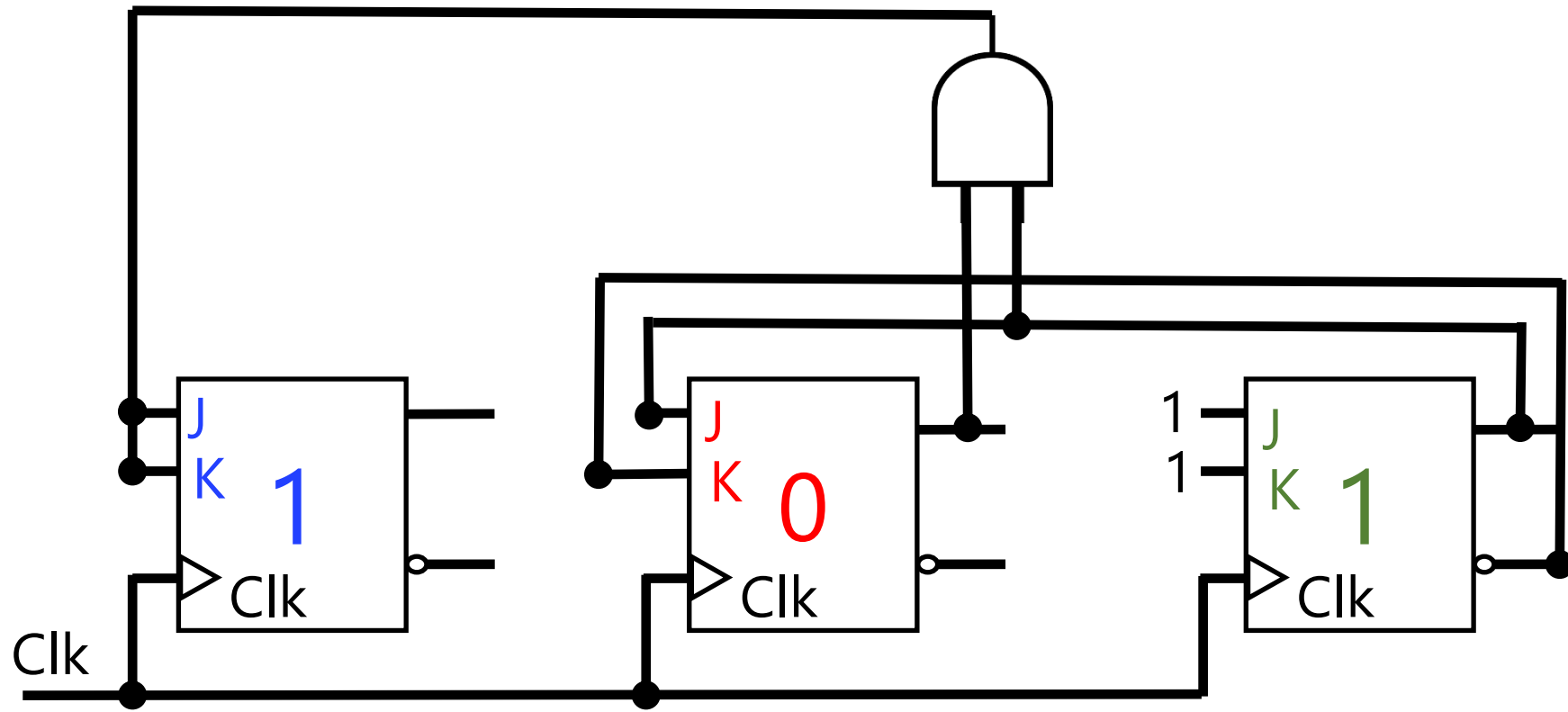


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	?	?
<div style="text-align: center;"> → 5 → ? 6 </div>					

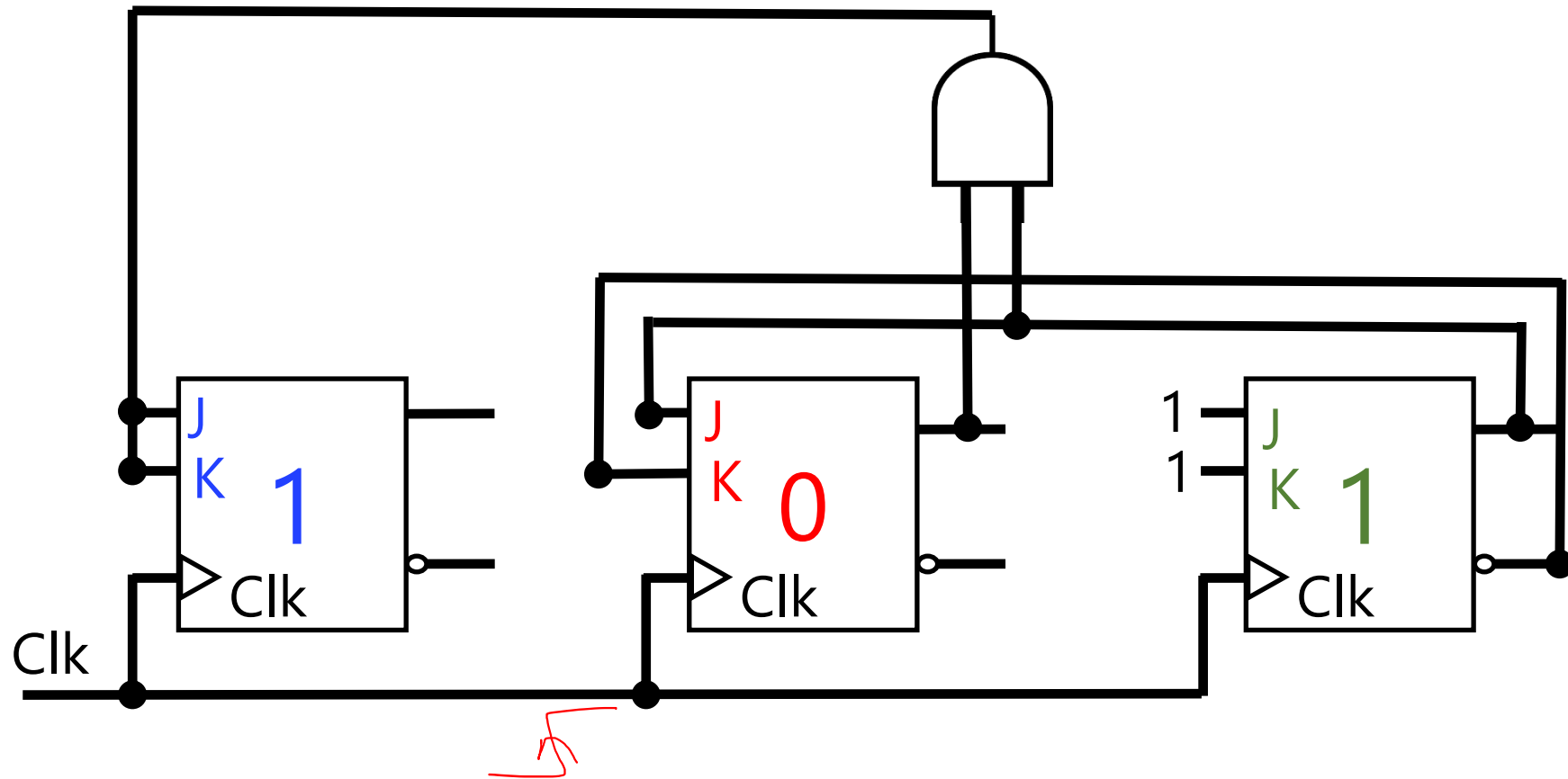


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	?	?
5 → ?					

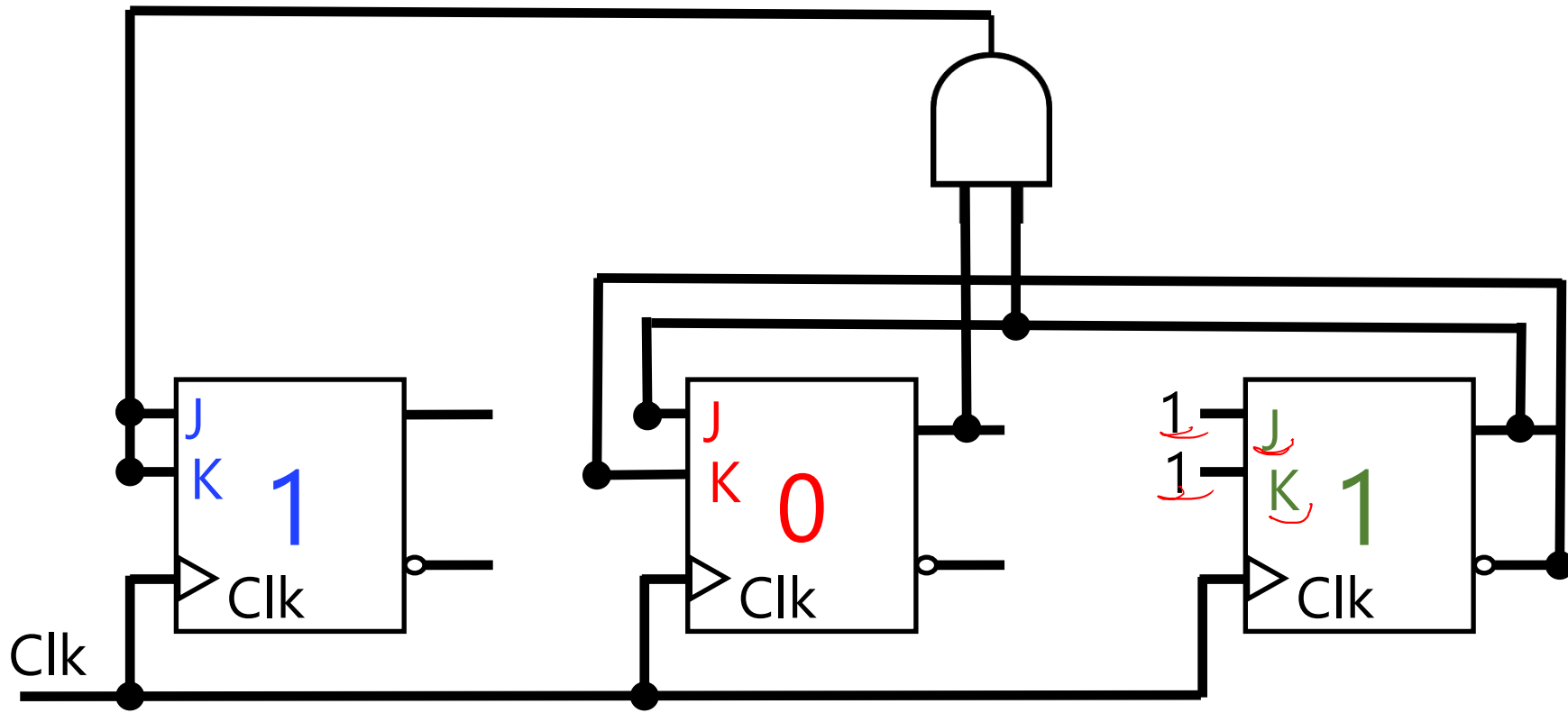


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	<u>1</u>	?	?	A= <u>1</u> , <u>J_A</u> =1, <u>K_A</u> =1 ----- Comp. → <u>0</u>
5 → ?					

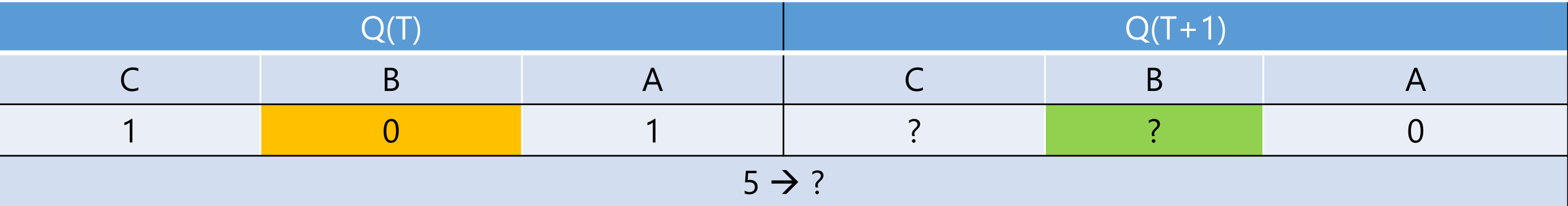


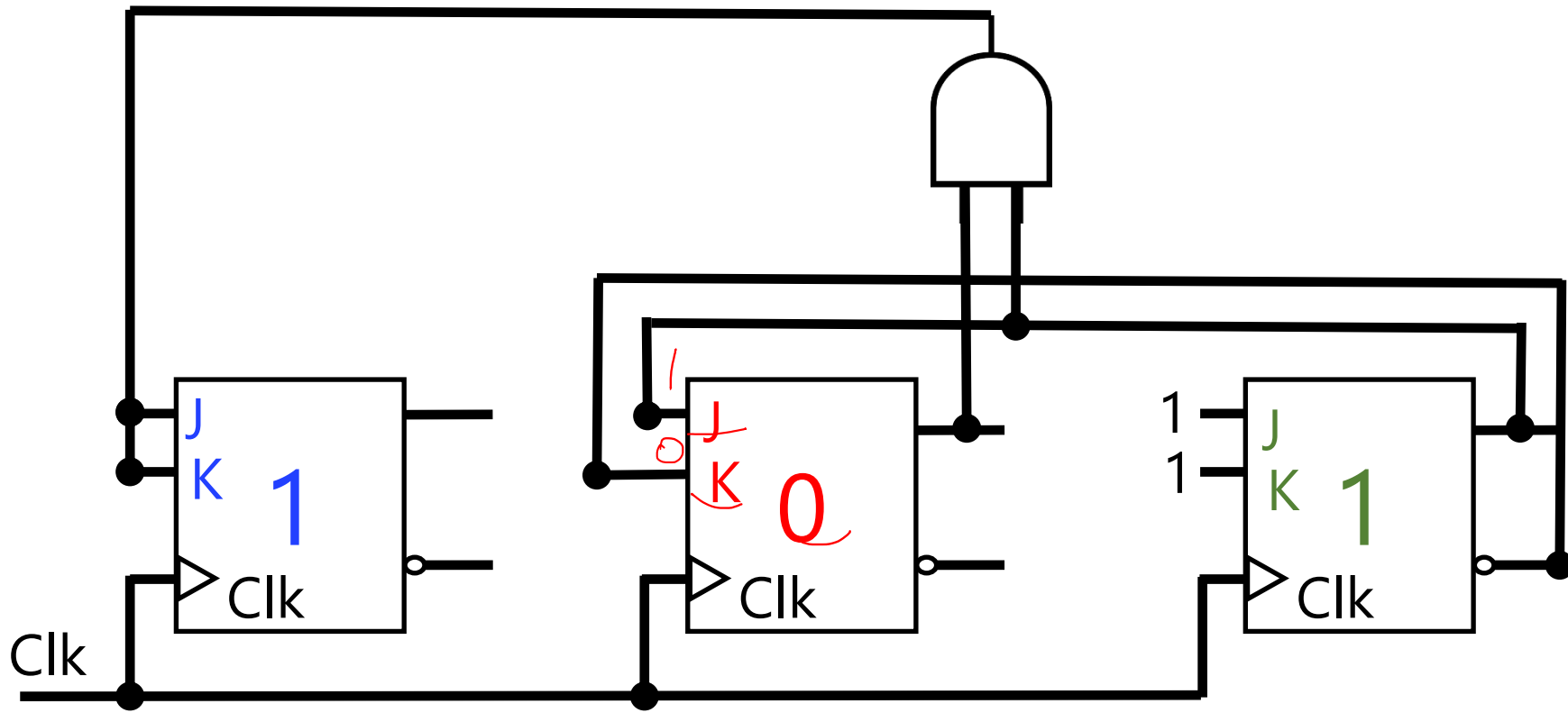


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	B=0, $J_B=A=1$, $K_B=A'=0$ ----- Set $\rightarrow 1$	0

5 \rightarrow ?

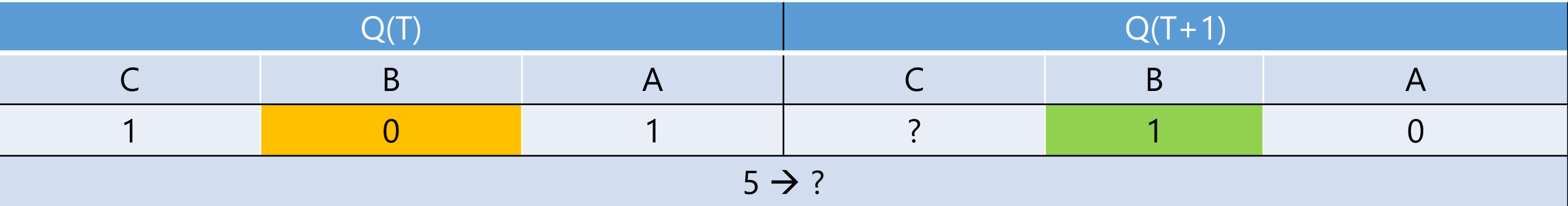

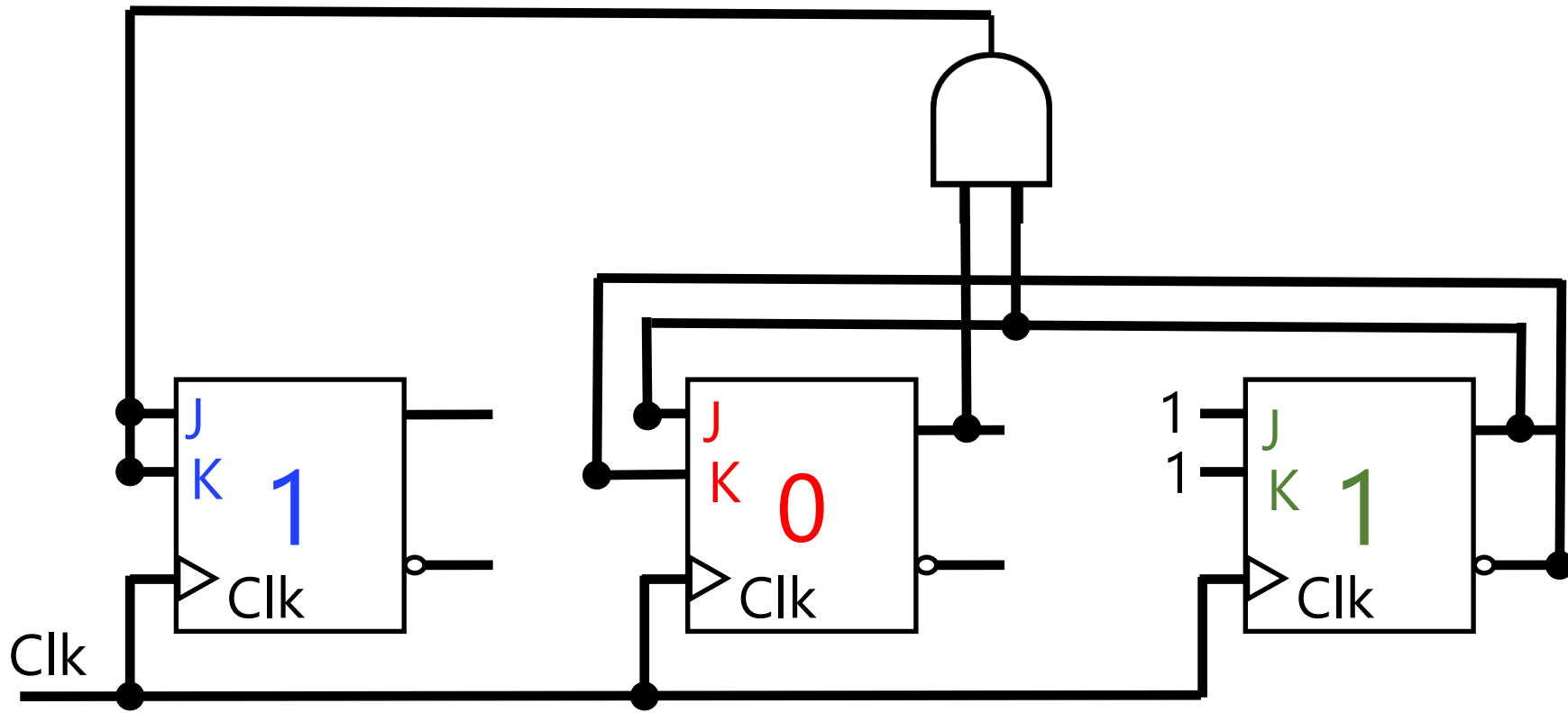


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	1	0
5 → ?					

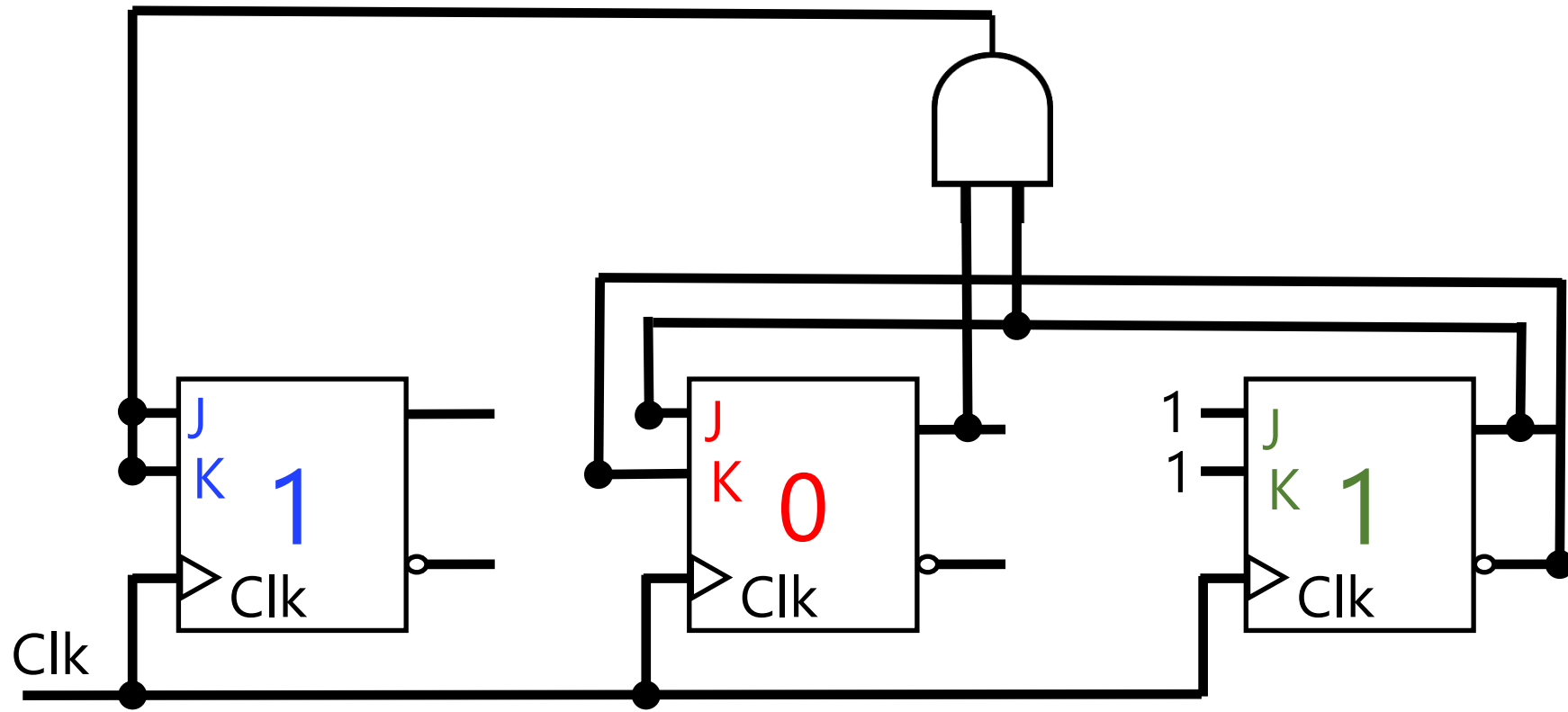

Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	$C=1, J_C=BA=01=0$ $K_C=BA=01=0$ ----- Store $\rightarrow 1$	1	0

5 \rightarrow ?

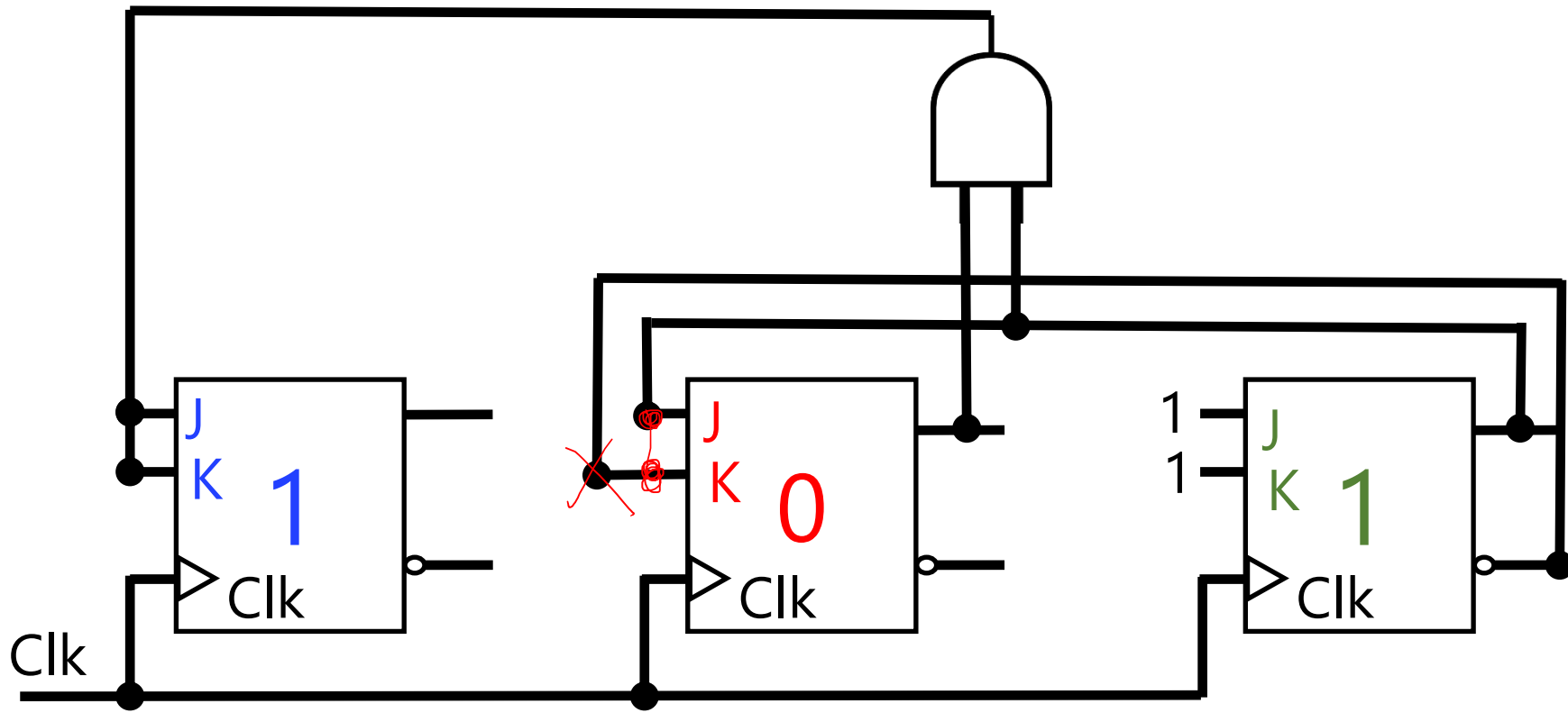

Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	1	1	0
0	1	0	0	0	1




Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
1. How many storage (flip-flops)? #FF
2. Form the state (transition) diagram
3. Form the state table
4. Fill the state table
5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
6. Input (excitation) equations for each FF
7. Minimization of input (excitation) equations
8. Draw/Sketch Logic Circuit
9. (Optional) Test

easy

Design (Recap)

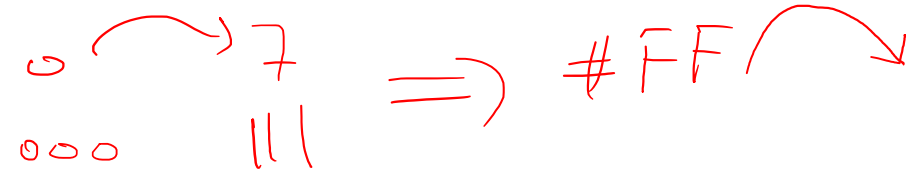0. Do we need combinational logic or sequential logic? Do we need memory?
1. How many storage (flip-flops)? #FF
2. Form the state (transition) diagram
3. Form the state table
4. Fill the state table
5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
6. Input (*excitation*) equations for each FF
7. Minimization of input (*excitation*) equations
8. Draw/Sketch Logic Circuit
9. (Optional) Test



Design (Advanced)

0. Do we need combinational logic or sequential logic? Do we need memory?

1. How many storage (flip-flops)? #FF

2. Form the state (transition) diagram

2.1. State Reduction

3. Form the state table

4. Fill the state table

5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed

6. Input (*excitation*) equations for each FF


7. Minimization of input (*excitation*) equations


8. Draw/Sketch Logic Circuit

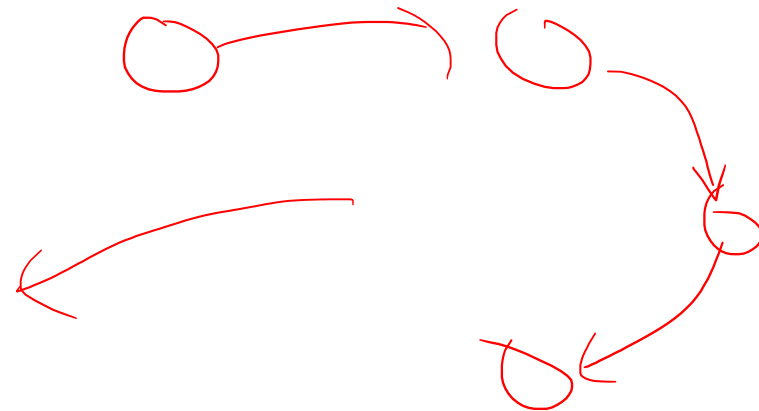9. (Optional) Test


Theory of Automata


COMP-2140: Computer Languages, Grammars, and Translators




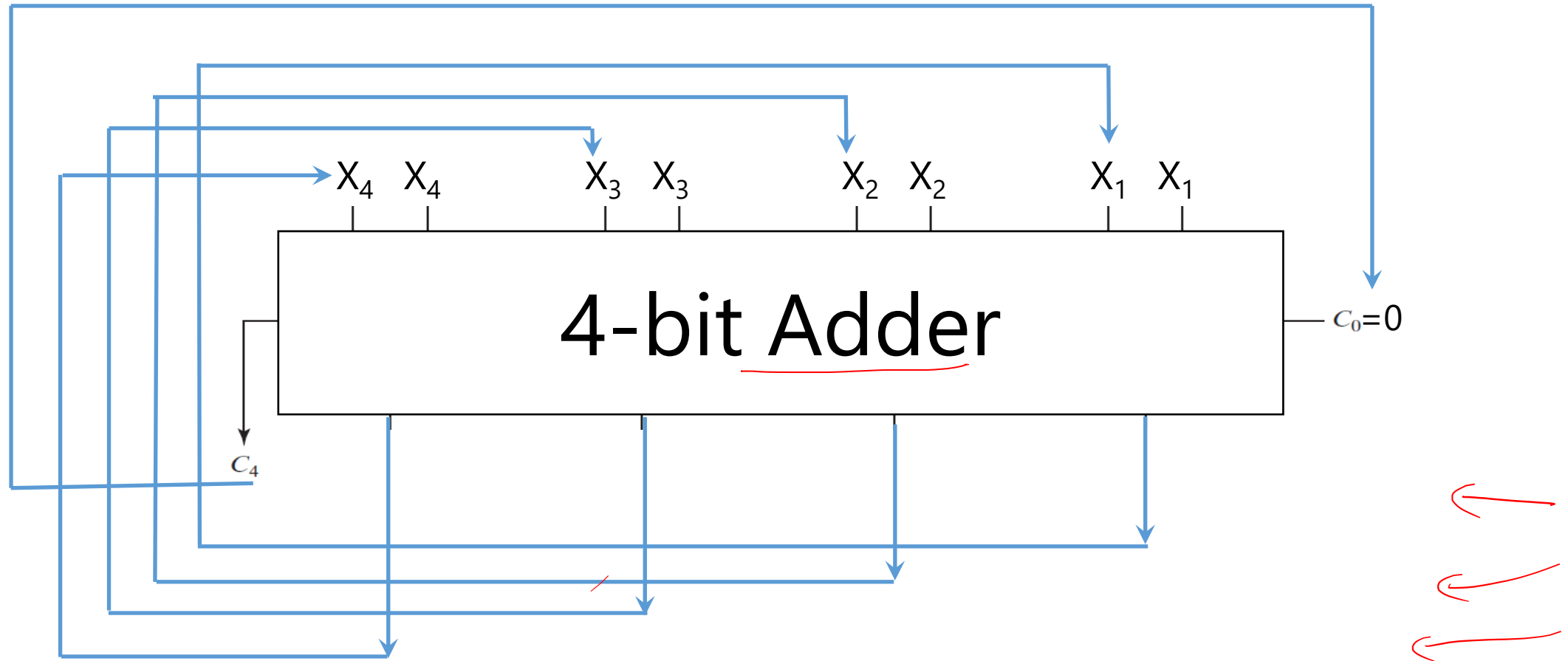

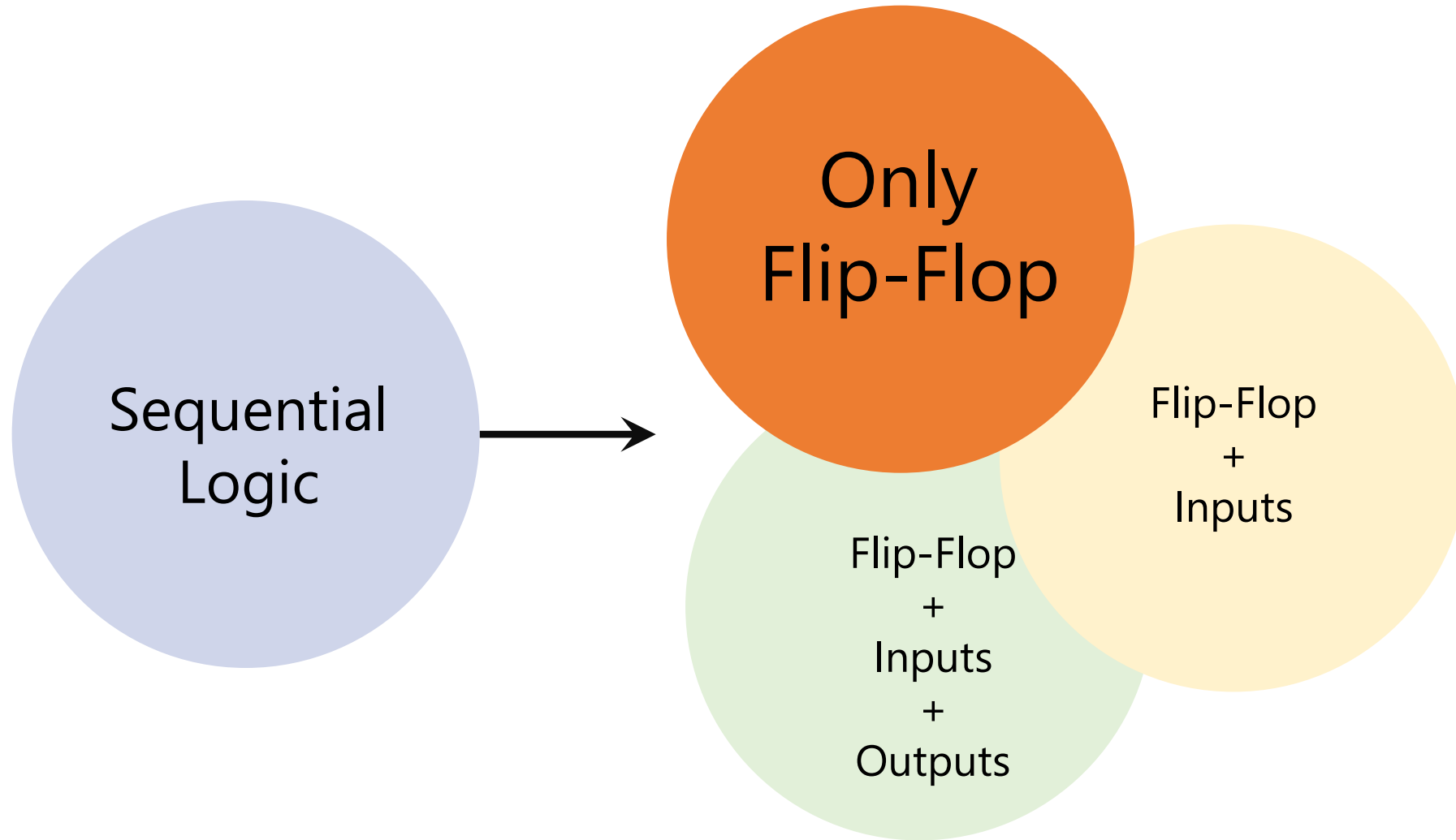
$X \times Y = X + \dots + X \rightarrow$ When to stop?
 Feedback \rightarrow Sequential Logic



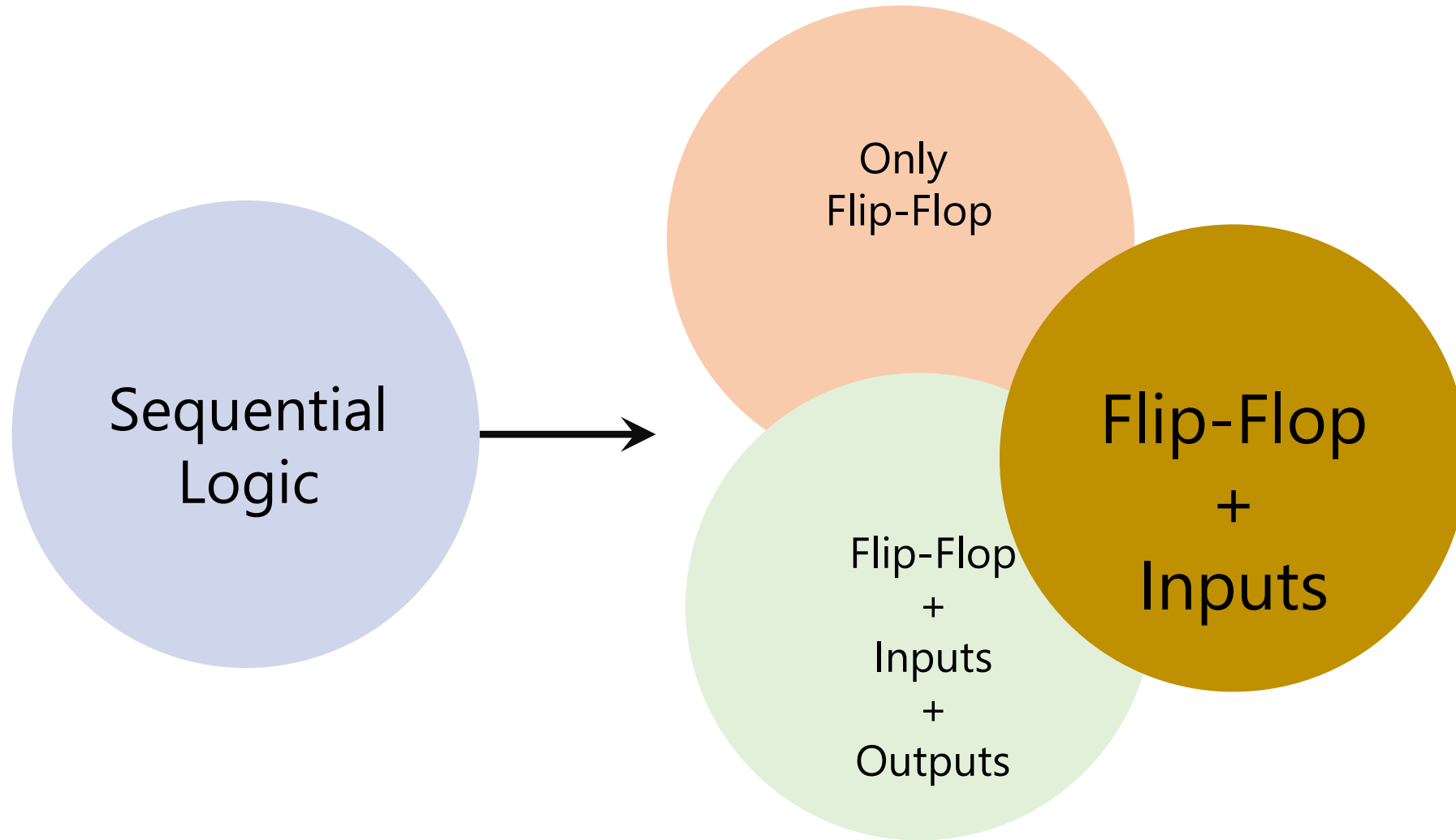

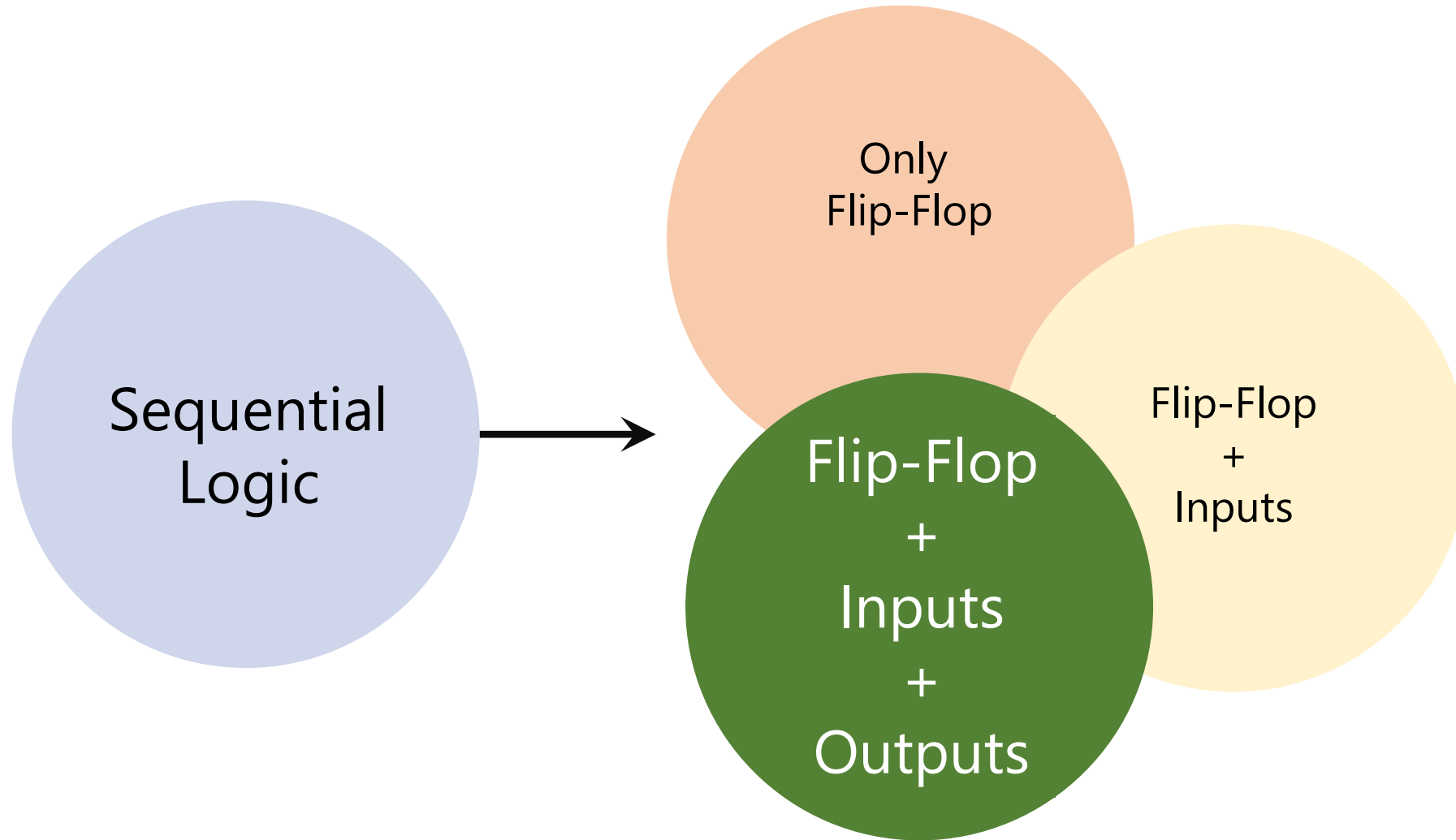

Analysis
vs.
Design

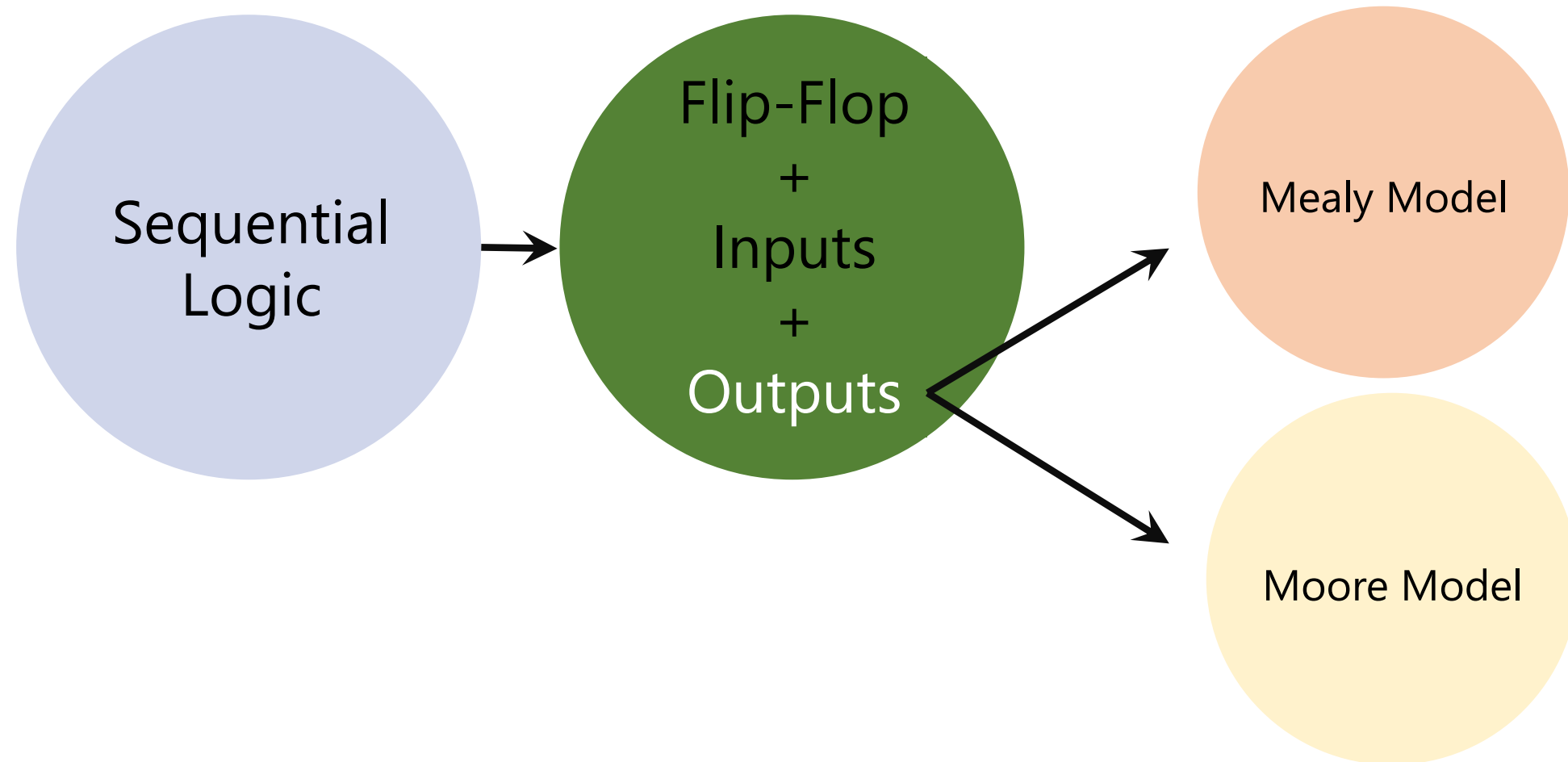



George H. Mealy


(1927 – 2010)

Mathematician and Computer Scientist

Invented Mealy Machine

Also a pioneer of modular programming

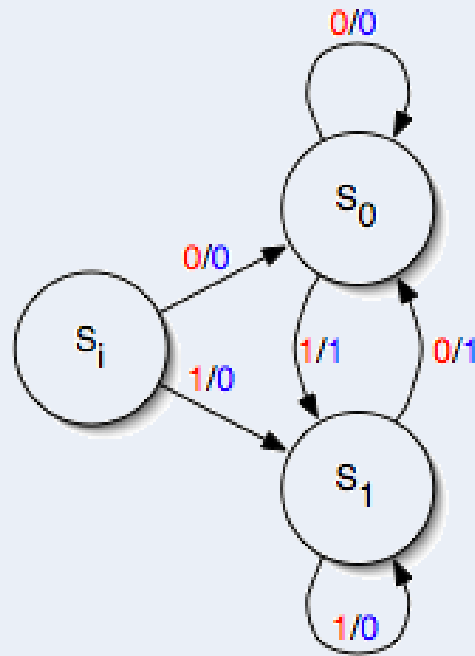Outputs = Function(Current State, Inputs)



Edward Forrest Moore


(1925 – 2003)

Mathematician and Computer Scientist

Inventor of the Moore Machine

Also an early pioneer of artificial life

Outputs = Function(Current State, ~~Inputs~~)

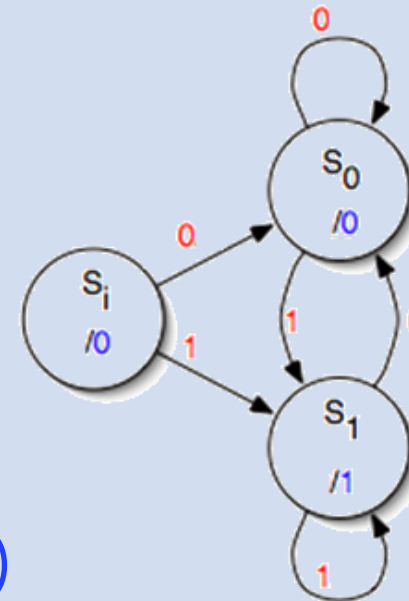


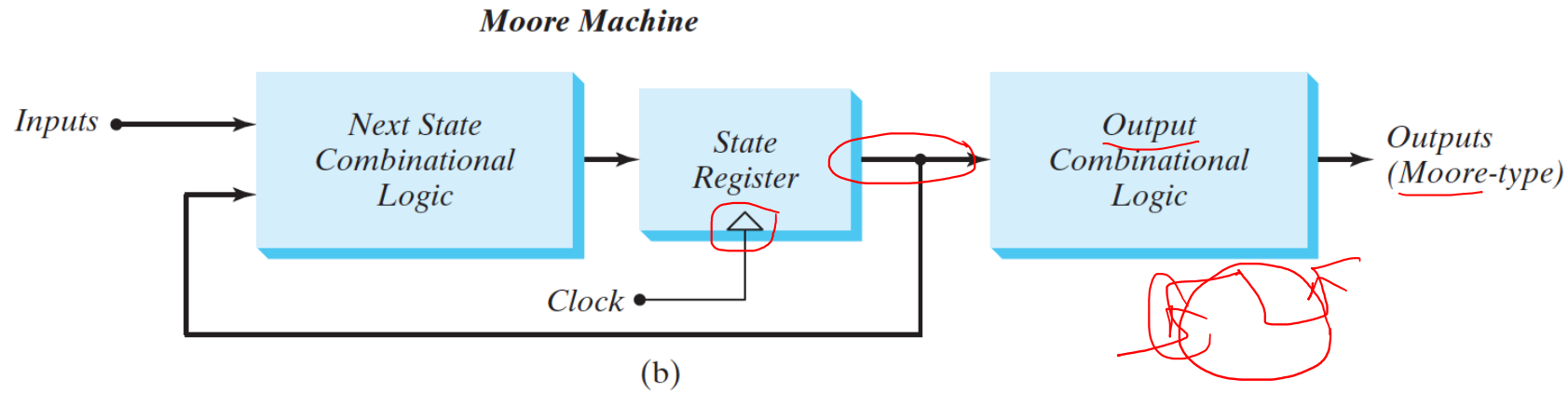


FIGURE 5.21
Block diagrams of Mealy and Moore state machines

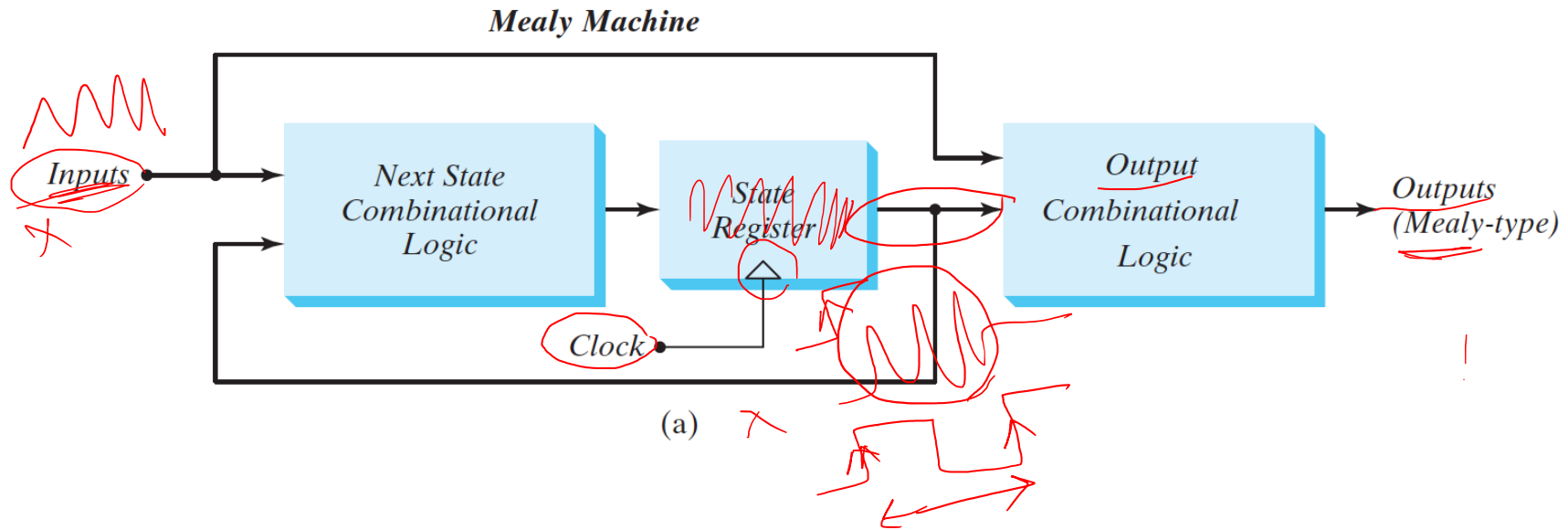

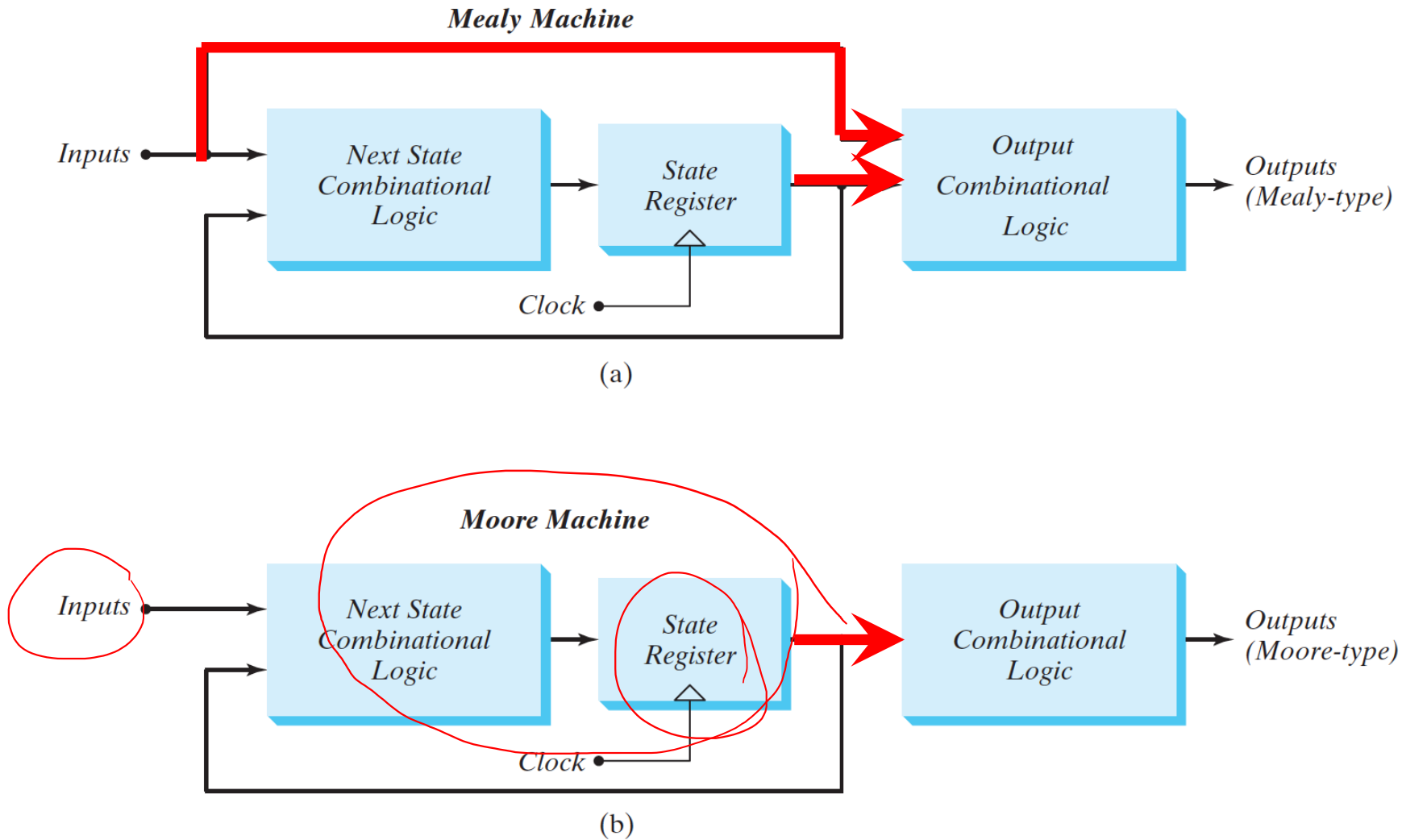


FIGURE 5.21
Block diagrams of Mealy and Moore state machines



Sequential
Logic

Flip-Flop
+
Inputs
+
Outputs

Mealy Model




Analysis (Moore model in output) by an example

Analysis (Recap)

0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? $2^{\#FF}$
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: $2^{\#FF}$
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-

Analysis (+ Input + Moore Model Output)

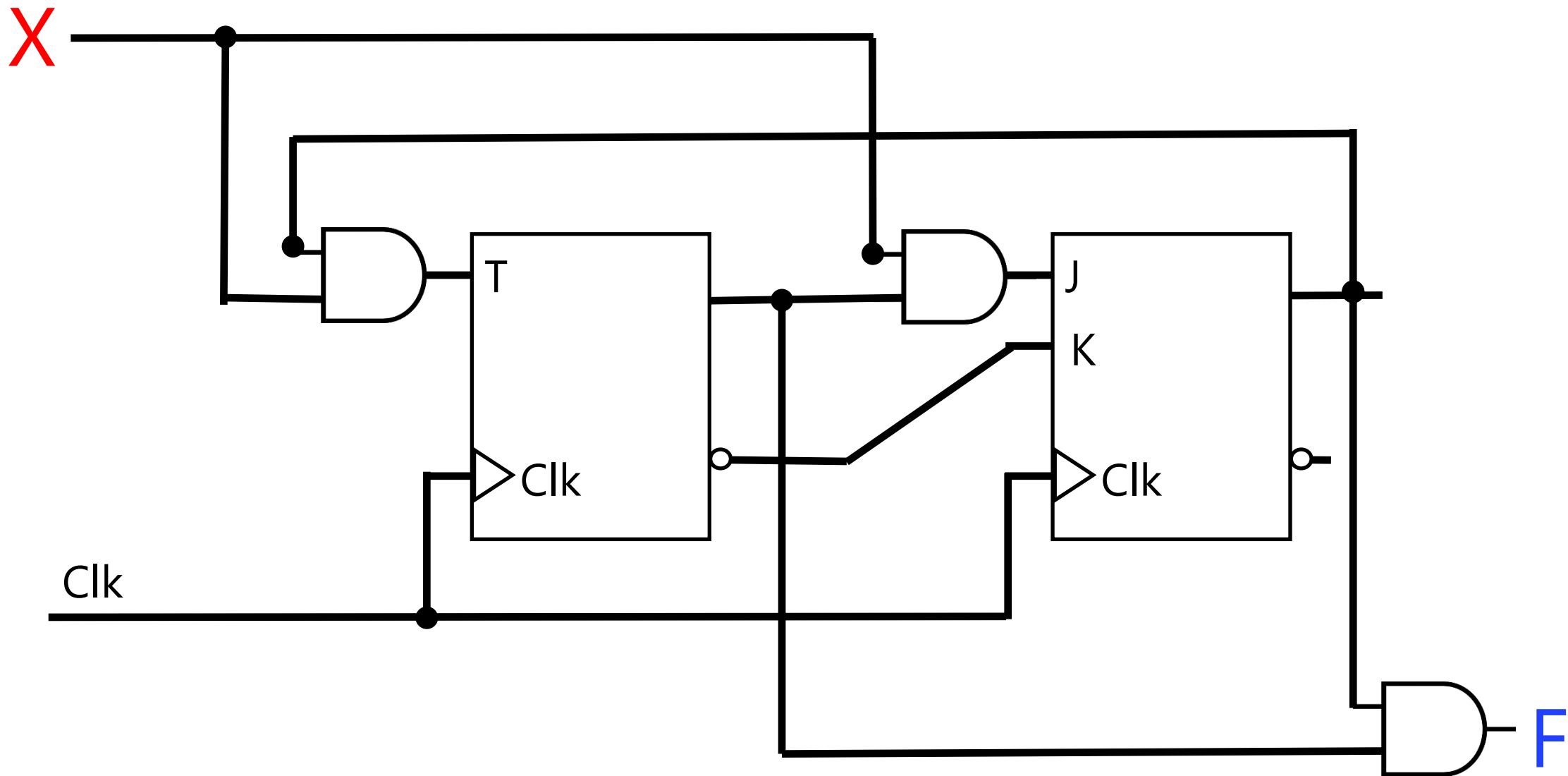0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? ~~$2^{\text{#FF}}$~~
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: ~~$2^{\text{#FF}}$~~
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-




Analysis (Recap)

0. Is the circuit sequential or combinational? Any FF or feedback → Sequential


Analysis (Recap)

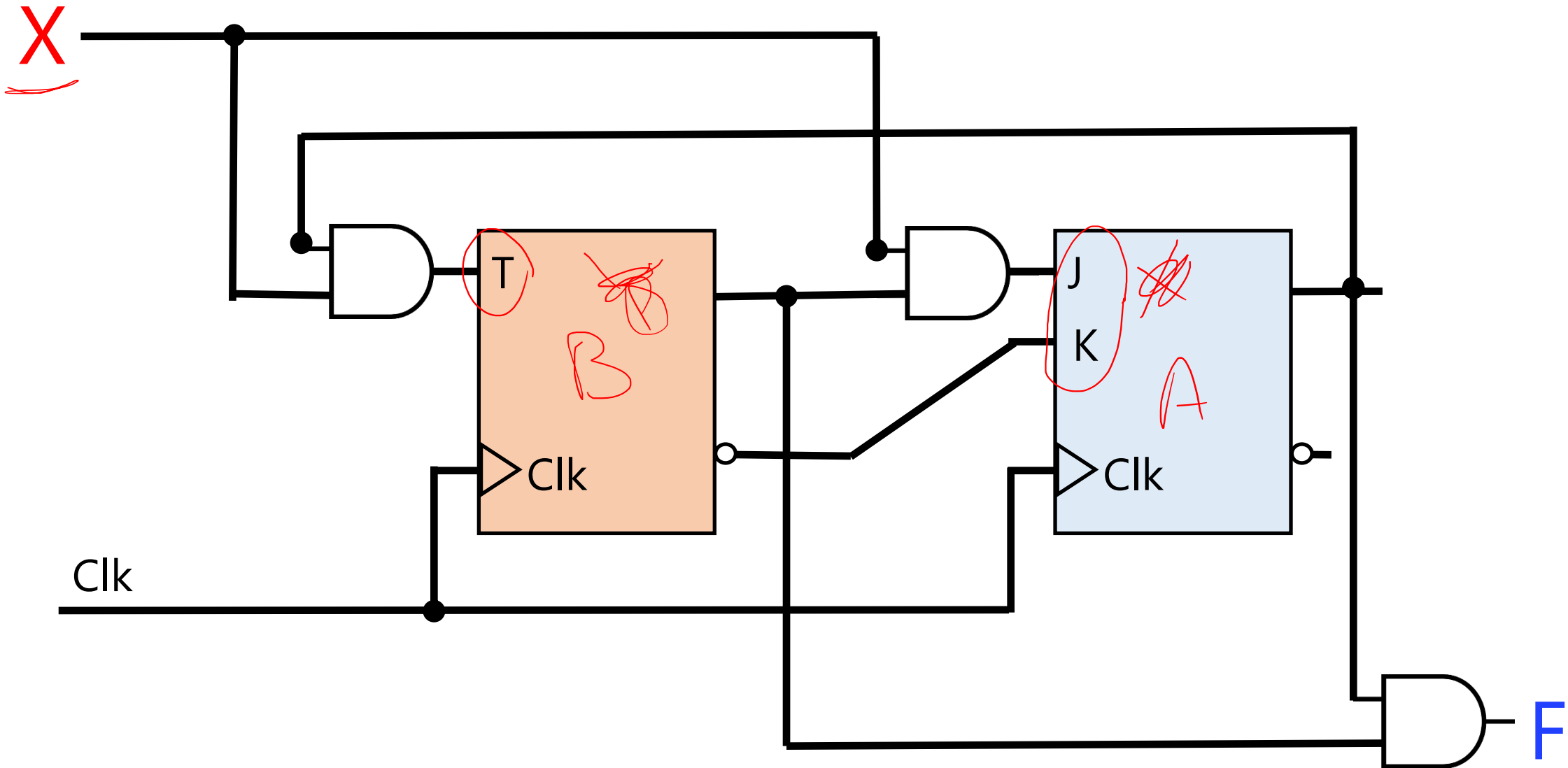- 0. Is the circuit sequential or combinational? **Sequential**
- 1. What are the flip-flops?



Analysis (Recap)

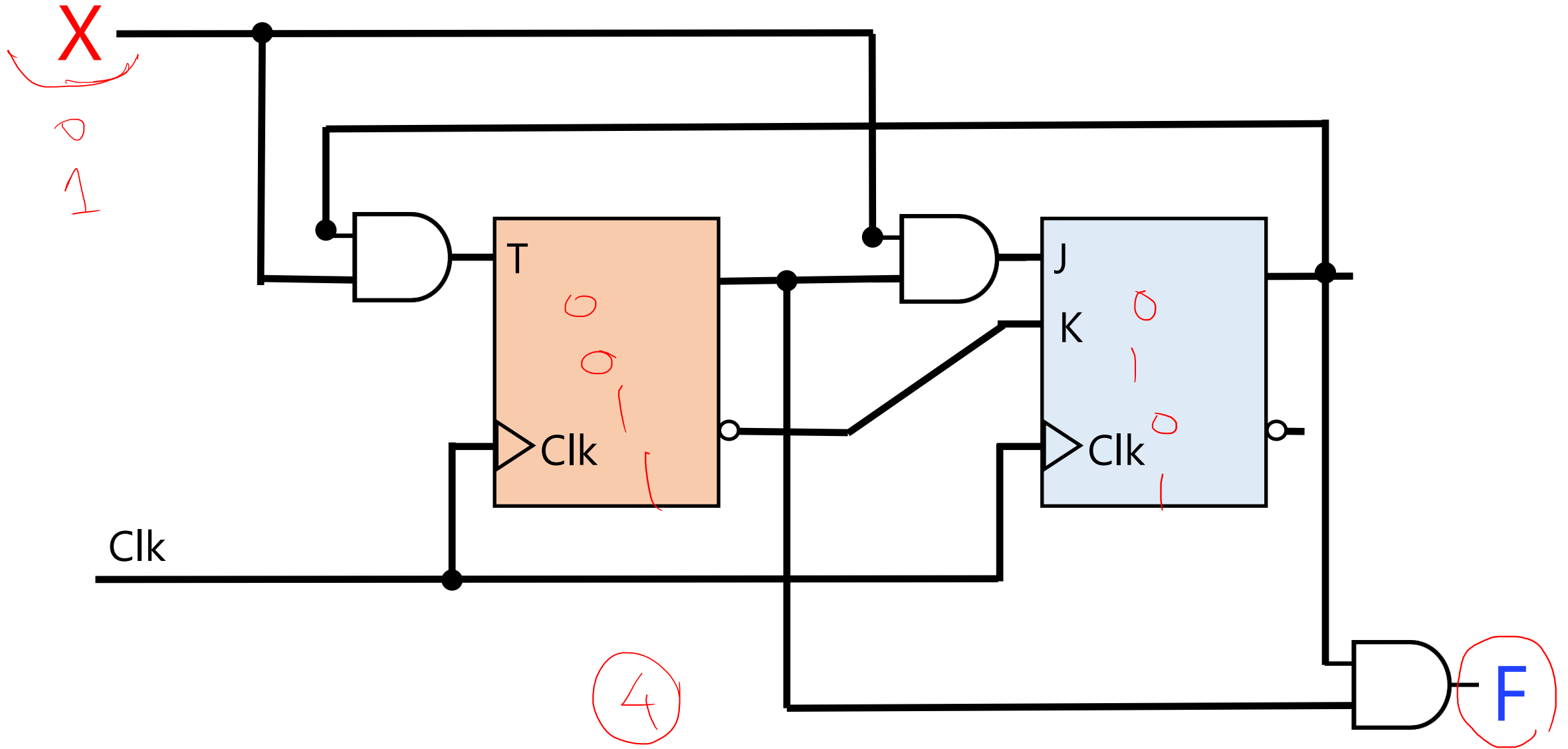0. Is the circuit sequential or combinational? Sequential
1. What are the flip-flops? T, JK
2. What are the state combinations?




#FFs + #Inputs = 2 + 1 $\rightarrow 2^3 = \underline{8}$ combinations

Analysis (Recap)

0. Is the circuit sequential or combinational? **Sequential**
 1. What are the flip-flops? **T, JK**
 2. What are the state combinations? $2^{\#FF} \times 2^{\#inputs} = 2^{\#FF + \#inputs} = 2^3 = 8$
 3. Form "State" table:
 - a) Columns:
 - For each FF, two columns: one for current state, one for next state
 - For each input, one column \Rightarrow left
 - For each output, one column \Rightarrow right
 - b) Rows: See item 2
-

[illegible]

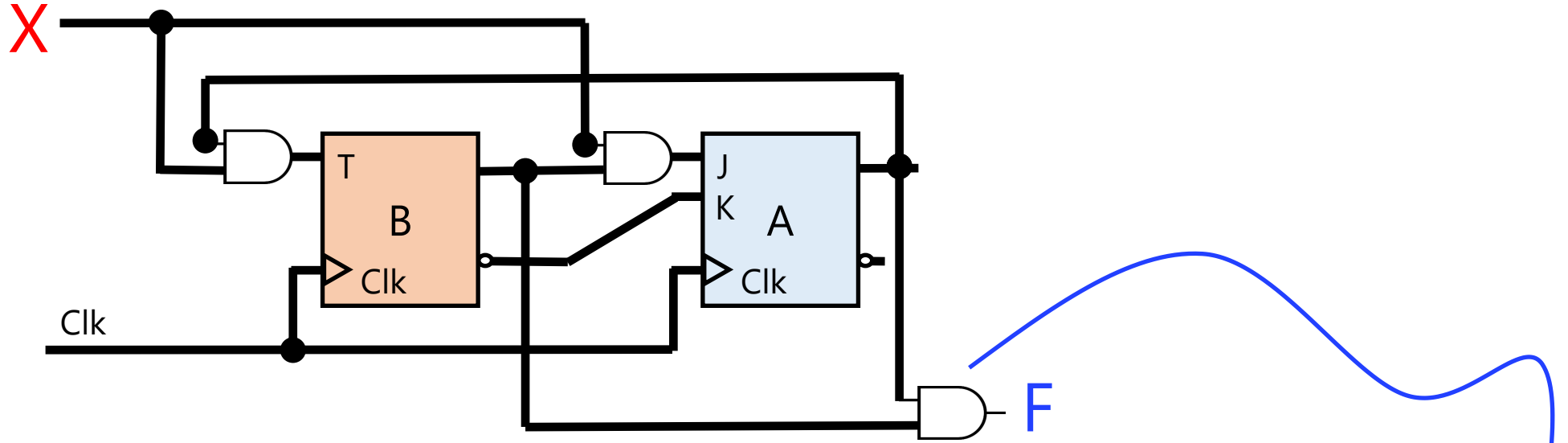


Q(T)		Q(T+1) when X=0		Q(T+1) when X=1		Outputs
B	A	B	A	B	A	F
						Moore model: does not depend on X


Alternative State Table

Analysis (Recap)

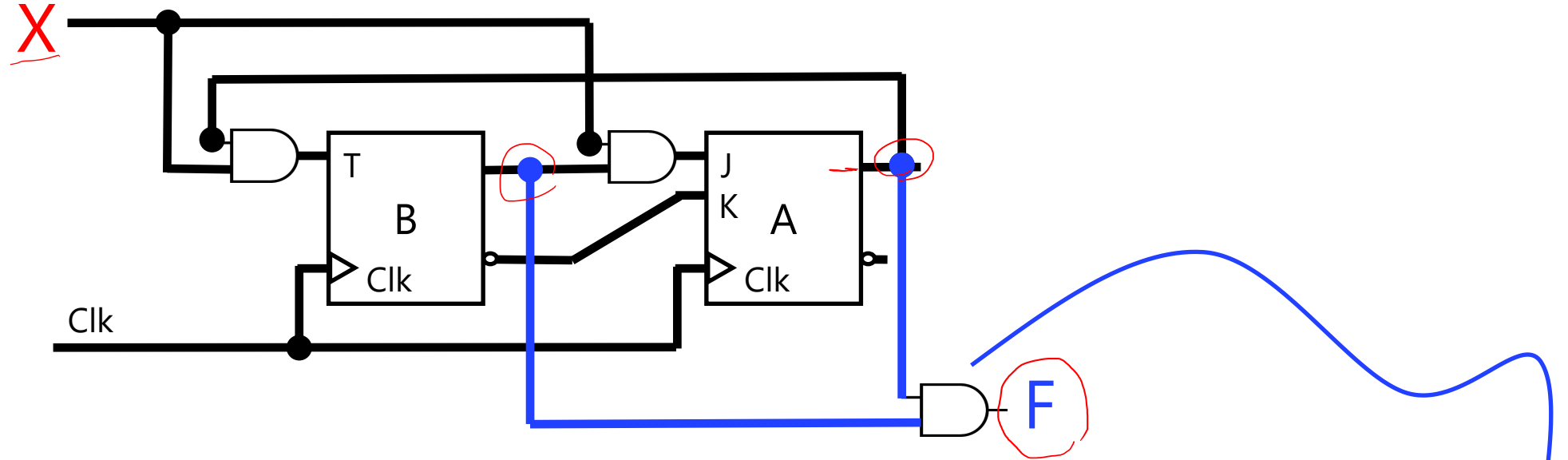
0. Is the circuit sequential or combinational? Sequential
 1. What are the flip-flops? T, JK
 2. What are the state combinations? $2^{\#FF} \times 2^{\#inputs} = 2^{\#FF+\#inputs} = 2^3 = 8$
 3. Form "State" table:
 - a) Columns:
 - For each FF, two columns: one for current state, one for next state
 - For each input, one column
 - For each output, one column
 - b) Rows: See item 2
 4. Fill the state table for
 - a) next state columns
 - b) the output value
-




Inputs	Q(T)		Q(T+1)		Outputs
<u>X</u>	B	A	B	A	$F=BA$
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

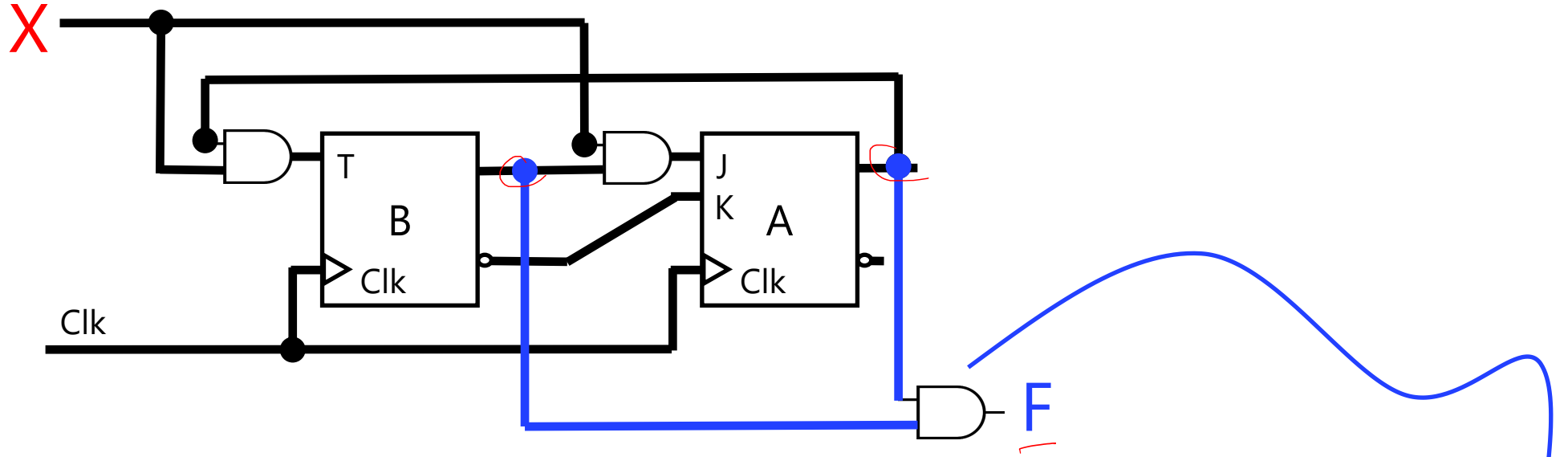


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	<u>F=BA</u>
0	<u>0</u>	<u>0</u>			<u>0</u>
0	<u>0</u>	<u>1</u>			<u>0</u>
0	1	0	Moore Model Only depends on current state X is not involved!		0
0	<u>1</u>	<u>1</u>			<u>1</u>
1	0	0			0
1	0	1			0
1	1	0			0
1	<u>1</u>	<u>1</u>			<u>1</u>

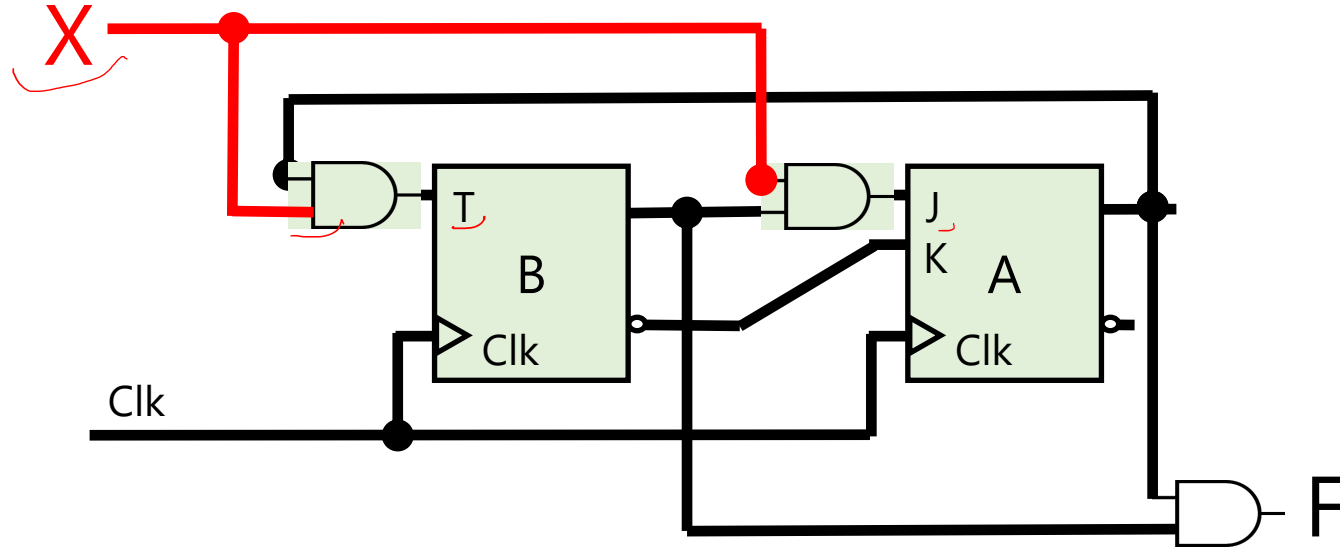


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

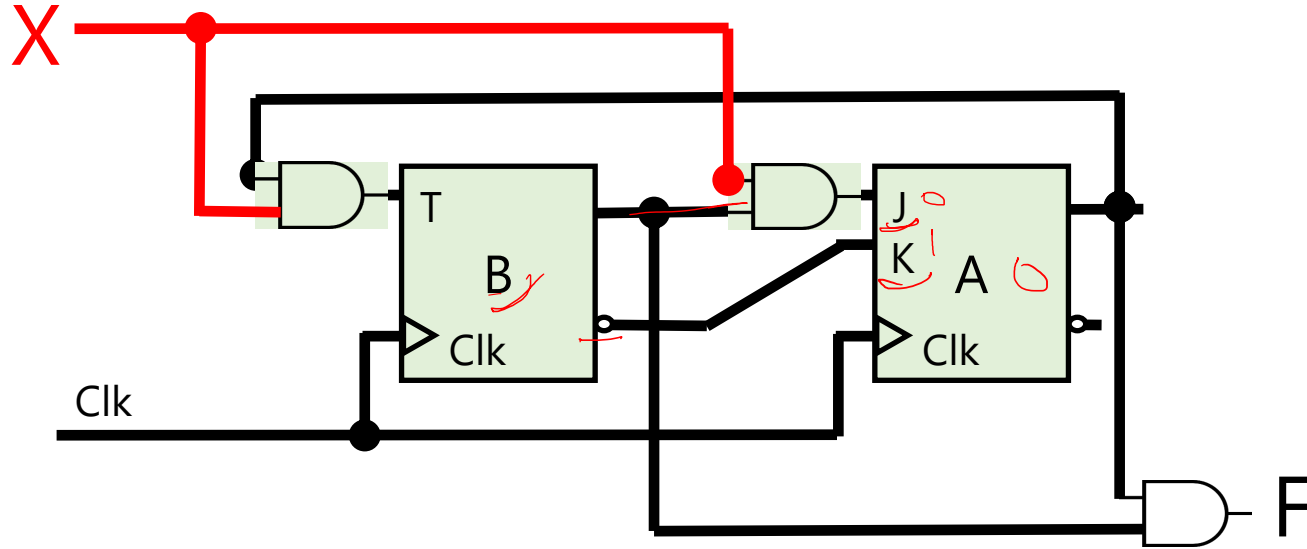


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
<u>0</u>	<u>0</u>	<u>0</u>		A=0 $J_A = XB = 00 = 0$ $K_A = B' = 0' = 1$ ----- Reset $\rightarrow 0$	0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0

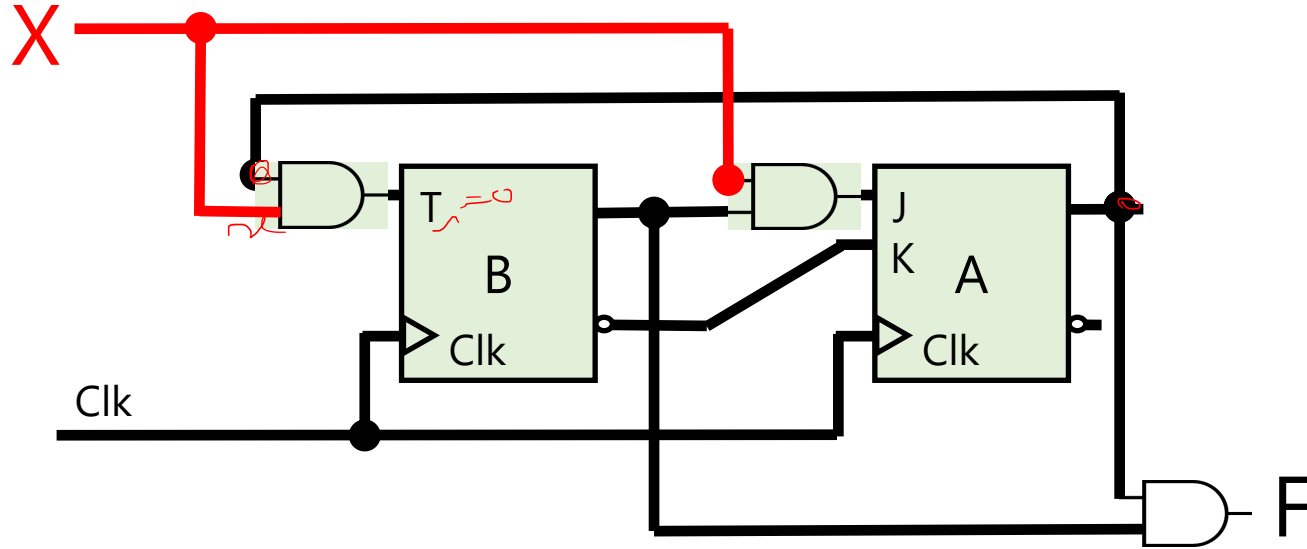


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	$F = BA$
<u>0</u>	0	<u>0</u>	$B = 0$ $T_B = \underline{XA} = 00 = 0$ ----- Store \rightarrow <u>0</u>	0	0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0
1	0	1			0

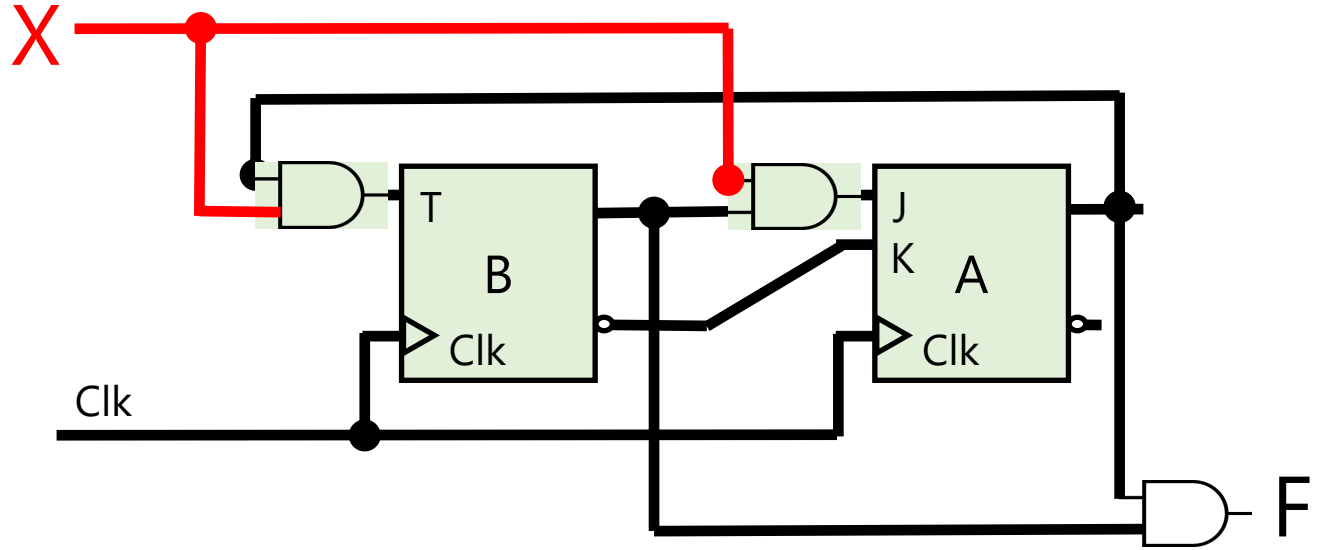


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0	0	0	0
0	0	1			0
0	1	0			0
0	1	1			1
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

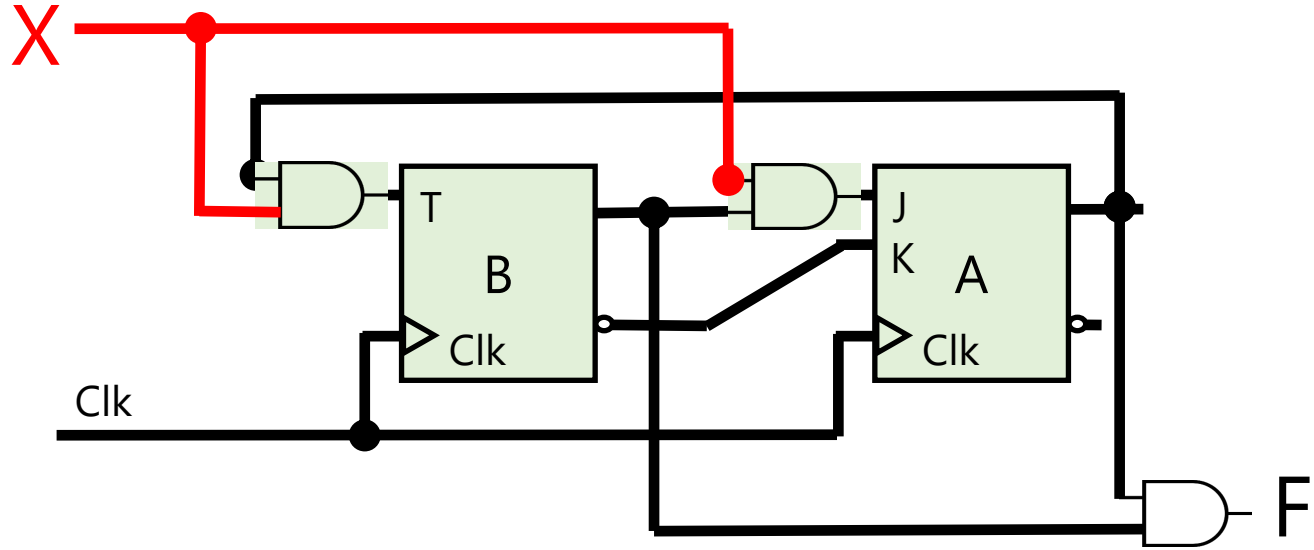

Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	?	0	0
1	1	0	1	1	0
1	1	1	0	1	1

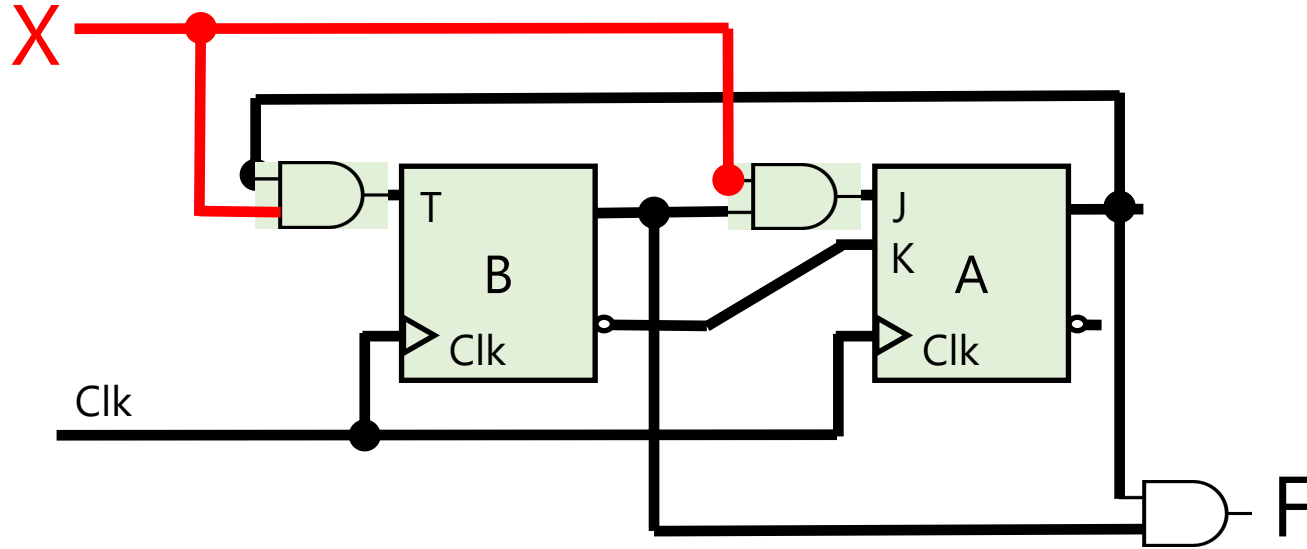



Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	B=0 TB=XA=11=1 ----- Comp. \rightarrow 1		0

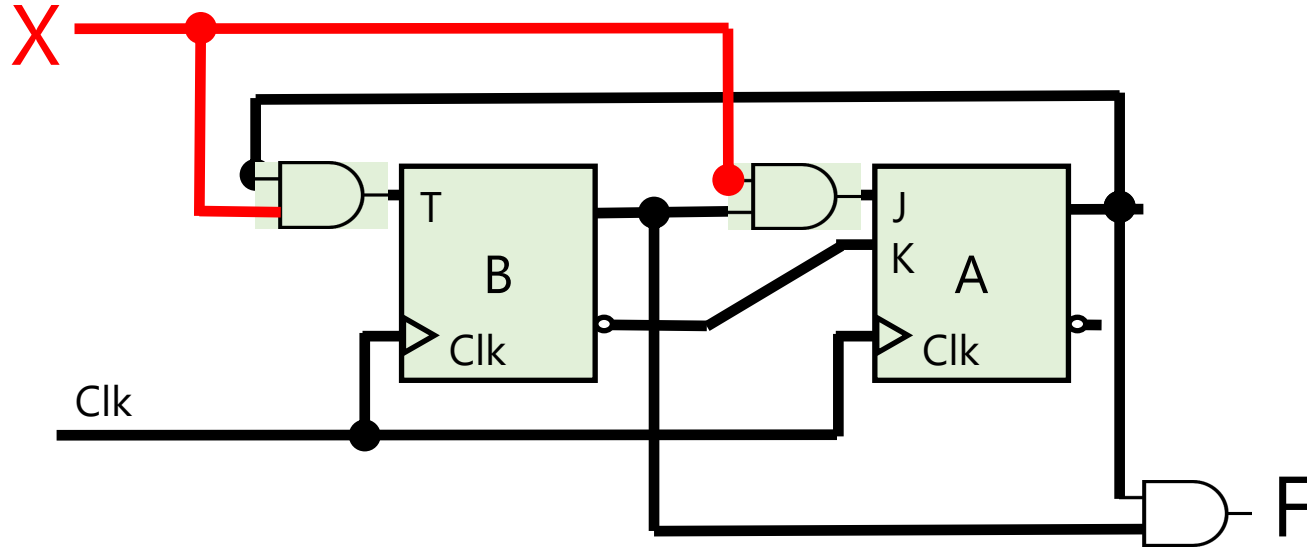


Inputs	Q(T)		Q(T+1)		Outputs
X	B	A	B	A	F=BA
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	0	1	1

Analysis (Recap)

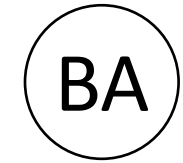
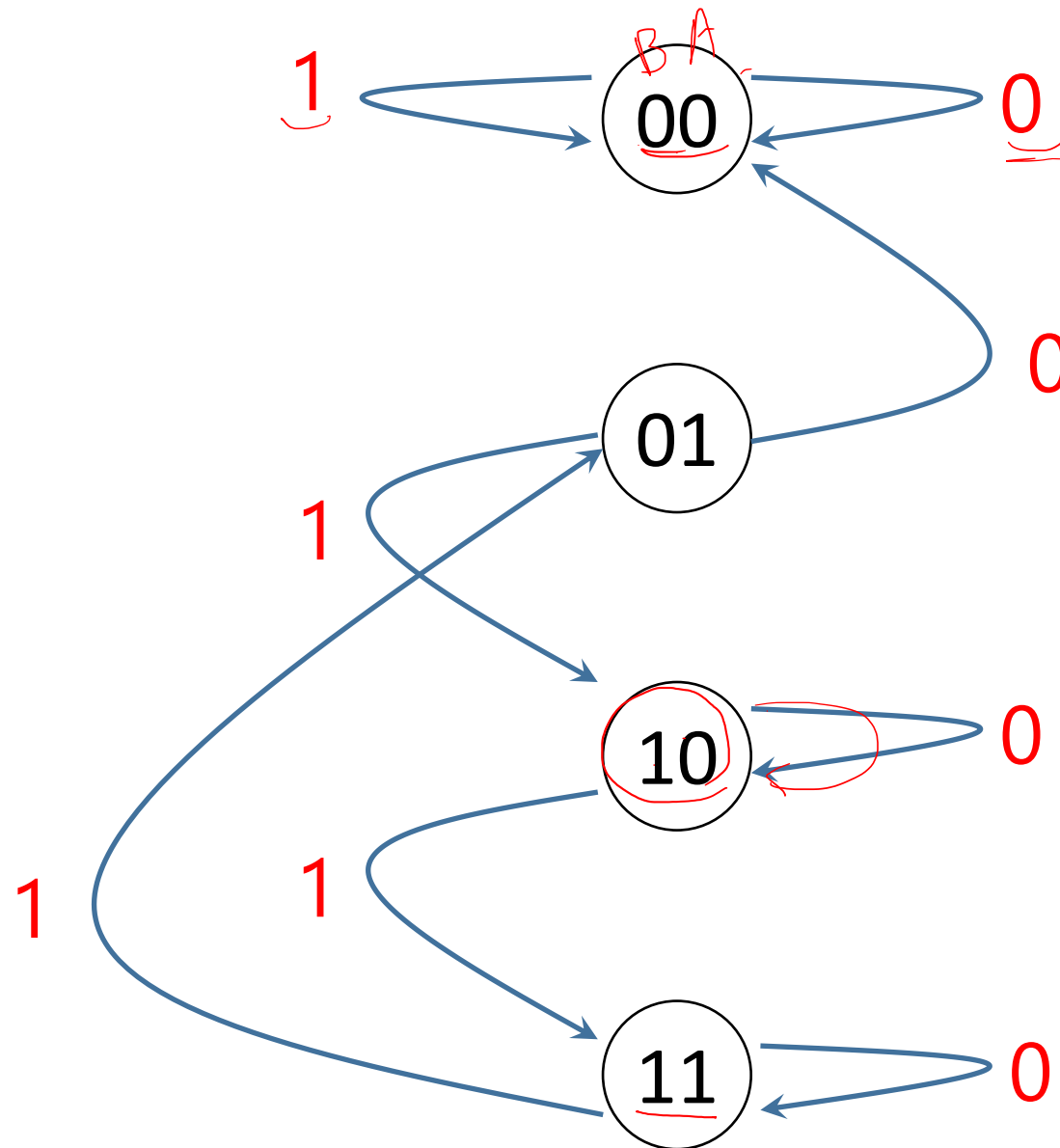
0. Is the circuit sequential or combinational? Sequential
 1. What are the flip-flops? T, JK
 2. What are the state combinations? $2^{\#FF} \times 2^{\#inputs} = 2^{\#FF+\#inputs} = 2^3 = 8$
 3. Form "State" table:
 - a) Columns:
 - For each FF, two columns: one for current state, one for next state
 - For each input, one column
 - For each output, one column
 - b) Rows: See item 2
 4. Fill the state table for
 - a) next state columns
 - b) the output value
 5. Form state (transition) diagram
 - a) nodes for states, directed edges for transitions between states
 - b) labels for edges by the value of input
 - c) labels for nodes by the value of output
-



Labels on edges
based on value of **X**

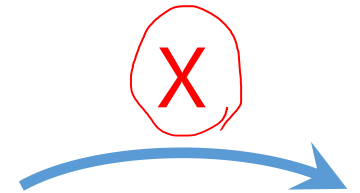

Labels on nodes
based on value of **F**

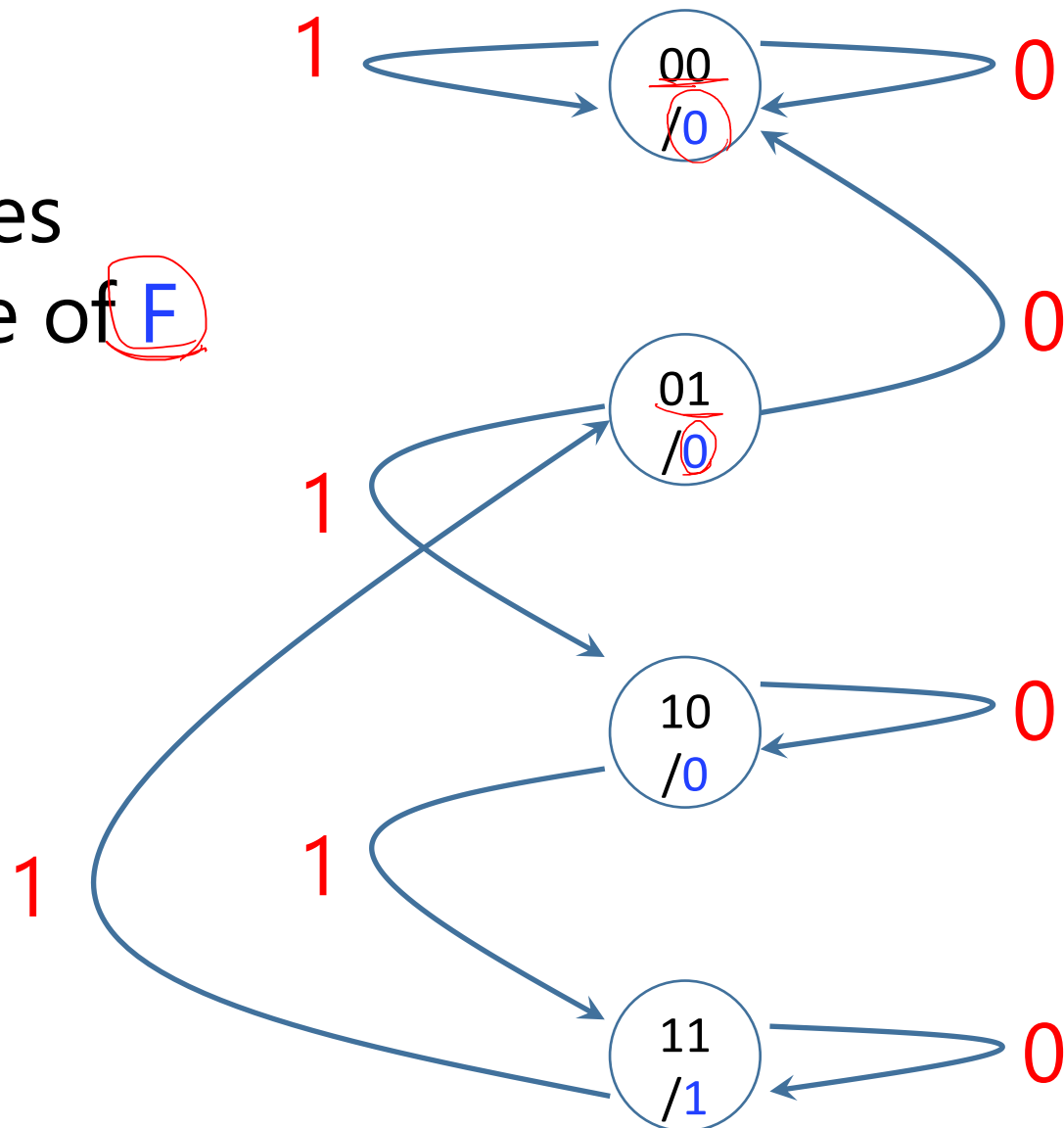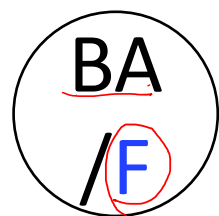

Analysis

6) (*Optional*) Path on State Transitions

Life lock!

