


SOP \Rightarrow ~~ANDs~~ \rightarrow OR

POS \Rightarrow ~~ORs~~ \rightarrow AND

OR
AND

GATE

UNIVERSALITY

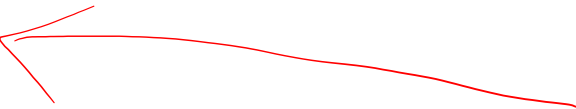
 $\{ \text{NOT, AND, OR, NAND, NOR, XOR, XNOR} \}$

UNIVERSAL SET

Is it possible to implement **ALL** the possible Boolean functions using **NOT, AND, OR, NAND, NOR**? **Yes!**

UNIVERSAL SET

What if we are not given some!

What if some are very costly! E.g., NOT

Can we reduce this set? E.g., building NOT by NAND/ NOR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR }	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR
{NOT, OR}	If we could design AND
→ {NOT}	If we could design AND, OR
→ {AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR
{NOT, OR}	If we could design AND
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

UNIVERSAL SET

{NOT, AND}



Augustus De Morgan
(1806–1871)

Mathematician
Logician

DE MORGAN'S LAWS

► $(Y + X) = Y'X'$

Hand-drawn red annotations on the equation $(Y + X) = Y'X'$. A red circle is drawn around the plus sign (+) in the left-hand side. A red arrow points from the plus sign to the prime symbol (') on the right-hand side. Another red arrow points from the prime symbol on the right-hand side back to the plus sign.



Augustus De Morgan
(1806–1871)


Mathematician
Logician


DE MORGAN'S LAWS

► $(Y + X)' = Y'X'$


$((Y + X)')' = (Y'X')'$

$Y + X = (Y'X')'$

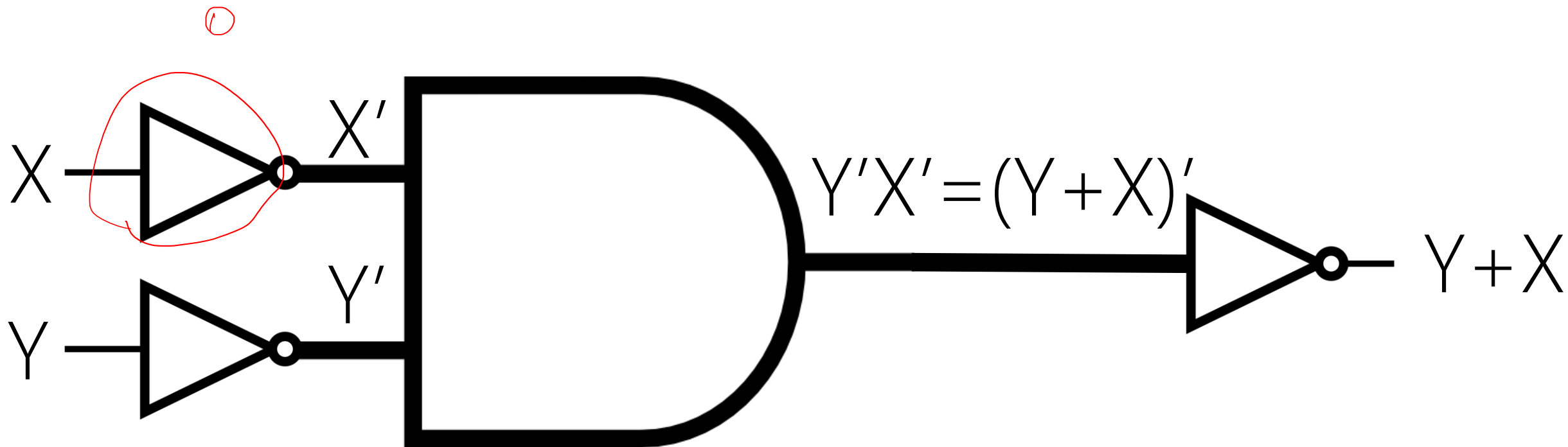

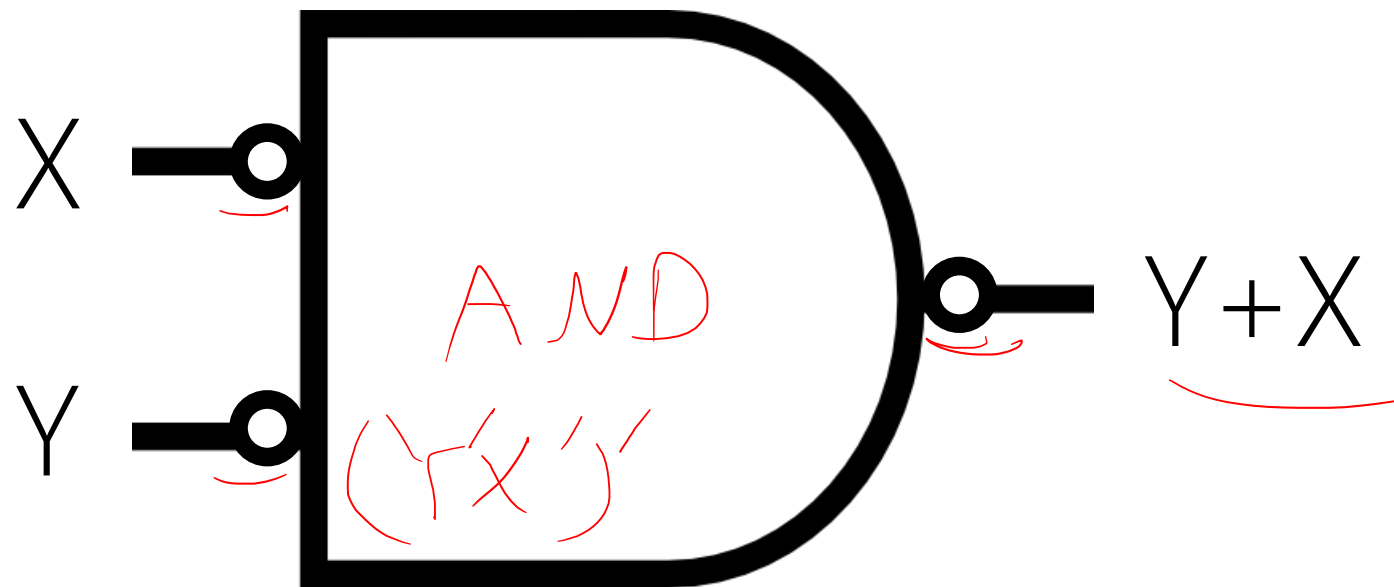

OR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
 {NOT, AND} ✓	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

UNIVERSAL SET

{NOT, OR}

AND



Augustus De Morgan
(1806–1871)

Mathematician
Logician

DE MORGAN'S LAWS

► $\underline{Y'} + \underline{X'} = (\underline{YX})$



Augustus De Morgan
(1806–1871)


Mathematician
Logician


DE MORGAN'S LAWS

► $Y' + X' = (YX)'$



$$(Y' + X')' = ((YX)')'$$

$$(Y' + X')' = YX$$

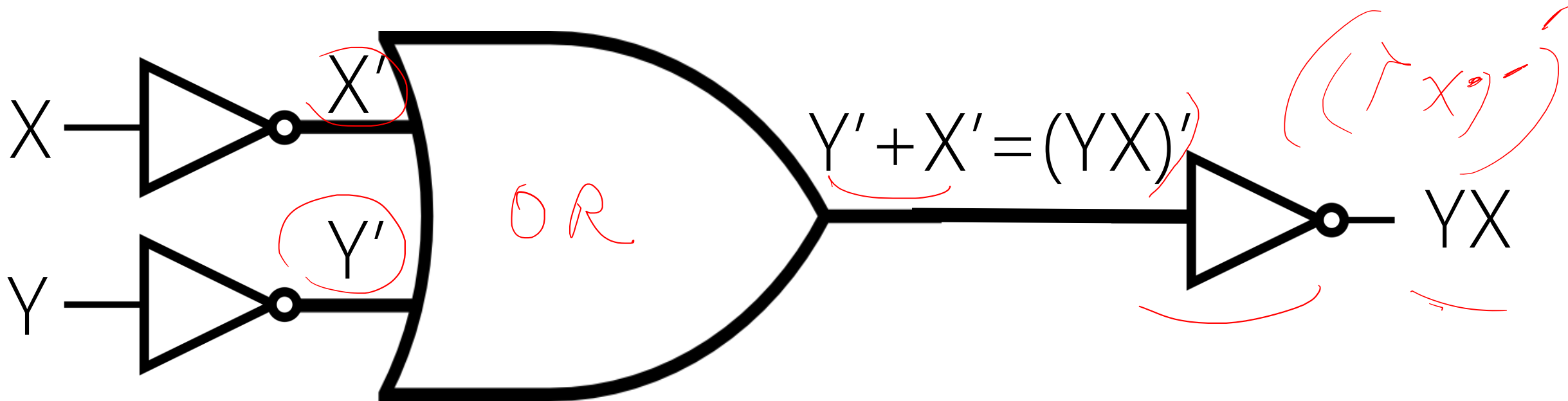

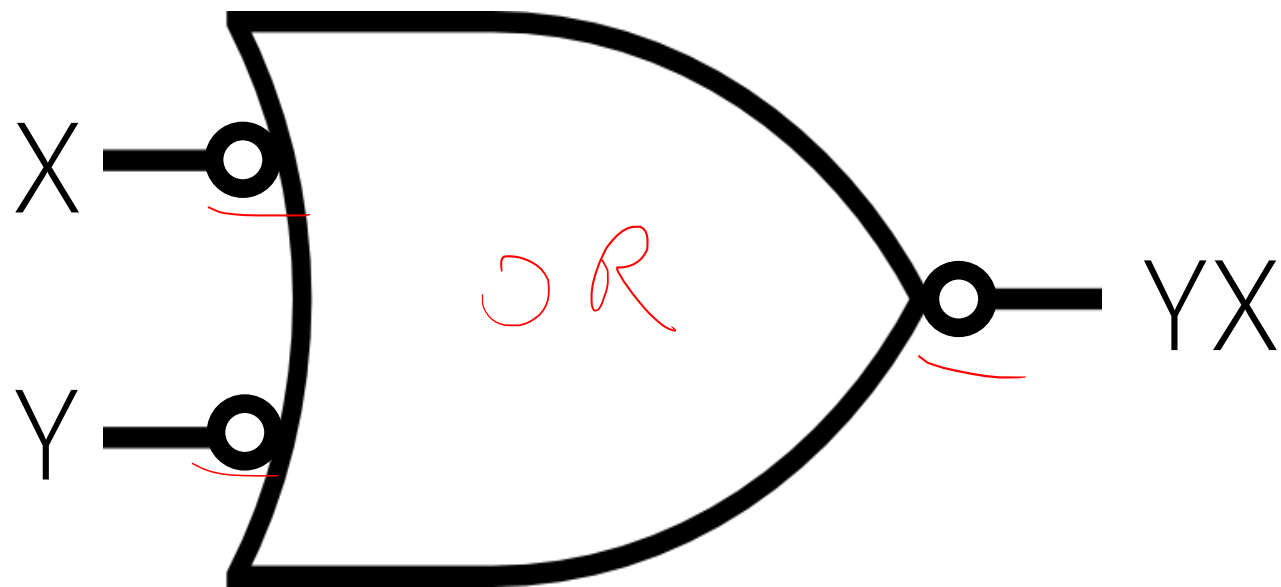

POS

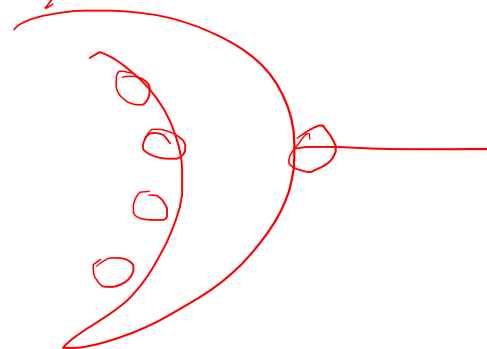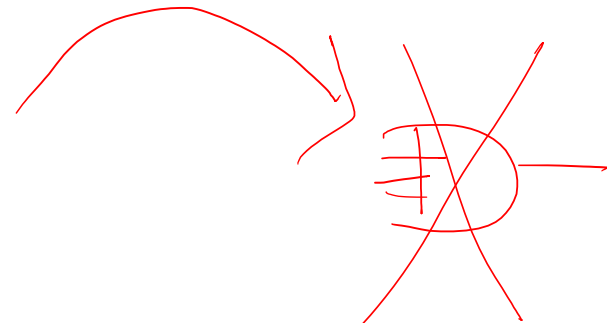


→ AND


SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

$$\text{NOT} \blacktriangleright (\underbrace{XX}_X)' = (X \uparrow X) = \underbrace{X'}_{X'}$$

NOT (AND)

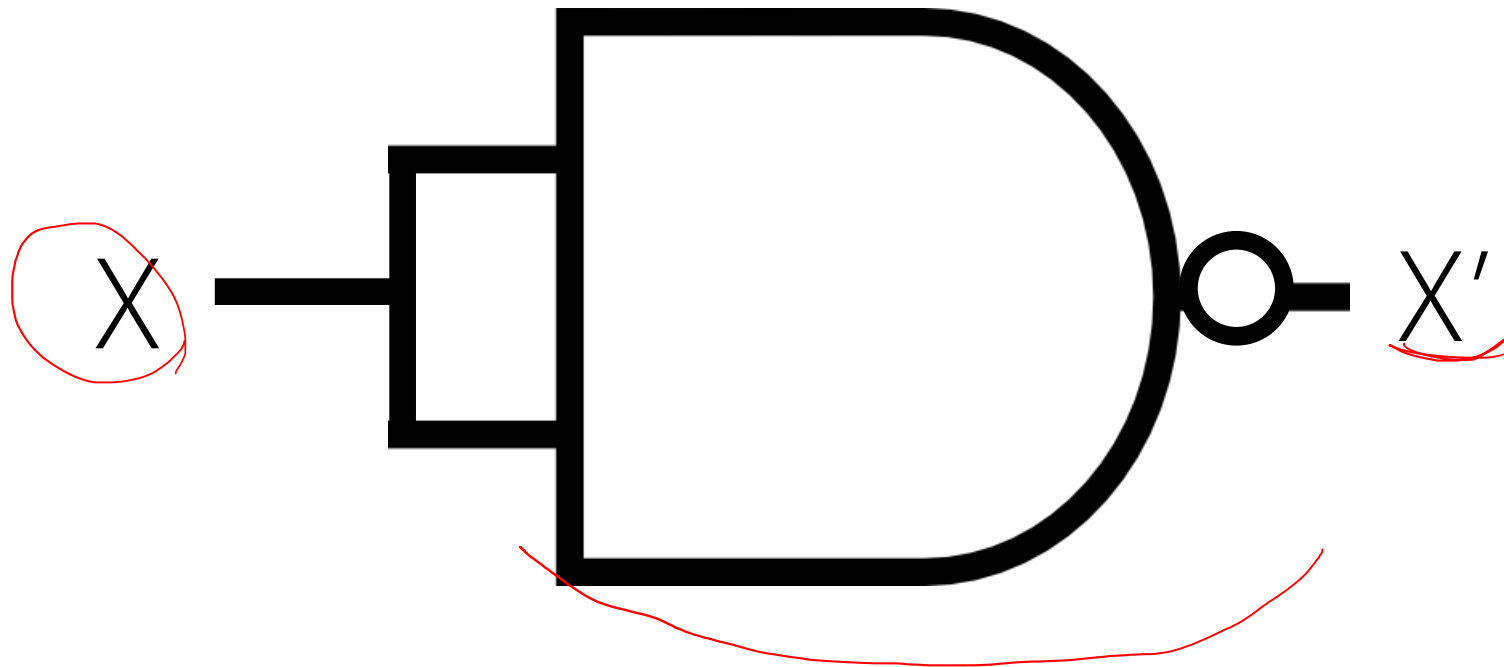
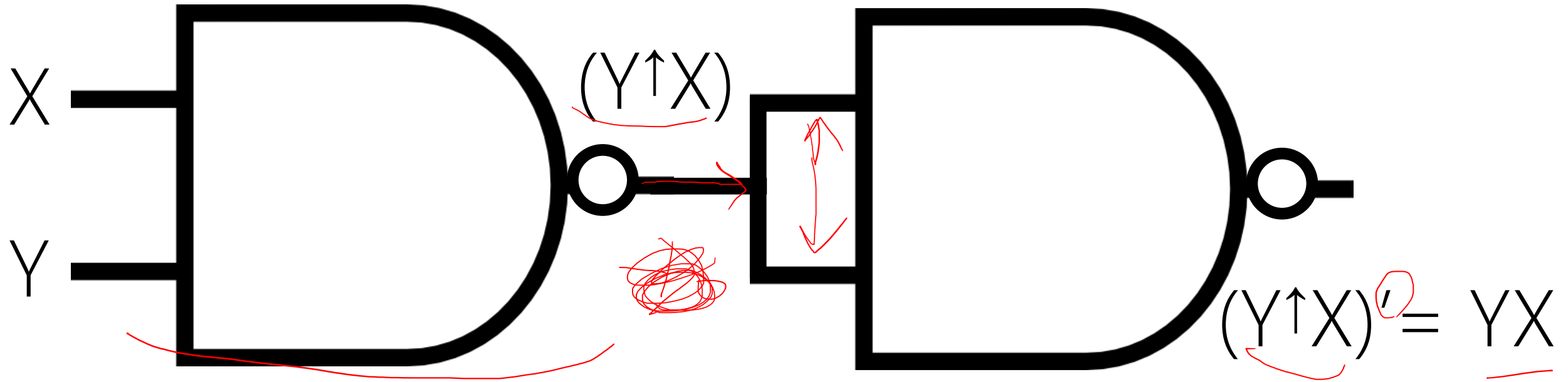
$$\text{AND} \blacktriangleright \text{NOT (NAND)} = ((Y \uparrow X))' = YX$$



OR ► DE MORGAN'S LAW

NAND → NOT } OR ✓
 → AND }


$$(Y + X)' = Y'X'$$

$$((Y + X)')' = (Y'X')'$$

$$\underline{Y + X} = (Y'X')'$$

$$\underline{Y + X} = \underline{Y' \uparrow X'}$$

OR: DE MORGAN'S LAW

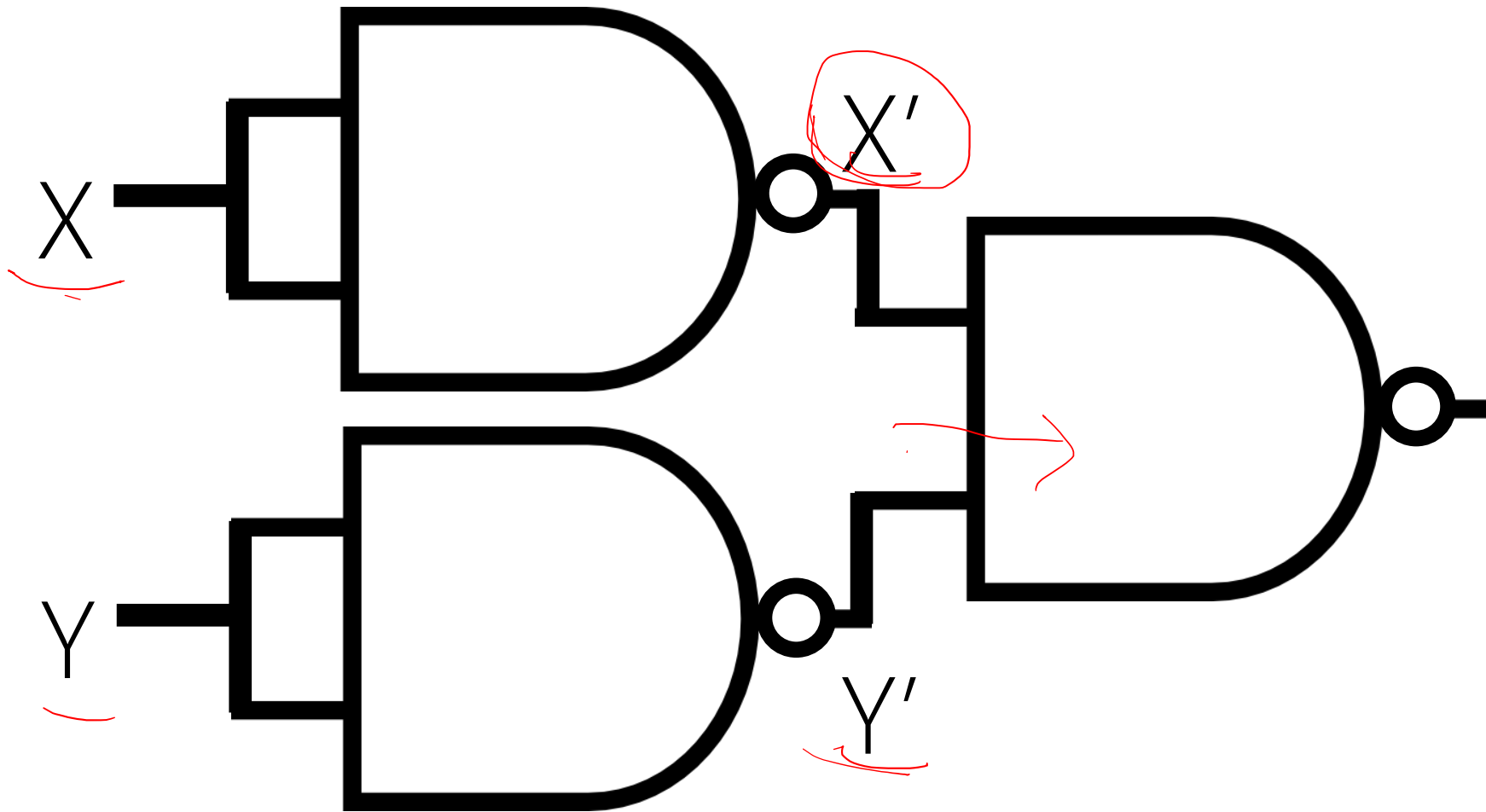




$$\begin{aligned} (Y'X')' &= \\ Y' \uparrow X' &= \\ \underline{Y + X} \end{aligned}$$

UNIVERSAL GATE


{NAND}

7400 Quad 2-input NAND Gates

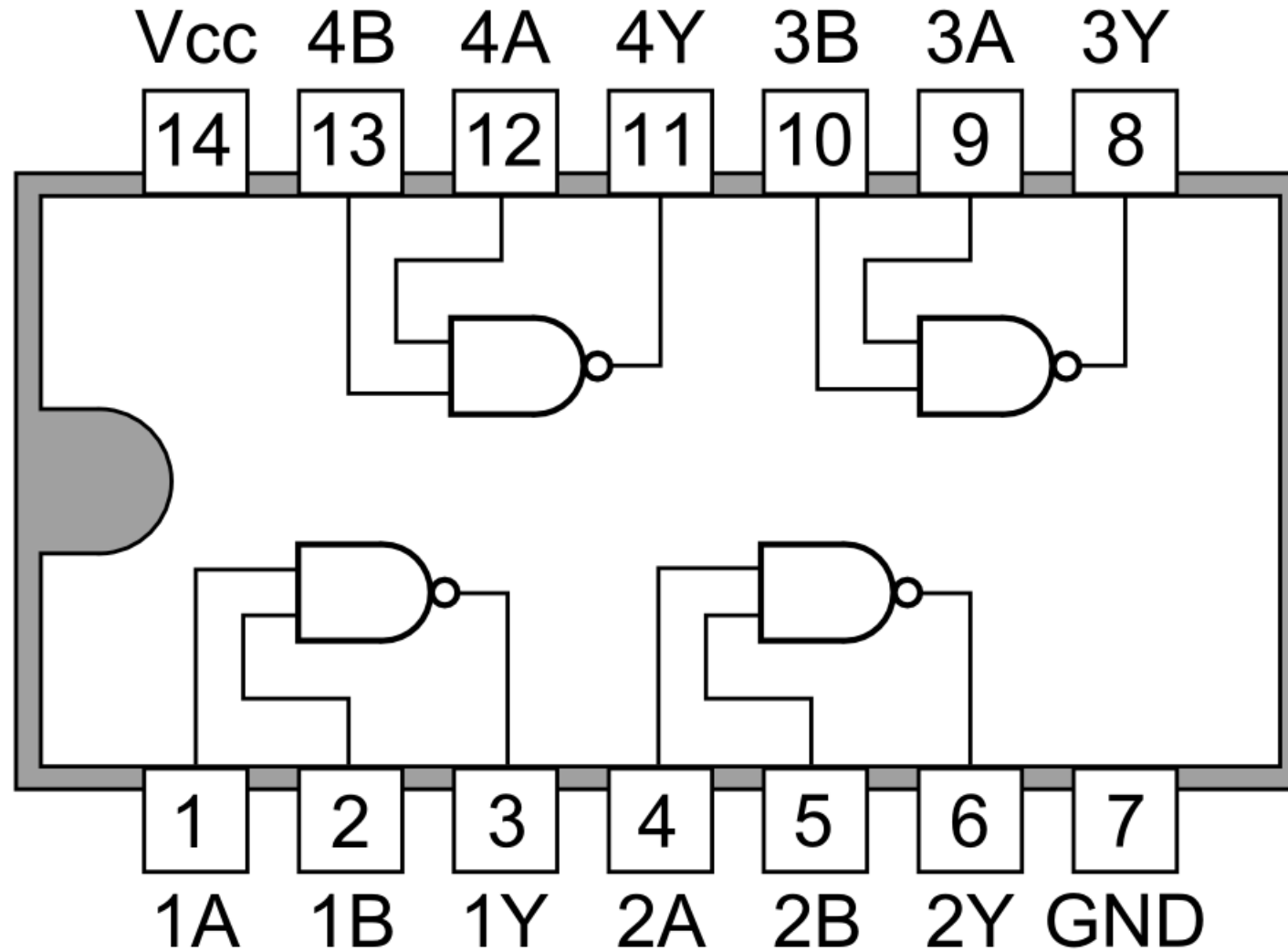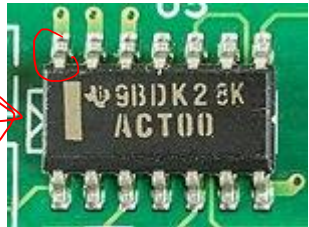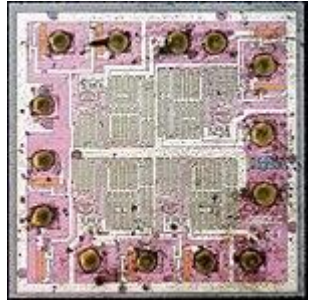
https://commons.wikimedia.org/wiki/7400_series_overview



7400 Quad 2-input NAND Gates

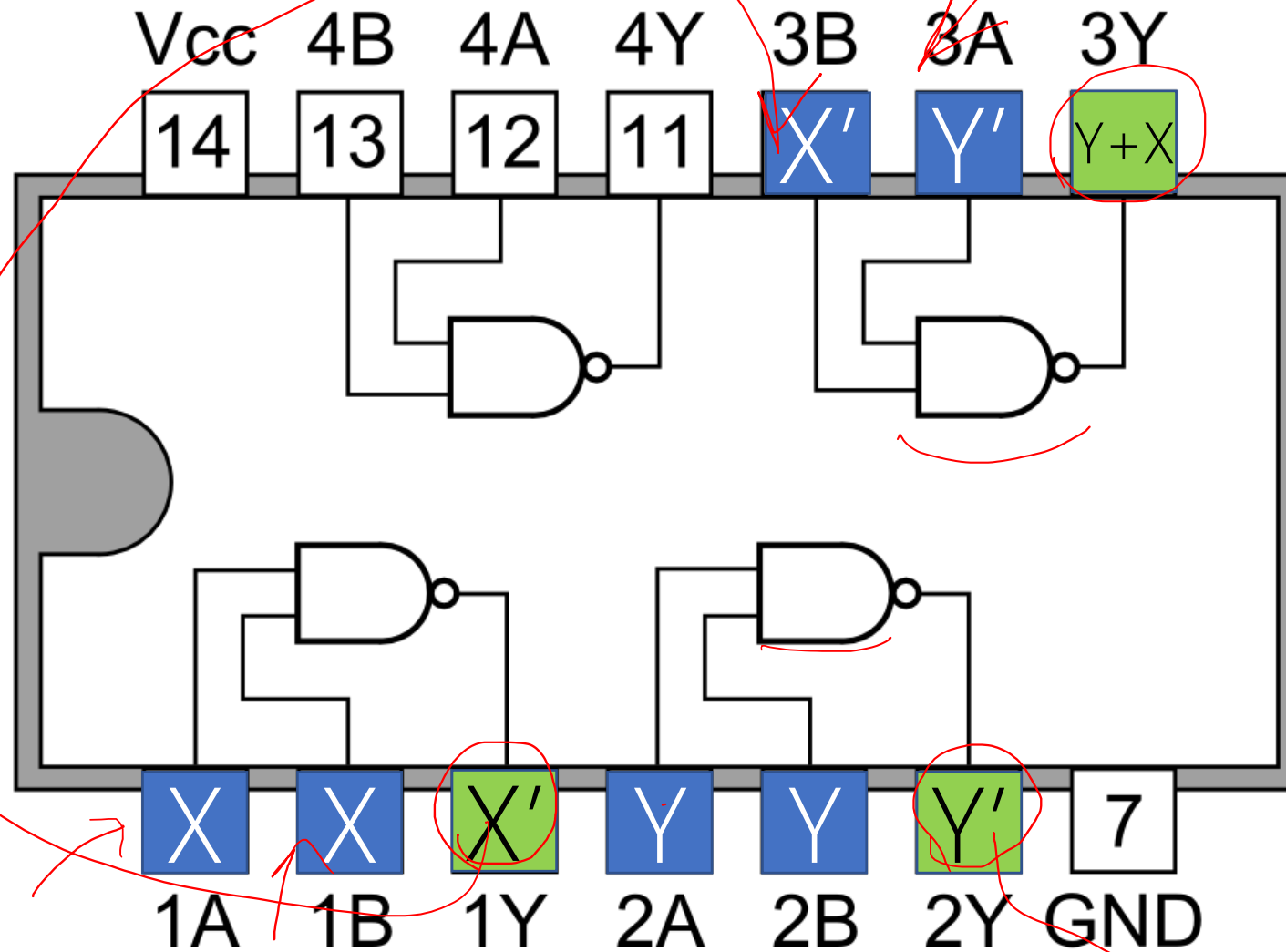

7400 Quad 2-input NAND Gates

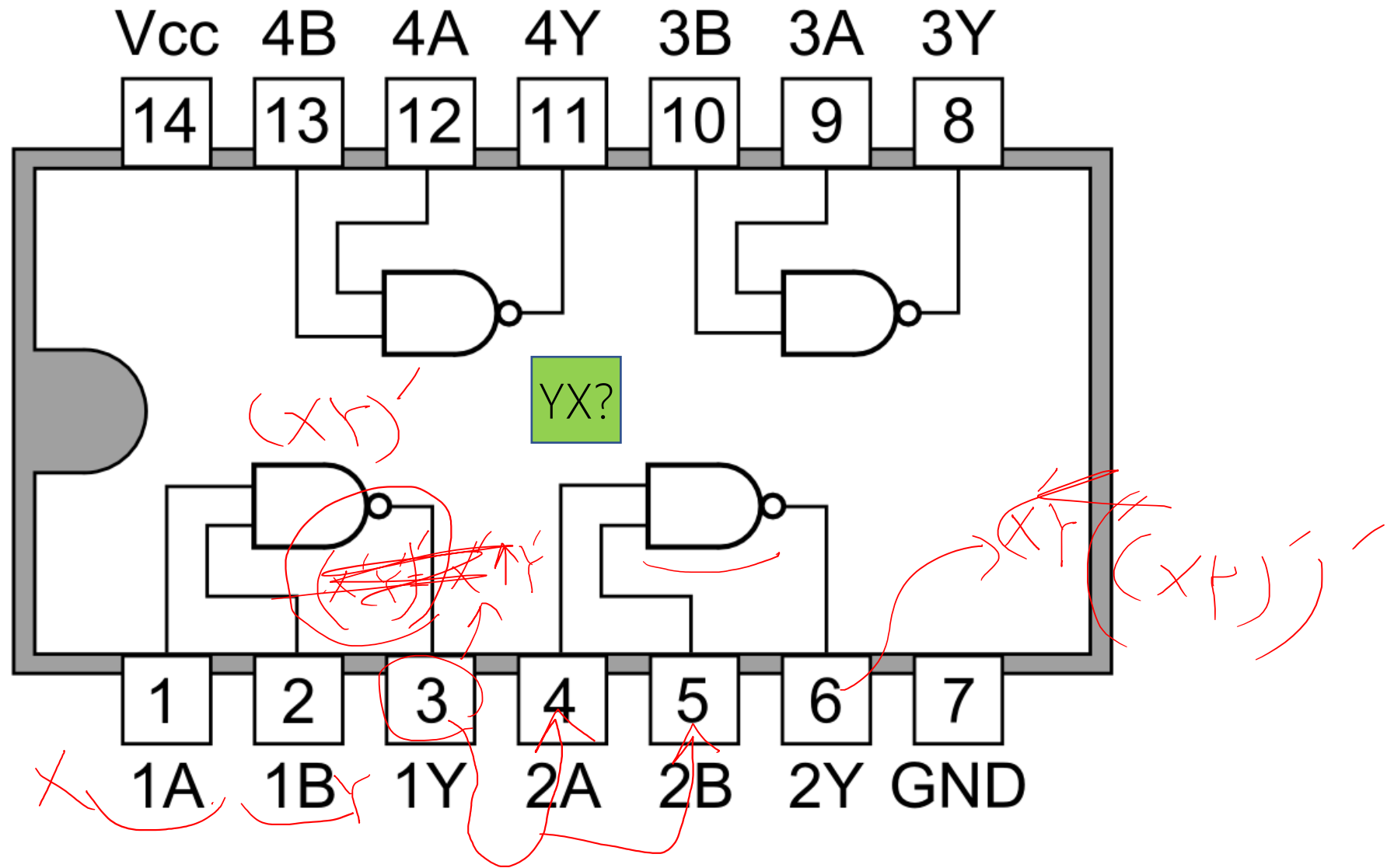

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

UNIVERSAL GATE

{NOR}

NOT ► $(X+X)' = (XX) = X'$



OR ► NOT (NOR)

AND ► DE MORGAN'S LAW


$$(Y'+X')' = YX = (Y'\downarrow X')$$

7402 Quad 2-input NOR Gates

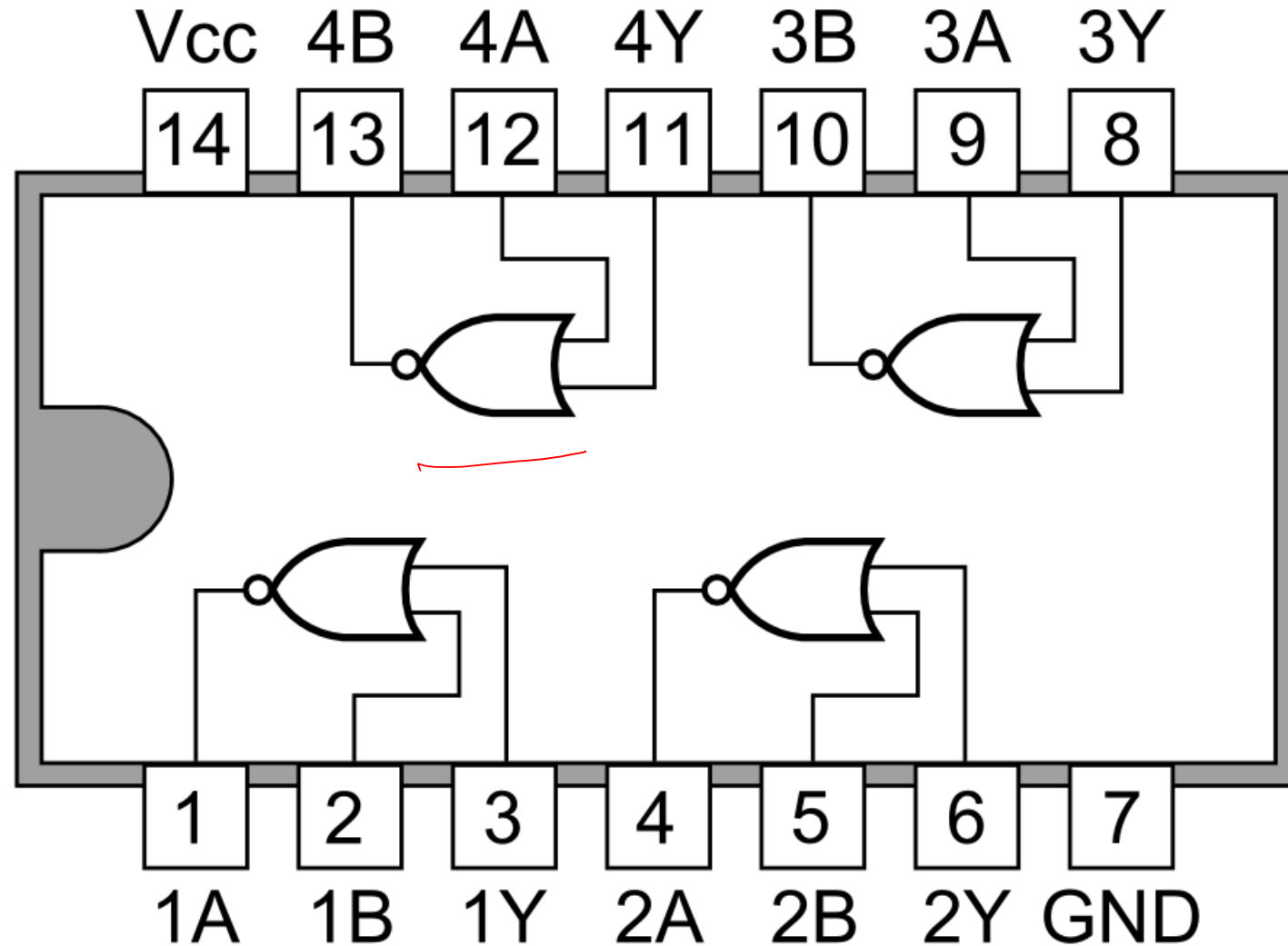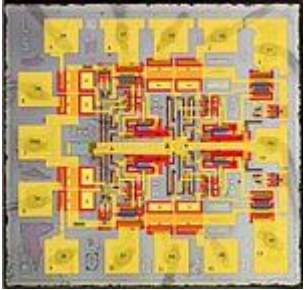https://commons.wikimedia.org/wiki/7400_series_overview




7402 Quad 2-input NOR Gates

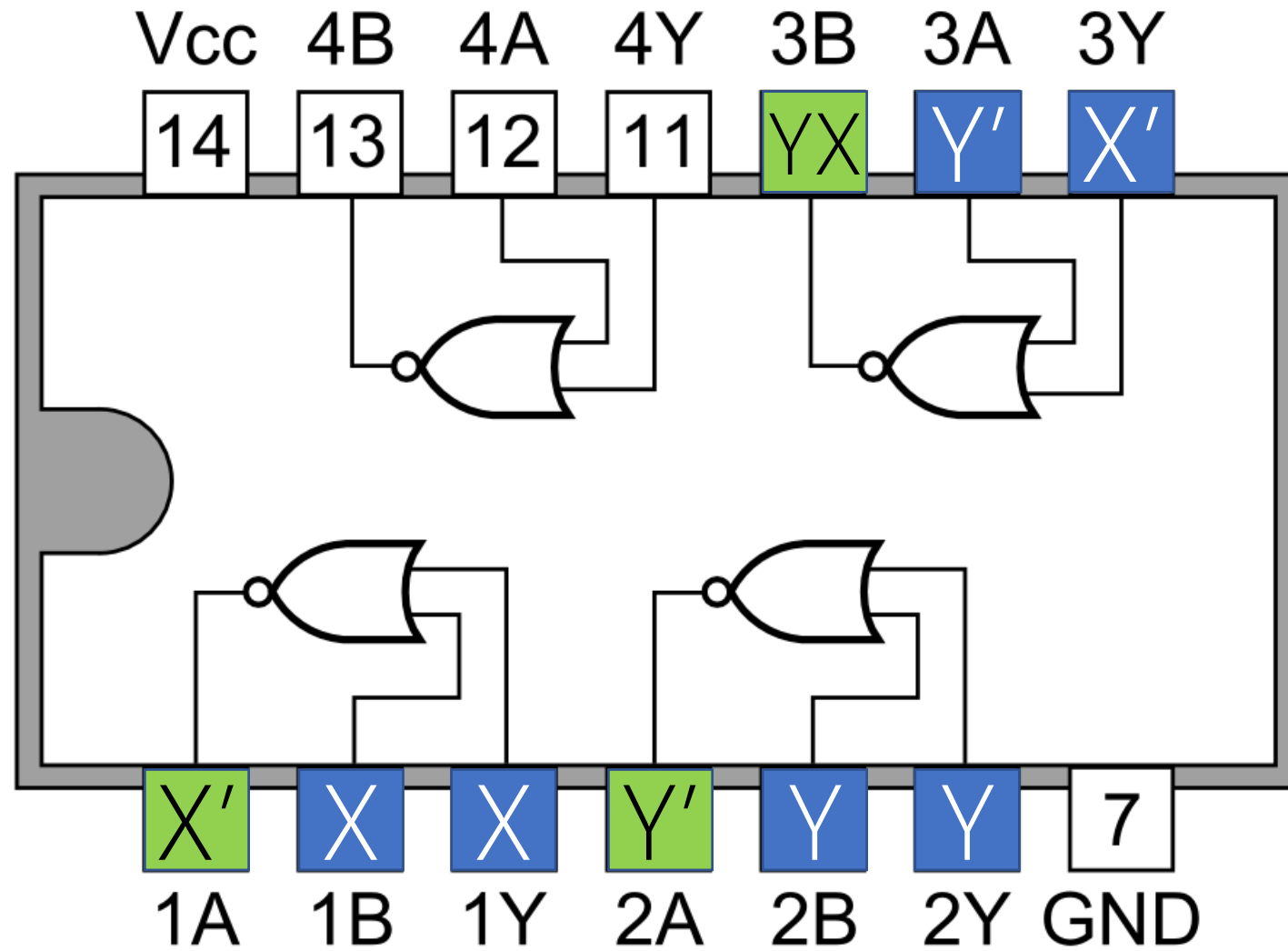


UNIVERSAL GATE

SoP \rightarrow {NAND}

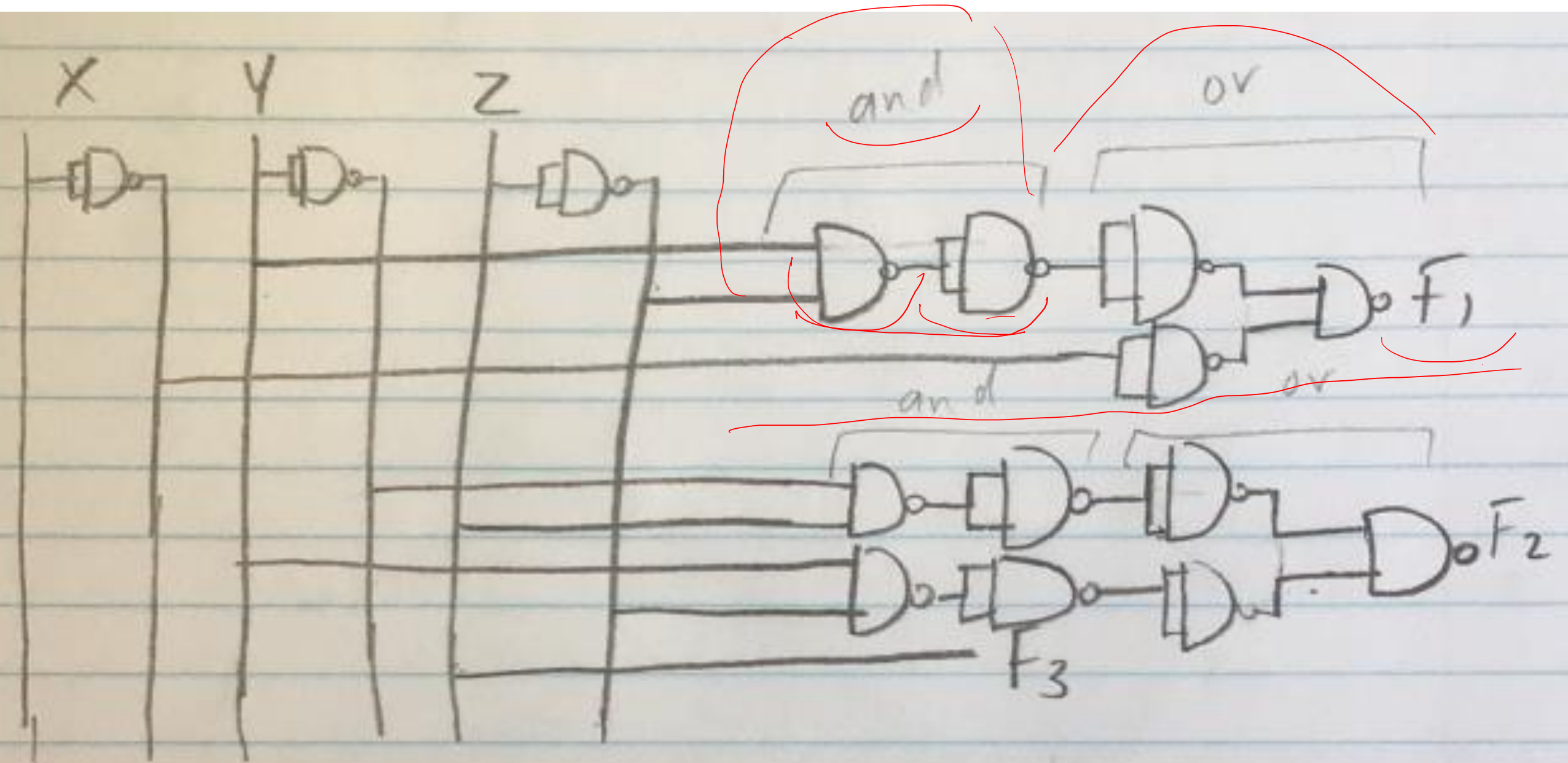


Credit goes to Haiqa Arain (Winter 2021)

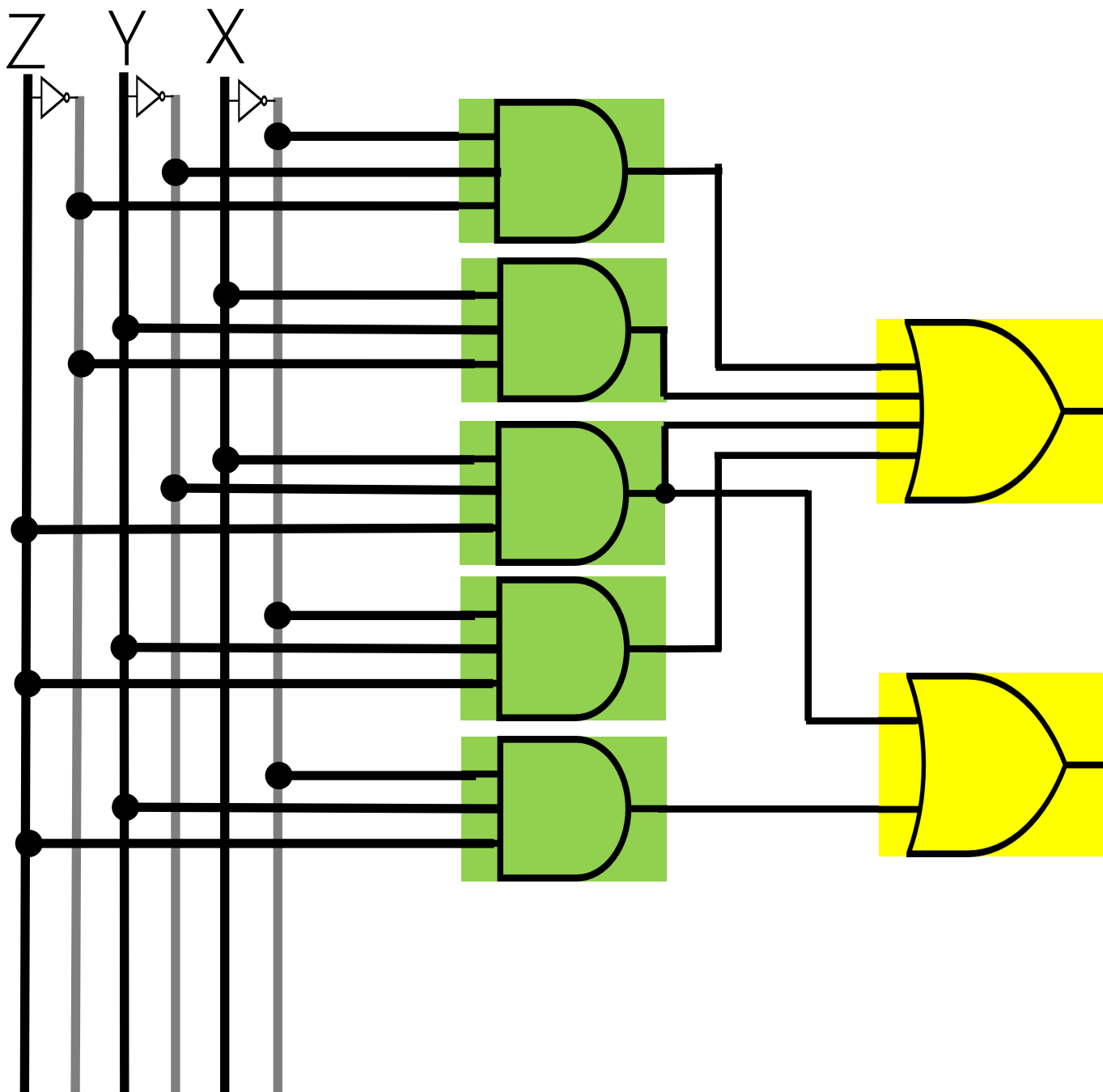


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$F_2 = ZY'X' + ZY'X$$

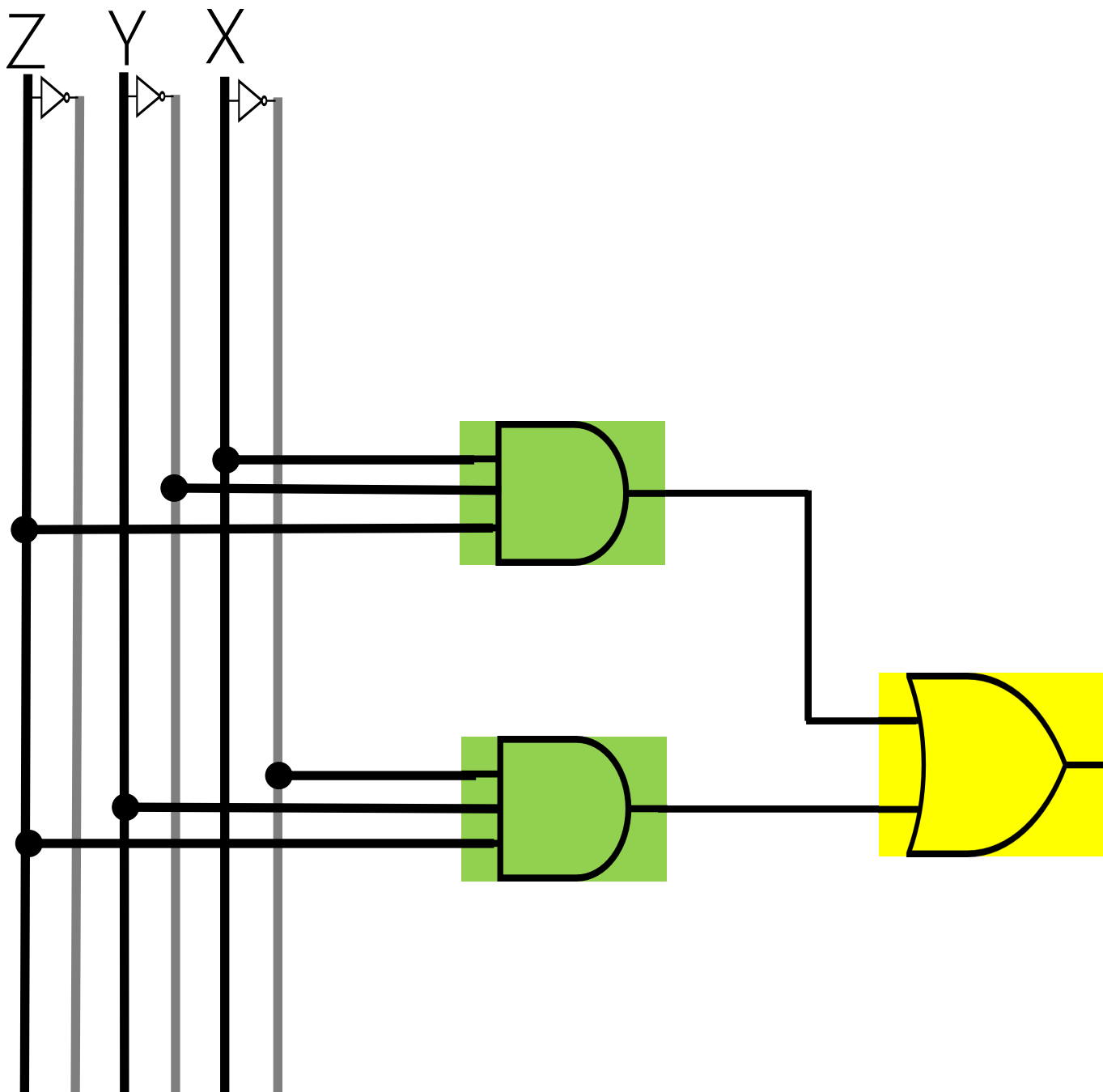


$$F_2 = ZY'X' + ZY'X$$

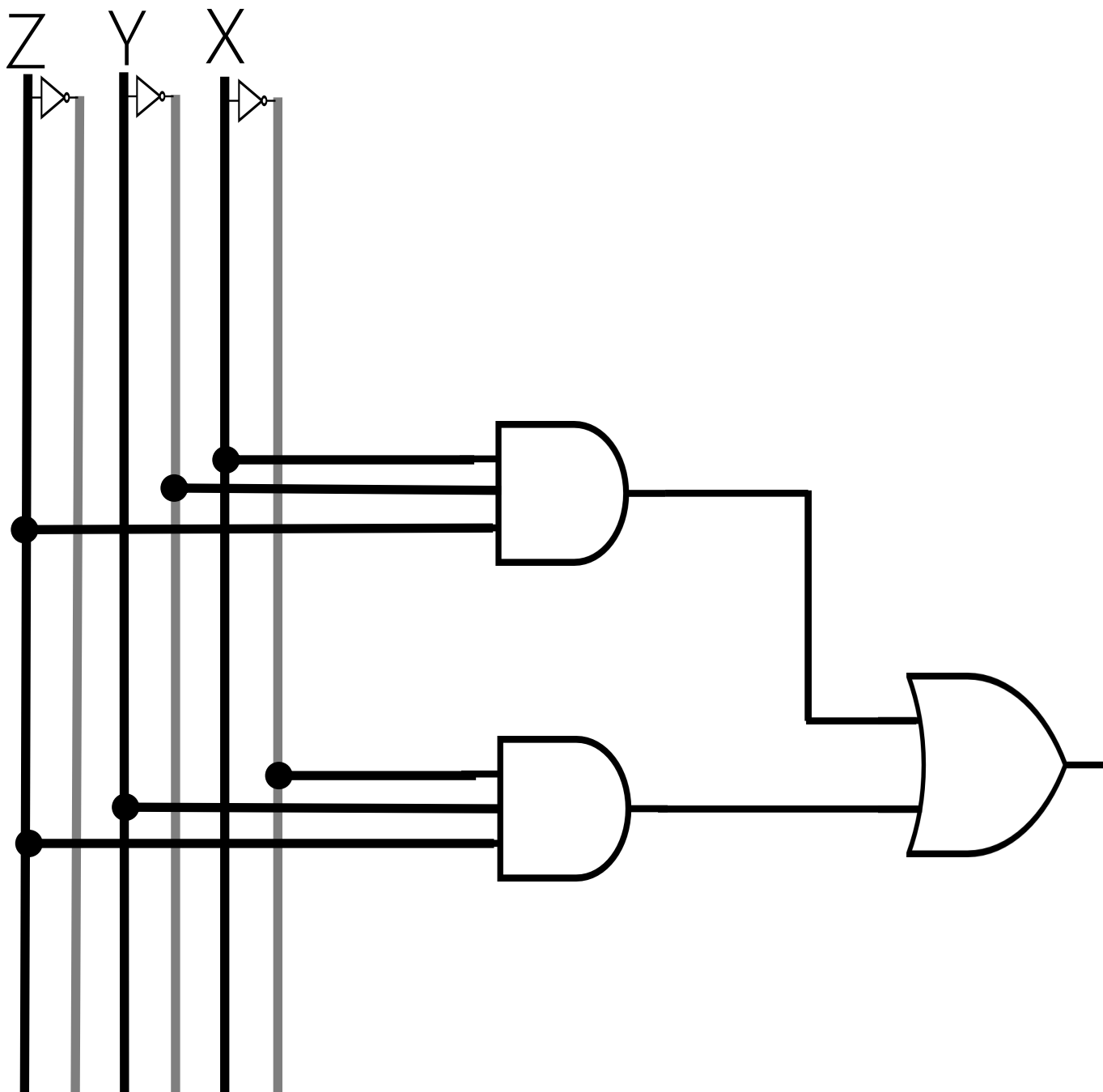


$$F_2 = m_4 + m_5$$


$$= ((F_2)')'$$

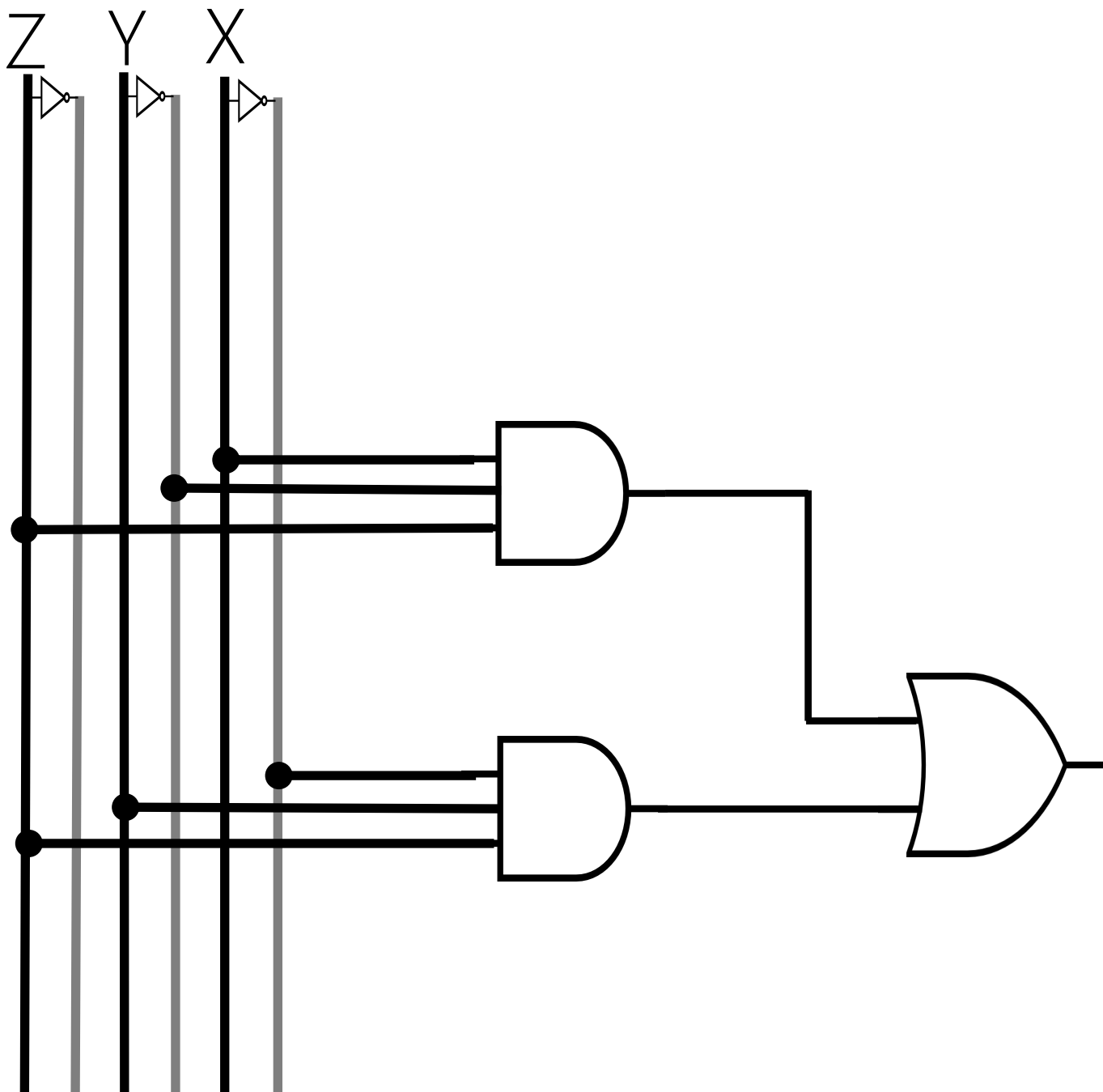

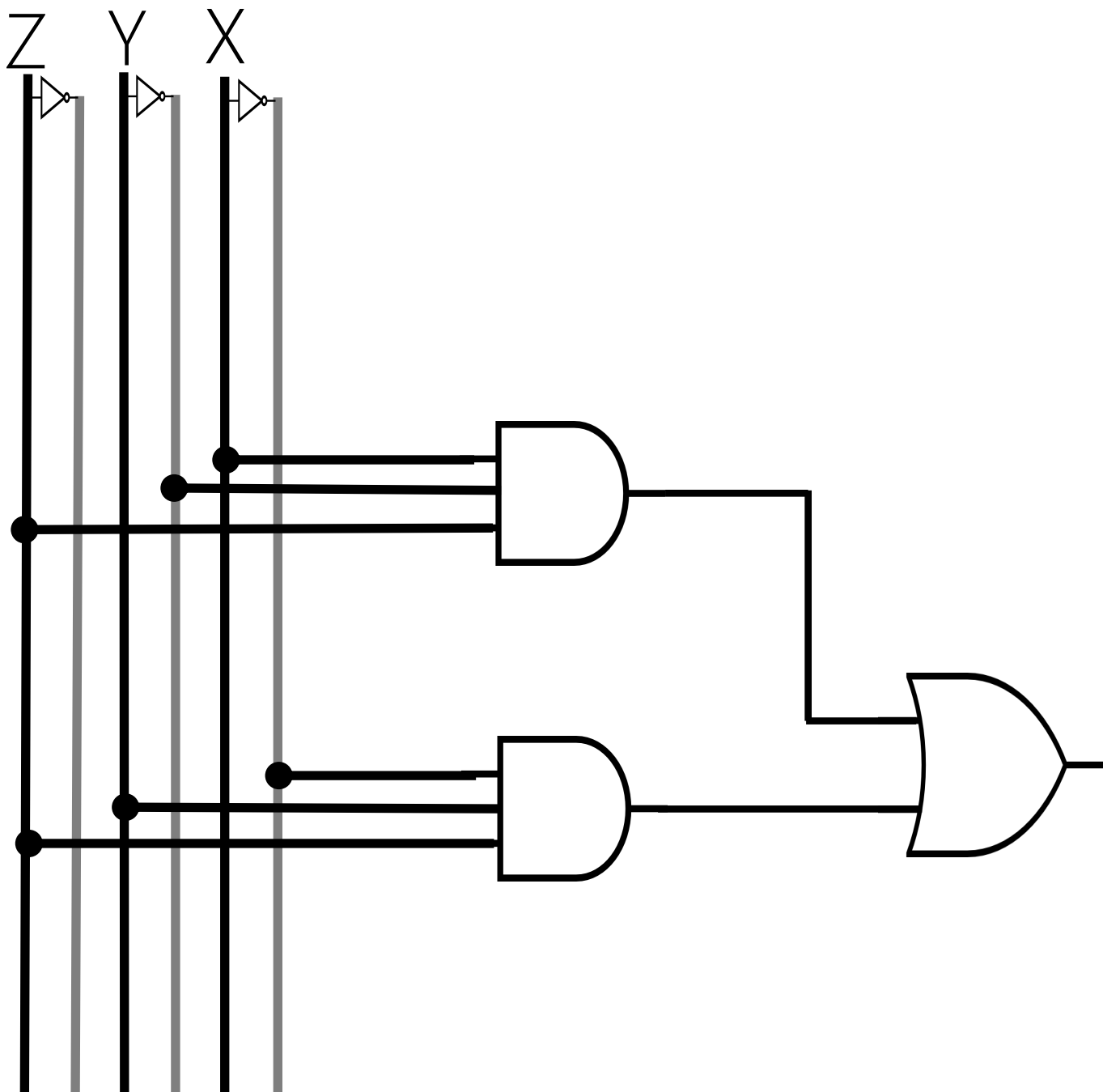
$$\begin{aligned}
 \underline{F_2} &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')'
 \end{aligned}$$



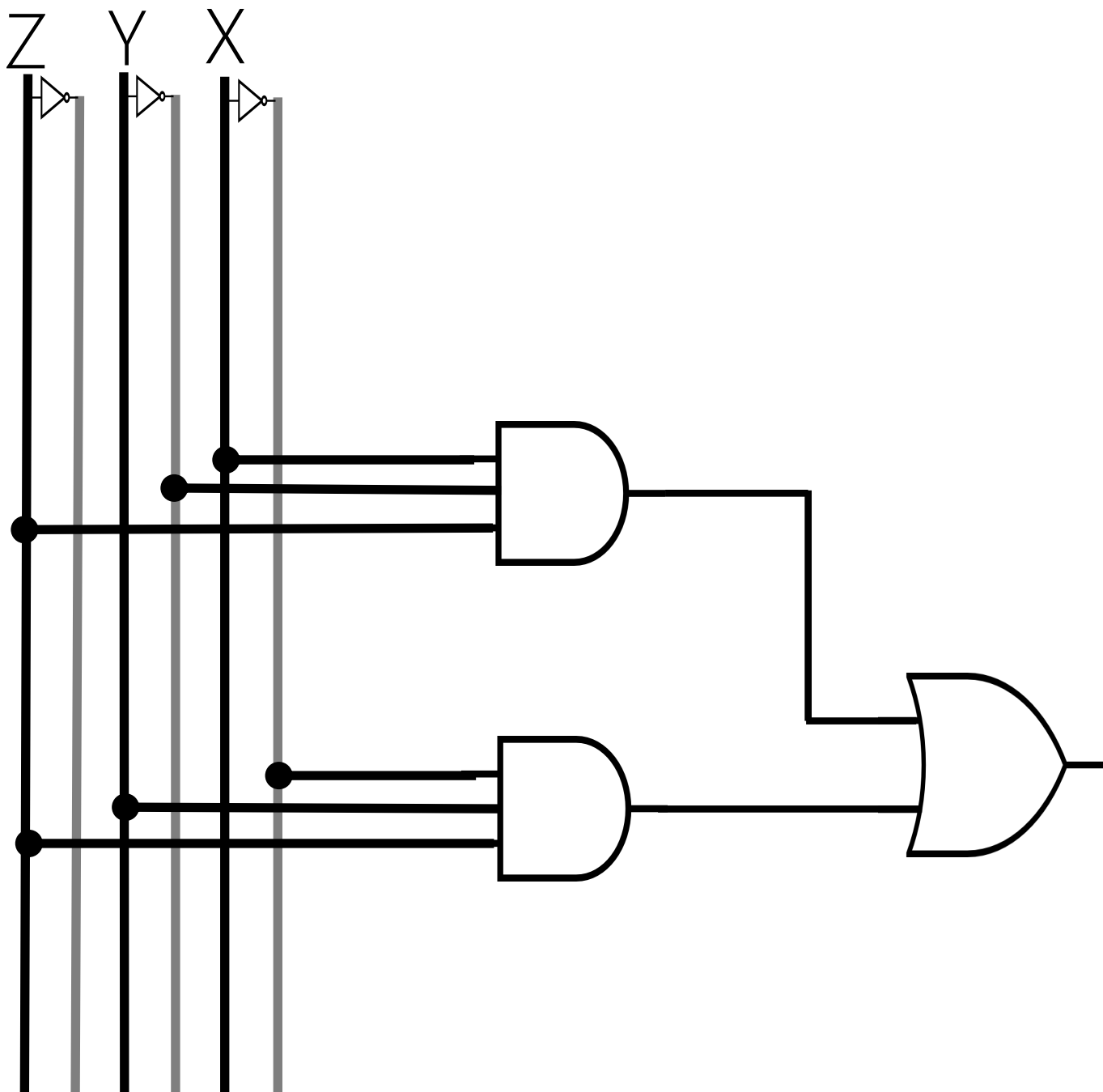
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m_4' m_5')'
 \end{aligned}$$



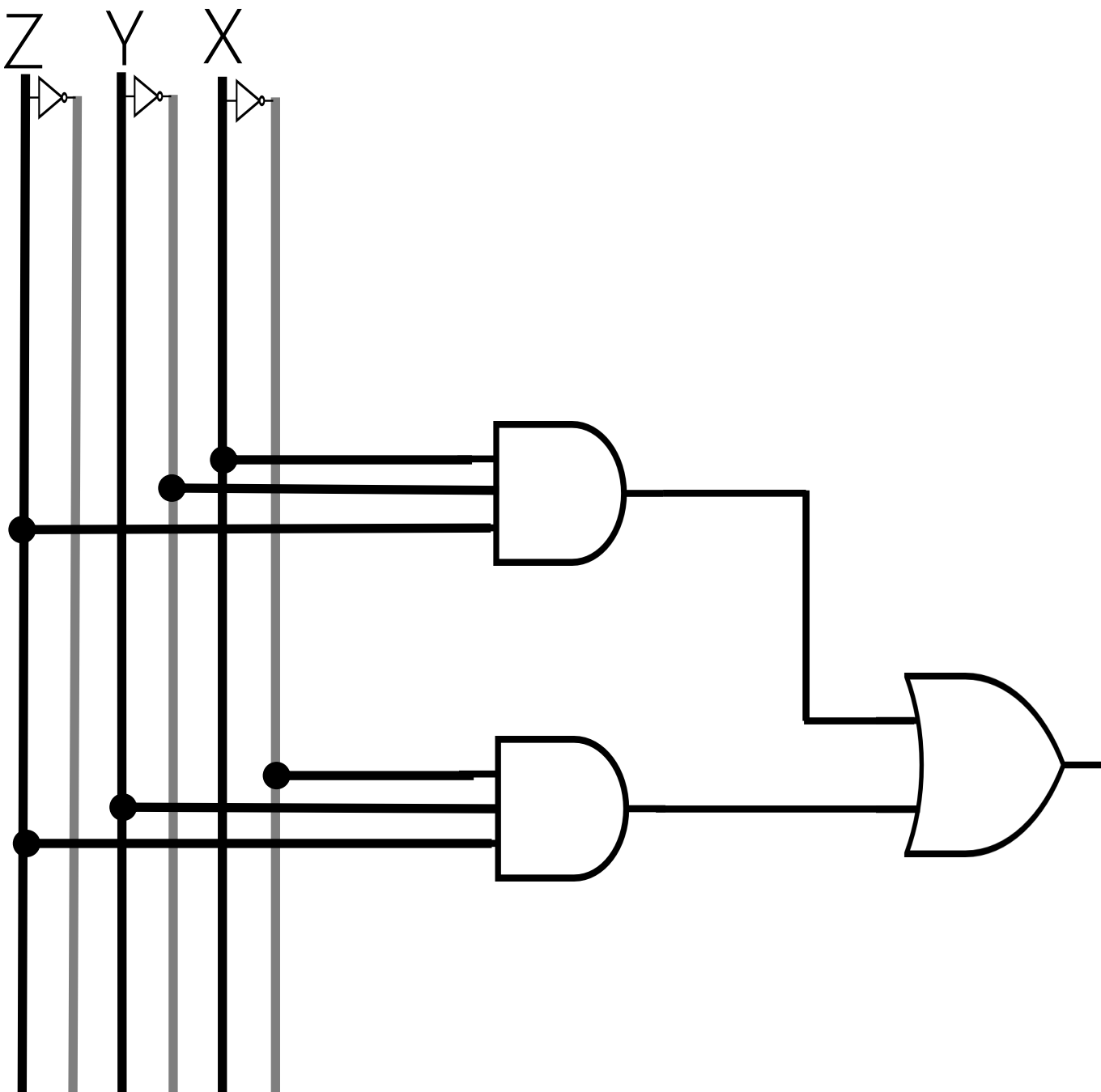
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')'
 \end{aligned}$$



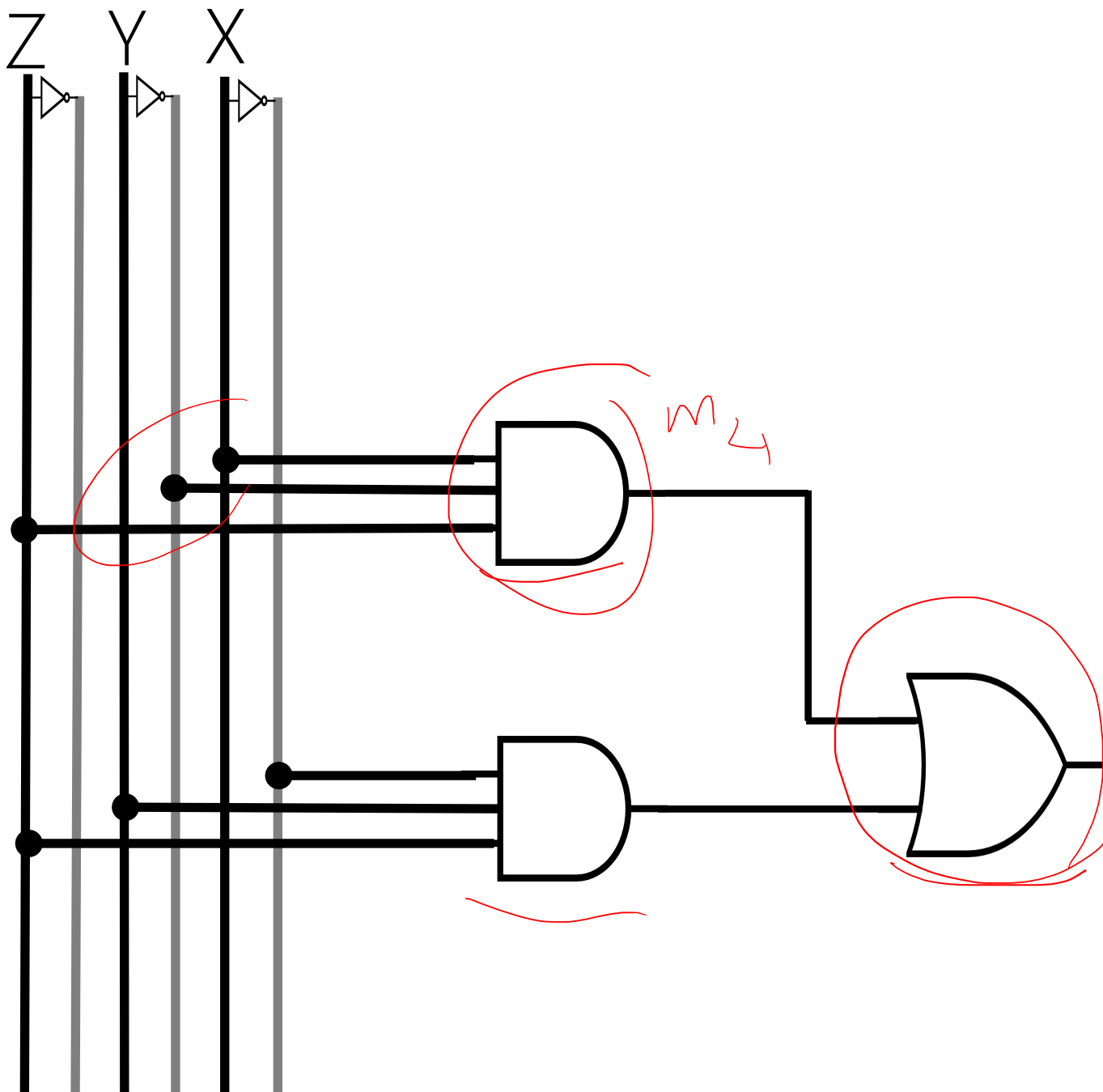
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')' \\
 &= ((Z \uparrow Y' \uparrow X') (Z \uparrow Y' \uparrow X))'
 \end{aligned}$$



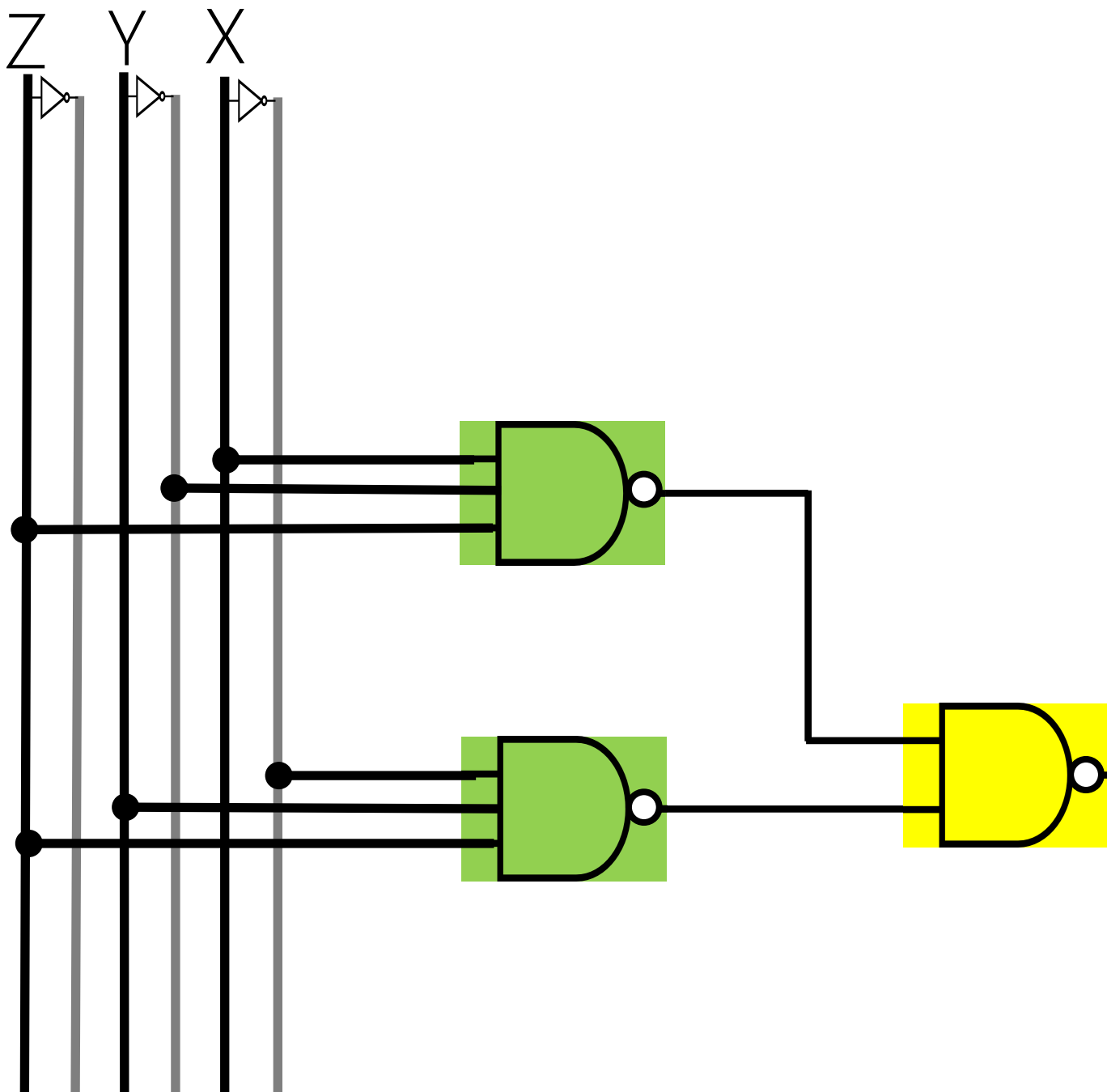
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')' \\
 &= ((Z \uparrow Y' \uparrow X') (Z \uparrow Y' \uparrow X))' \\
 &= ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))
 \end{aligned}$$


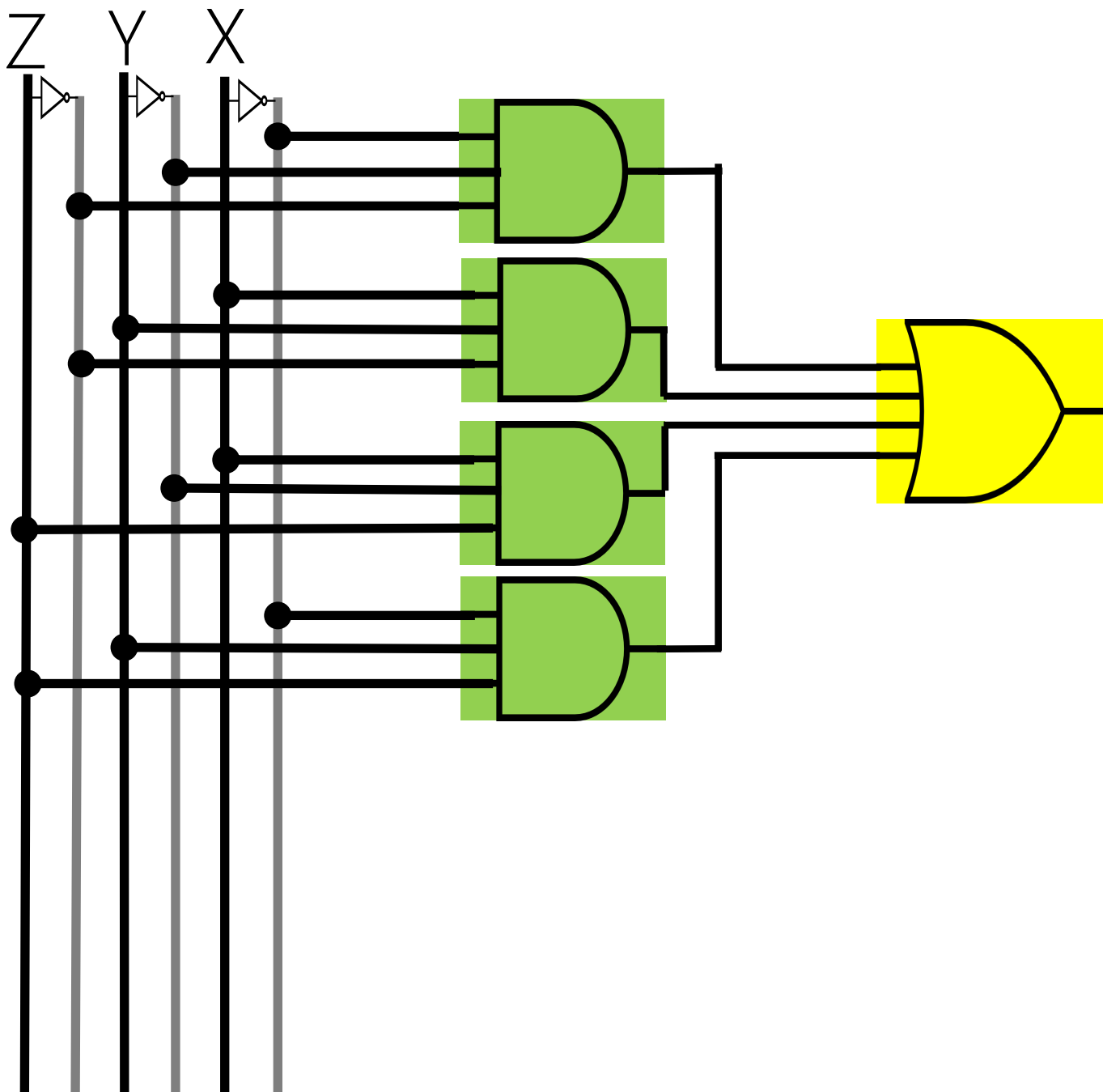
$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$





$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

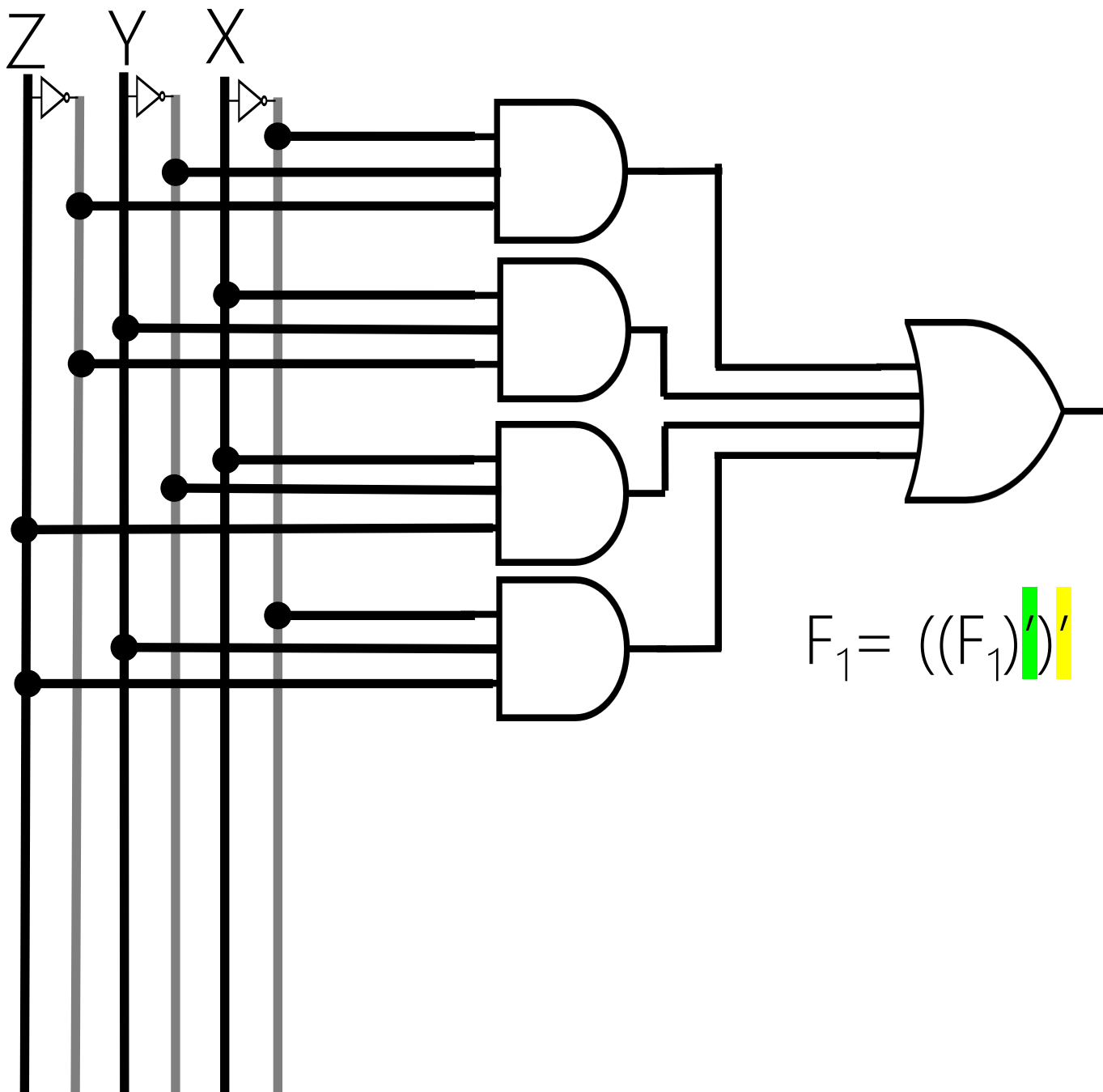


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$


$$F_1 = ((F_1)')'$$

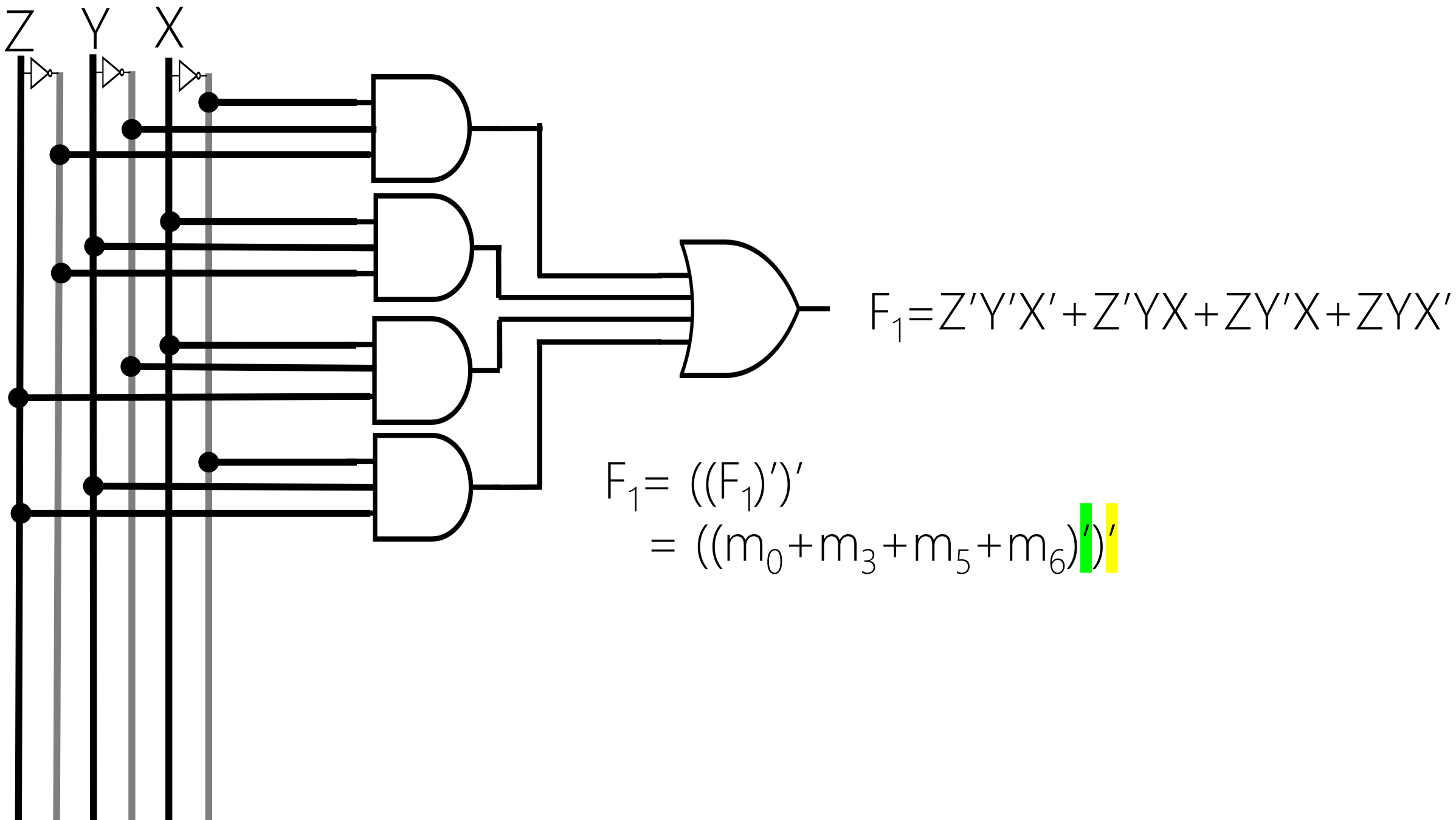

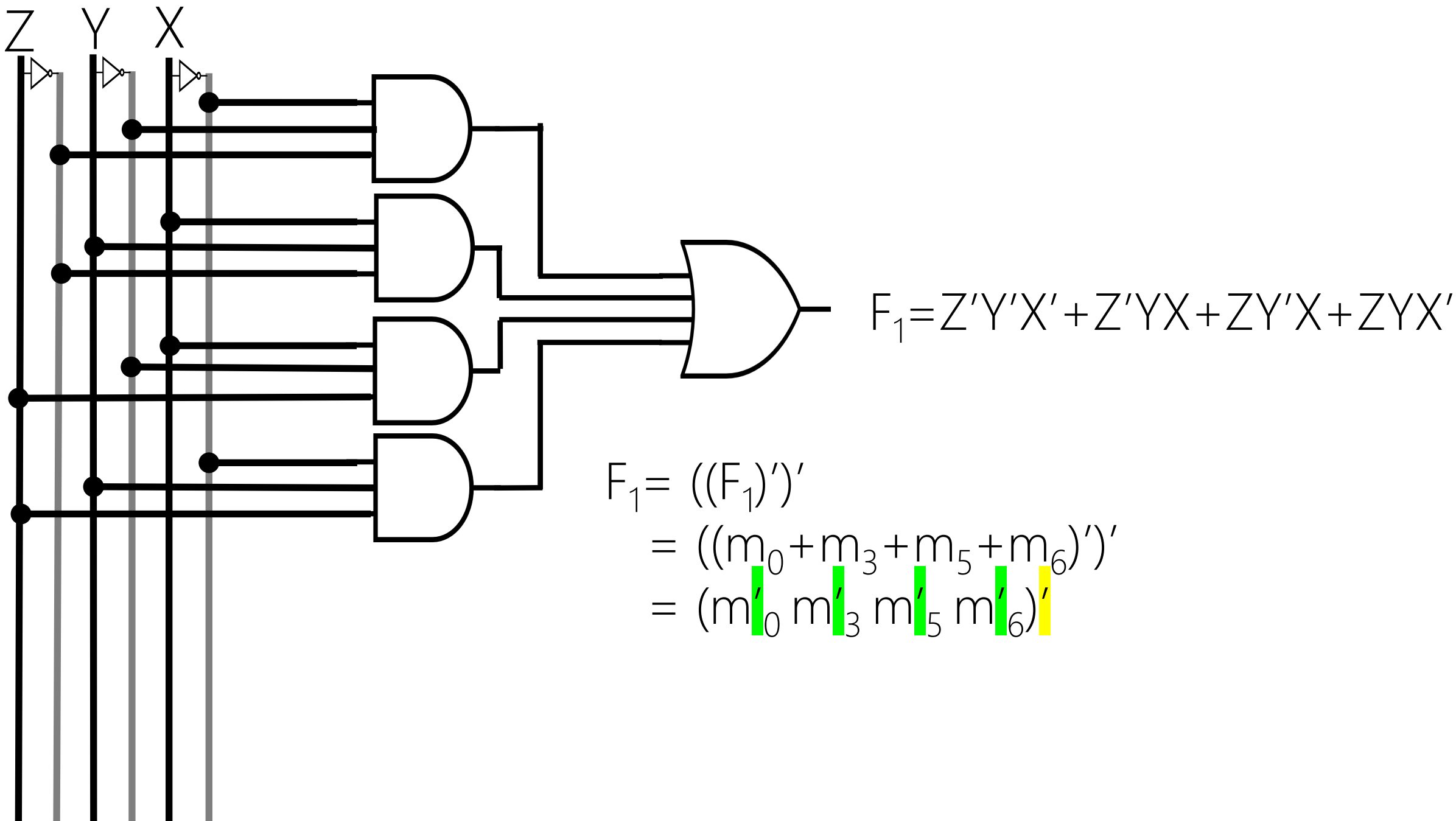

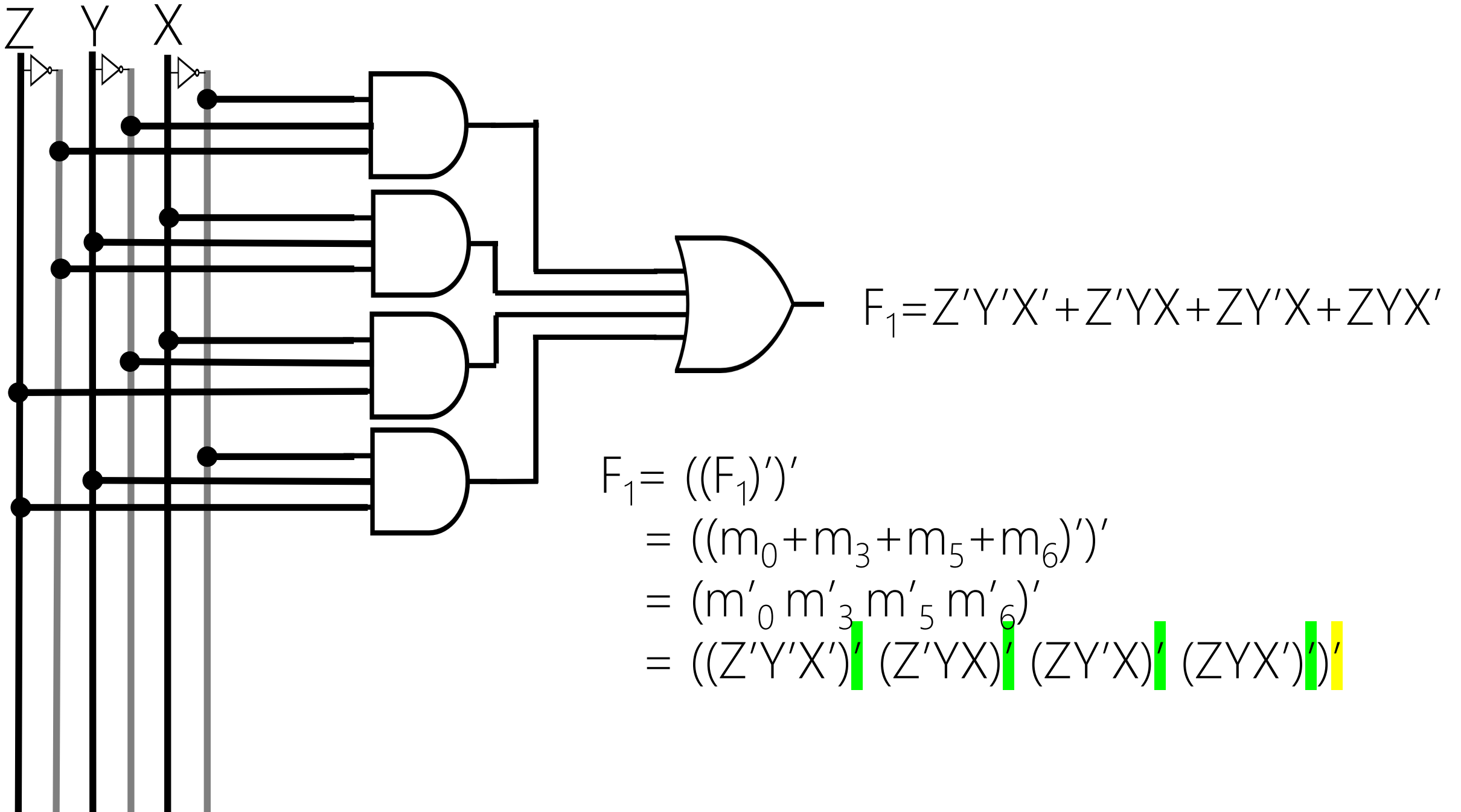
$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)'
 \end{aligned}$$



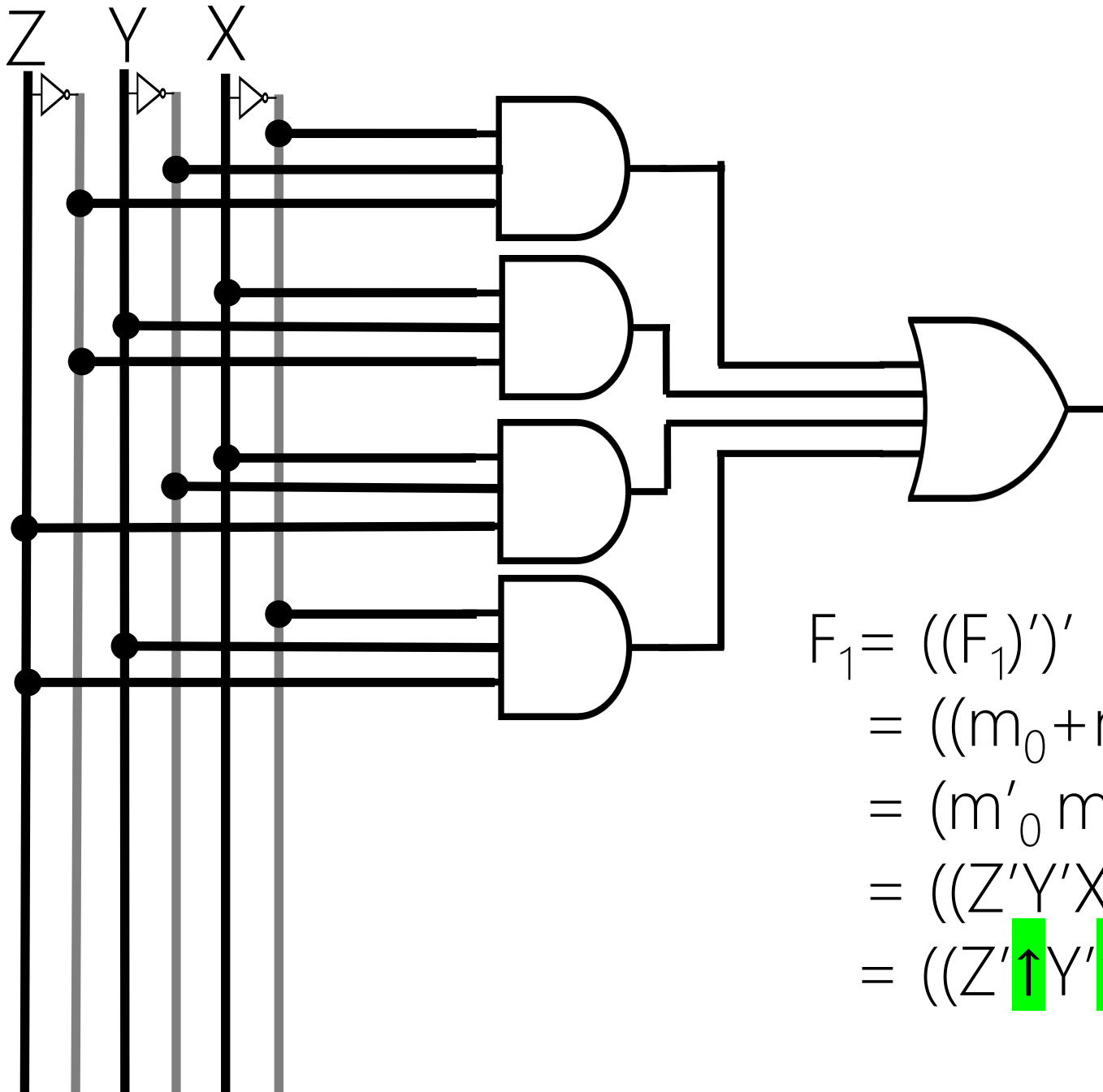


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$
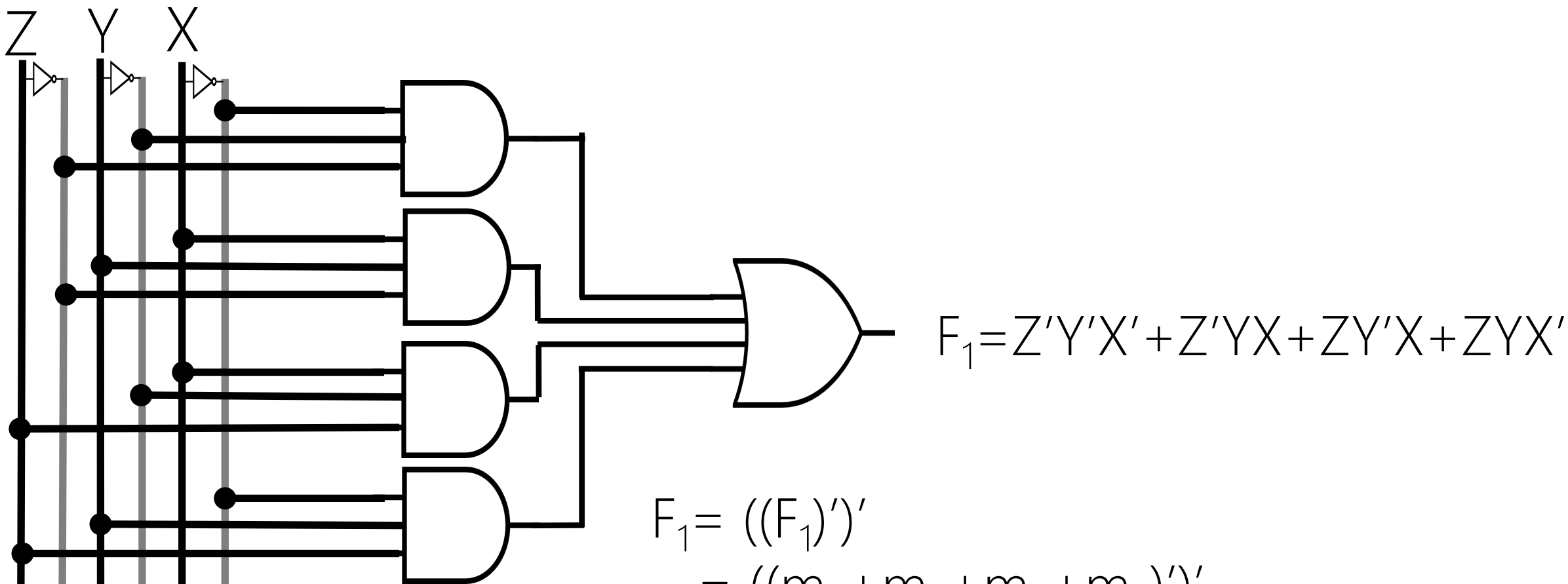
$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (ZYX')')' \\
 &= ((Z'\uparrow Y'\uparrow X') (Z'\uparrow Y\uparrow X) (Z\uparrow Y'\uparrow X) (Z\uparrow Y\uparrow X'))'
 \end{aligned}$$




$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (ZYX'))' \\
 &= ((Z' \uparrow Y' \uparrow X') (Z' \uparrow Y \uparrow X) (Z \uparrow Y' \uparrow X) (Z \uparrow Y \uparrow X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))
 \end{aligned}$$

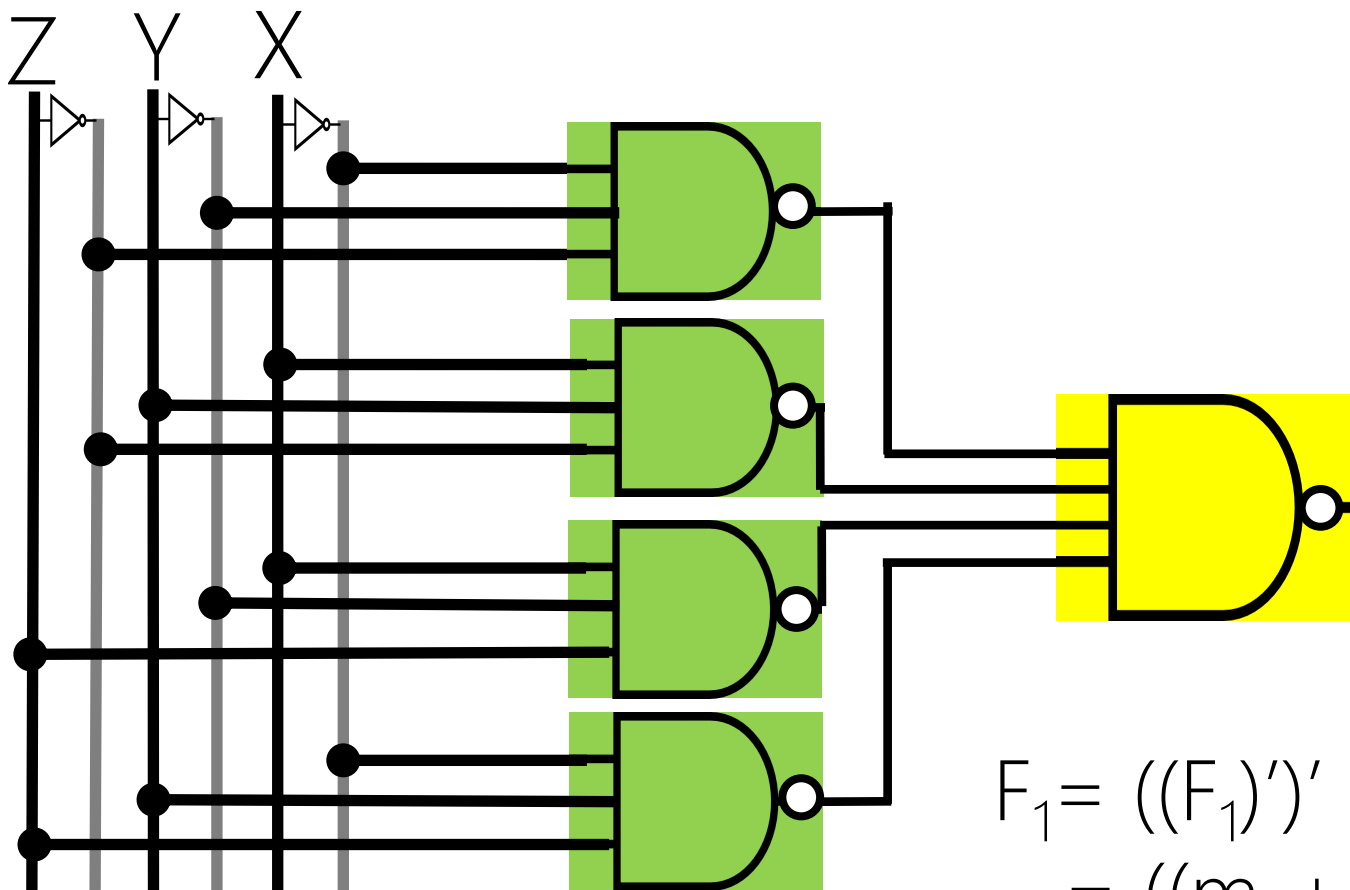

$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (Z Y X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') (Z' \uparrow Y \uparrow X) (Z \uparrow Y' \uparrow X) (Z \uparrow Y \uparrow X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))
 \end{aligned}$$


Z Y X

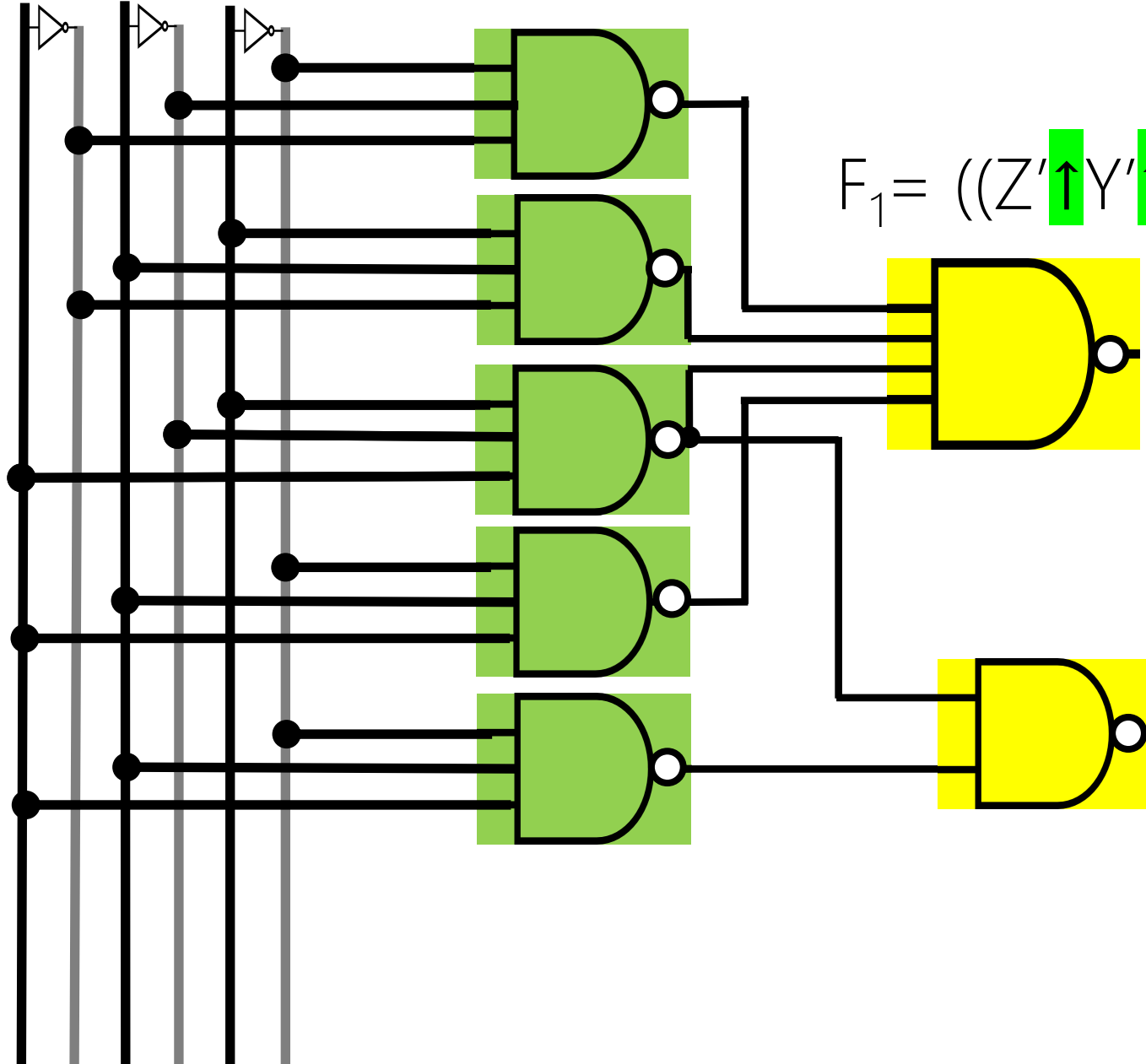

$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$

Z Y X

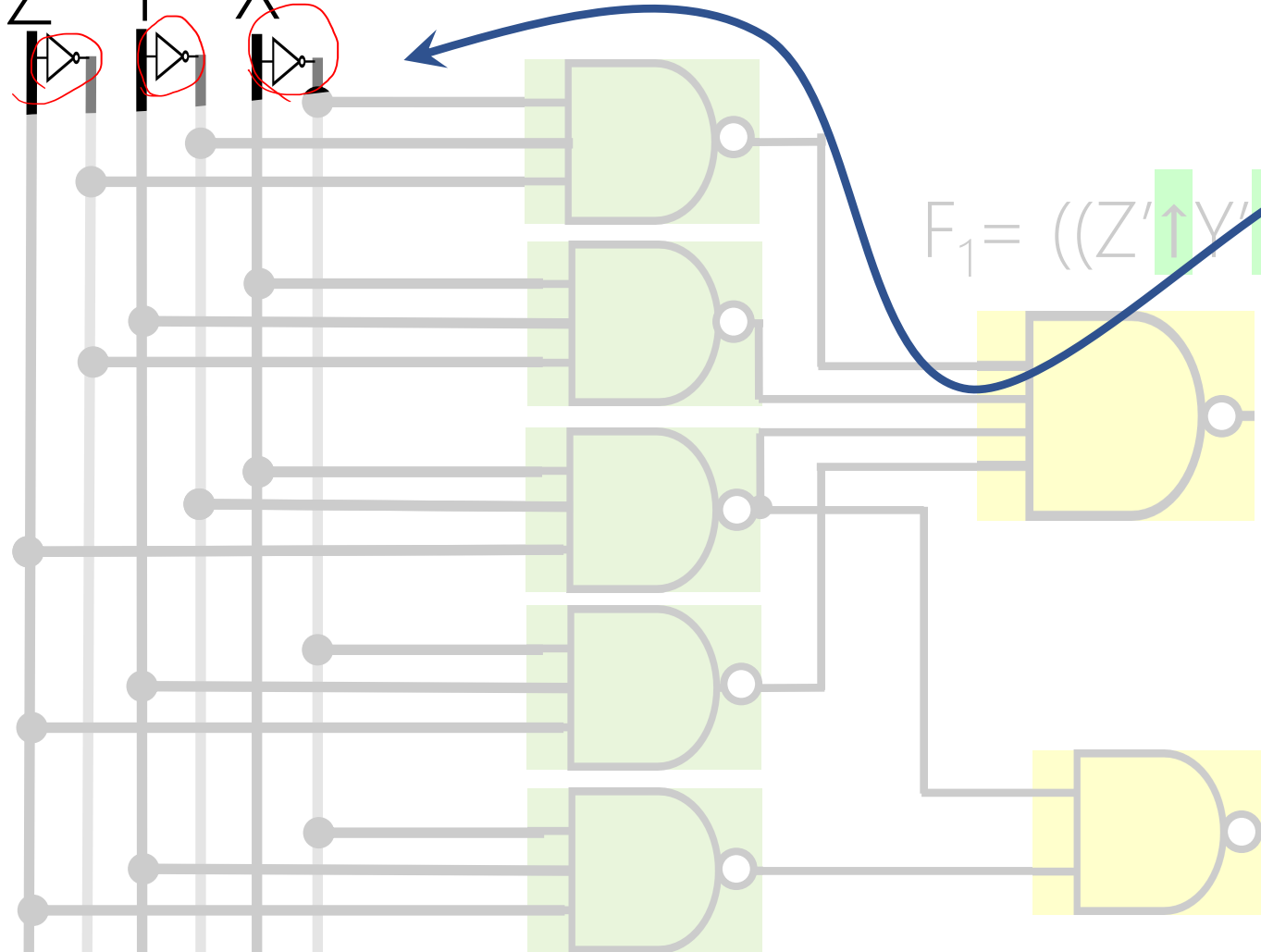


$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

NOT by NAND?


$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$

Z Y X

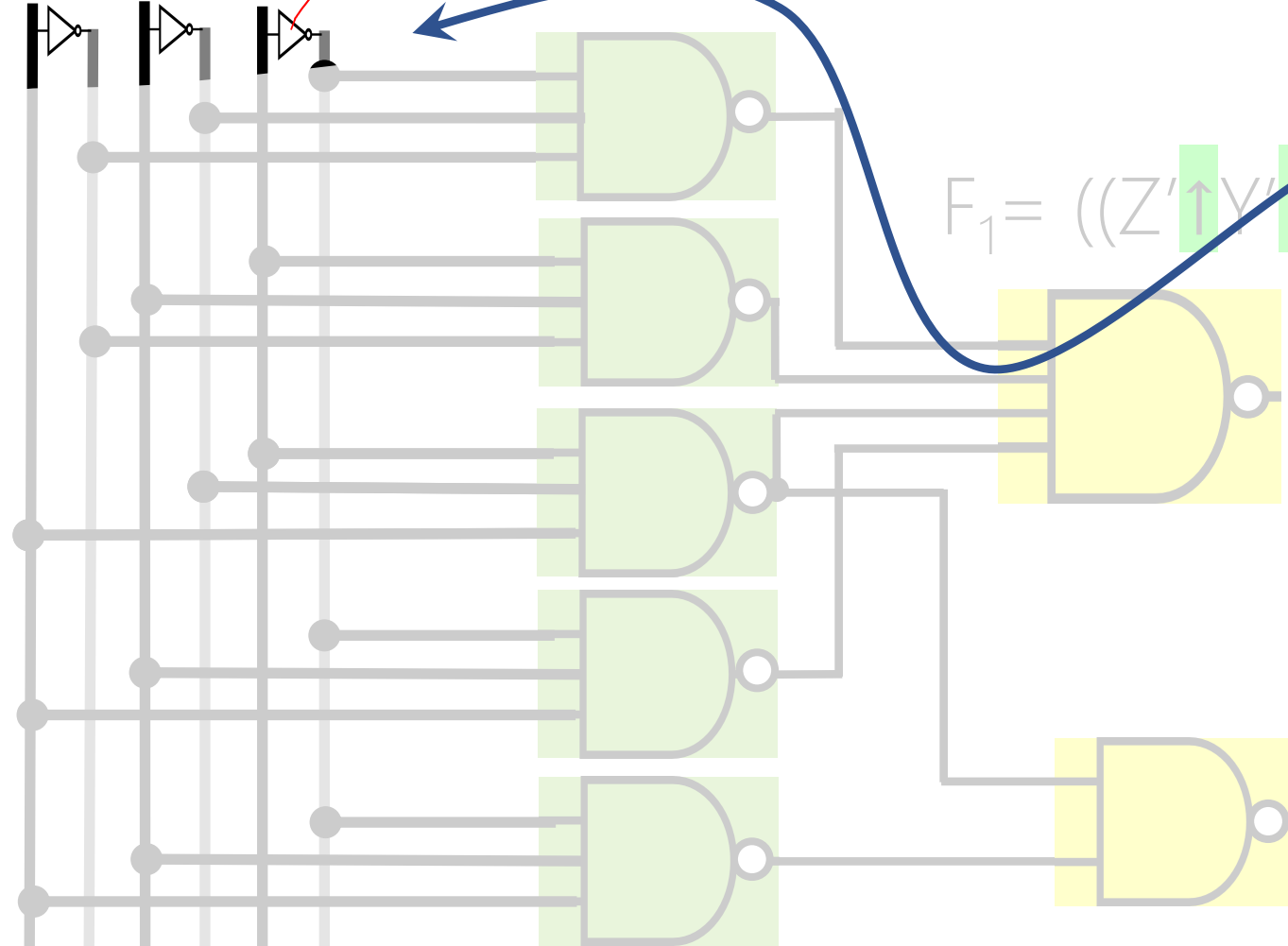

$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

NOT by NAND?

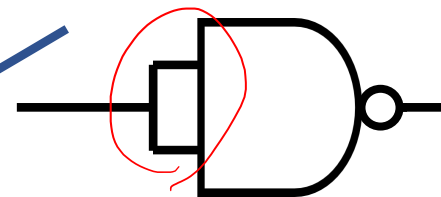

$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$

UNIVERSAL GATE {NAND}

$$F = (F')' = (\text{SoP}')'$$

$\begin{matrix} \text{=} & \uparrow & \uparrow & \uparrow \end{matrix}$

UNIVERSAL GATE

{NOR}

UNIVERSAL GATE

$\text{PoS} \rightarrow \{\text{NOR}\}$

$$F_{\text{PoS}} = (F')'$$

Lecture Assignment

RECAP

Any Boolean Function F:

- Sum (OR) of Products (ANDs)
- Sum of **minterms** for Entries with **1**
 - ANDs-OR
 - NAND via $(F')'$
- Product (AND) of Sums (ORs)
- Product of **MAXTERMS (NOT minterms)** for Entries with **0**
 - ORs-AND
 - NOR via $(F')'$

UNIVERSAL GATE

SoP \rightarrow {NAND}

SoP \rightarrow {NOR} ?

PoS \rightarrow {NOR}

PoS \rightarrow {NAND} ?

Lecture Assignment