

---

# UNIVERSALITY

---

---

# UNIVERSAL SET

---

Is it possible to implement ALL the possible Boolean functions using NOT, AND, OR, NAND, NOR? Yes!

---

# UNIVERSAL SET

---

What if we are not given some!

What if some are very costly! E.g., NOT

Can we reduce this set? E.g., building NOT by NAND/ NOR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR
{NOT, OR}	If we could design AND
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

---

# UNIVERSAL SET

## {NOT, AND}

---



Augustus De Morgan  
(1806–1871)


Mathematician  
Logician

### DE MORGAN'S LAWS


►  $(Y + X)' = Y'X'$

$$((Y + X)')' = (Y'X')'$$

$$Y + X = (Y'X')'$$

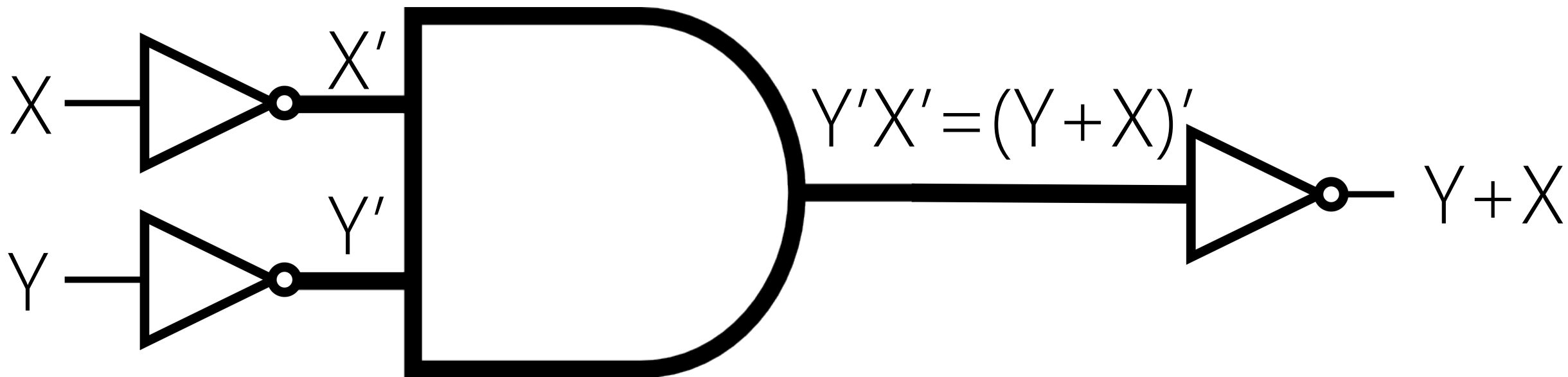



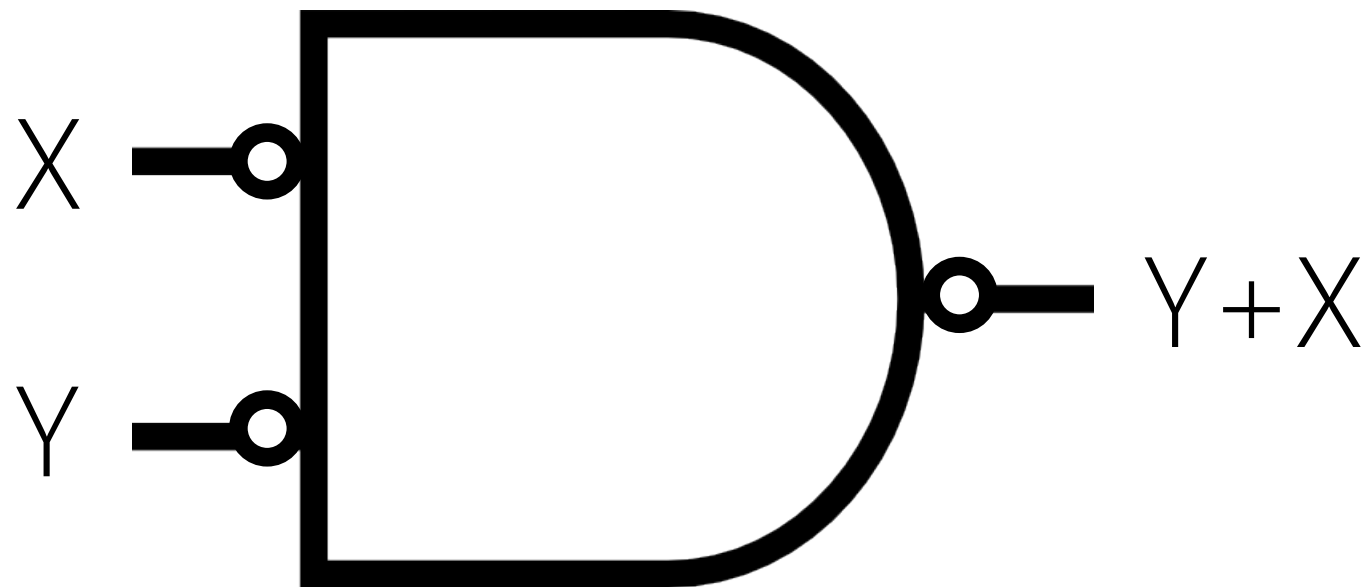

OR

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

---

UNIVERSAL SET  
{NOT, OR}

---



Augustus De Morgan  
(1806–1871)


Mathematician  
Logician


### DE MORGAN'S LAWS

►  $Y' + X' = (YX)'$

$$(Y' + X')' = ((YX)')'$$

$$(Y' + X')' = YX$$

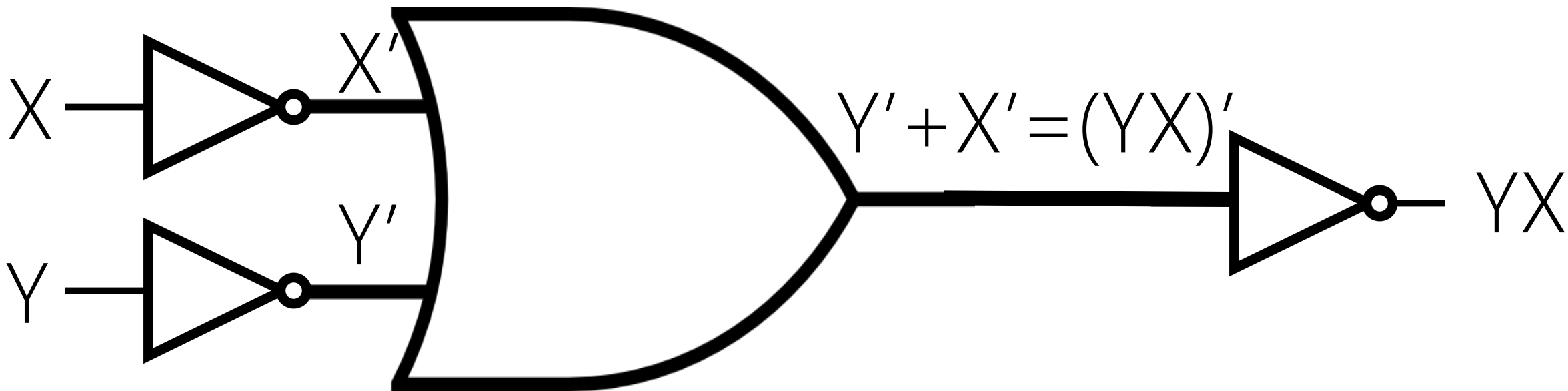

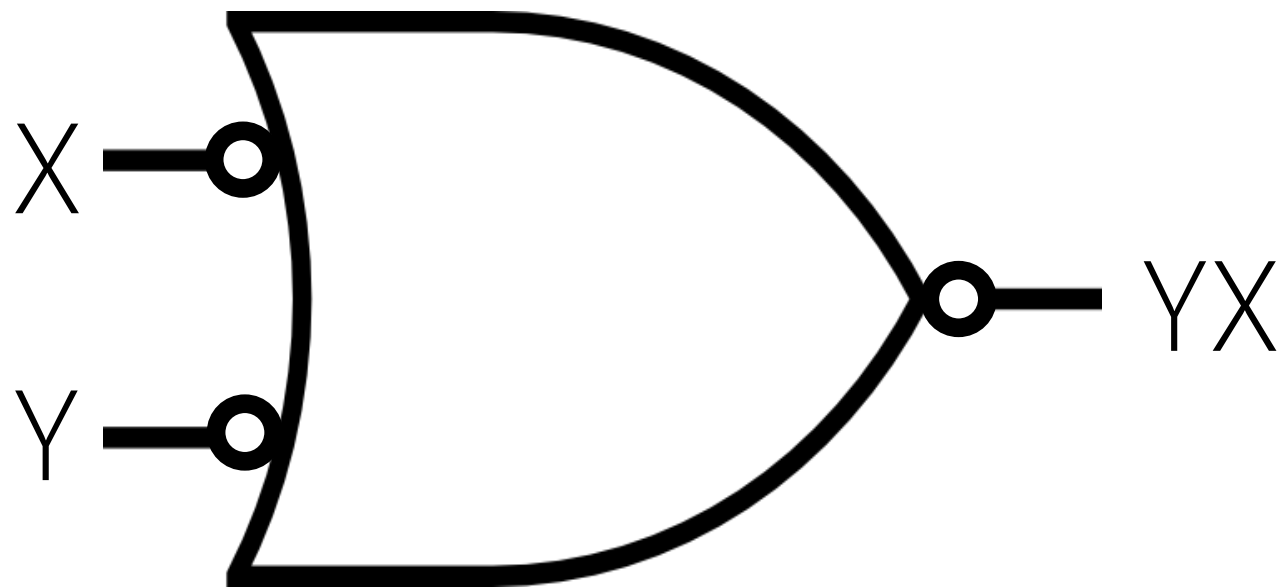

AND

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

---


# UNIVERSAL GATE

## {NAND}


---



NOT ►  $(XX)' = (X \uparrow X) = X'$

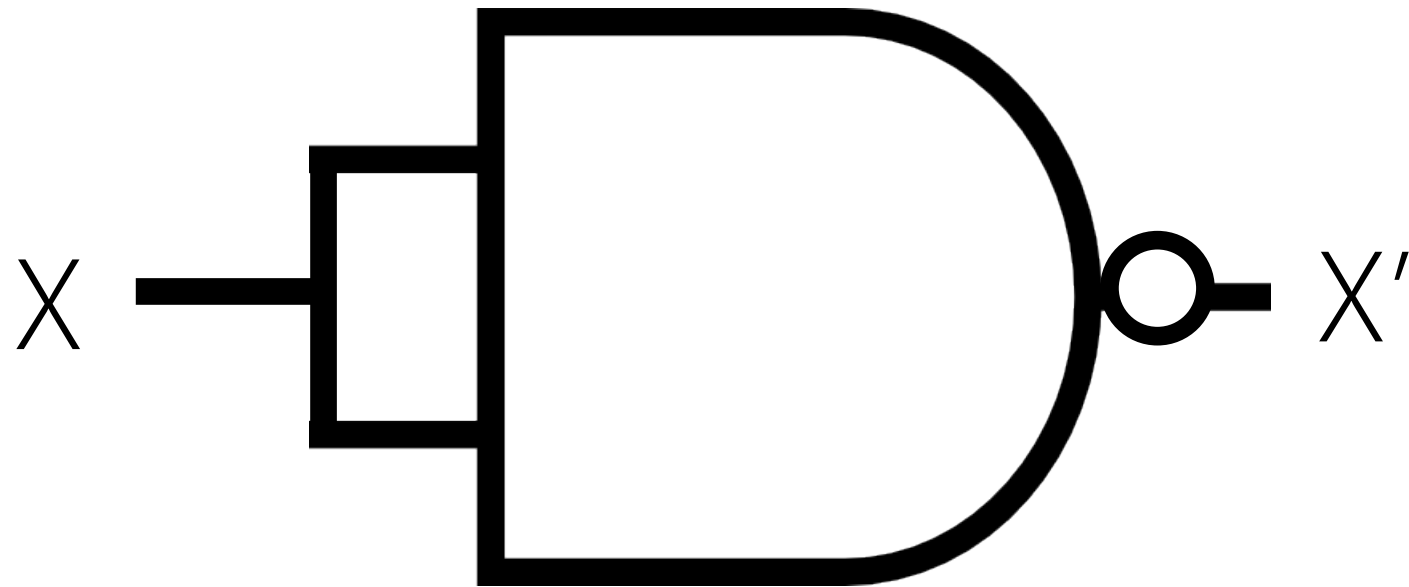
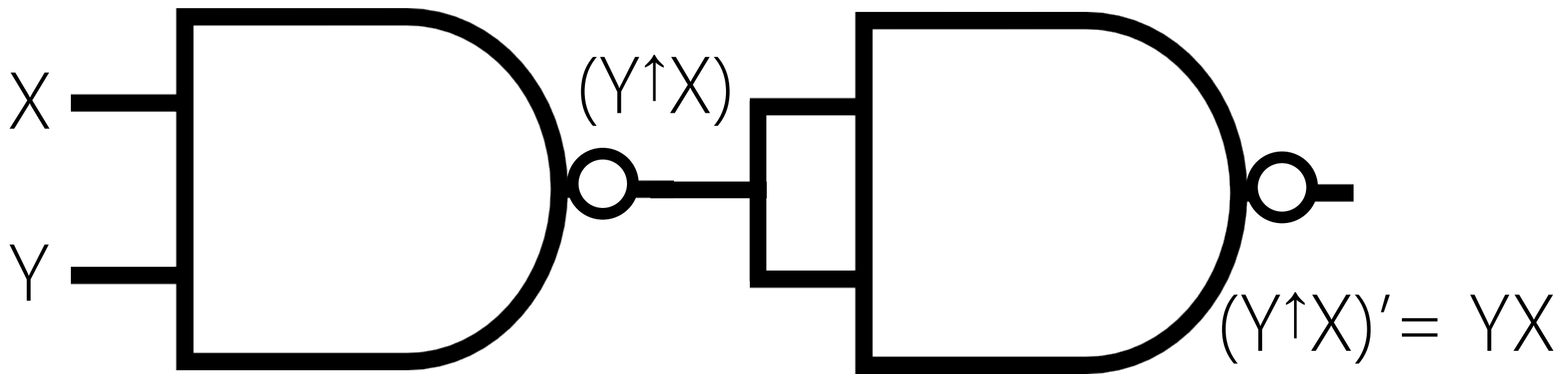
$$\text{AND} \blacktriangleright \text{NOT (NAND)} = ((Y \uparrow X))' = YX$$



# OR ► DE MORGAN'S LAW


$$(Y + X)' = Y'X'$$

$$((Y + X)')' = (Y'X')'$$

$$Y + X = (Y'X')'$$



$$Y + X = Y' \uparrow X'$$

# OR: DE MORGAN'S LAW

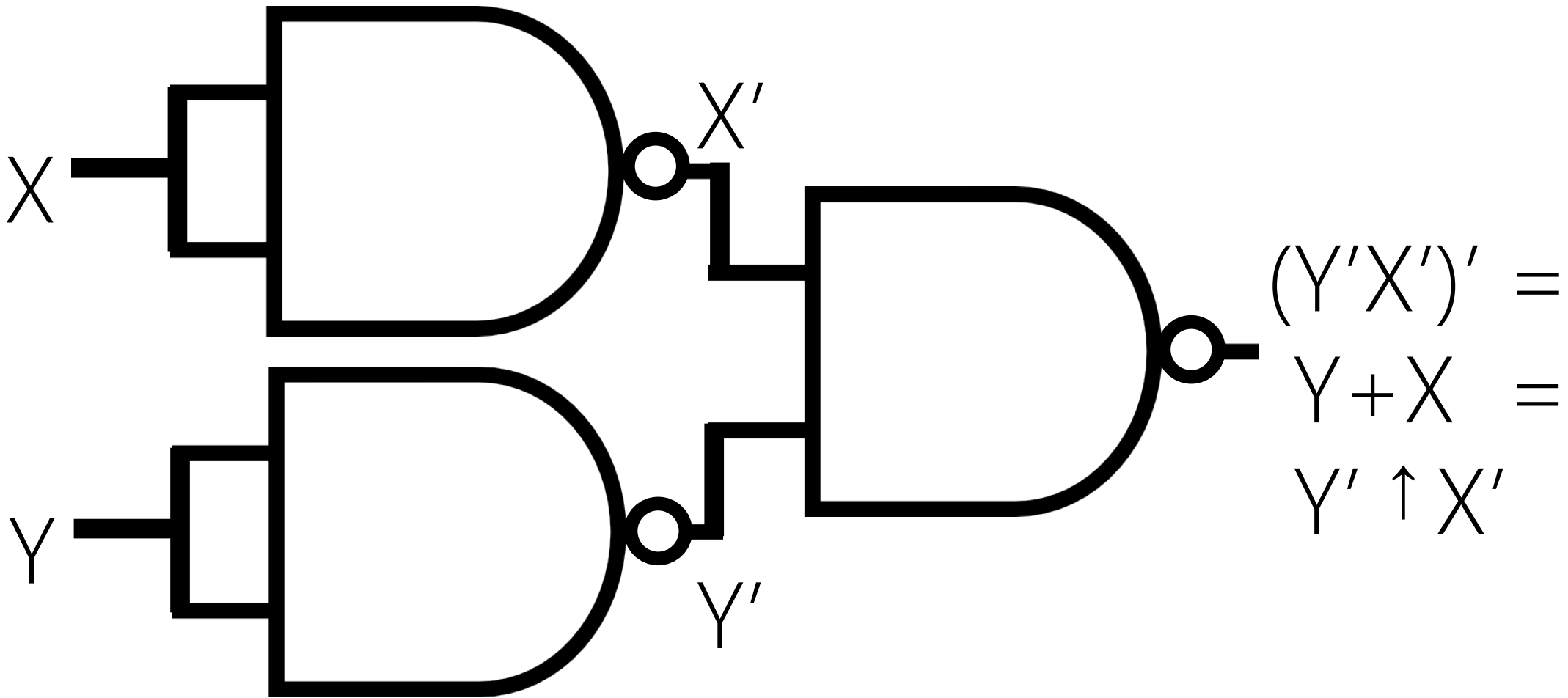

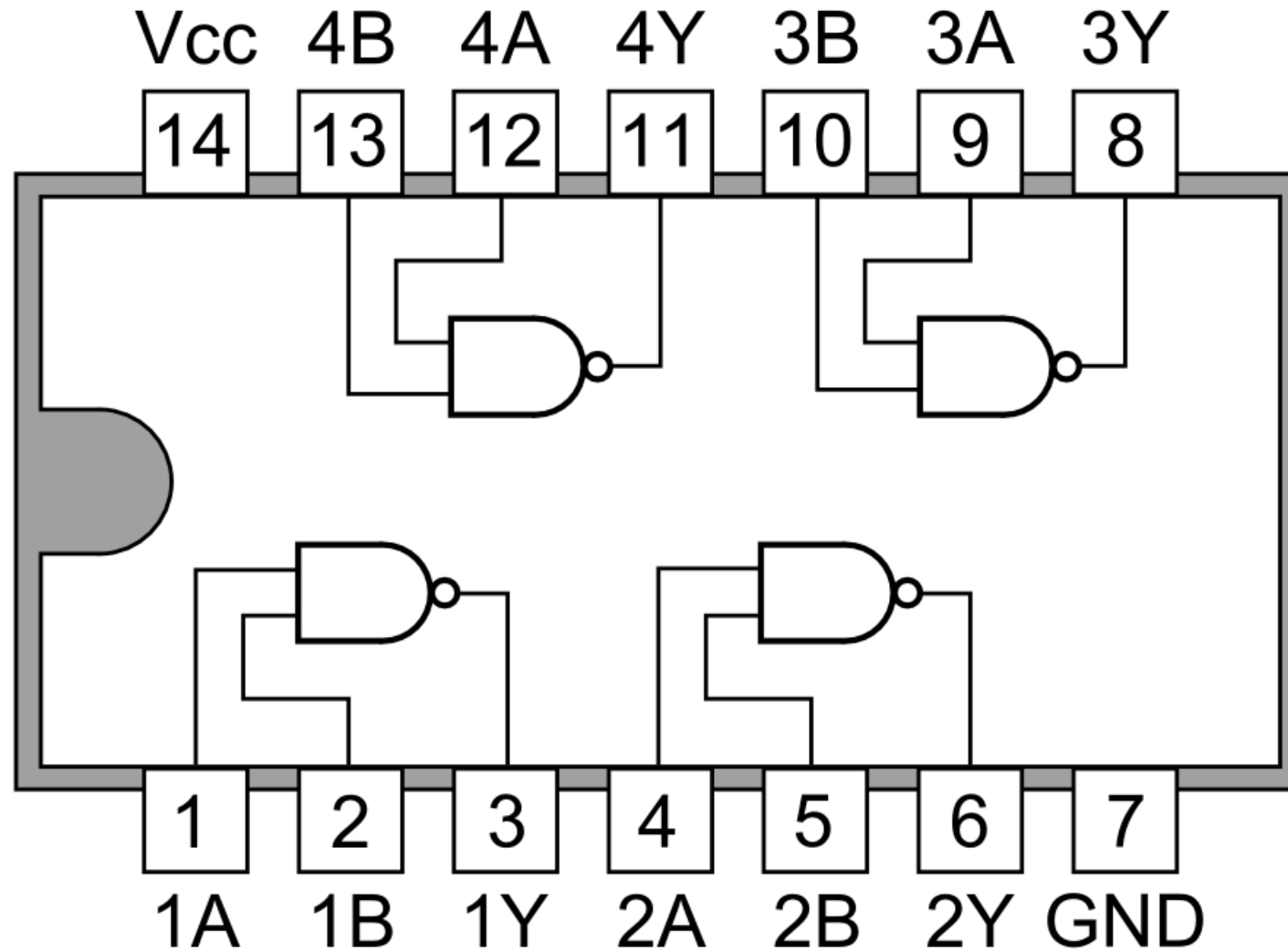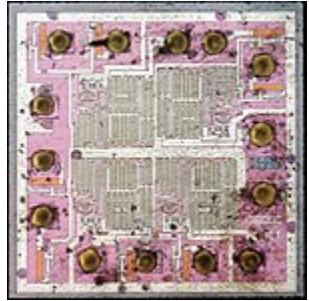
# 7400 Quad 2-input NAND Gates

[https://commons.wikimedia.org/wiki/7400\\_series\\_overview](https://commons.wikimedia.org/wiki/7400_series_overview)



# 7400 Quad 2-input NAND Gates

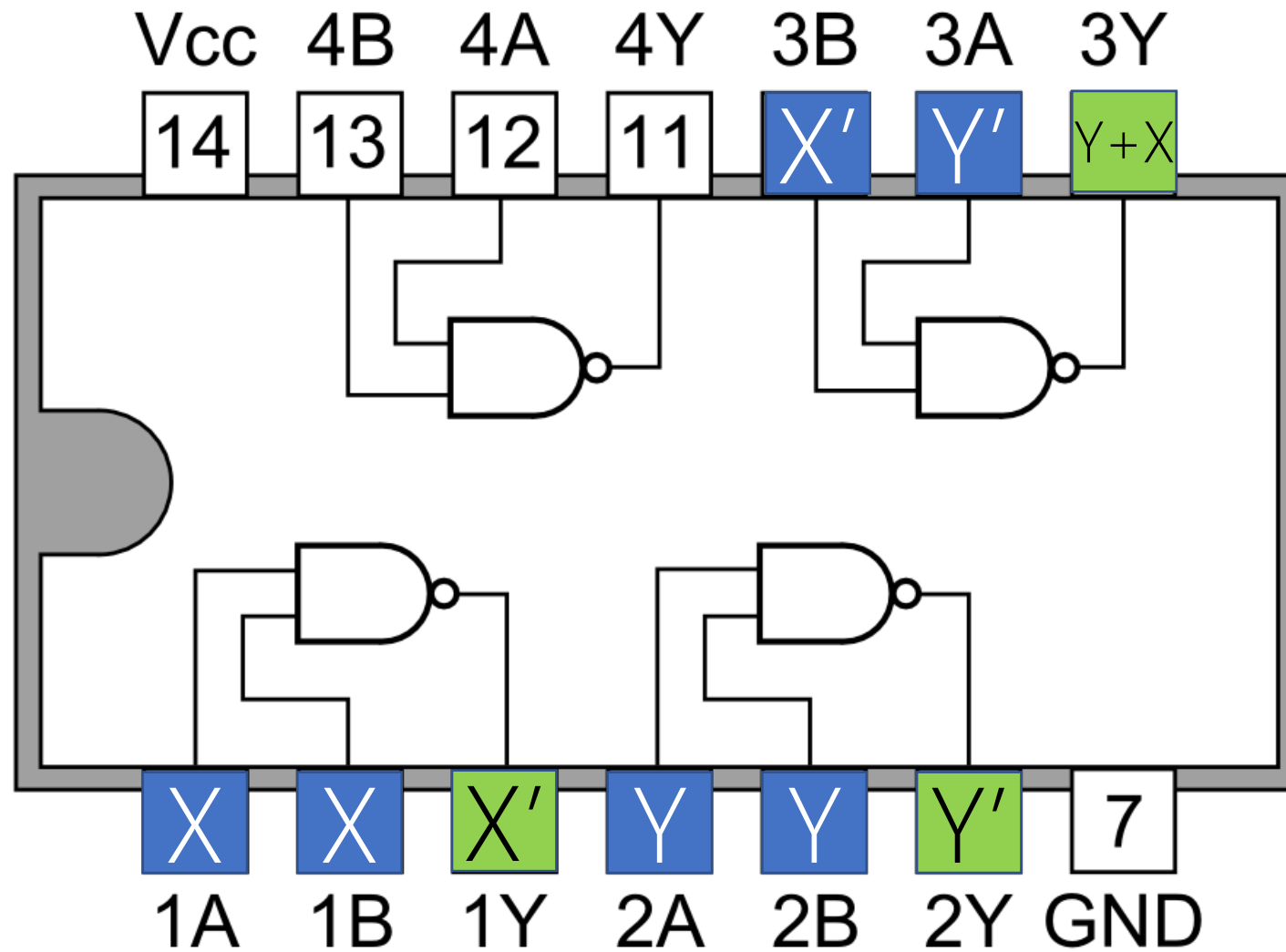

SET	UNIVERSAL SET
{NOT, AND, OR, NAND, NOR}	Yes! (a Full Set)
{NOT, AND, OR}	Yes, (a Full Set) NAND = AND-NOT NOR = OR-NOT
{NOT, AND}	If we could design OR (a Complete Set)
{NOT, OR}	If we could design AND (a Complete Set)
{NOT}	If we could design AND, OR
{AND}	If we could design NOT, OR
{OR}	If we could design NOT, AND
{NAND}	If we could design NOT, AND, OR
{NOR}	If we could design NOT, AND, OR

---

# UNIVERSAL GATE

## {NOR}

---



NOT    ►  $(X+X)' = (XX) = X'$



OR    ► NOT (NOR)

AND    ► DE MORGAN'S LAW  
 $(Y'+X')' = YX = (Y'\downarrow X')$



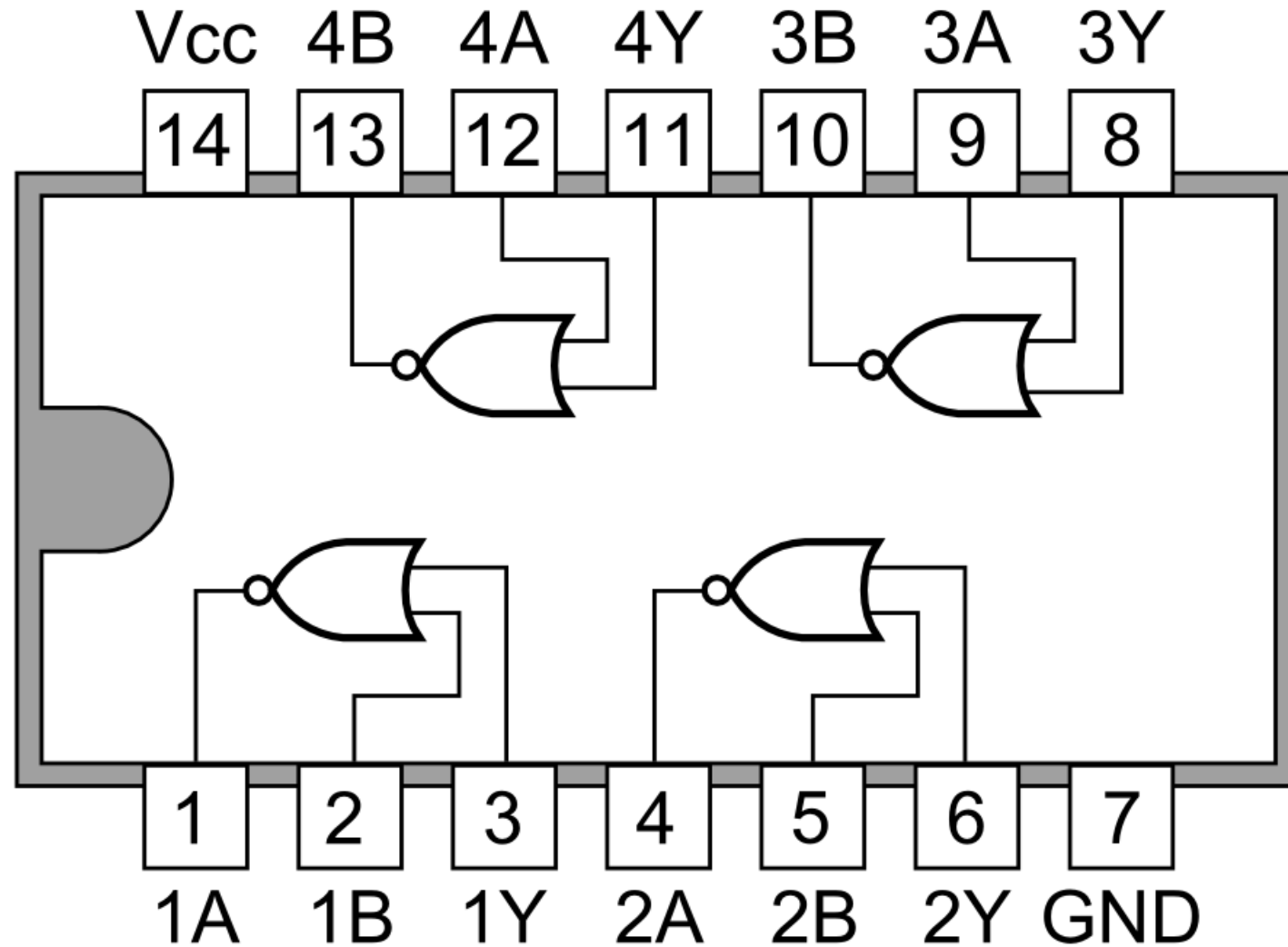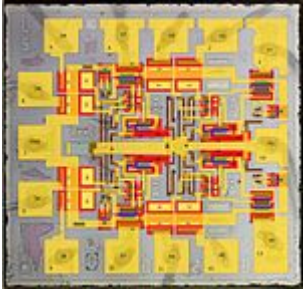
# 7402 Quad 2-input NOR Gates

[https://commons.wikimedia.org/wiki/7400\\_series\\_overview](https://commons.wikimedia.org/wiki/7400_series_overview)



# 7402 Quad 2-input NOR Gates

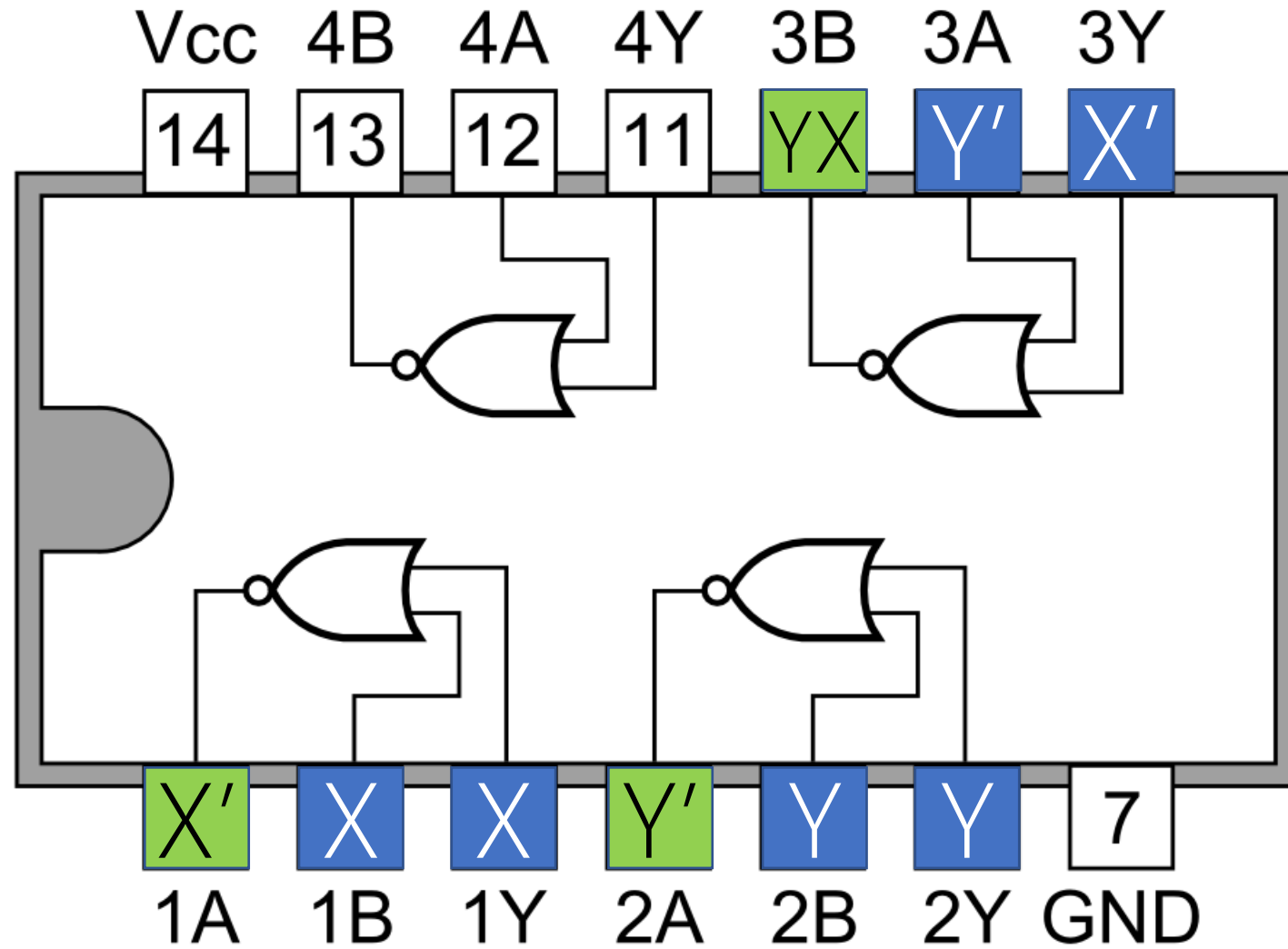


---

UNIVERSAL GATE


SoP  $\rightarrow$  {NAND}

---

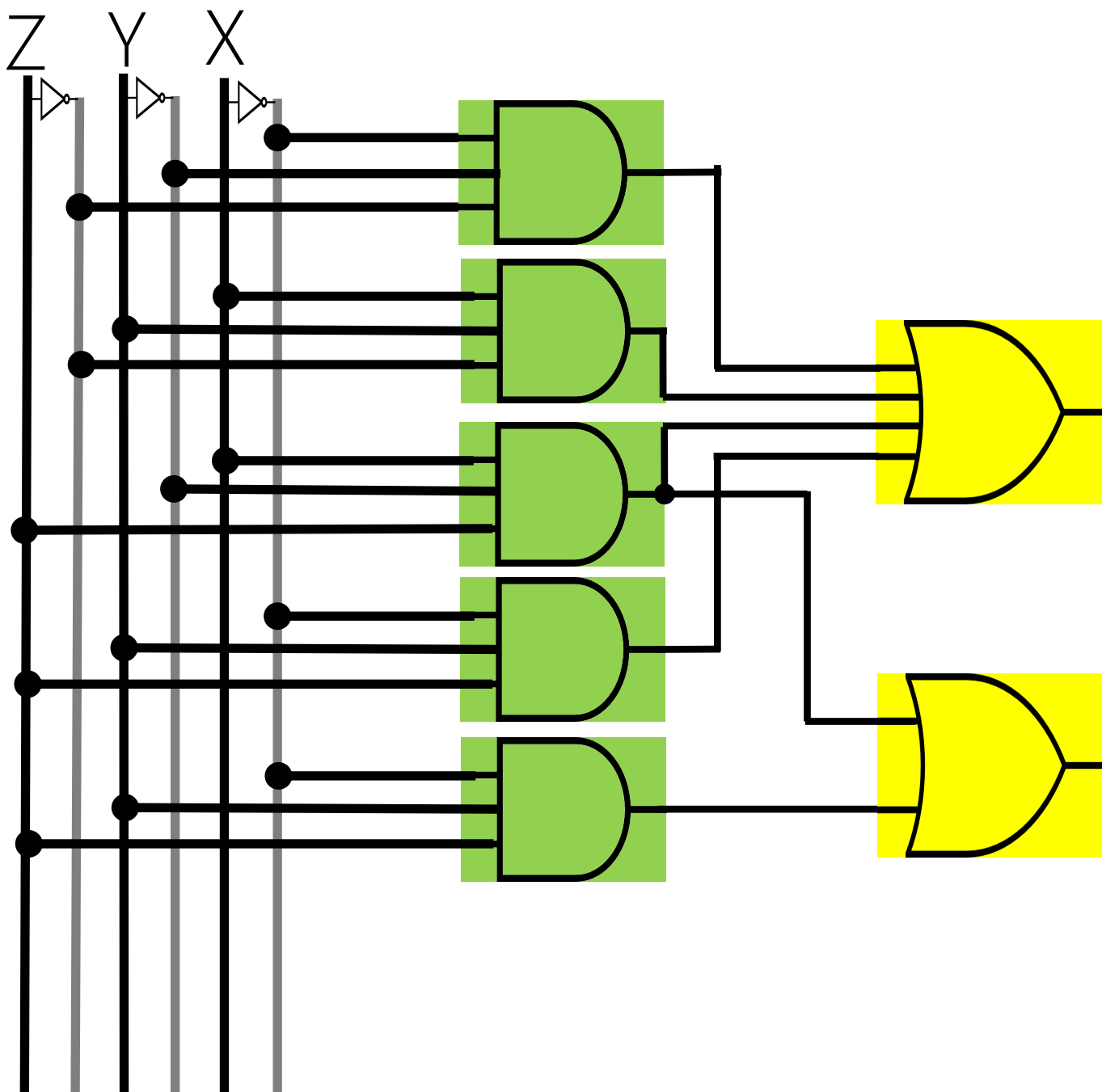


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$F_2 = ZY'X' + ZY'X$$

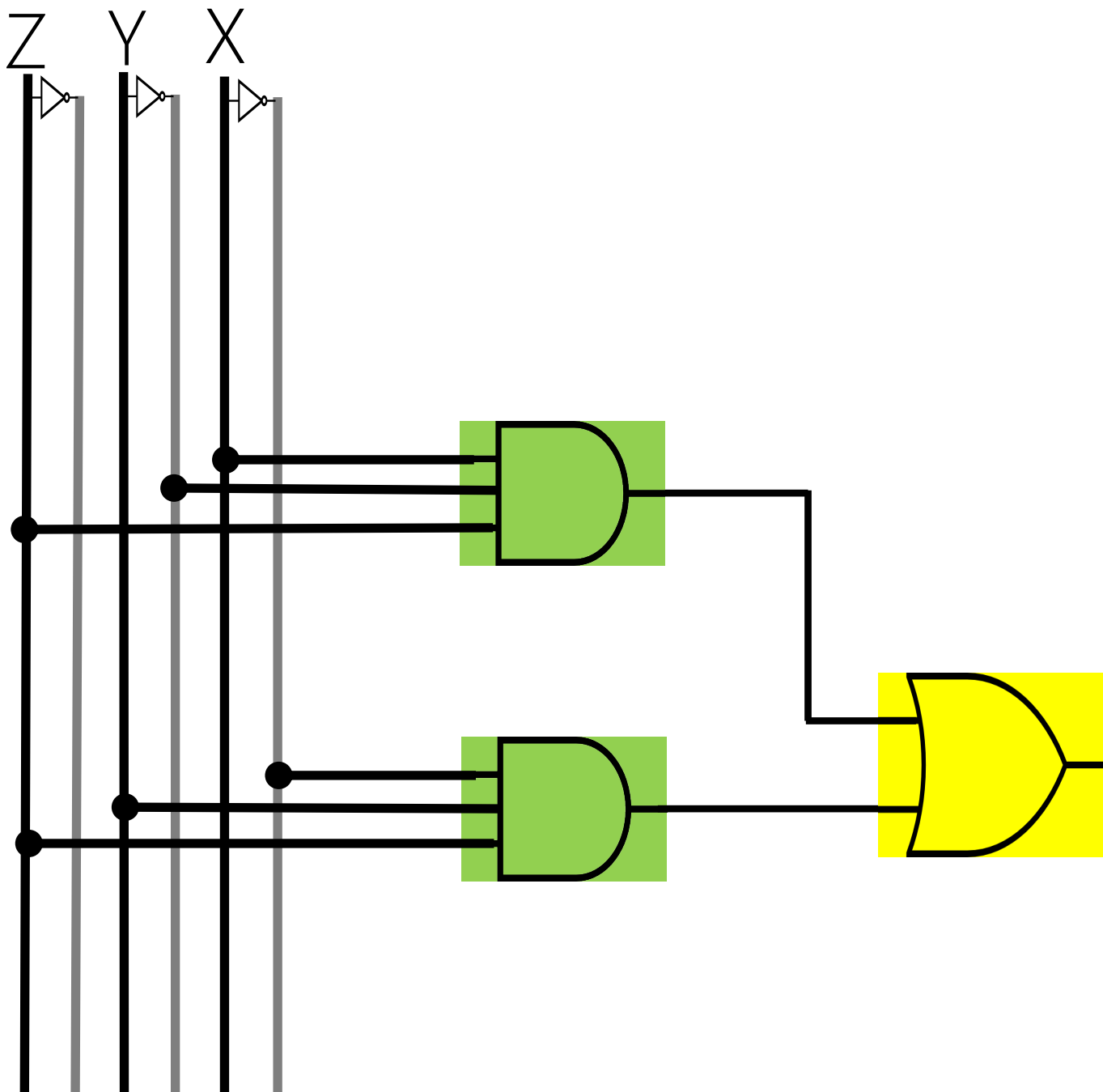


$$F_2 = ZY'X' + ZY'X$$

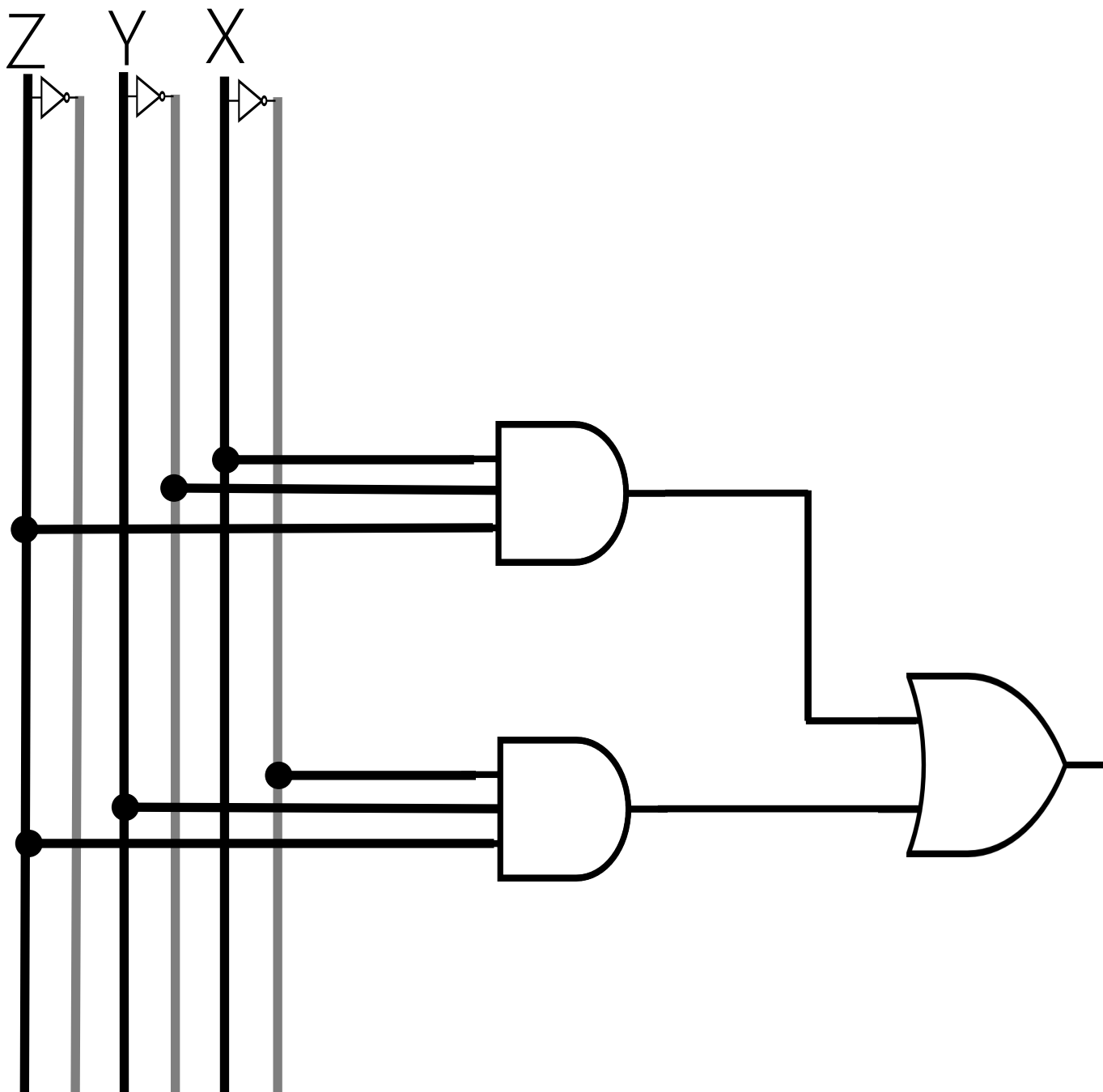


$$F_2 = m_4 + m_5$$

$$= ((F_2)')'$$




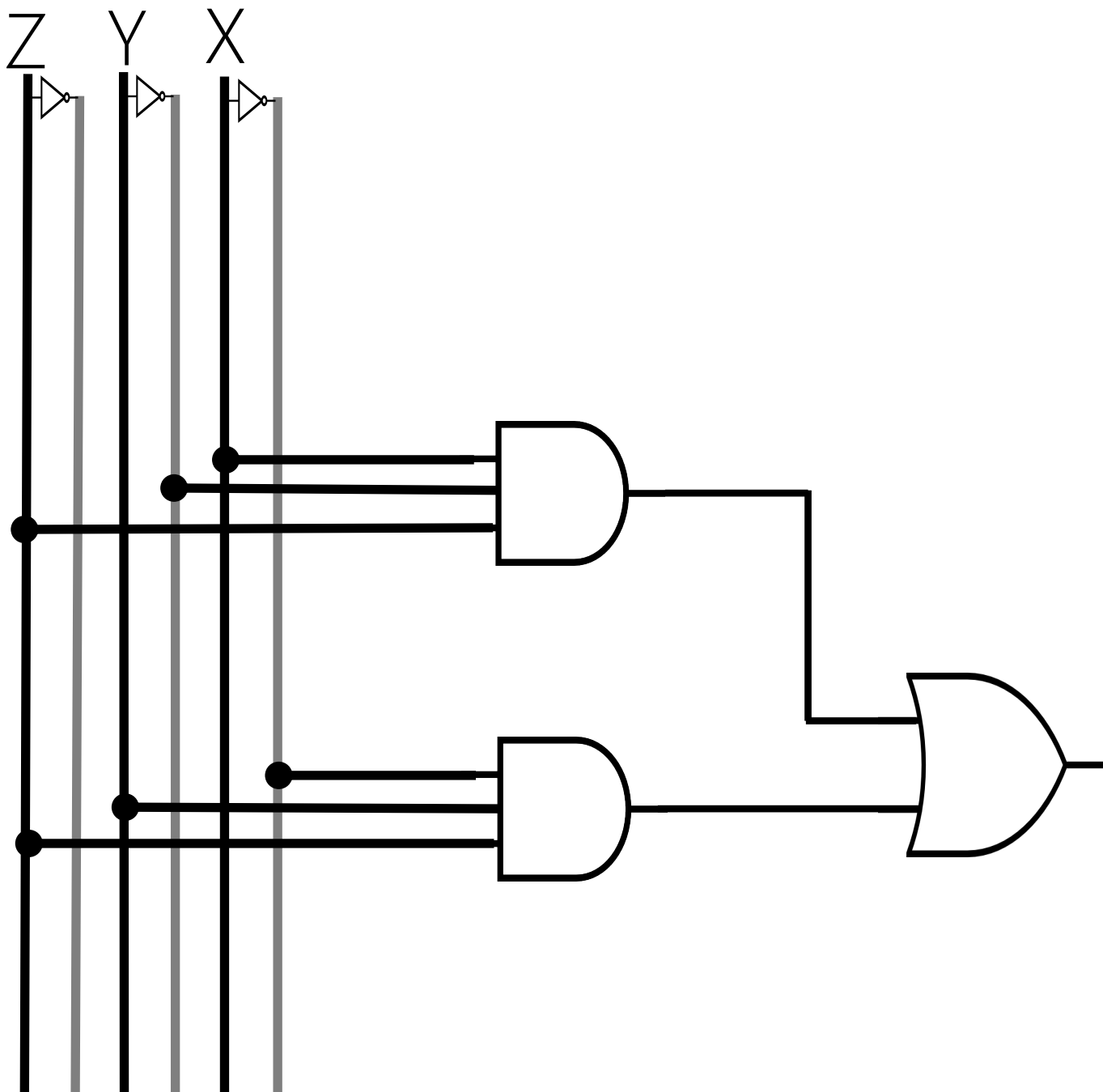

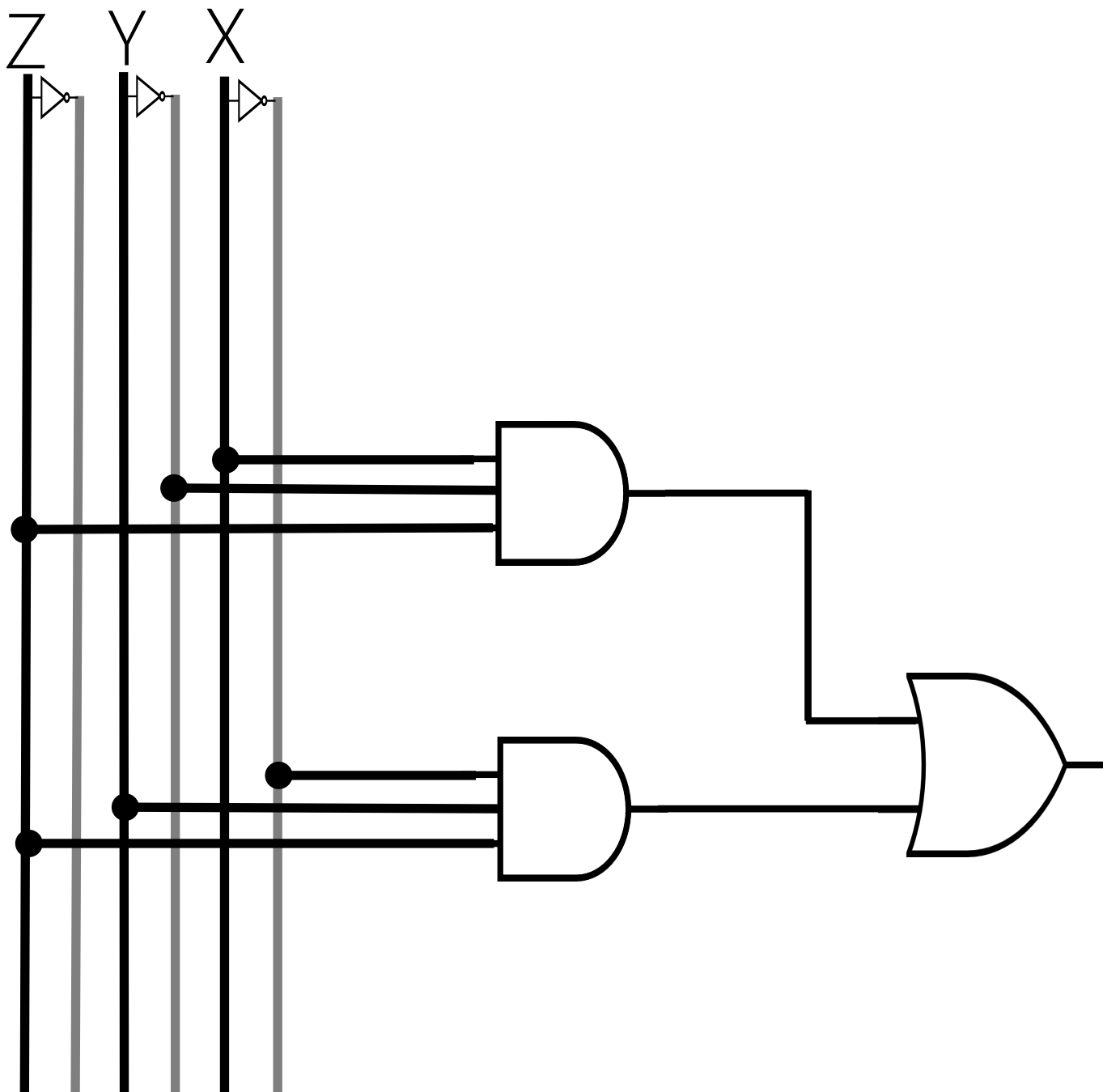
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')'
 \end{aligned}$$



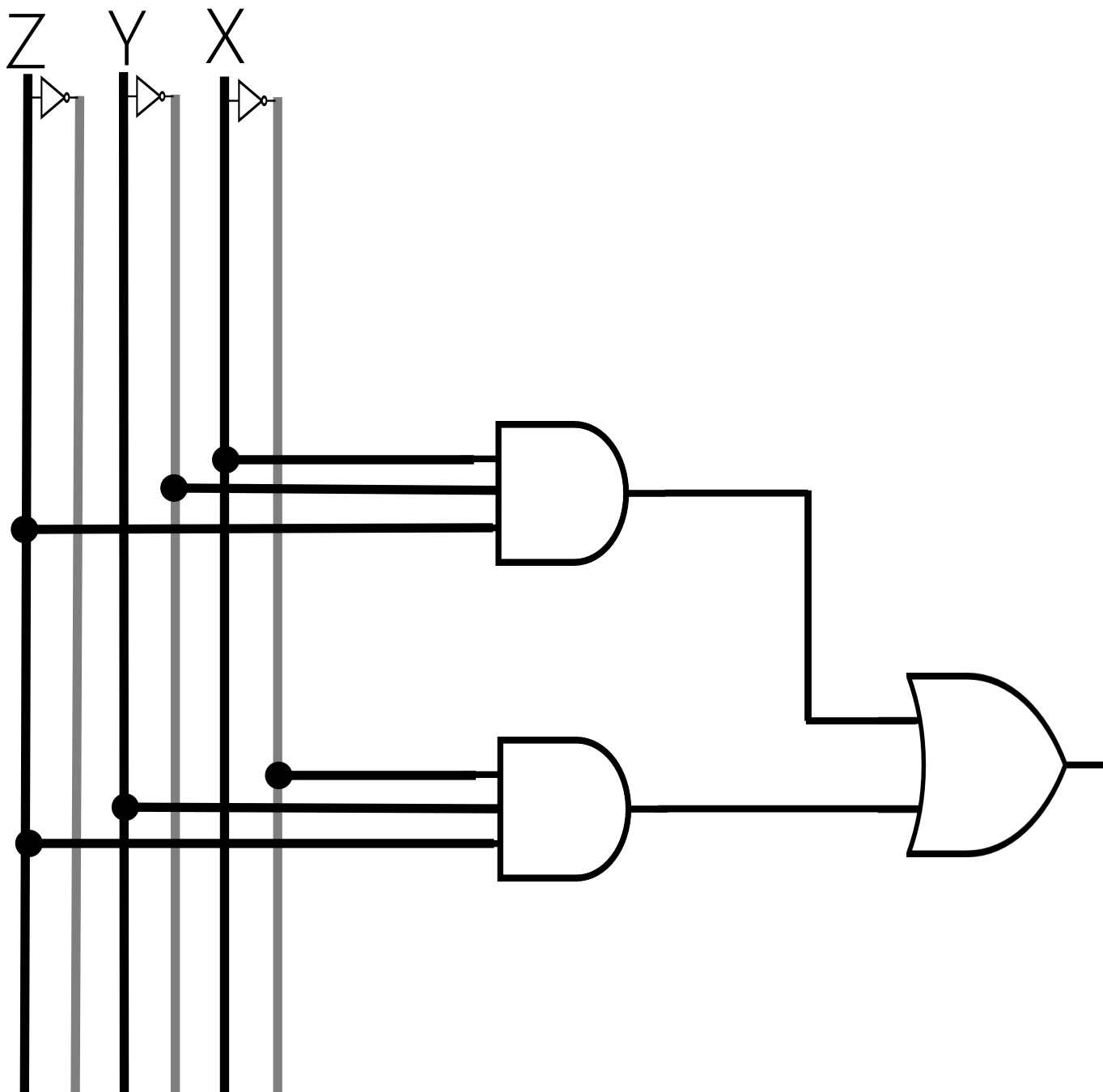
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m_4' m_5')'
 \end{aligned}$$



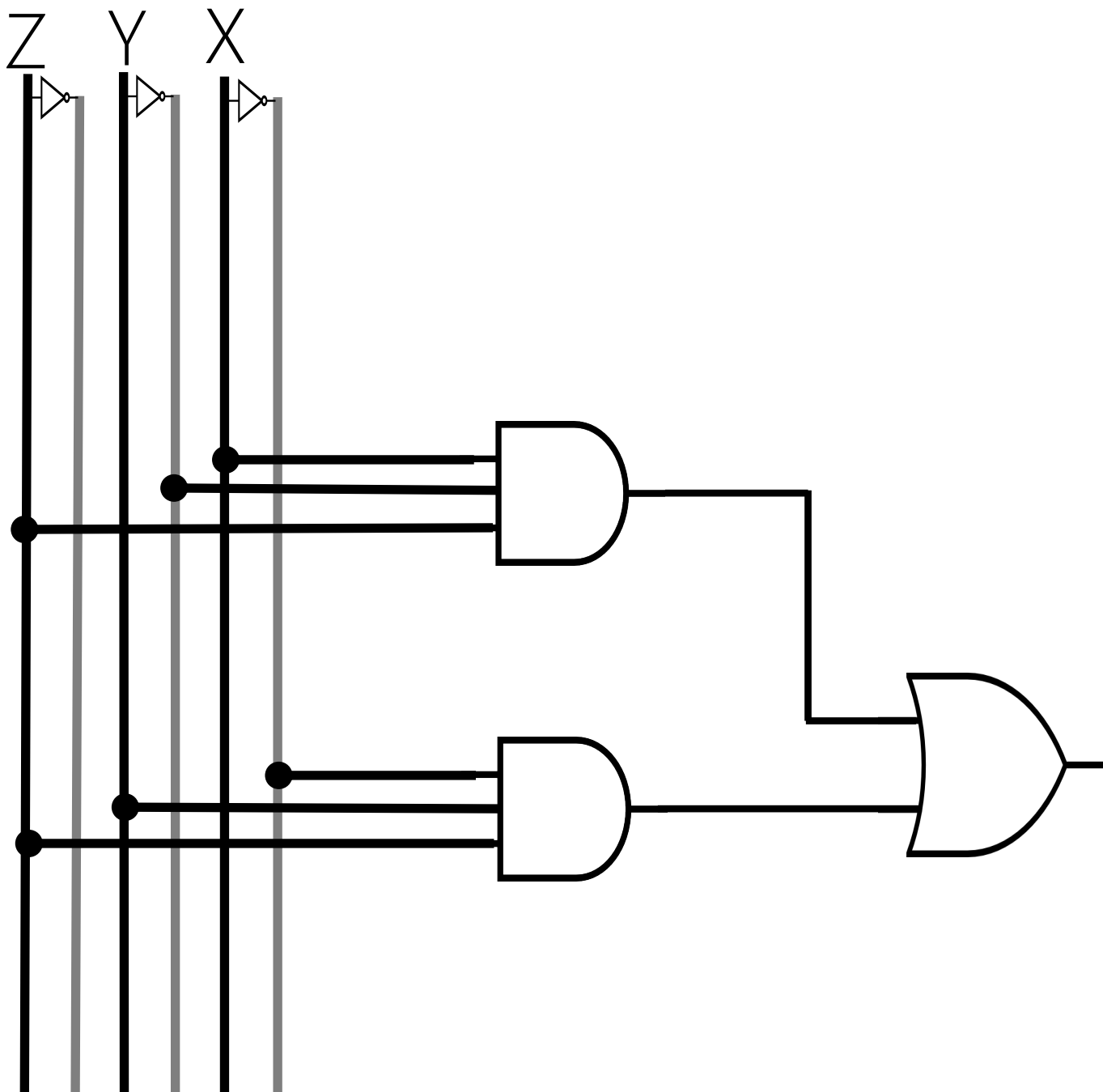
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')'
 \end{aligned}$$



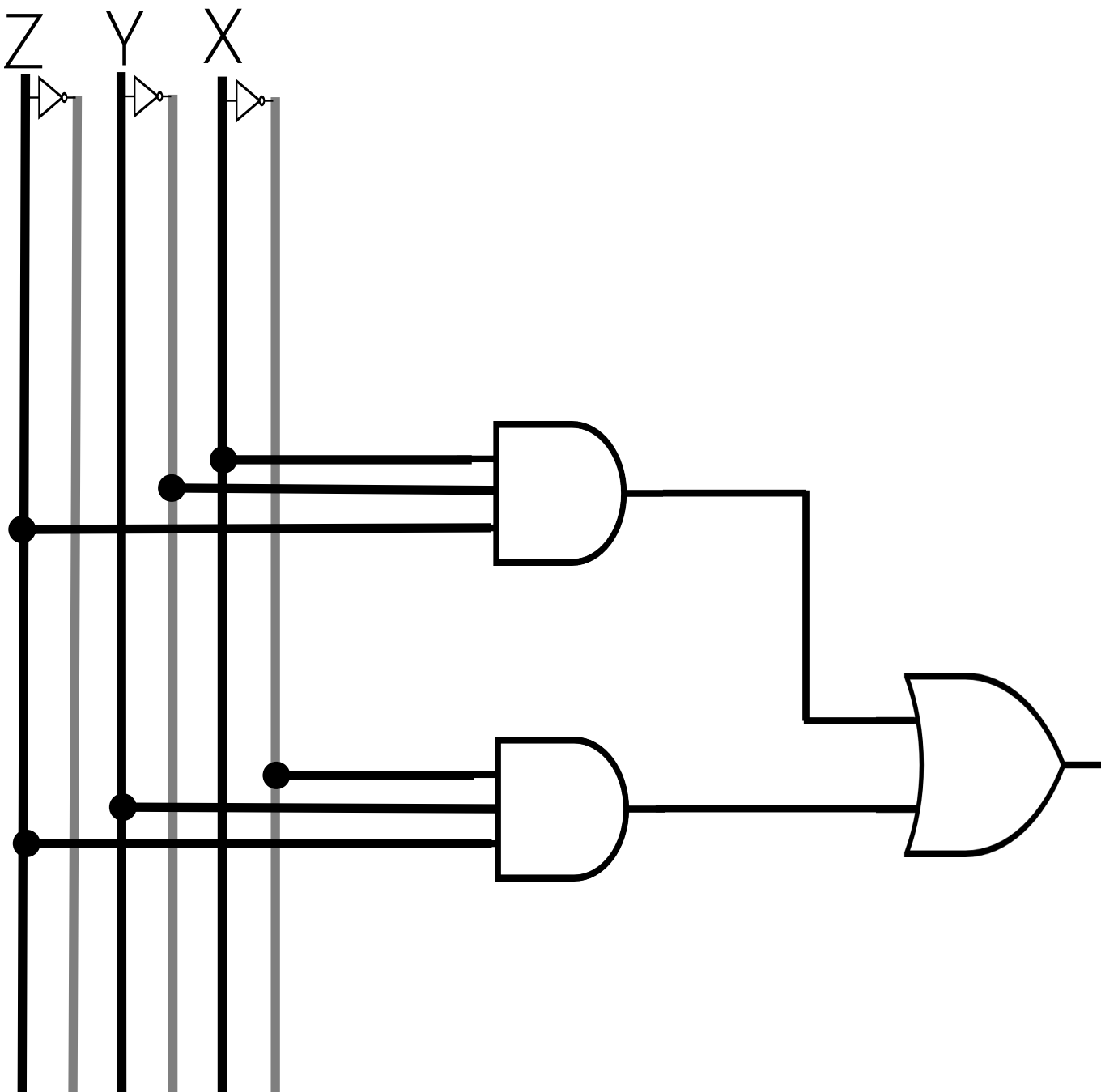
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')' \\
 &= ((Z \uparrow Y' \uparrow X') (Z \uparrow Y' \uparrow X))'
 \end{aligned}$$



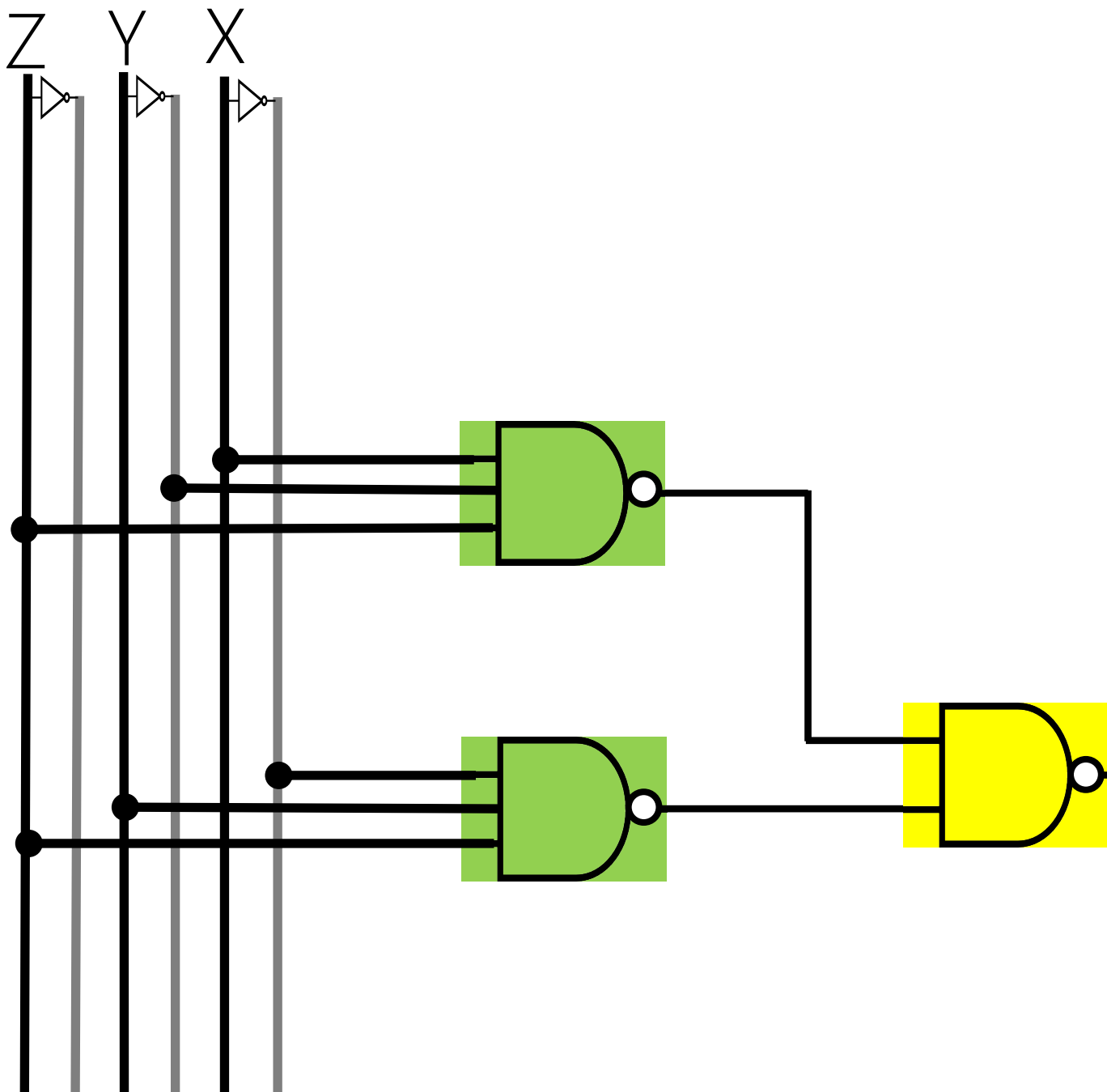
$$\begin{aligned}
 F_2 &= m_4 + m_5 \\
 &= ((F_2)')' \\
 &= ((m_4 + m_5)')' \\
 &= (m'_4 m'_5)' \\
 &= ((ZY'X')' (ZY'X)')' \\
 &= ((Z \uparrow Y' \uparrow X') (Z \uparrow Y' \uparrow X))' \\
 &= ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))
 \end{aligned}$$


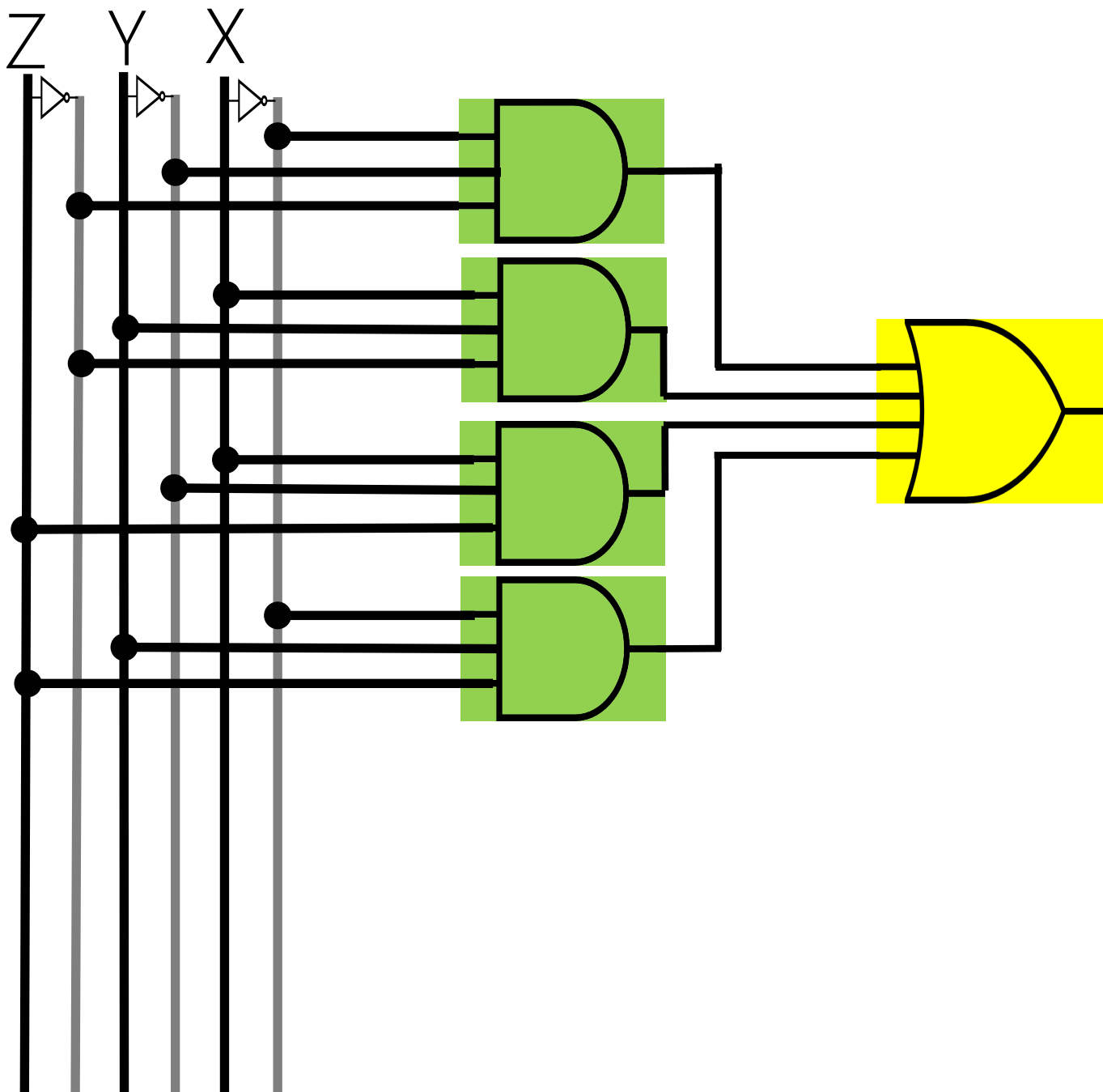
$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$




$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

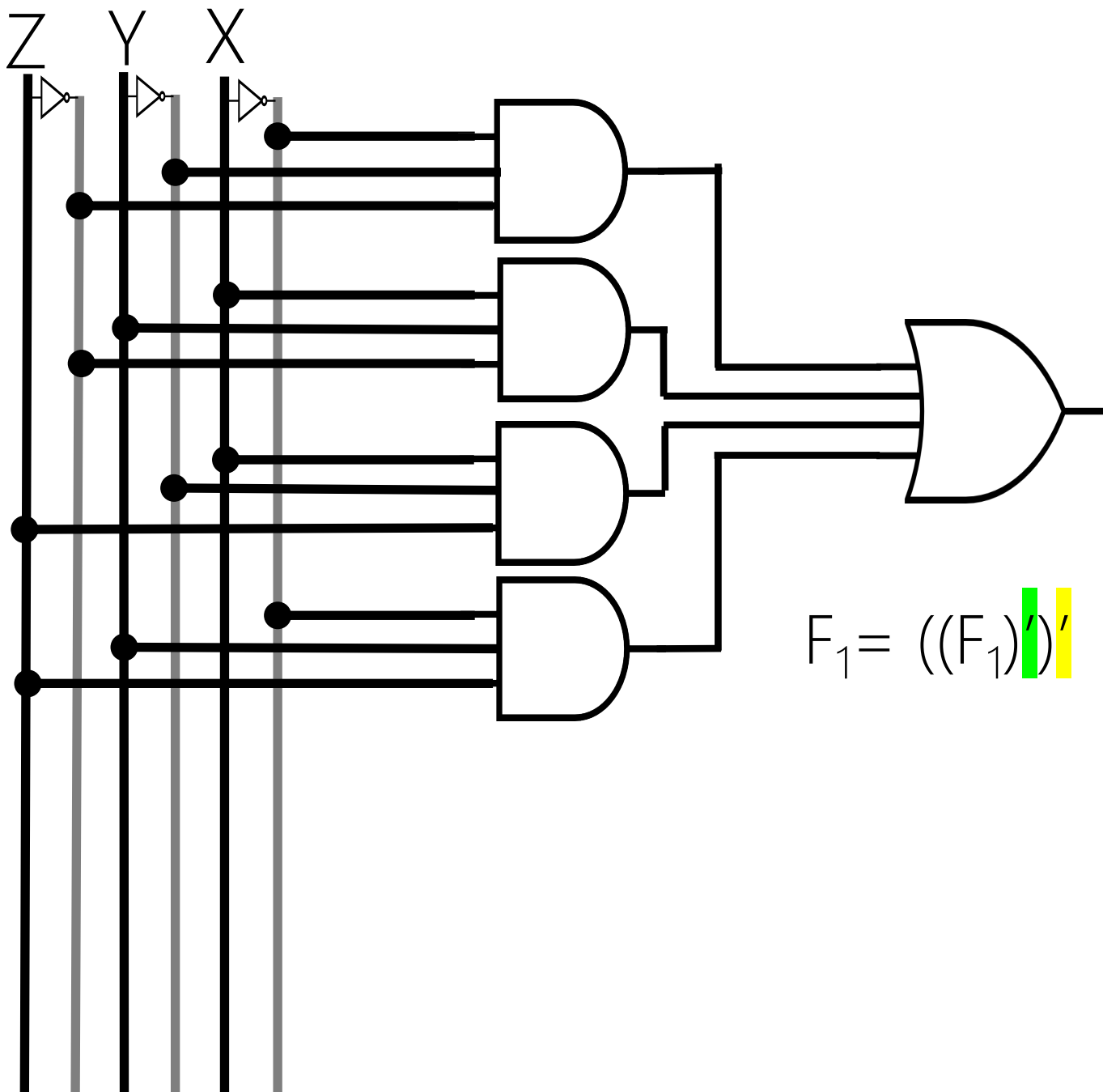

$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$F_1 = ((F_1)')'$$




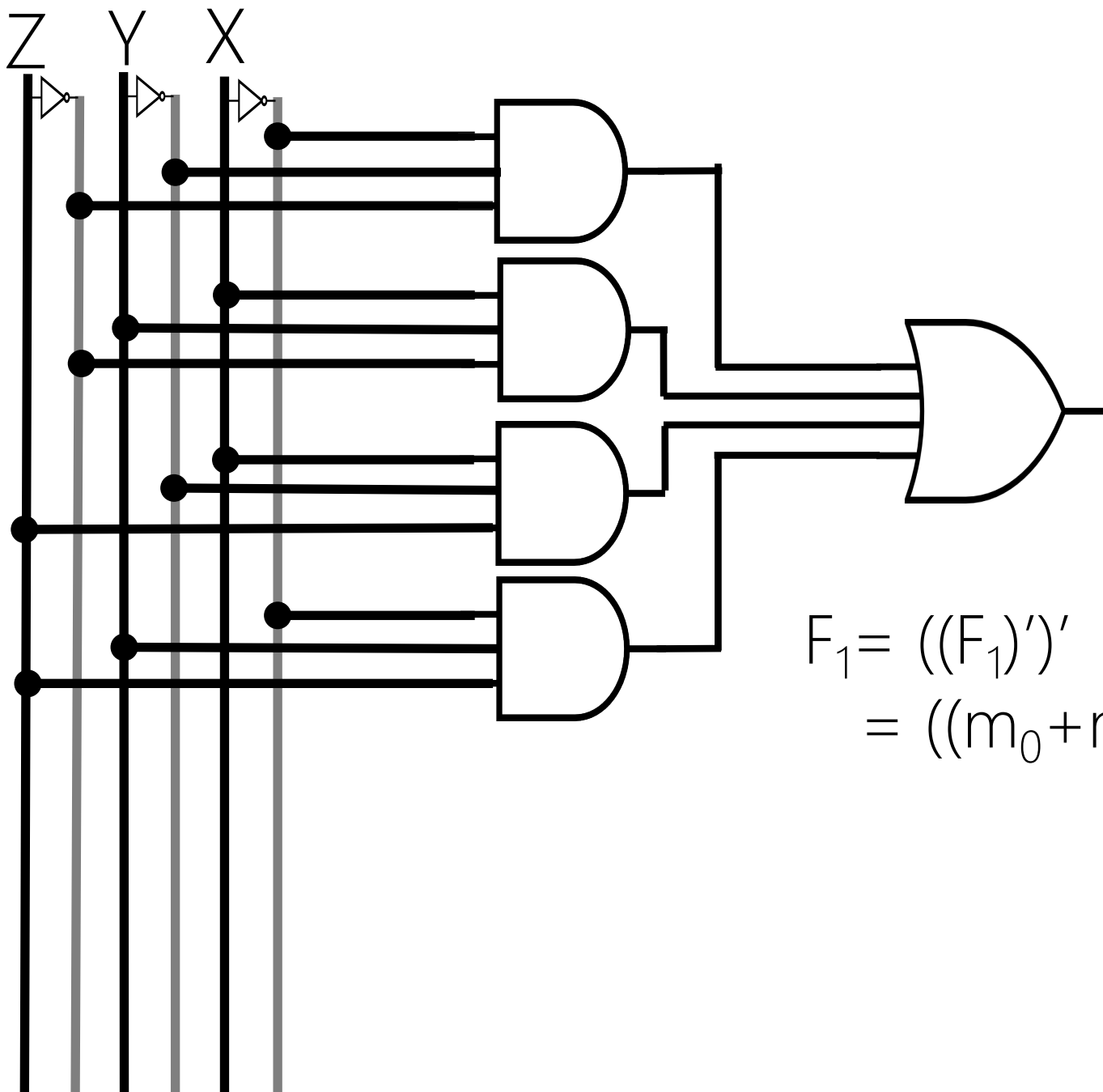


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$F_1 = ((F_1)')'$$


$$= ((m_0 + m_3 + m_5 + m_6)')'$$

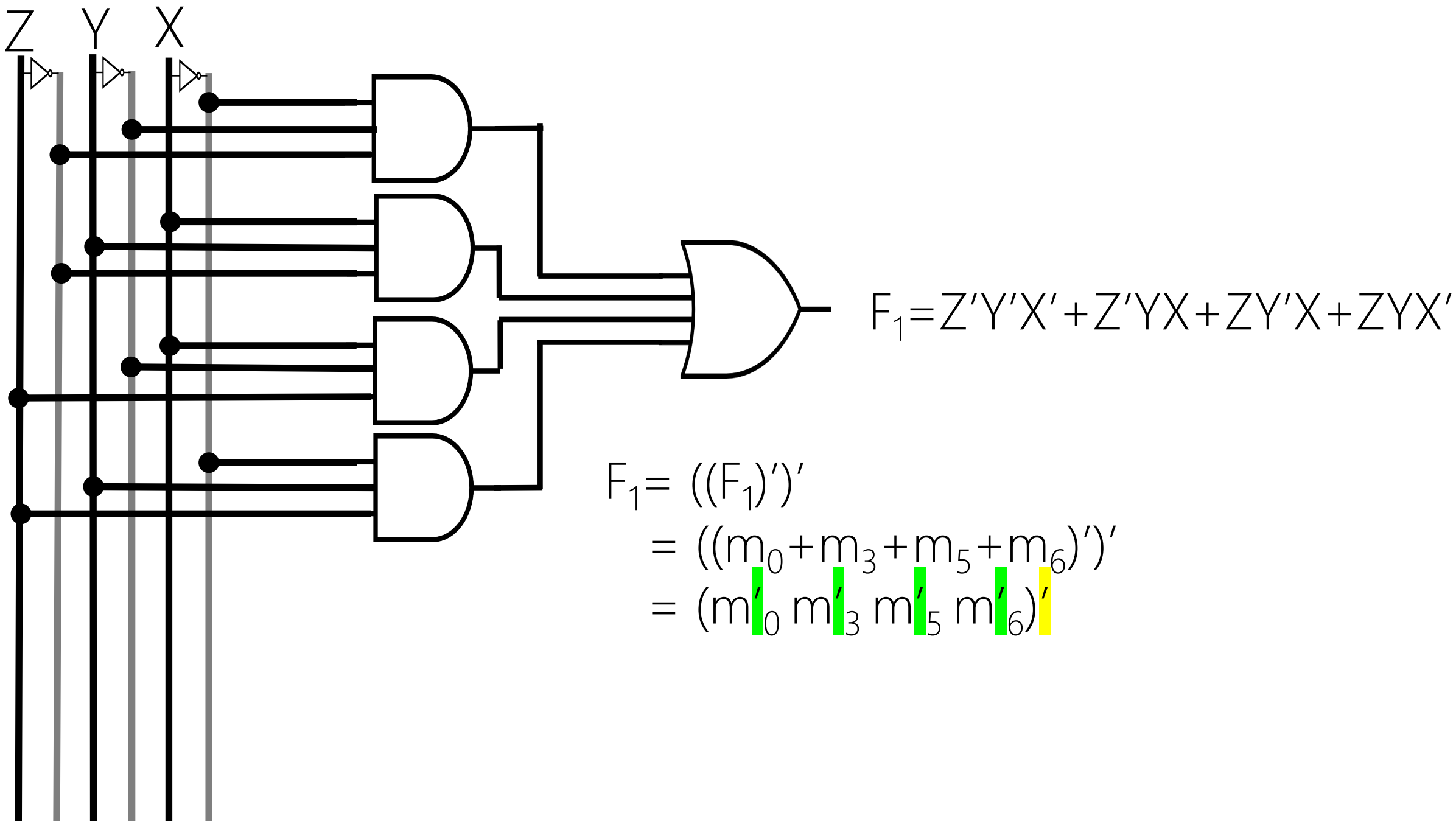

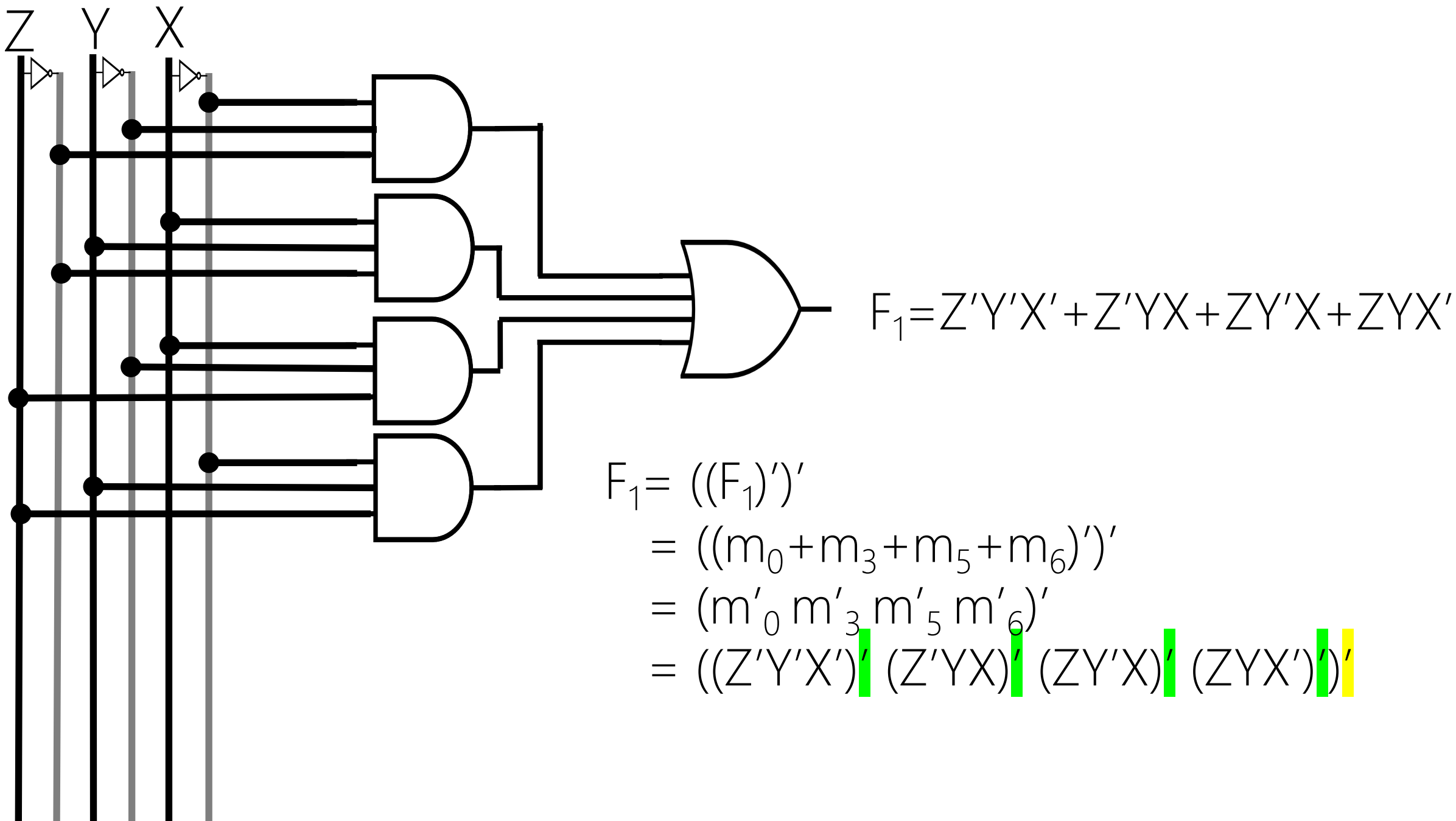
$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)'
 \end{aligned}$$


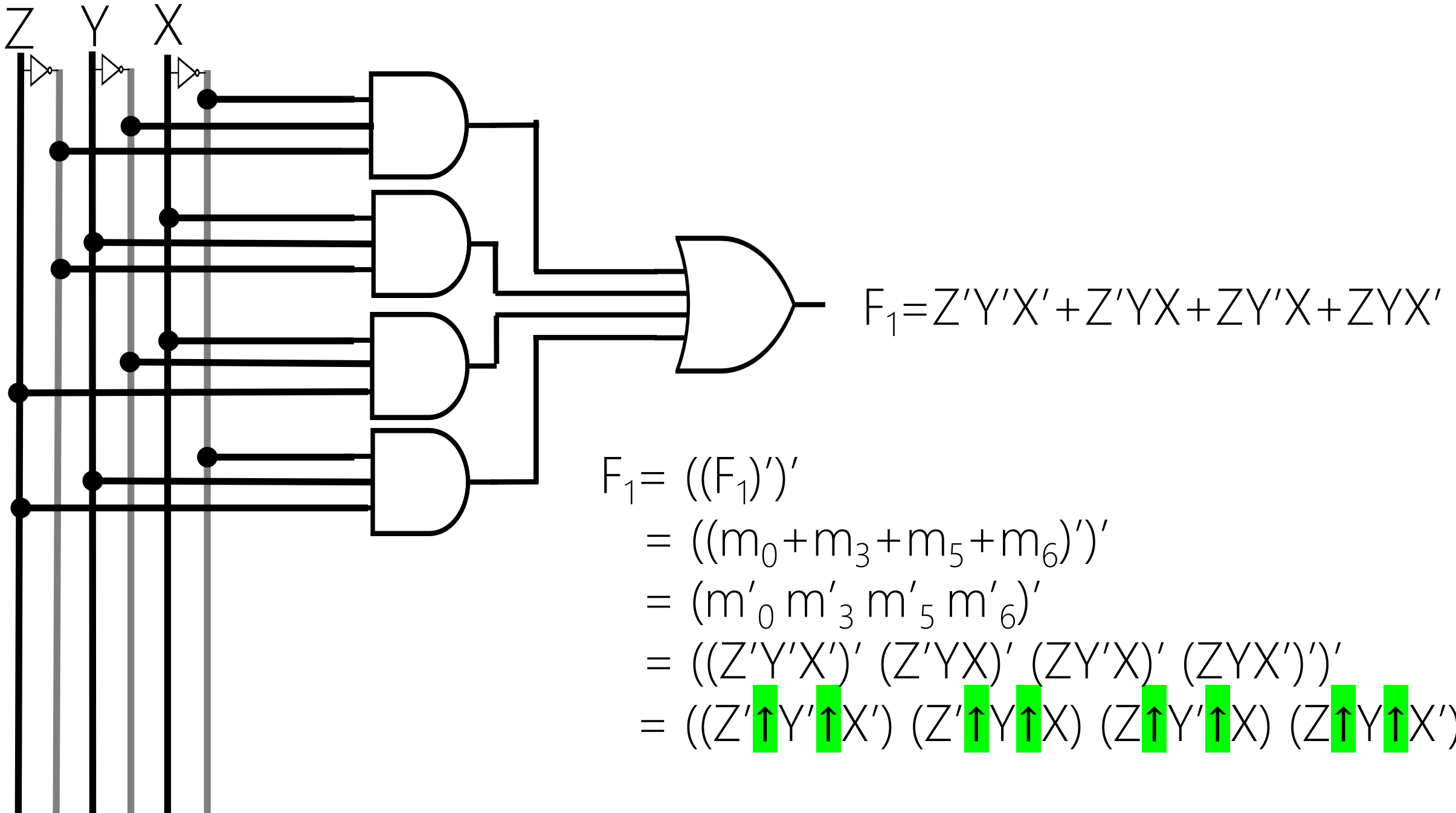
$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (ZYX')')'
 \end{aligned}$$



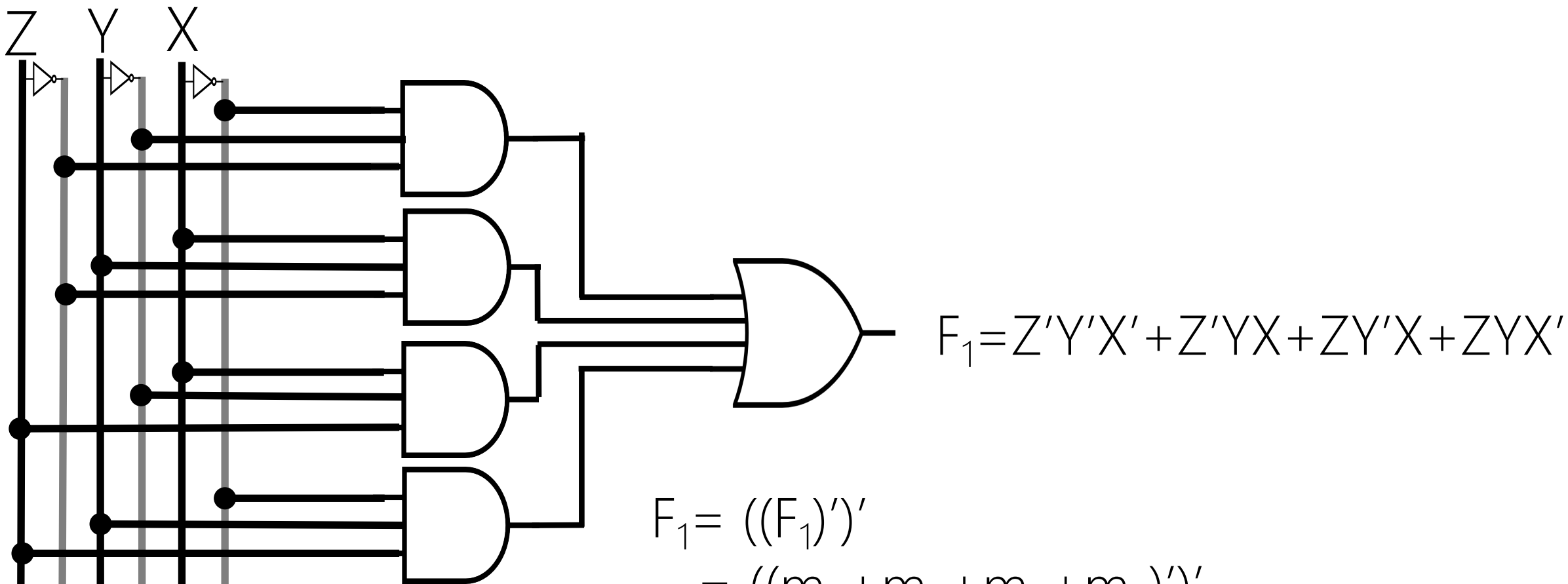
$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (ZYX')')' \\
 &= ((Z'\uparrow Y'\uparrow X') (Z'\uparrow Y\uparrow X) (Z\uparrow Y'\uparrow X) (Z\uparrow Y\uparrow X'))'
 \end{aligned}$$




$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (ZYX'))' \\
 &= ((Z' \uparrow Y' \uparrow X') (Z' \uparrow Y \uparrow X) (Z \uparrow Y' \uparrow X) (Z \uparrow Y \uparrow X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))
 \end{aligned}$$

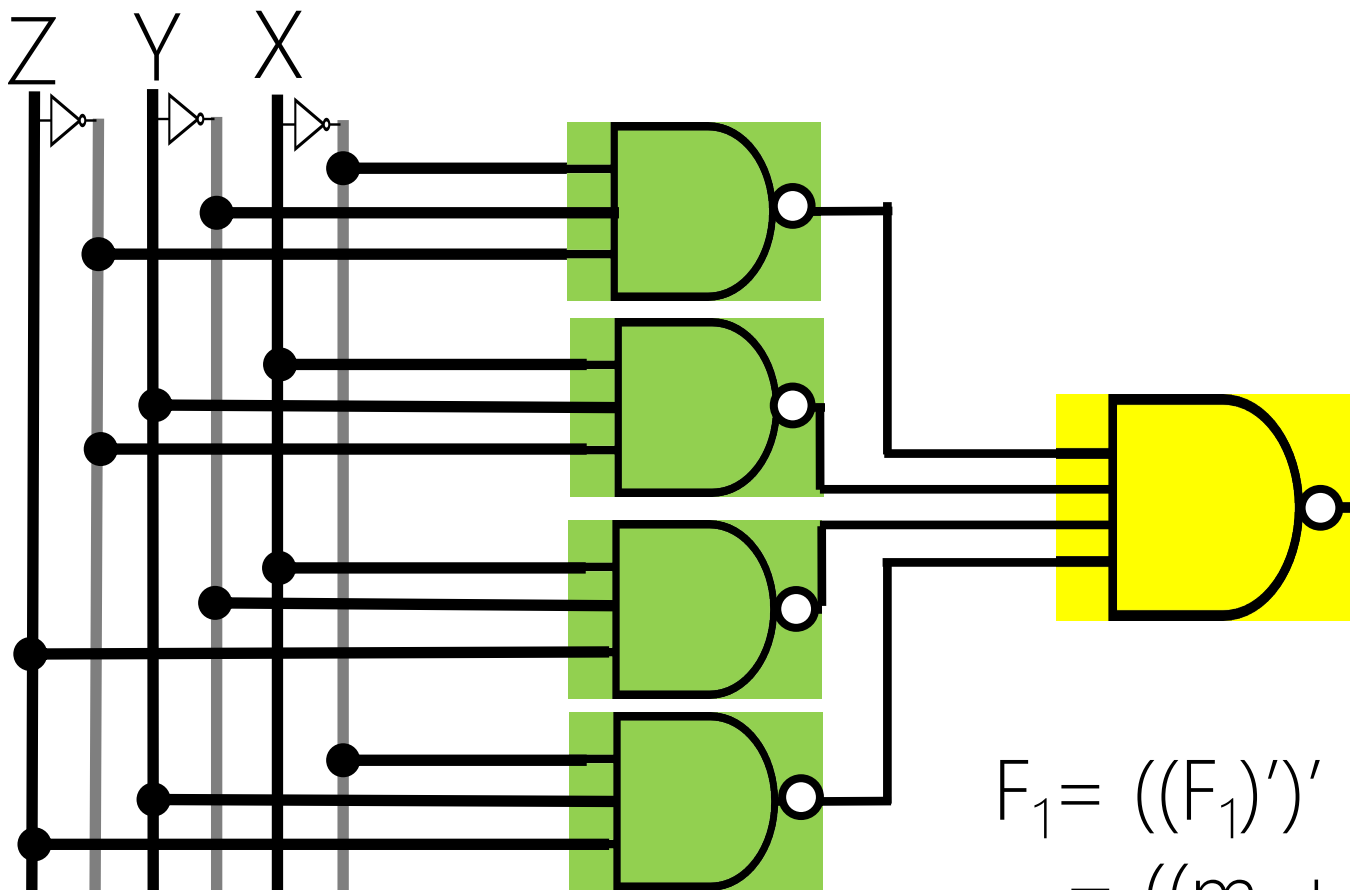

$$\begin{aligned}
 F_1 &= ((F_1)')' \\
 &= ((m_0 + m_3 + m_5 + m_6)')' \\
 &= (m'_0 m'_3 m'_5 m'_6)' \\
 &= ((Z'Y'X')' (Z'YX)' (ZY'X)' (Z Y X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') (Z' \uparrow Y \uparrow X) (Z \uparrow Y' \uparrow X) (Z \uparrow Y \uparrow X'))' \\
 &= ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))
 \end{aligned}$$


Z Y X

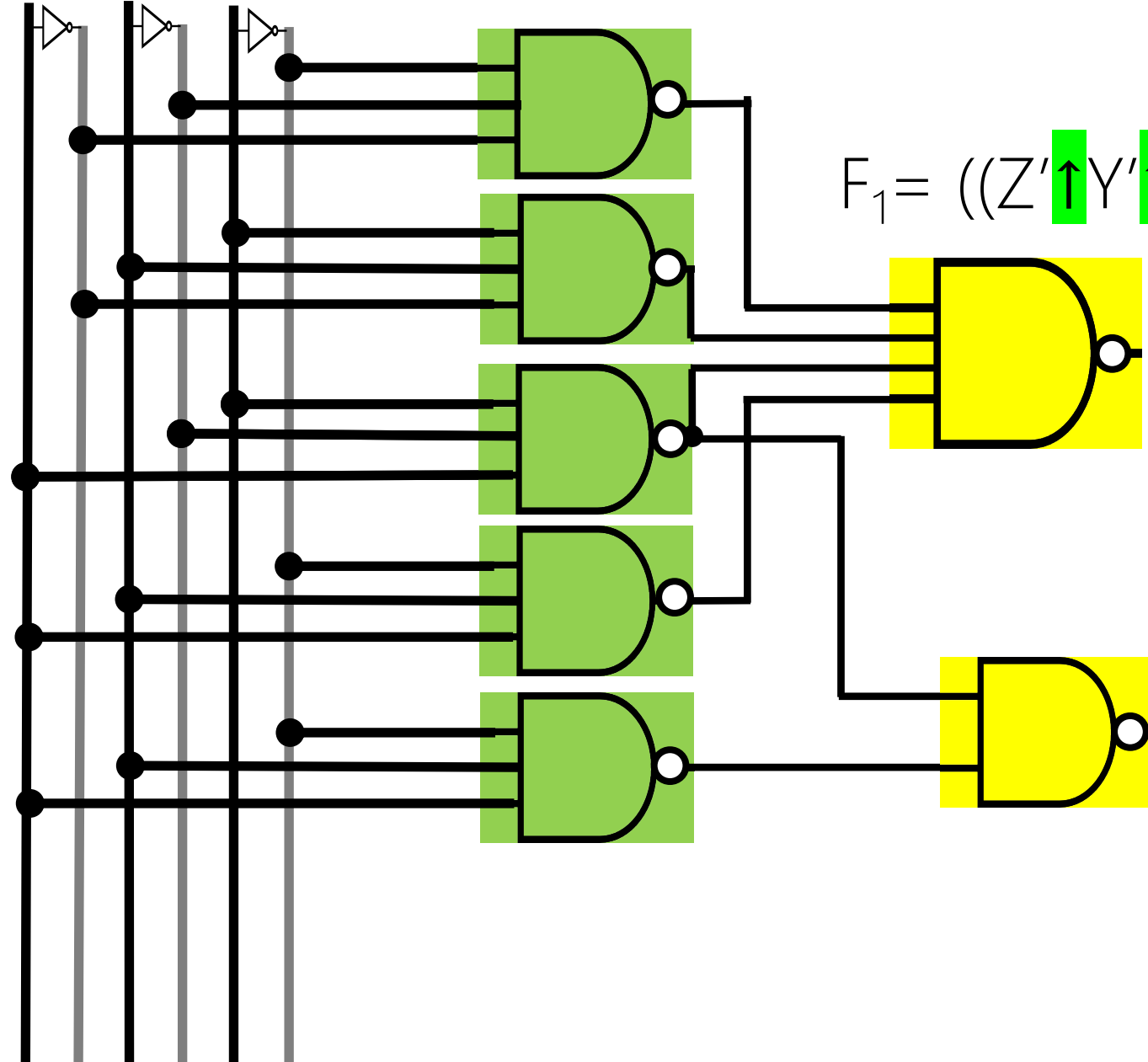

$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$

Z Y X

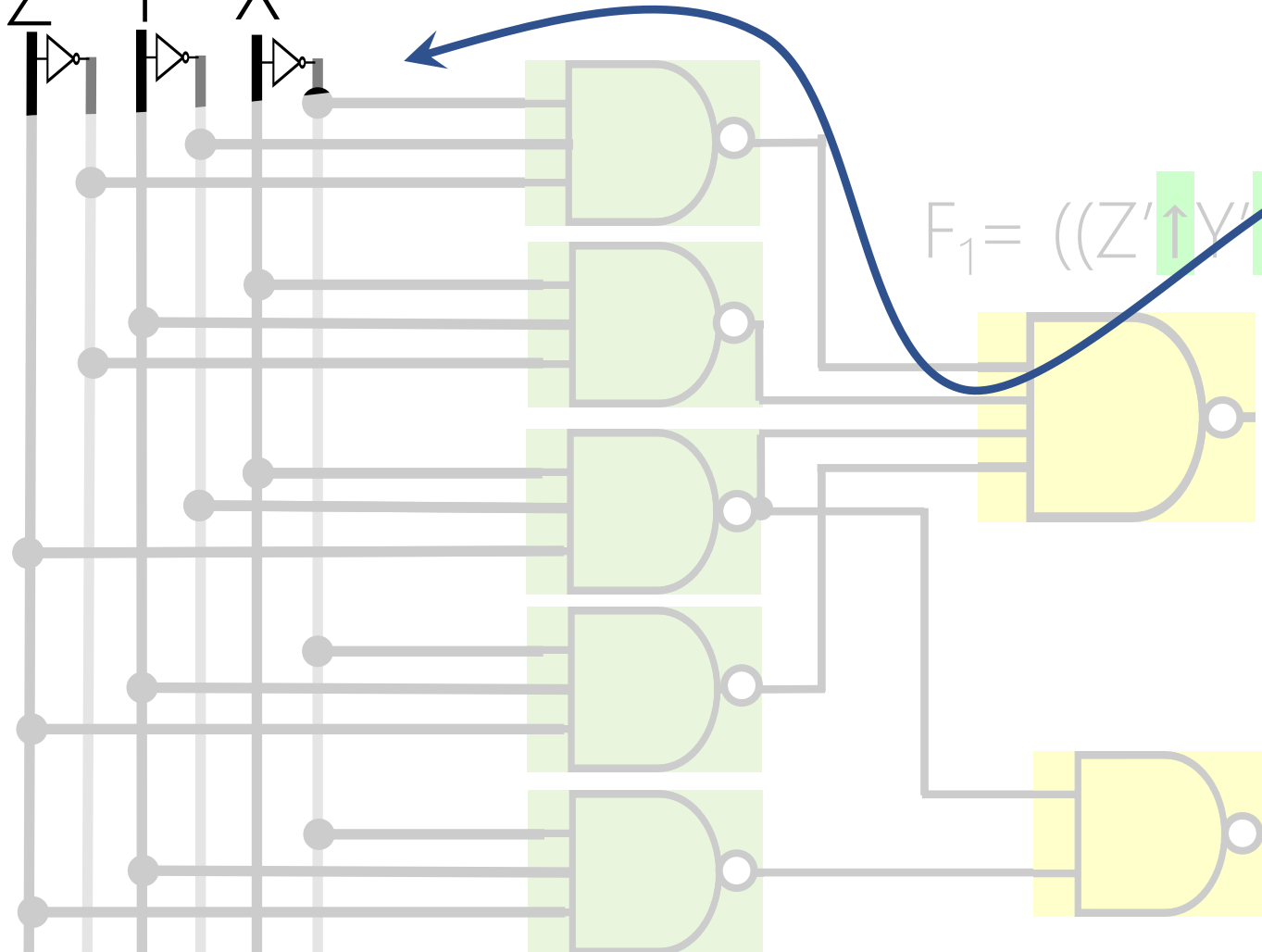


$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

NOT by NAND?

$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$




Z Y X

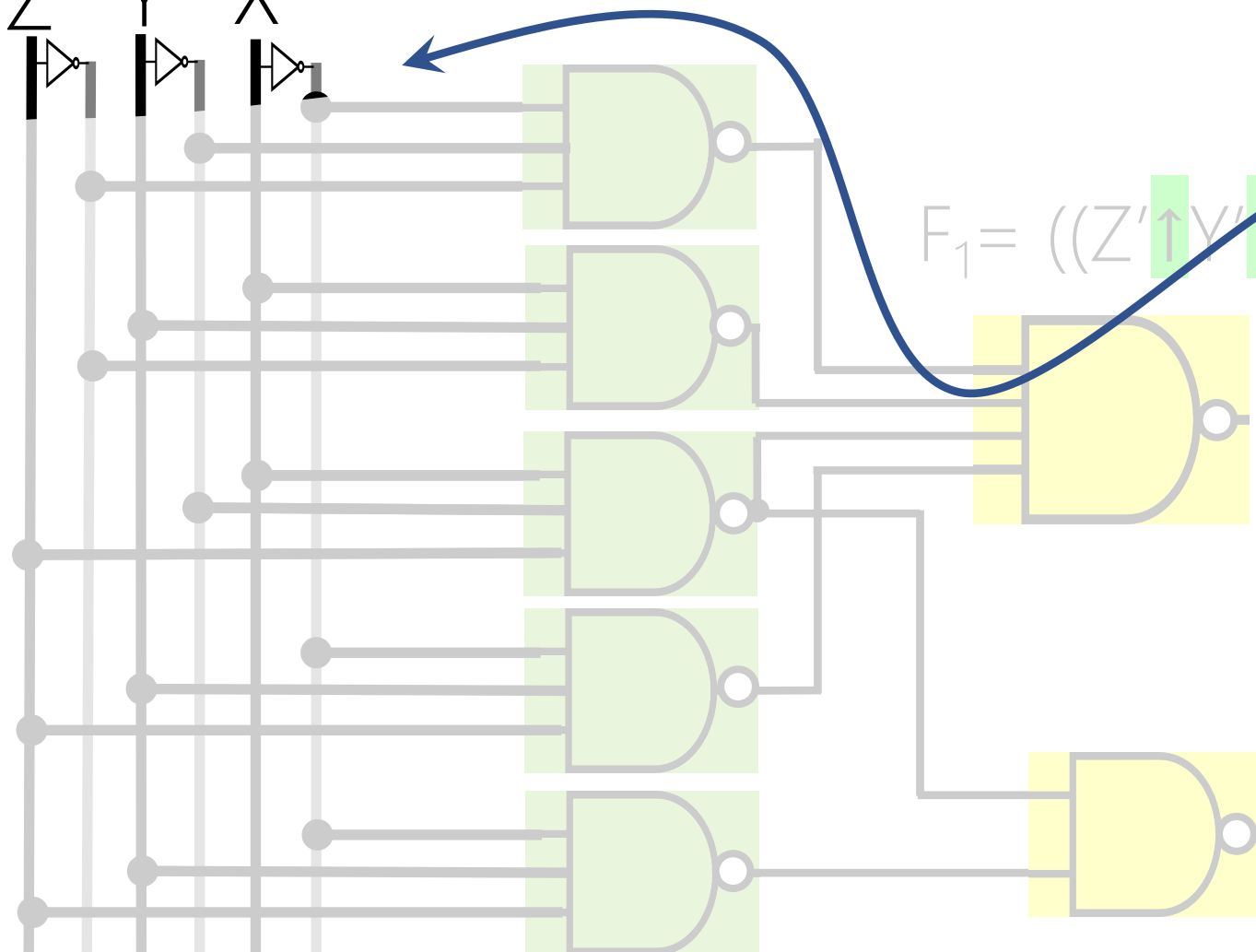

$$F_1 = ((Z' \uparrow Y' \uparrow X') \uparrow (Z' \uparrow Y \uparrow X) \uparrow (Z \uparrow Y' \uparrow X) \uparrow (Z \uparrow Y \uparrow X'))$$

NOT by NAND?

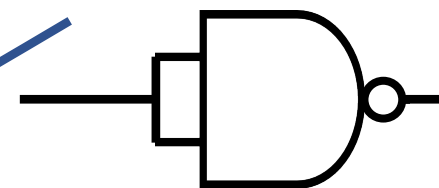

$$F_2 = ((Z \uparrow Y' \uparrow X') \uparrow (Z \uparrow Y' \uparrow X))$$

---

UNIVERSAL GATE {NAND}

$$F = (F')' = (\text{SoP}')'$$

---

---

# UNIVERSAL GATE

## {NOR}

---

---

# UNIVERSAL GATE

$\text{PoS} \rightarrow \{\text{NOR}\}$

---

$$F_{\text{PoS}} = (F')'$$

Lecture Assignment

# RECAP

Any Boolean Function F:

- Sum (OR) of Products (ANDs)
- Sum of **minterms** for Entries with **1**
  - ANDs-OR
  - NAND via  $(F')'$
- Product (AND) of Sums (ORs)
- Product of **MAXTERMS (NOT minterms)** for Entries with **0**
  - ORs-AND
  - NOR via  $(F')'$

---

# UNIVERSAL GATE

SoP  $\rightarrow$  {NAND}

SoP  $\rightarrow$  {NOR} ?

PoS  $\rightarrow$  {NOR}

PoS  $\rightarrow$  {NAND} ?

---

Lecture Assignment