
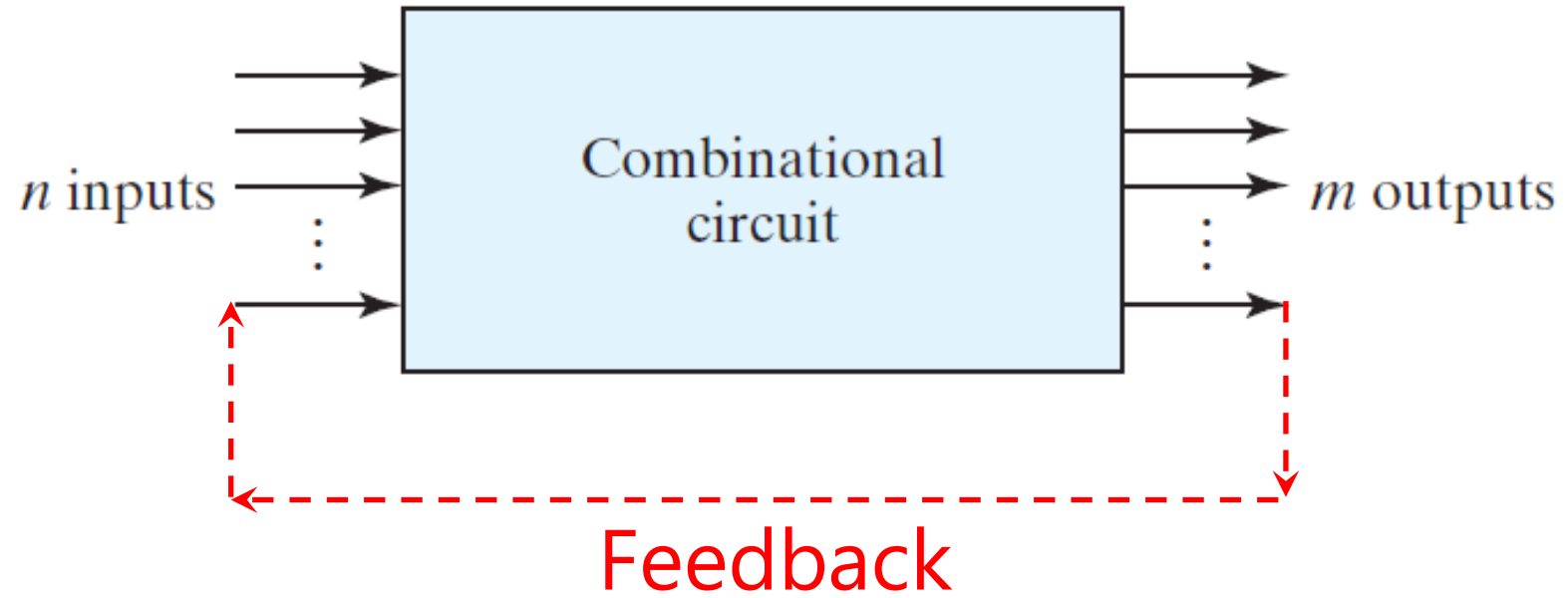


 

Sequential Logic

Sequential Logic






S	R	Q	Q'
0	0	Q_t	Q'_t
0	1	0	1
1	0	1	0
1	1	x	x

Voltage

R

S

 


Time


S and R control **how** the
state changes.

Put a gate/latch on **when** change applies
SR w/ enable input



SR *Latch*

 

E	S	R	S	R	Q	Q'
0	x	x	0	0	Q_t	Q'_t
1	0	0	0	0	Q_t	Q'_t
1	0	1	0	1	0	1
1	1	0	1	0	1	0
1	1	1	1	1	x	x

 


Voltage

  


Time

Voltage

 


Voltage

 


Time

Voltage

 


Voltage

 


Gate is closed! Store.

Time

Voltage

 


Voltage

 

SR *Latch*

NAND

 


(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

FIGURE 5.5
SR latch with control input

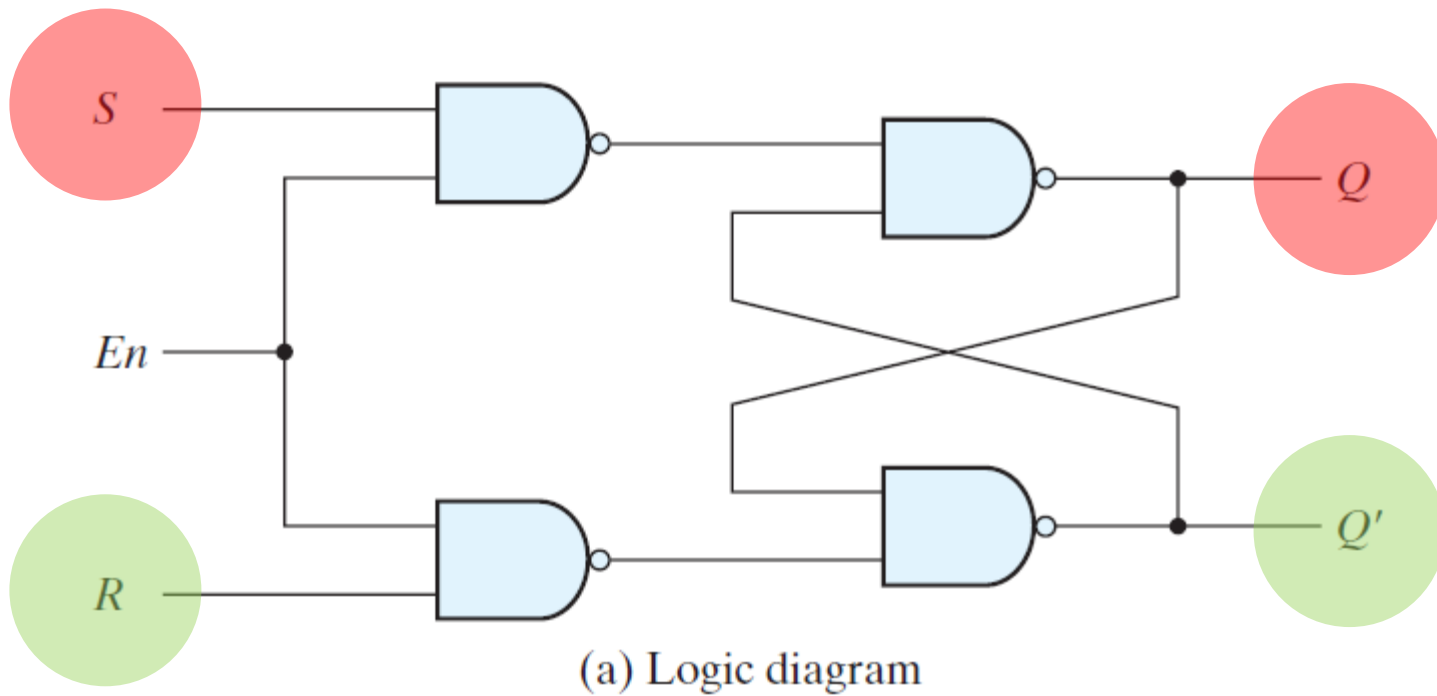


En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

FIGURE 5.5
SR latch with control input


Block Diagram

 

Characteristic Table

S	R	Q
0	0	Q_t
0	1	0
1	0	1
1	1	\times

State Transition Diagram

 


Other *Latches*




Let's avoid the forbidden action! $R \neq S$
 $R = S'$ and $S = R'$



X	E	S	R	Q	Q'
0	0	x	x	Q_t	Q'_t
1	0	x	x	Q_t	Q'_t
0	1	0	1	0	1
1	1	1	0	1	0
Never happens		1	1	\times	\times

 

X	E	S	R	Q	Q'
0	0	x	x	Q_t	Q'_t
1	0	x	x	Q_t	Q'_t
0	1	0	1	0	1
1	1	1	0	1	0
Never happens		1	1	\times	\times

 


X	E	S	R	Q	Q'
0	0	\times	\times	Q_t	Q'_t
1	0	\times	\times	Q_t	Q'_t
0	1	0	1	0	1
1	1	1	0	1	0
Never happens		1	1	\times	\times




D	E	Q
0	0	Q_t
1	0	Q_t
0	1	0
1	1	1



D	Q
0	0
1	1

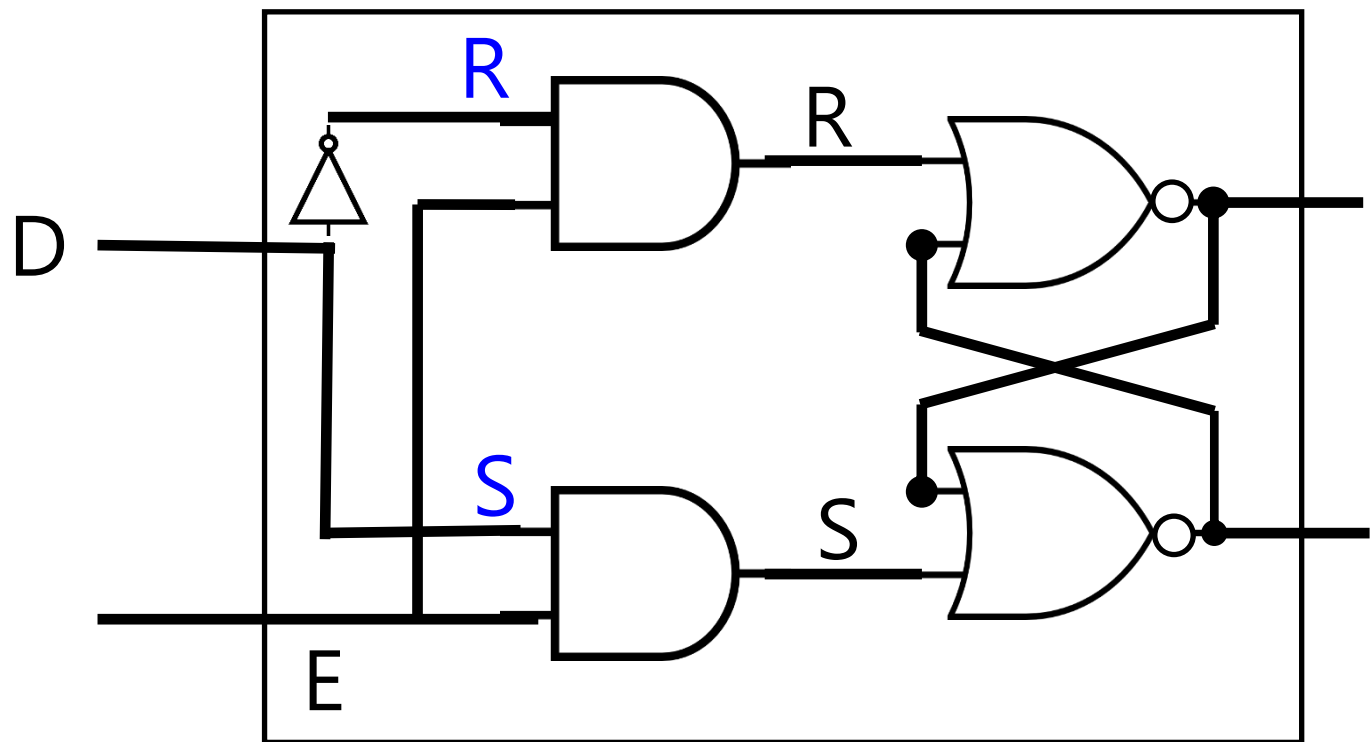


Block Diagram

 


Characteristic Table


D	Q
0	0
1	1


State Transition Diagram

 



T *Latch*

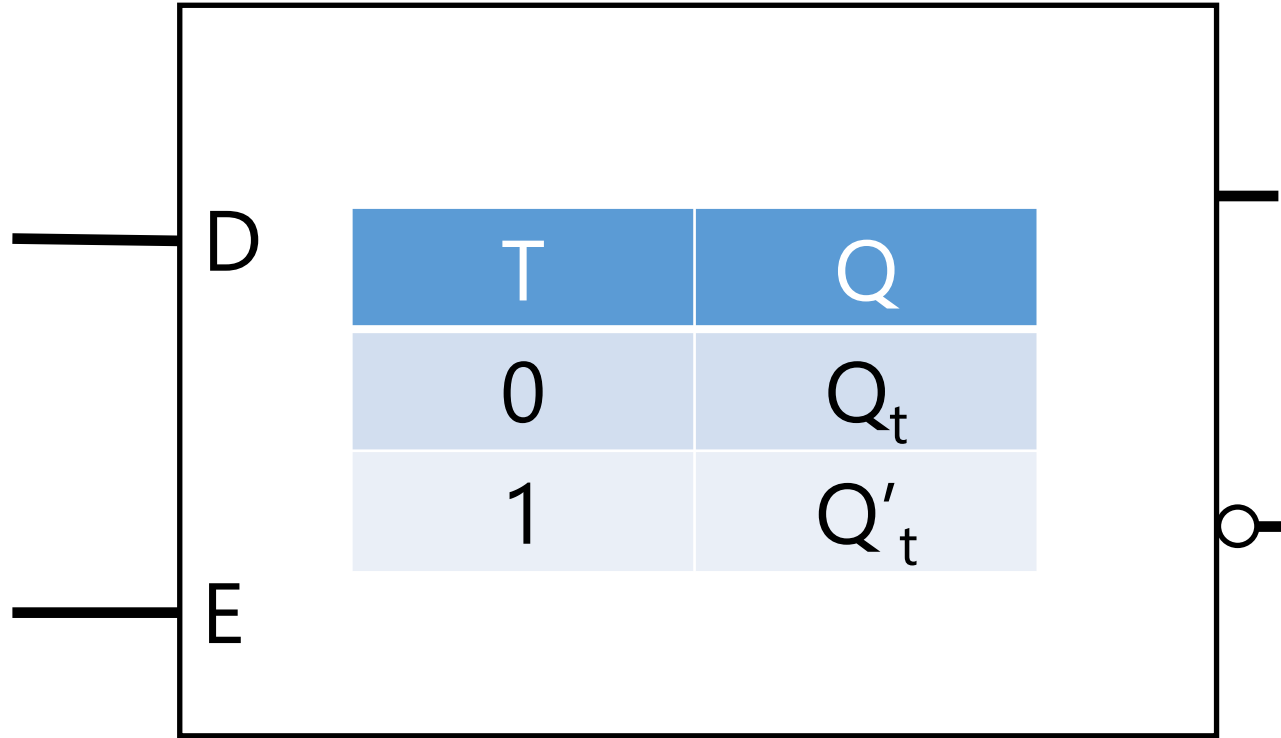

 


 

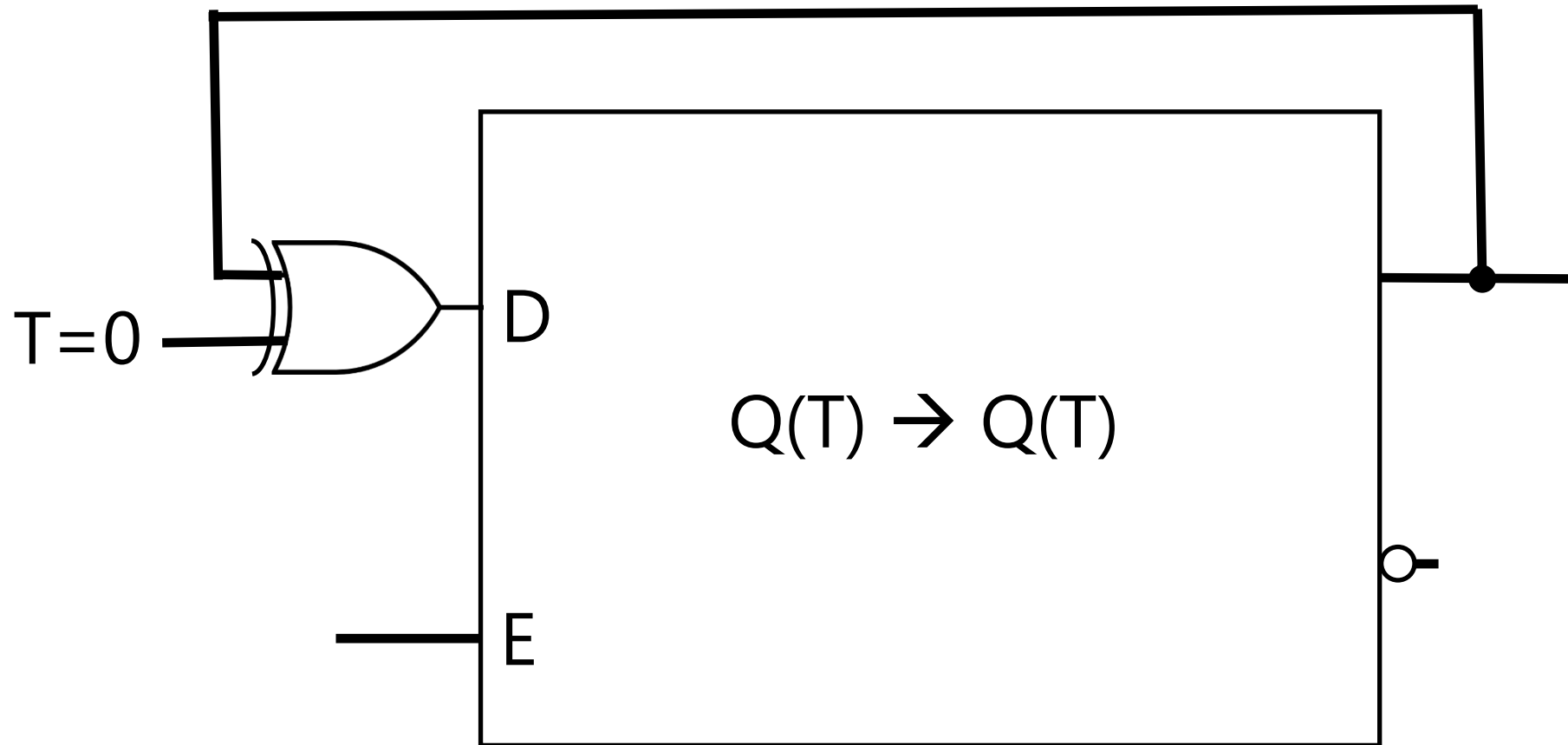


 

Store

 


T	D	Q
0	$Q \oplus 0$	Q
1	$Q \oplus 1$	Q'

 


Complement

T	D	Q
0	$Q \oplus 0$	Q
1	$Q \oplus 1$	Q'

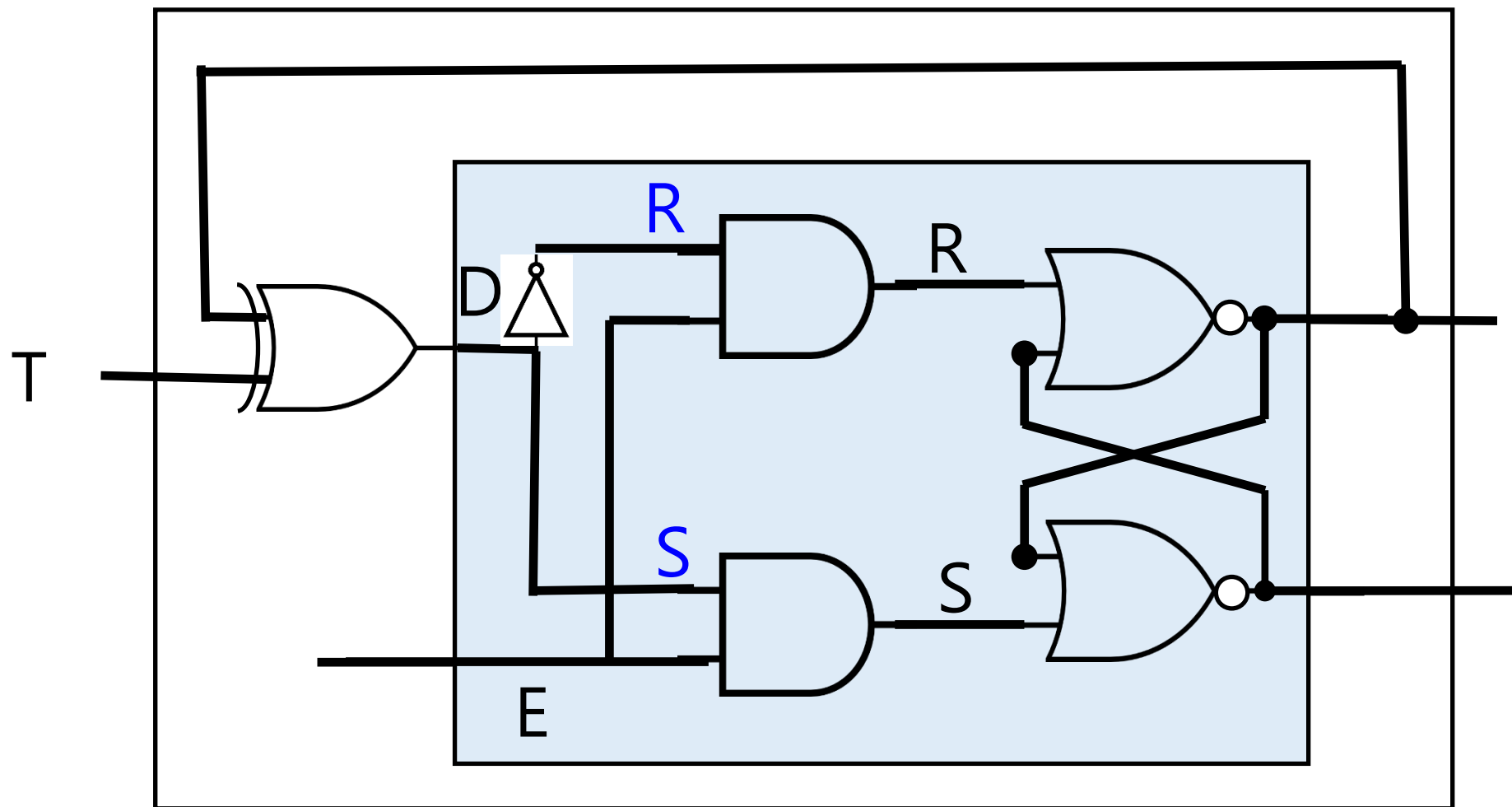


Block Diagram

 

Characteristic Table

T	Q
0	Q_t
1	Q'_t


State Transition Diagram

 


JK Latch



 
Jack St. Clair Kilby
(Nov. 8, 1923 – June 20, 2005)
Electrical Engineer
The 1st integrated circuit
1958
Nobel Prize in Physics, 2000






 


 Although you have to guess, we'll see a design algorithm it 😊




 


S	R	S	R	Q
0	0	0	0	Store = $Q_t = 1$
0	1	0	1	Reset = 0
1	0	0	0	Store = $Q_t = 1$
1	1	0	1	Reset = 0

 

S	R	S	R	Q
0	0	0	0	Store = $Q_t = 0$
0	1	0	0	Store = $Q_t = 0$
1	0	1	0	Set = 1
1	1	1	0	Set = 1

 


S	R	S	R	Q
0	0	0	0	Store= $Q_t=1$
0	1	0	1	Reset=0
1	0	0	0	Store= $Q_t=1$
1	1	0	1	Reset=0

 

S	R	S	R	Q
0	0	0	0	Store= $Q_t=0$
0	1	0	0	Store= $Q_t=0$
1	0	1	0	Set=1
1	1	1	0	Set=1

S=J	R=K	Q
0	0	Store= Q_t
0	1	Reset = 0
1	0	Set = 1
1	1	Comp. = Q'_t


Block Diagram

 





Characteristic Table

J	K	Q
0	0	Q_t
0	1	0
1	0	1
1	1	Q'_t

State Transition Diagram

 

Recap

    

S	R	Q
0	0	Q_t
0	1	0
1	0	1
1	1	\times

D	Q
0	0
1	1


T	Q
0	Q_t
1	Q'_t

J	K	Q
0	0	Q_t
0	1	0
1	0	1
1	1	Q'_t

Clock

shortened as *clk*

 timing device that generates a train of pulses



One period is called **pulse**!


Clock

shortened as *clk*

Synchronize *all* the memory units
when to work

Clock


Positive Level (default)

 



Clock

Negative Level

 




Clock
Frequency (Hz)





Heinrich Rudolf Hertz



A Metric for Speed

 

How many pulse in **1** sec?

  

How many pulse in **1** sec?

  

How long is one pulse?
 $1/\text{freq. (Hz)}$




Intel® Xeon® Platinum 8380HL Processor (38.5M Cache, 2.90 GHz)

 - 38.5 MB Cache
- 28 Cores 1,000,000,000 (one billion) Hz (hertz)
- 56 Threads 1,000,000,000 (one billion) pulse per sec!
- 4.30 GHz Max Turbo Frequency

Microprocessor clock speed

Microprocessor clock speed measures the number of pulses per second generated by an oscillator that sets the tempo for the processor. It is measured in hertz (pulses per second).



Source: Ray Kurzweil (2005, updated to 2016). The Singularity Is Near: When Humans Transcend Biology.




Speed - DDR4-2666 ⓘ

Warranty - Manufact

CAS latency - 19 ⓘ

 The number of transfers per clock cycle times the clock frequency, expressed as MegaTransfers per second.




CPU: X Hz

Memory: Y Hz

Mainboard (BUS): Z Hz

Final Speed?

 

CPU: X Hz

Memory: Y Hz


Mainboard (BUS): Z Hz

At market:

$$X > Y = Z$$

$$X = 2.9\text{GHz}$$

$$Y = Z = 2.6\text{GHz}$$

 

CPU: X Hz

Memory: Y Hz

Mainboard (BUS): Z Hz

Final Speed:

CPU internal: X

CPU external \leftrightarrow Memory

$Y=Z= 2.6\text{GHz}$

Overclock?

Flip-Flop
