
DESIGN

an algorithm for designing any digital units (logic circuits), given truth table

minterm
aka. Standard Product

TRUTH TABLE


en.wikipedia.org/wiki/Truth_table

SUM OF PRODUCTS (SOP) 2 LEVELS AND-OR

with *product* meaning the ANDing
with *sum* meaning the ORing


Z	Y	X	$F(Z,Y,X)=m_0+m_3+m_5+m_6=\sum m(0,3,5,6)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z Y X

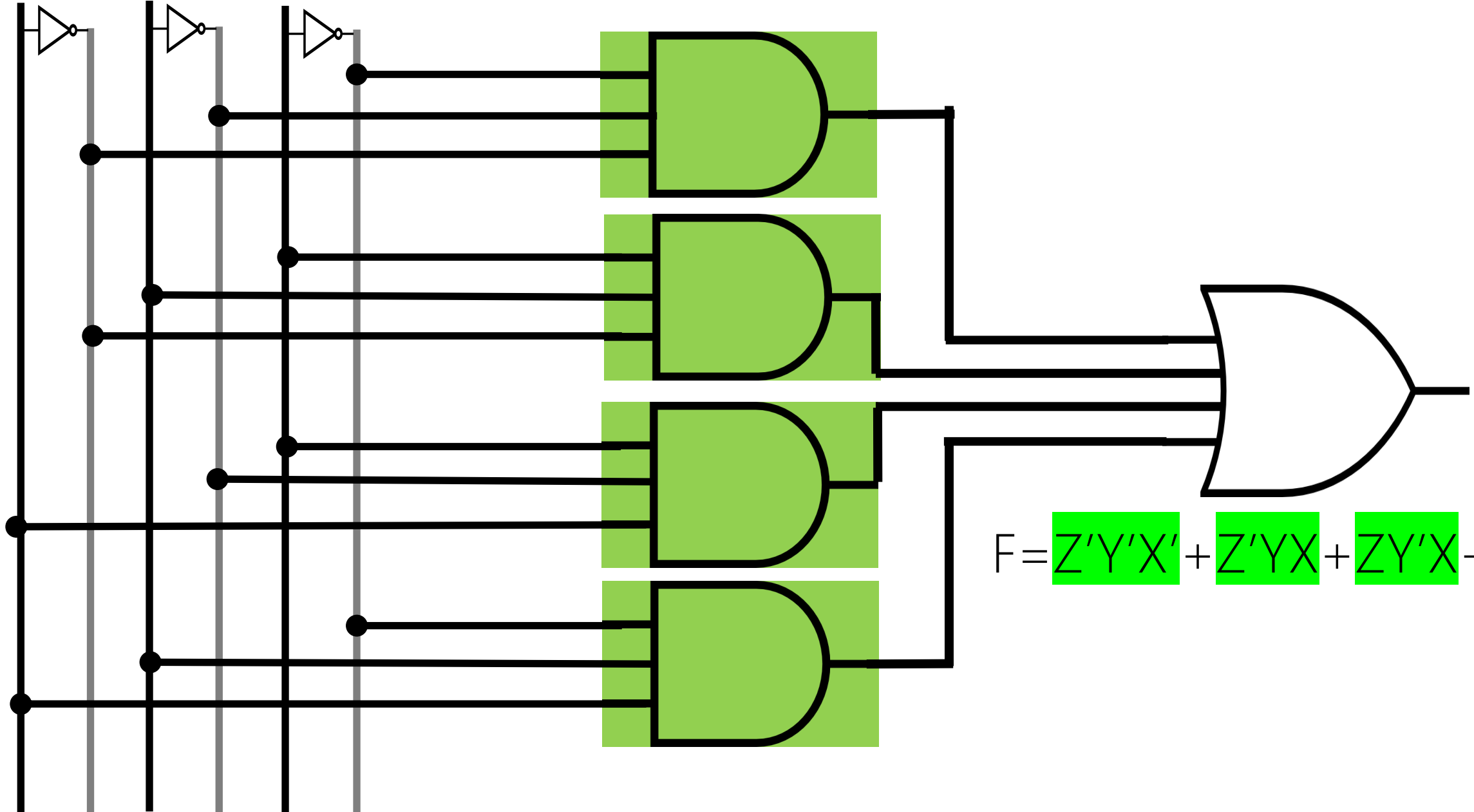

$$F = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

Z Y X

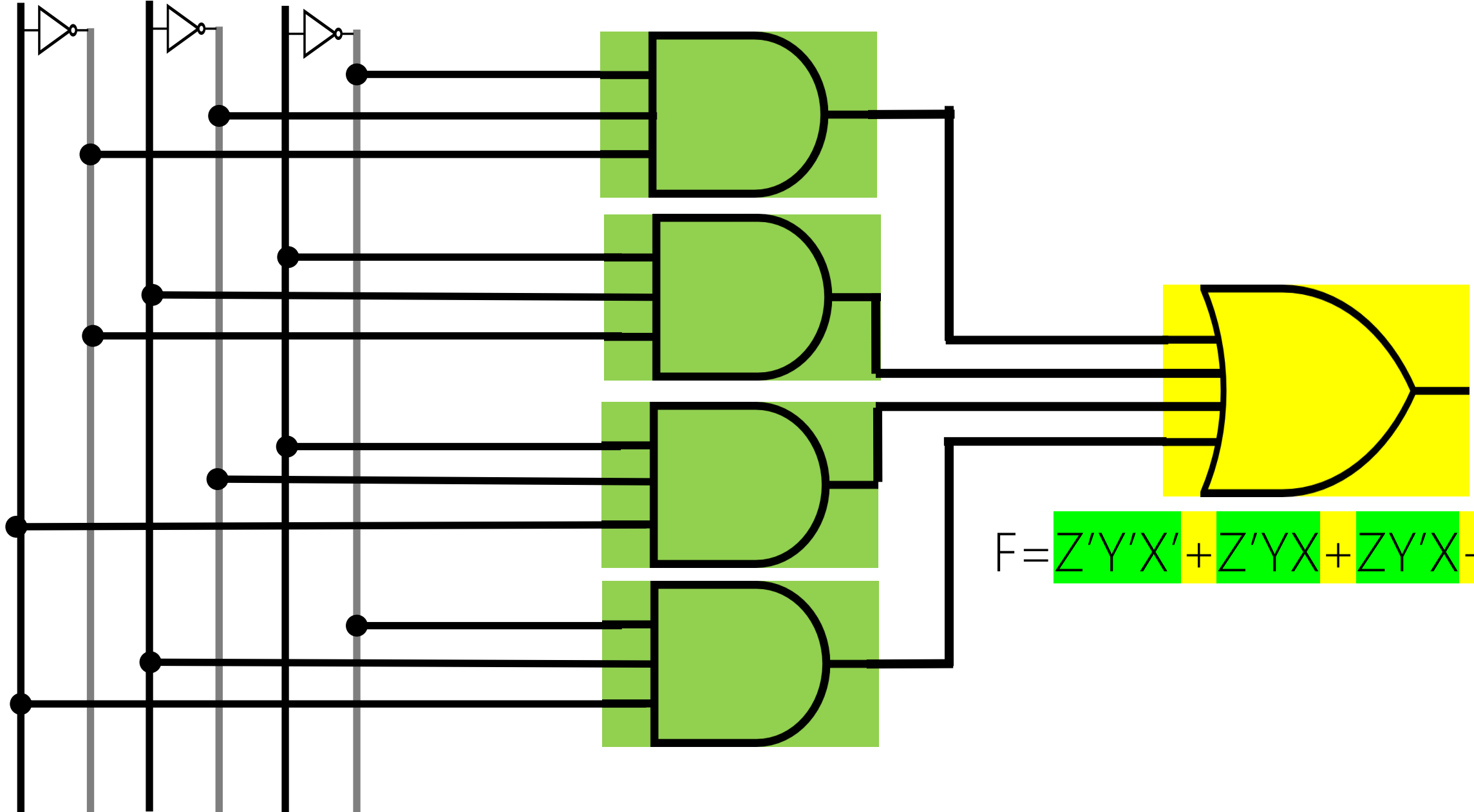


$$F = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

MULTIPLE BOOLEAN FUNCTIONS

F_1, F_2, \dots


Z	Y	X	$F_1(Z,Y,X)=\sum m(0,3,5,6)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z Y X

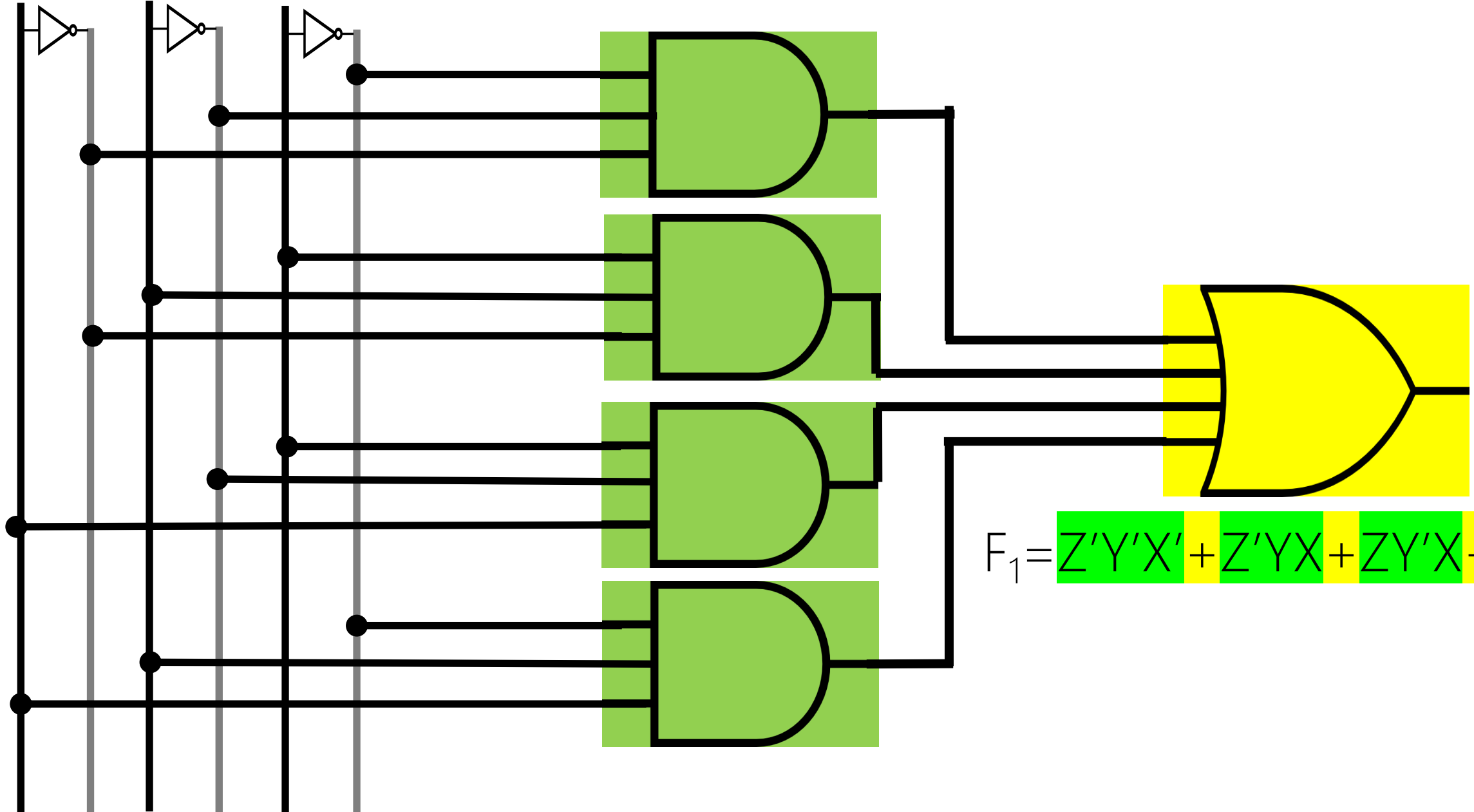


$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

Z	Y	X	$F_2(Z,Y,X)=\sum m(4,5)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

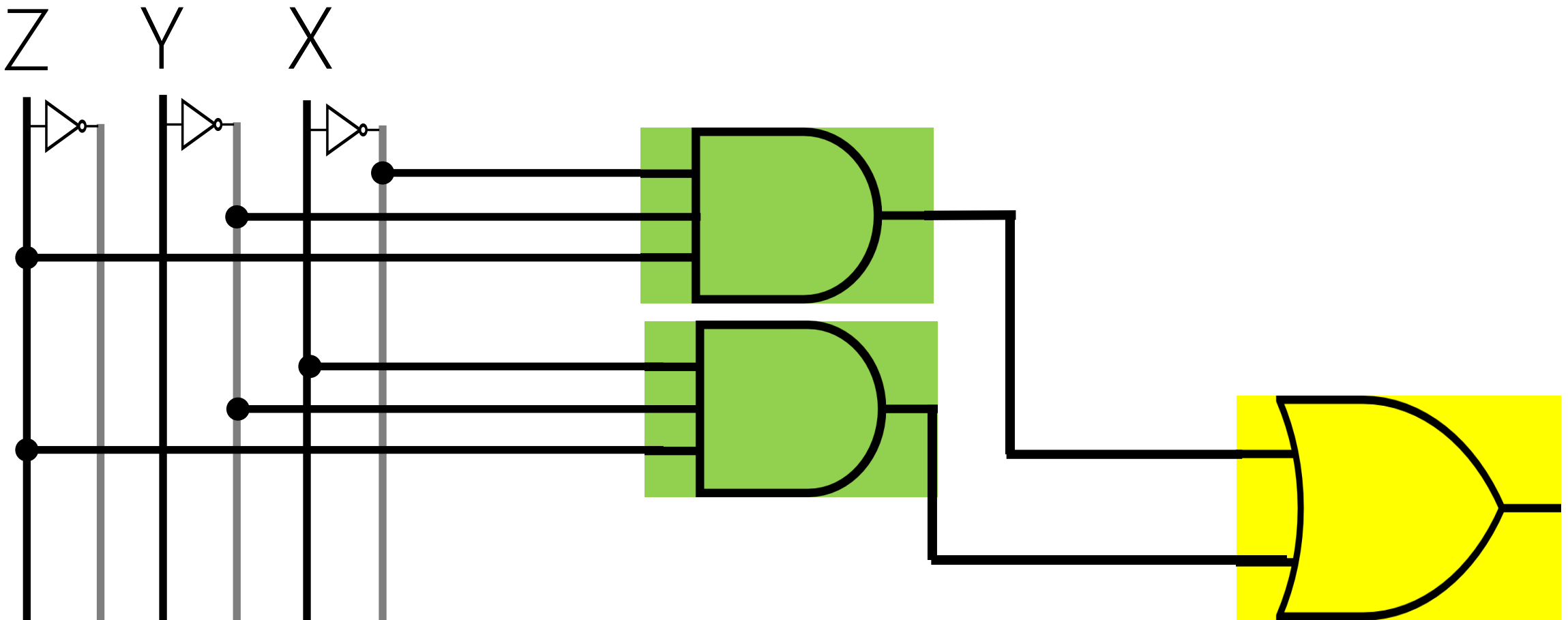

$$F_2 = ZY'X' + ZY'X$$

Z	Y	X	$F_1(Z,Y,X)=\sum m(0,3,5,6)$	$F_2(Z,Y,X)=\sum m(4,5)$
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	1
1	1	0	1	0
1	1	1	0	0

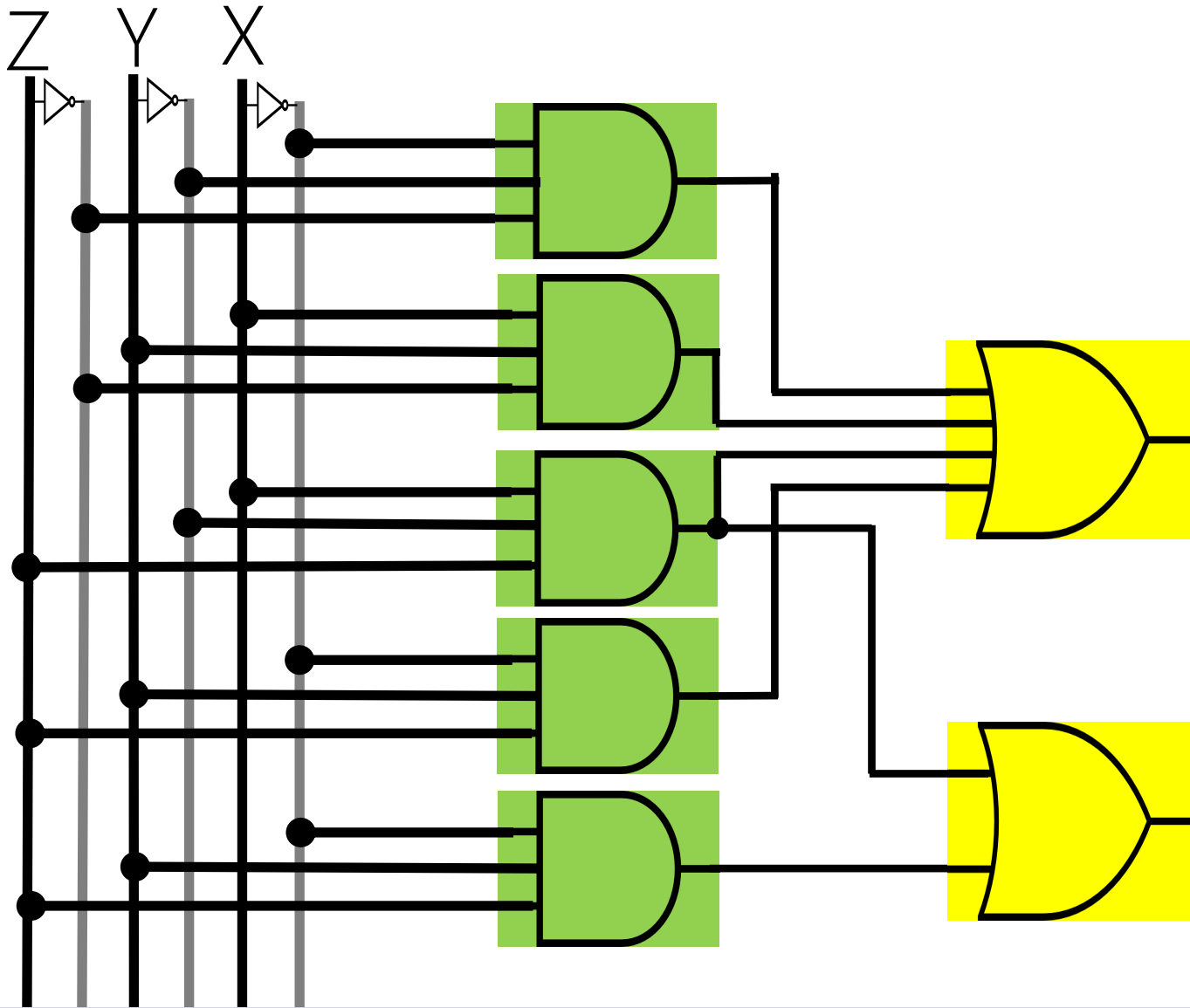

$$F_1 = Z'Y'X' + Z'YX + ZY'X + ZYX'$$

$$F_2 = ZY'X' + ZY'X$$

RE-USE minterms

SHOW THE REMAINDER (MOD)
NUMBER % 3 = ?

TRUTH TABLE \leftrightarrow minterm

[illegible][illegible]

WHAT IS THE RANGE OF NUMBERS?

WHAT IS THE RANGE OF NUMBERS?

$$[0, 15]_{10}$$

HOW MANY INPUT **BINARY** VARIABLES?

$$[0, 15]_{10} = [0, 1111]_2 = [0000, 1111]_2$$

W	Z	Y	X
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

WHAT IS THE RANGE OF OUTPUT?

WHAT IS THE RANGE OF OUTPUT?

The remainder of any number divided by 3 is 0, 1, 2

WHAT IS THE RANGE OF OUTPUT?

$$[0, 2]_{10}$$

HOW MANY **BOOLEAN** FUNCTION?

$$[0, 2]_{10} = [0, 10]_2 = [00, 10]_2$$

W	Z	Y	X	F ₁	F ₂
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

W	Z	Y	X	F ₁	F ₂
0	0	0	0	0	0
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

W	Z	Y	X	F ₁	F ₂
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

W	Z	Y	X	F ₁	F ₂
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

W	Z	Y	X	F ₁	F ₂
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

W	Z	Y	X	F ₁	F ₂
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	0

minterms


W	Z	Y	X	$F_1=m_2+m_5+m_8+m_{11}+m_{14}$	F_2
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	0

W	Z	Y	X	$F_1=\sum m(2,5,8,11,14)$	$F_2=m_1+m_4+m_7+m_{10}+m_{13}$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	0

W	Z	Y	X	$F_1=\sum m(2,5,8,11,14)$	$F_2=\sum m(1,4,7,10,13)$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	0	0

Circuit /Logic Diagram

W Z Y X

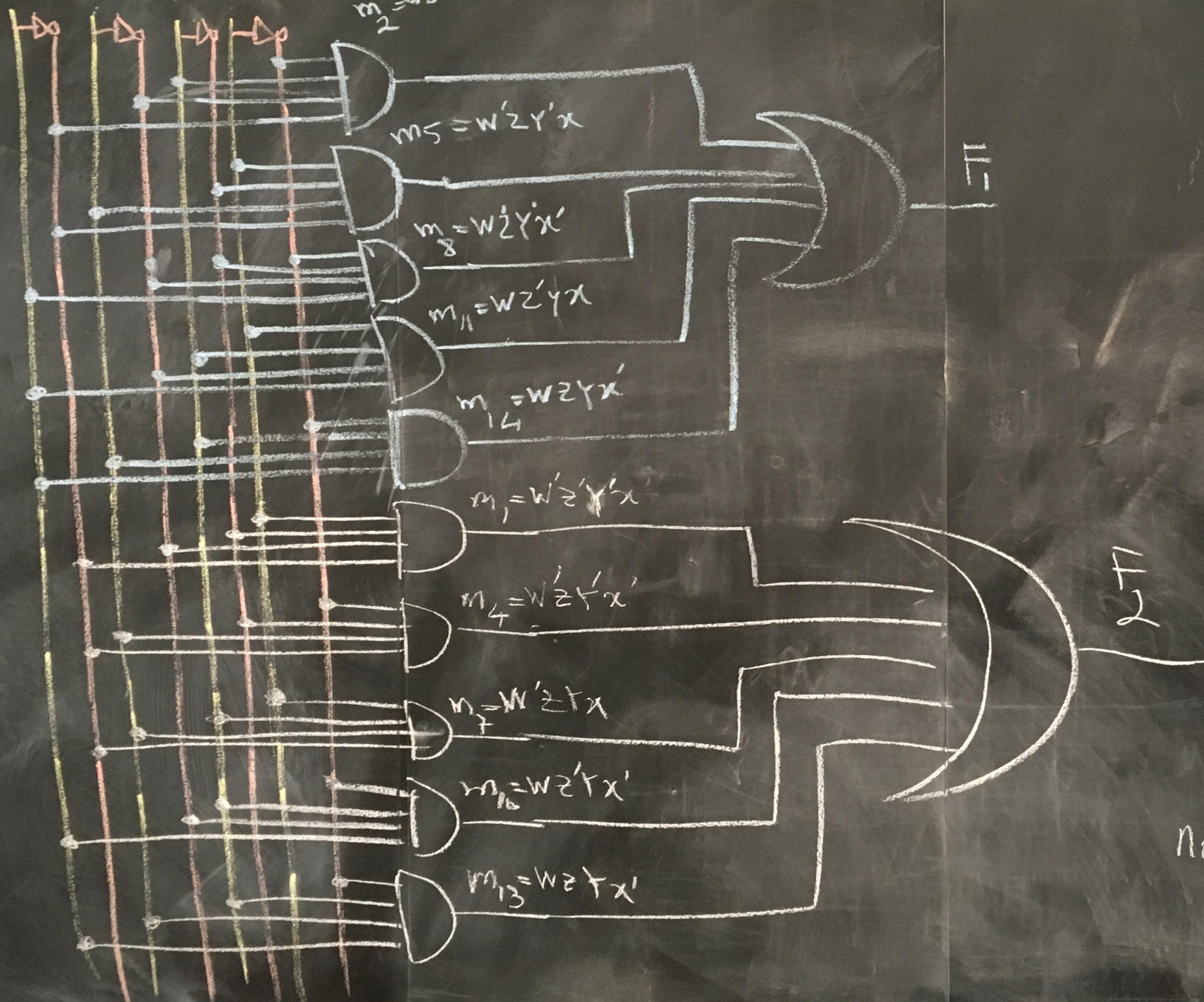

$$F_1 = \sum m(2, 5, 8, 11, 14)$$

$$F_2 = \sum m(1, 4, 7, 10, 13)$$

No reuse for minterms

DESIGN II

a new algorithm for designing any logic circuits, given truth table

MAXTERM

aka. Standard Sum

X' vs. X

1 binary variable appear either:

- in its normal form X , or
- in its complement form X'

$$M_0 = m'_0$$

$$M_1 = m'_1$$

$$(X') = (X')' = X$$

$$X'$$

$Y + X$ vs. $Y + X'$ vs. $Y' + X$ vs. $Y' + X'$

2 binary variables appear either in one of these forms:



Augustus De Morgan
(1806–1871)

Mathematician
Logician

DE MORGAN'S LAWS

▶ $(YX)' = Y' + X'$

▶ $(Y + X)' = Y'X'$

$$M_0 = m'_0$$

$$(Y'X')' = Y + X$$

$$M_1 = m'_1$$

$$(Y'X)' = Y + X'$$

$$M_2 = m'_2$$

$$(YX')' = Y' + X$$

$$M_3 = m'_3$$

$$(YX)' = Y' + X'$$

$Z + Y + X$ vs. $Z + Y + X'$ vs. ...

3 binary variables appear either in one of these forms: how many?

$Z + Y + X$ vs. $Z + Y + X'$ vs. ...

3 binary variables appear either in one of these forms: how many?

Each variable can take 2 forms (normal and complement)

We have 3 variables, $2 \times 2 \times 2 = 2^3 = 8$

$M_0 = m'_0$	$(Z'Y'X')' = Z + Y + X$
$M_1 = m'_1$	$(Z'Y'X)' = Z + Y + X'$
$M_2 = m'_2$	$(Z'YX')' = Z + Y' + X$
$M_3 = m'_3$	$(Z'YX)' = Z + Y' + X'$
$M_4 = m'_4$	$(ZY'X')' = Z' + Y + X$
$M_5 = m'_5$	$(ZY'X)' = Z' + Y + X'$
$M_6 = m'_6$	$(ZYX')' = Z' + Y' + X$
$M_7 = m'_7$	$(ZYX)' = Z' + Y' + X'$

$$A_n + \dots A_2 + A_1 + A_0 \text{ vs. } A_n + \dots A_2 + A_1 + A'_0 \dots$$

n binary variables appear either in one of these forms: how many?

Each variable can take 2 forms (normal and complement)

We have n variables, $2 \times 2 \times 2 \times \dots \times 2 = 2^n$


$M_0 = m'_0$	$A_n + A_2 + A_1 + A_0$
$M_1 = m'_1$	$A_n + \cdots A_2 + A_1 + A'_0$
$M_2 = m'_2$	$A_n + \cdots A_2 + A'_1 + A_0$
\vdots	\vdots
\vdots	\vdots
$M_{2^n-3} = m'_{2^n-3}$	$A'_n + \cdots A'_2 + A_1 + A'_0$
$M_{2^n-2} = m'_{2^n-2}$	$A'_n + \cdots A'_2 + A'_1 + A_0$
$M_{2^n-1} = m'_{2^n-1}$	$A'_n + \cdots A'_2 + A'_1 + A'_0$

TRUTH TABLE

en.wikipedia.org/wiki/Truth_table

TRUTH TABLE \leftrightarrow MAXTERM

Y	X	$F = m_0 + m_1$
0	0	1
0	1	1
1	0	0
1	1	0

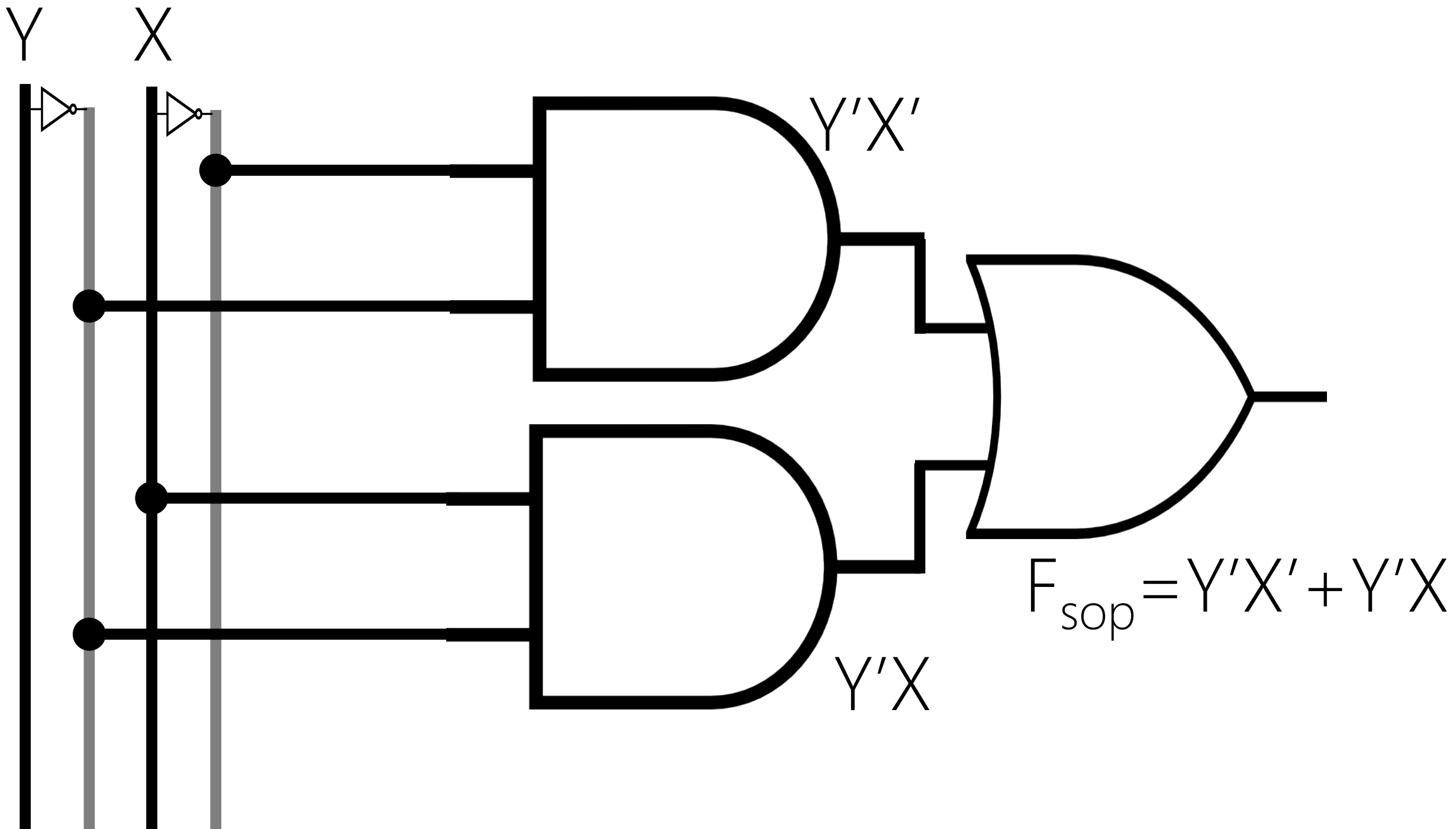

Y	X	$F = m_0 + m_1$	$F' = m_2 + m_3$
0	0	1	0
0	1	1	0
1	0	0	1
1	1	0	1

Y	X	$F=m_0+m_1$	$F'=m_2+m_3$	$(F')'=(m_2+m_3)'$
0	0	1	0	1
0	1	1	0	1
1	0	0	1	0
1	1	0	1	0


Y	X	$F = (F')' = (m_2 + m_3)' = m'_2 m'_3$
0	0	1
0	1	1
1	0	0
1	1	0

Y	X	$F = (F')' = m'_2 m'_3 = M_2 M_3$
0	0	1
0	1	1
1	0	0
1	1	0


Y	X	$F = (F')' = m'_2 m'_3 = M_2 M_3$
0	0	1
0	1	1
1	0	0
1	1	0


Y	X	$F = (F')' = M_2 M_3 = \prod M(2,3)$
0	0	1
0	1	1
1	0	0
1	1	0

Y	X	$F = \prod M(2,3) = (Y' + X)(Y' + X')$
0	0	1
0	1	1
1	0	0
1	1	0

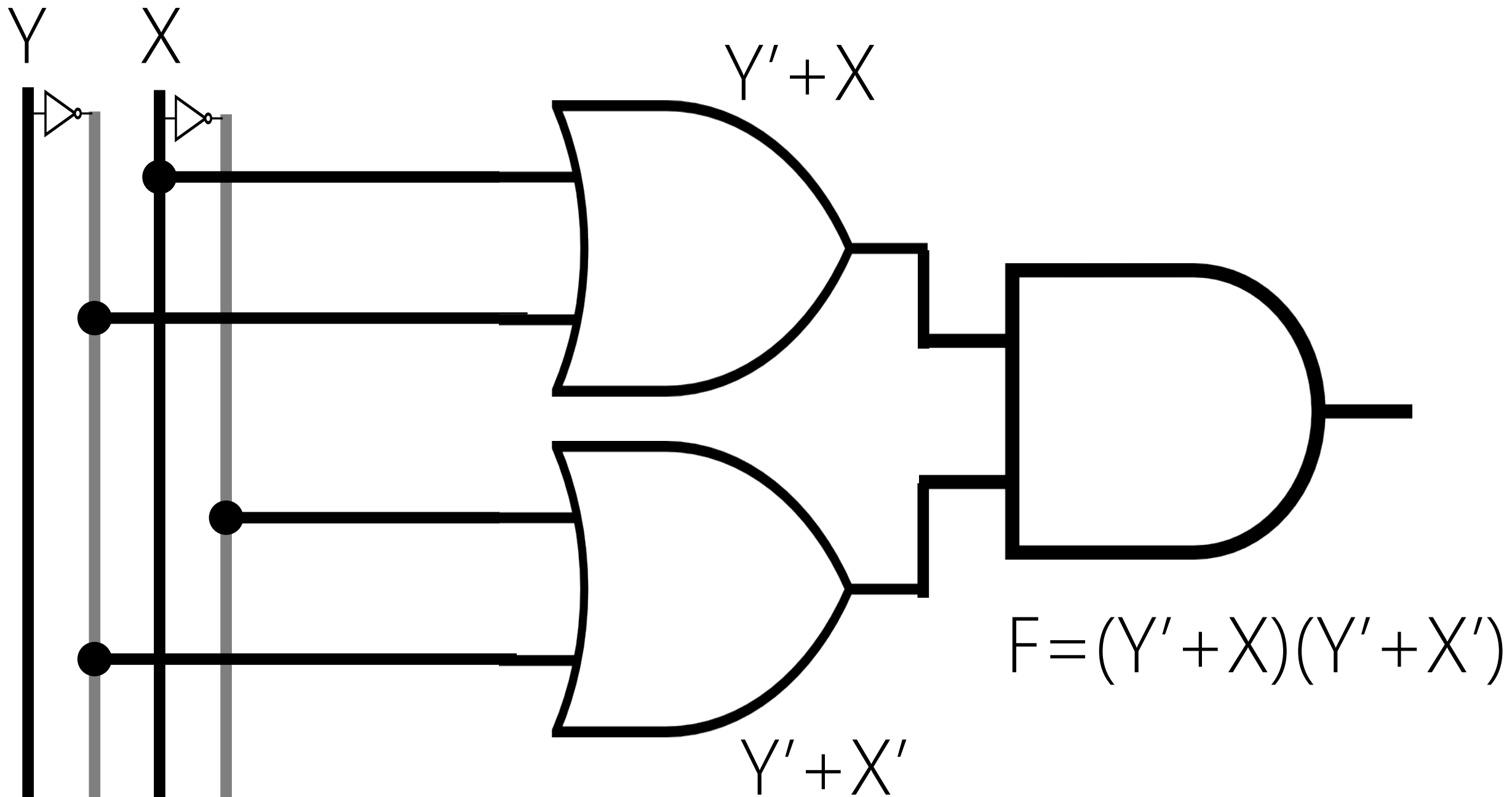


PRODUCT OF SUMS (POS)

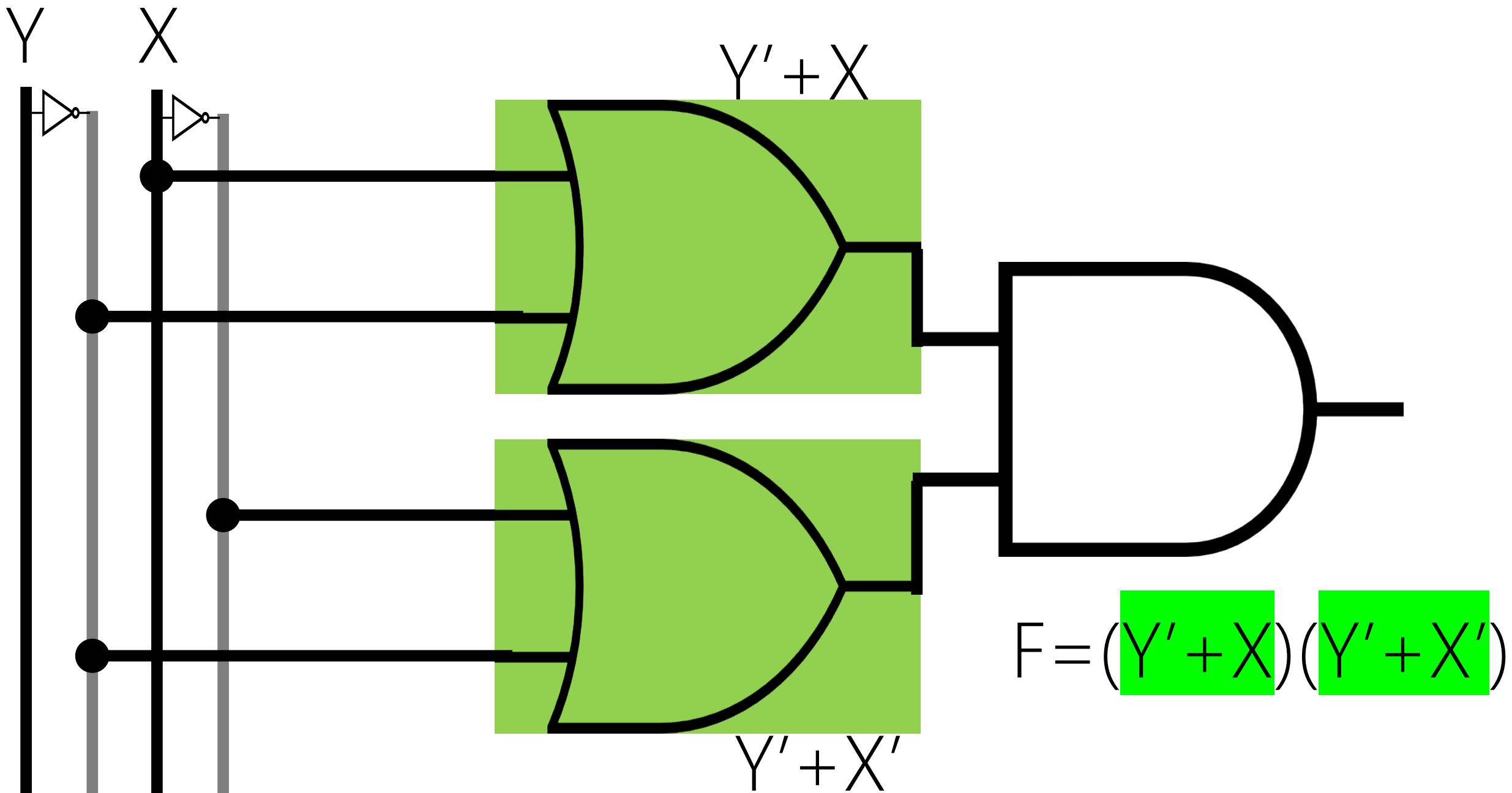

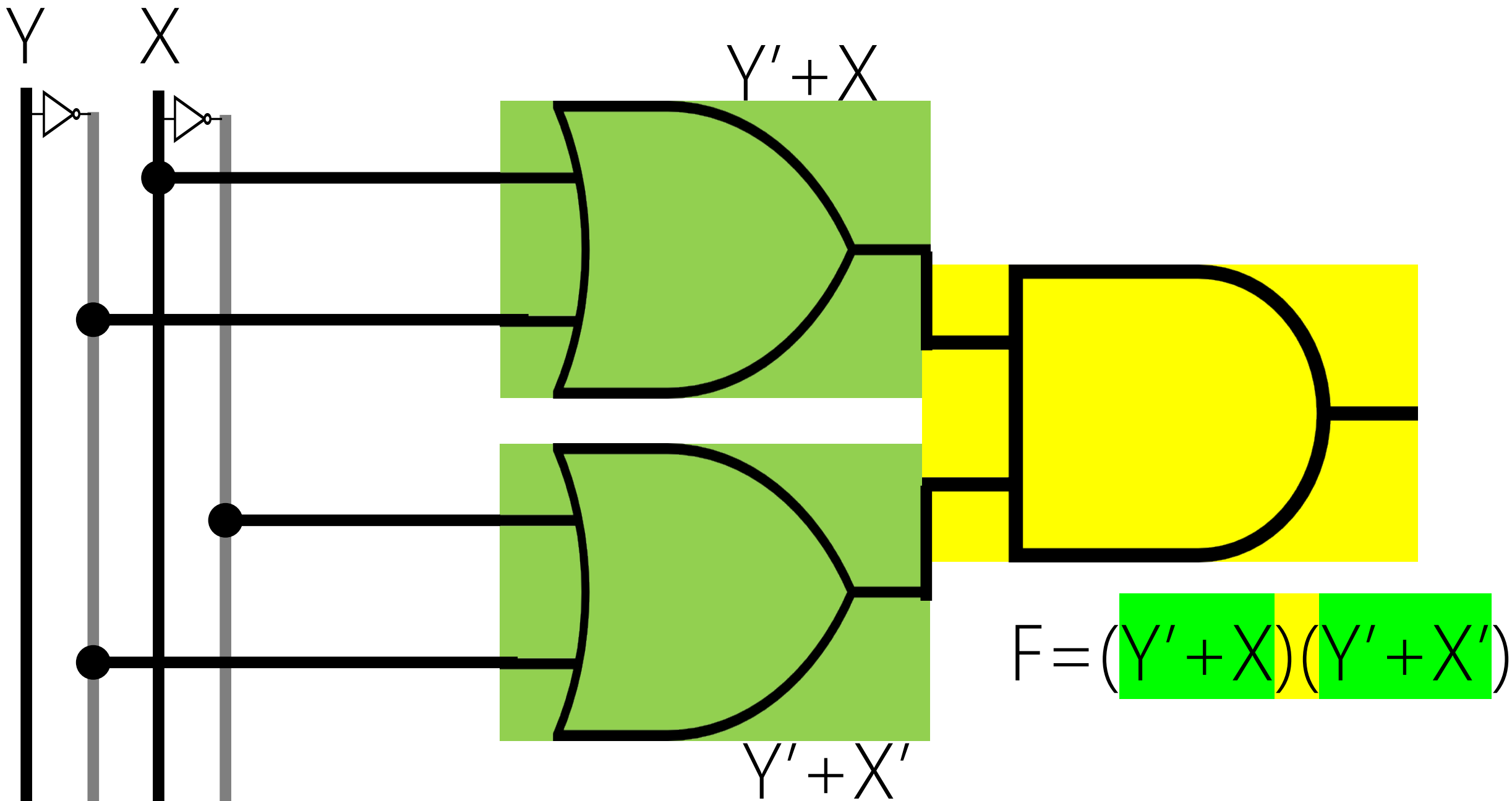

2 LEVELS
OR → AND

Y	X	$F=F(Y,X)=m_0+m_1+m_3=\sum \mathbf{m}(0,1,3)$
0	0	1
0	1	1
1	0	0
1	1	1

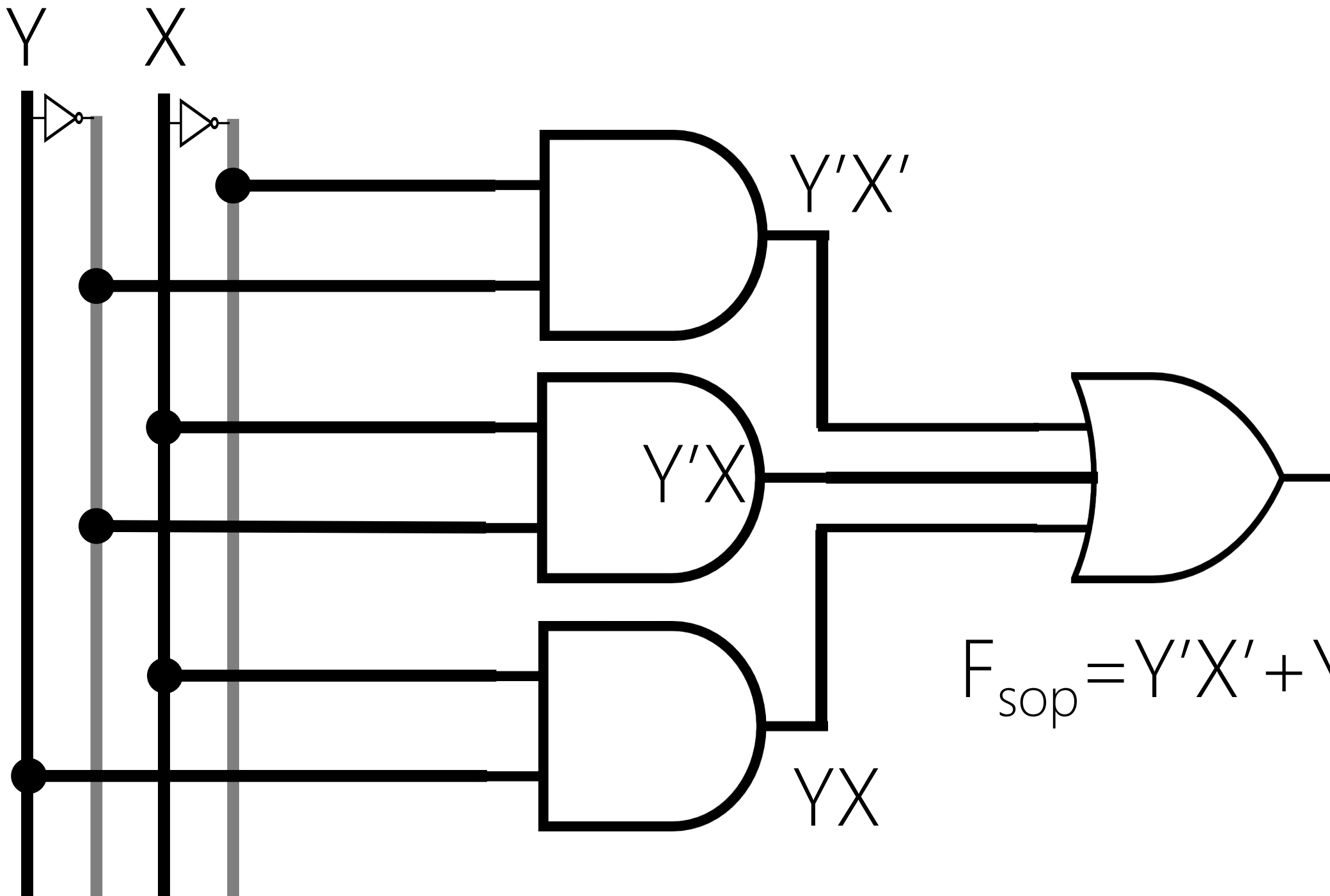


$$F_{\text{sop}} = Y'X' + Y'X + YX$$


Y	X	$F = \sum m(0,1,3)$	$F' = m_2$
0	0	1	0
0	1	1	0
1	0	0	1
1	1	1	0

Y	X	$F = \sum m(0,1,3)$	$F' = m_2$	$(F')' = m'_2$
0	0	1	0	1
0	1	1	0	1
1	0	0	1	0
1	1	1	0	1

Y	X	$F = \sum m(0,1,3)$	$F' = m_2$	$(F')' = M_2$
0	0	1	0	1
0	1	1	0	1
1	0	0	1	0
1	1	1	0	1

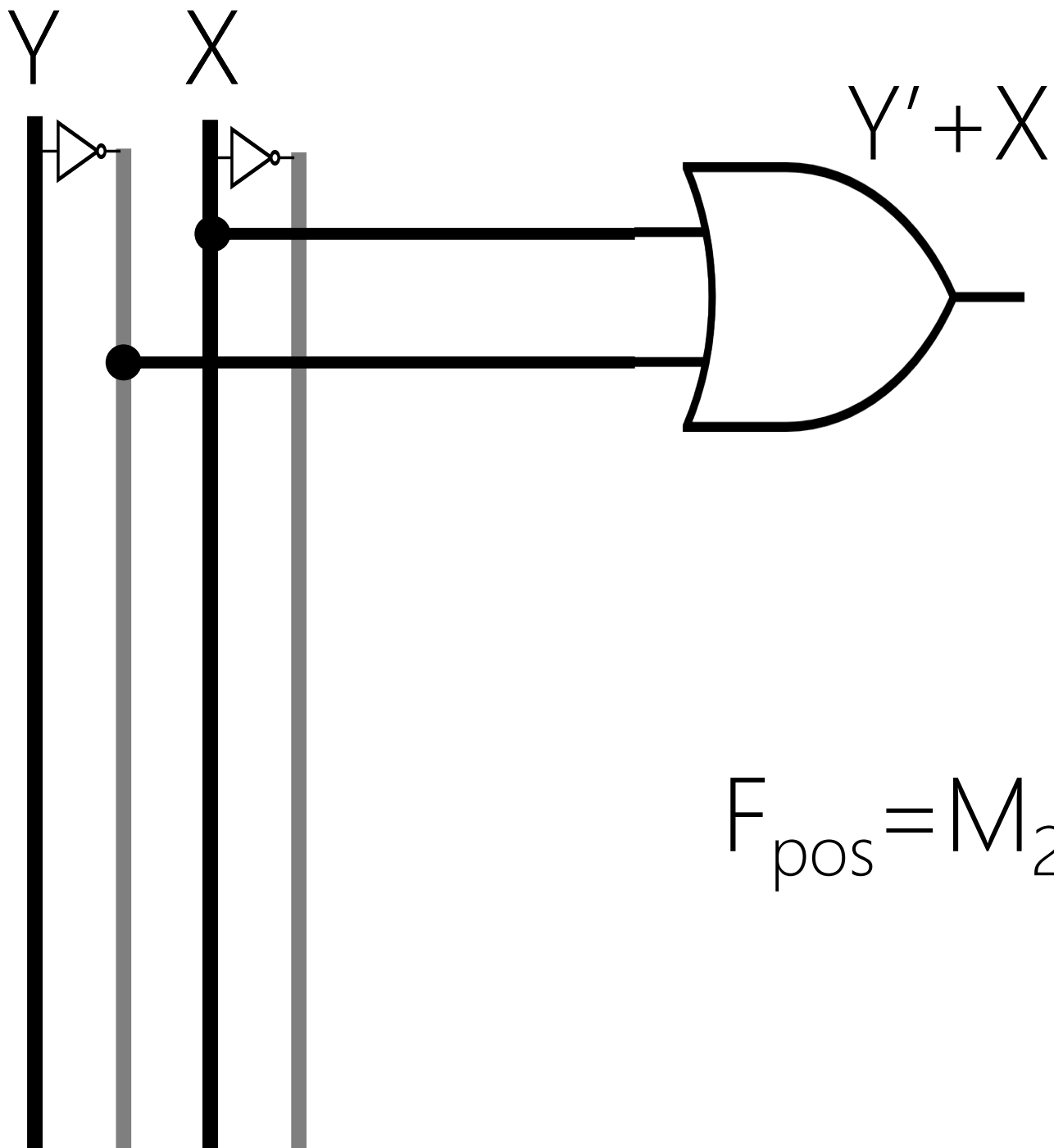
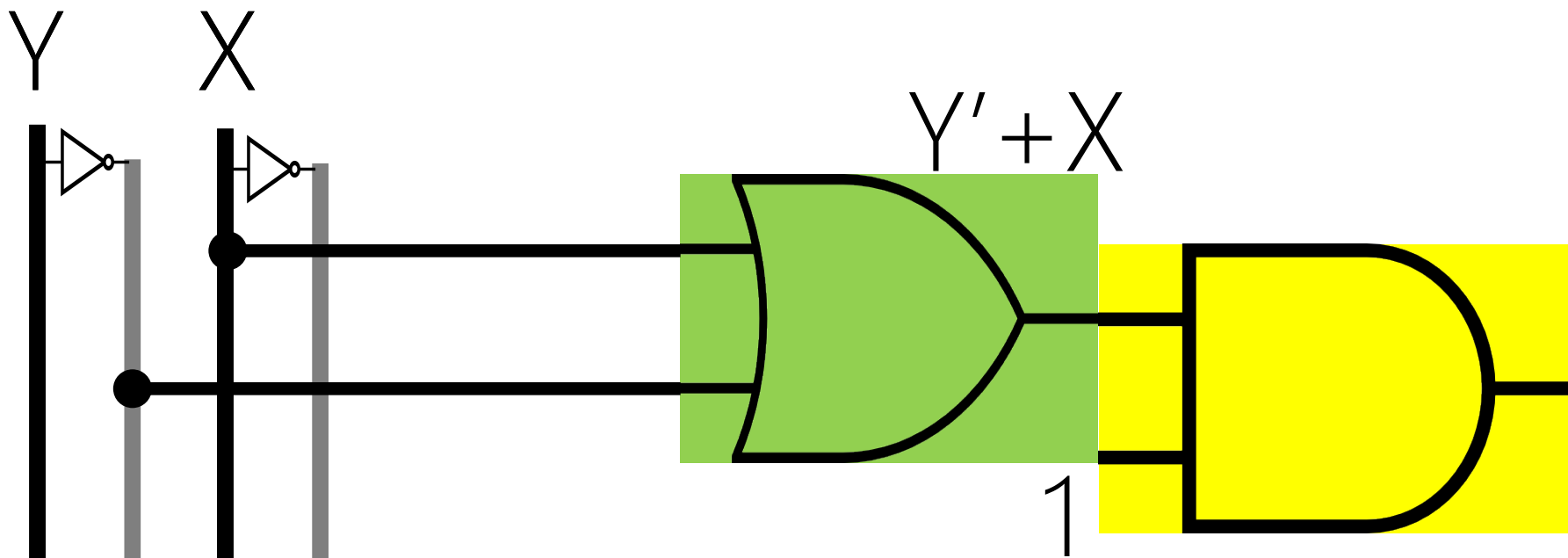
$$F_{\text{pos}} = M_2 = m'_2 = (YX')' = (Y' + X)$$



$$F_{\text{pos}} = M_2 = m'_2 = (YX')' = (Y' + X)(1)$$

DESIGN I vs. II
SoP vs. PoS

Lecture Assignment


Given 3 inputs, design a circuit to
determine if there is even
number of 1

Z	Y	X	F(Z,Y,X)=?
0	0	0	?
0	0	1	?
0	1	0	?
0	1	1	?
1	0	0	?
1	0	1	?
1	1	0	?
1	1	1	?

Z	Y	X	F(Z,Y,X)=?
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z	Y	X	F(Z,Y,X)=Σm(0,3,5,6)
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z Y X

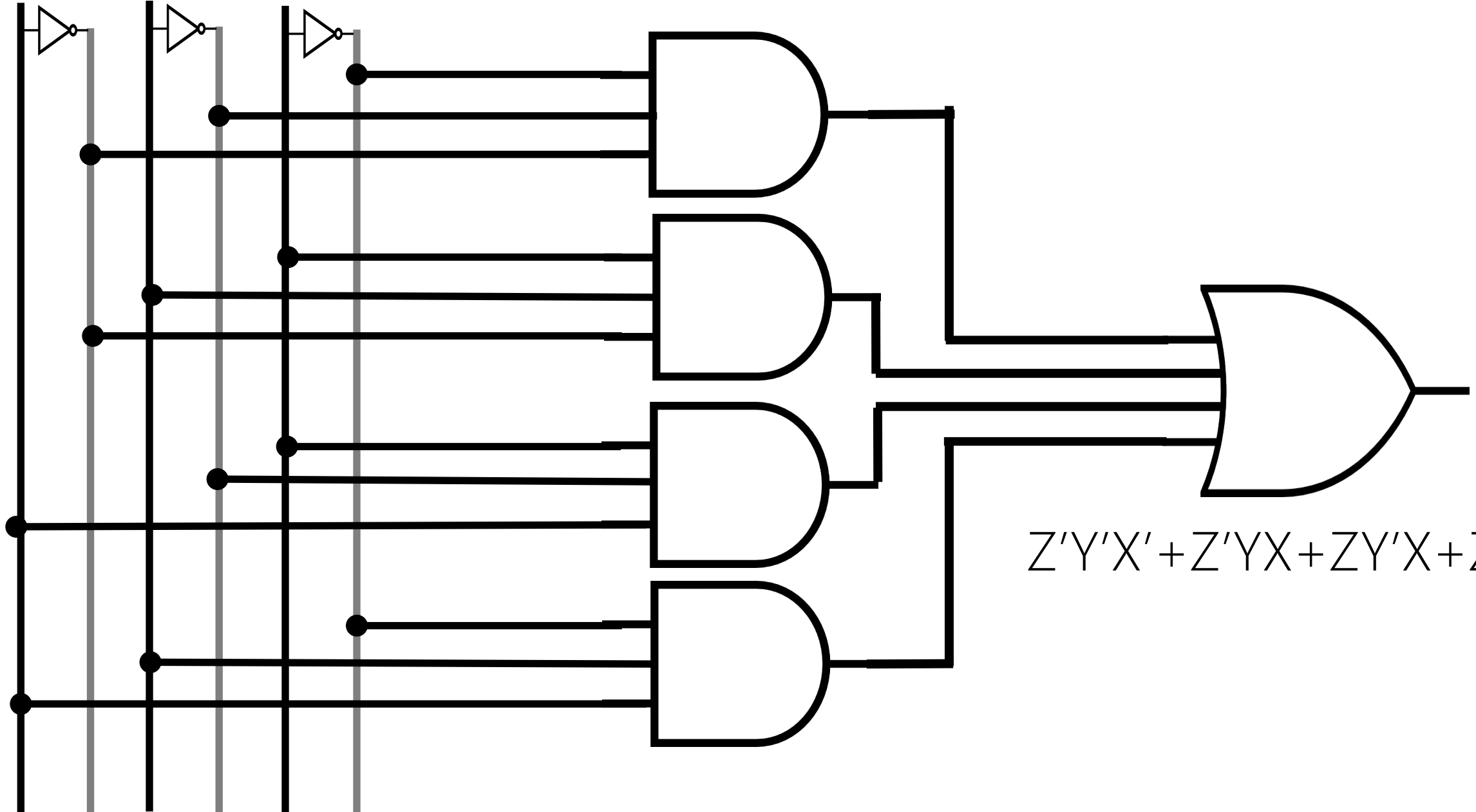

$$Z'Y'X' + Z'YX + ZY'X + ZYX'$$

Z	Y	X	$F(Z,Y,X)=M_1$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


Z	Y	X	$F(Z,Y,X)=M_1M_2$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z	Y	X	$F(Z,Y,X)=M_1M_2M_4$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z	Y	X	$F(Z,Y,X)=M_1M_2M_4M_7$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z	Y	X	$F(Z,Y,X)=M_1M_2M_4M_7=\prod M(1,2,4,7)$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Z Y X

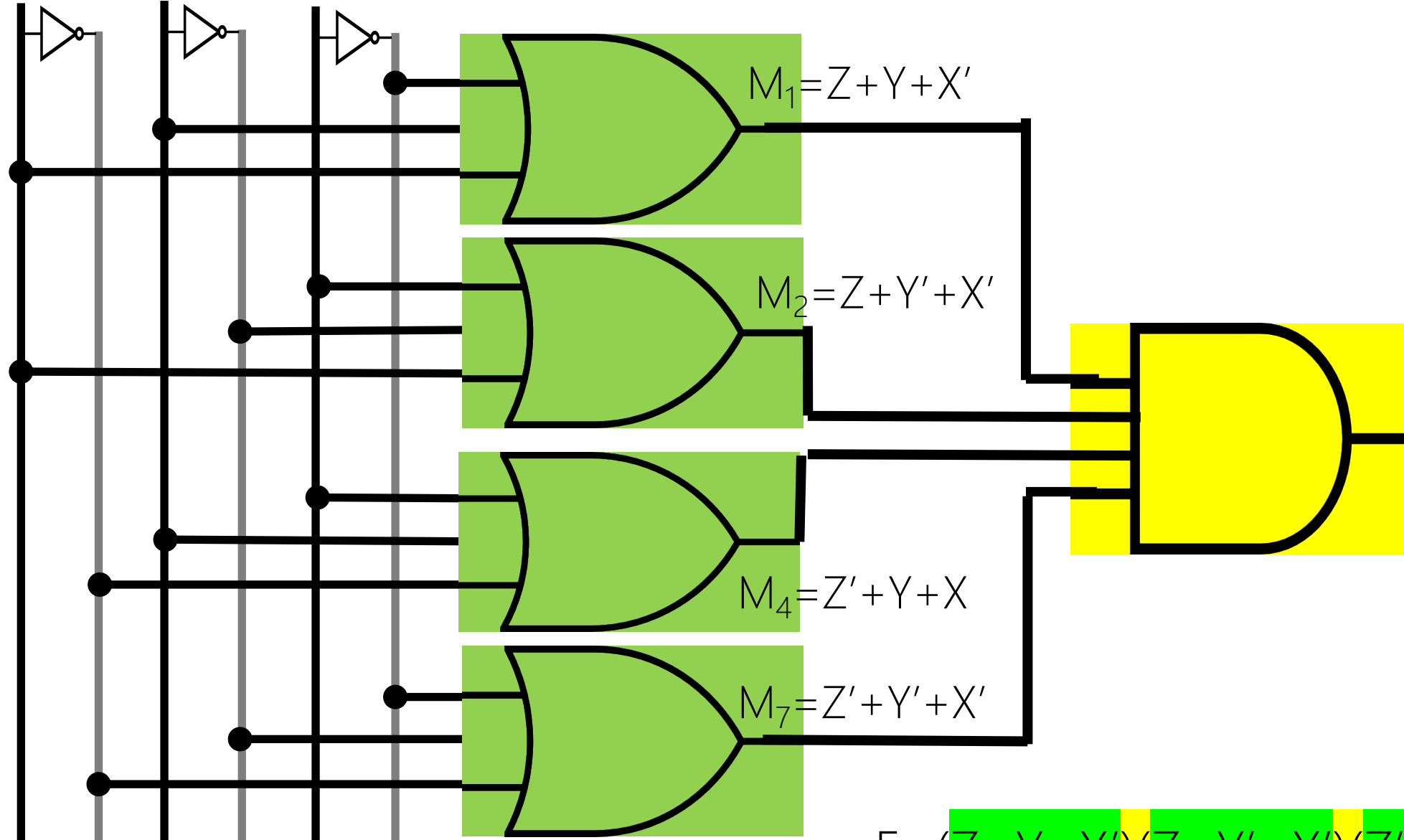

$$F = (Z + Y + X')(Z + Y' + X')(Z' + Y + X)(Z' + Y' + X')$$

UNIVERSALITY
