 


W2021: A Digital Odyssey

The Ultimate Trip.




Number Systems | $(12)_{10} \rightarrow (1100)_2$


| Logic Gates | 

| Combinational Logic | 

| Flip-Flops |

 





| Sequential Logic |

 

| Computer Systems

Flip-Flop

A single edge triggered latch

    


S	R	Q
0	0	Q_t
0	1	0
1	0	1
1	1	\times

D	Q
0	0
1	1

T	Q
0	Q_t
1	Q'_t


J	K	Q
0	0	Q_t
0	1	0
1	0	1
1	1	Q'_t

Single Edge *Positive*

 

Analysis: Given a sequential circuit, show the behavior
vs.

 
Design: Given a behavior, build the sequential circuit



Analysis (Recap)

0. Is the circuit sequential or combinational? Any FF or feedback → Sequential
 1. What are the flip-flops? RS, D, T, JK, or mixed (e.g., 2 JK, 1 RS, ...)
 2. What are the state combinations? $2^{\#FF}$
 3. Form "State" table:
 - a) Columns: for each FF, two columns:
 - one for current state,
 - one for next state
 - b) Rows: for each state combination
 - In total: $2^{\#FF}$
 4. Fill the state table for next state columns based on:
 - a) the current state
 - b) the inputs to the FFs
 5. Form State Transition Diagram
 6. (Optional) Analyze paths and states in state transition diagram
-

Analysis by an example

 


Analysis

0) Is it sequential circuit?

At least one FF \rightarrow Yes

At least one feedback \rightarrow Yes

Otherwise \rightarrow No

 


Analysis

1) What are the FFs?

1.1. We pick a name for each FF

1.2. We note the type of FF

 


Analysis

2) What are the state combinations
(possibilities)?

Each FF can have $\{0,1\}$ states

In total, $2^{\#FFs}$

 


#FFs = 3 $\rightarrow 2^3 = 8$ combinations

Analysis

3) Form a 'State' Table

- 3.1. For each FF, one column for **current** state
- 3.2. For each FF, one column for **next** state
- 3.3. For each combination of current state one row

 [illegible]


Analysis

4) Fill the 'State' table


For each FF, we determine the **next** state based on

I) current state

 
II) the current value of inputs to the FF



Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0			$Q_A(T)=0$ $J_A=Q'_B(T)=1$ $K_A=Q_B(T)=0$ ----- Set Action: 1
0	0	1			
0	1	0			
0	1	1			
1	0	0			

 

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0		$Q_B(T)=0$ $T_B=Q'_C(T)=1$ ----- $\text{Comp. } (Q_B(T)) = 1$	1
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			

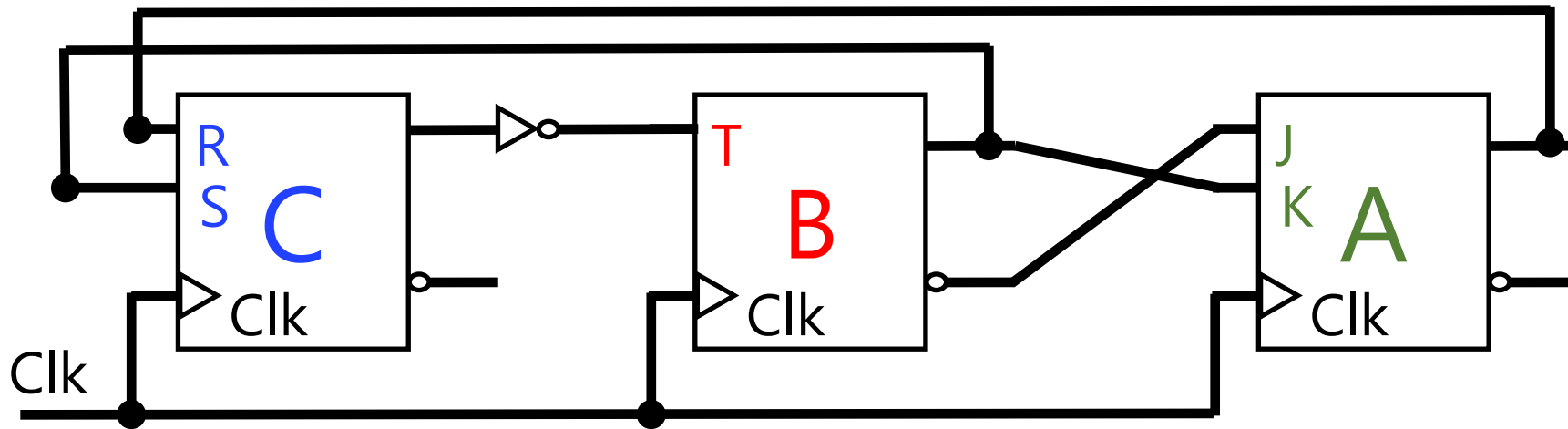


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	$Q_C(T)=0$ $R_C=Q_A(T)=0$ $S_C=Q_B(T)=0$ ----- Store $Q_C(T) = 0$	1	1
0	0	1			
0	1	0			
0	1	1			
1	0	0			

Analysis

$$Q_A(T) = A, Q'_A(T) = A'$$

 For simplicity, the **current status** of a FF can be assume to be as a **binary variable**





Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	1	1
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	×	0	0
1	0	0	1	0	1
1	0	1	0	0	1
1	1	0	0	1	0
1	1	1	×	1	0

Analysis

5) State Transition Diagram

 - 5.1. for each state combination (each row), a node
- 5.2. from one state (node) to another state, a directed edge



 

Design by an example

Counter

Count from 0 to N

Design

0. Do we need combinational logic or sequential logic?

Do we need memory?

Counter

Count from 0 to N

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow \dots \rightarrow N-1 \rightarrow N$

Counter

Count from 0 to N

$0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow \dots \rightarrow N-1 \rightarrow N$

At each step, we have to see at number we are and then move to next number: $i \rightarrow i+1$

Counter

Count from 0 to N

We need a storage to store current number.

We need a sequential circuit!

Design

1. How many storage (flip-flops)?

Depends on the **storage** you need to store
the **current state** in **binary system**!

Counter

Count from 0 to N

$N = 7$

$1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 5 \rightarrow 6 \rightarrow 7$

$000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111$


For each intermediate state, we need 3 bits \rightarrow 3 flip-flops


Design

 2. Form the state (transition) diagram


Same as analysis,

- For each state \rightarrow one node
- For each state transition to next state \rightarrow a directed edge



 

Loop to the
beginning!

 


Stuck in 7
Just one time counter!

Design

3. Form the state table

Same as analysis, **two columns** for **each flip-flop** (storage unit)


- a) One for current state $Q(T)$
- b) One for next state $Q(T+1)$

 [illegible]


Design

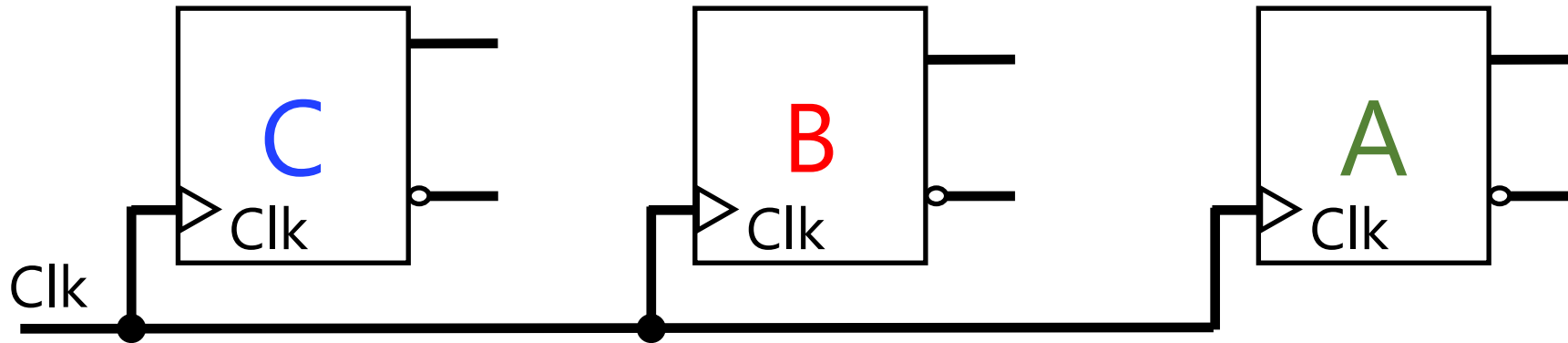4. Fill the state table


Unlike analysis, here we already know what is going to be the next state $Q(T+1)$ based on current state $Q(T)$




Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

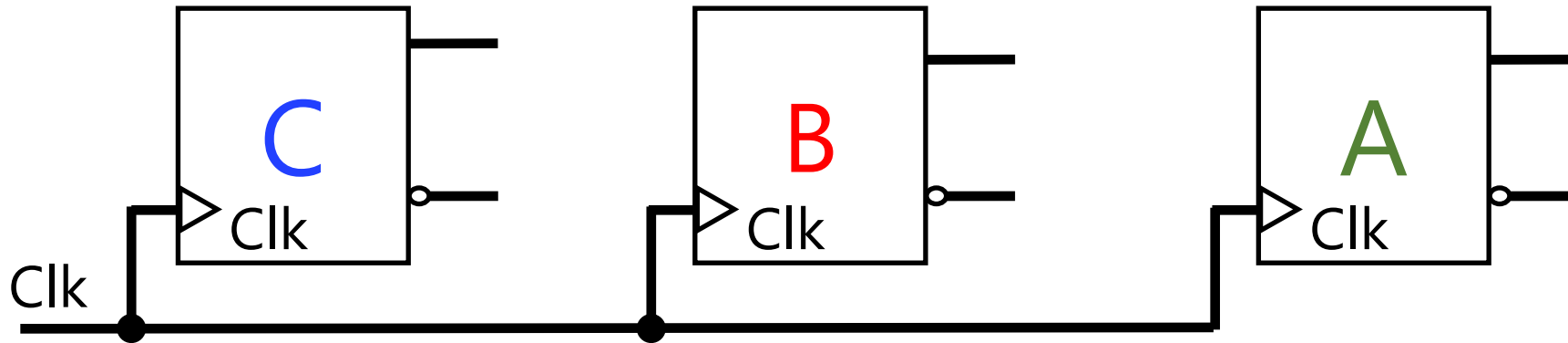


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

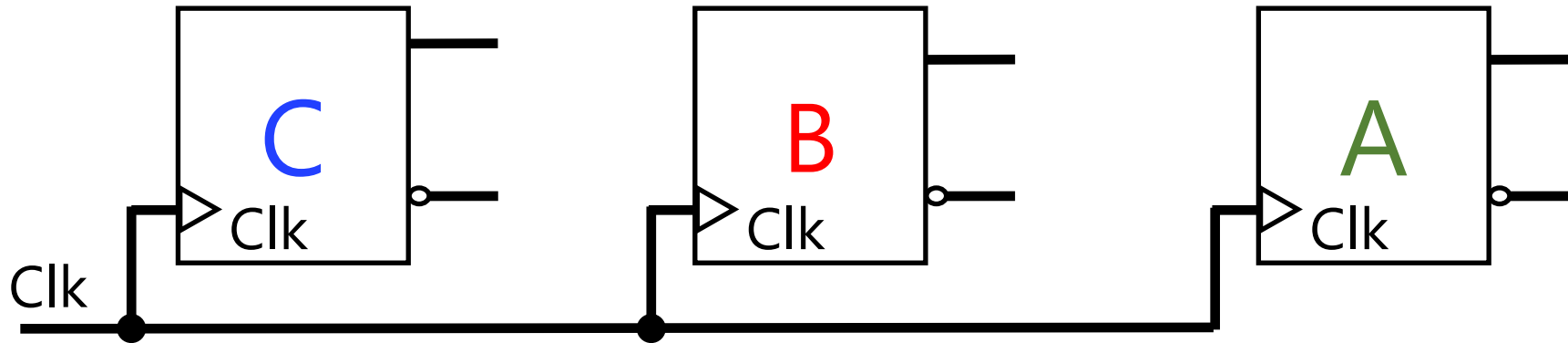


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

 


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0			
1	0	1			
1	1	0			
1	1	1			

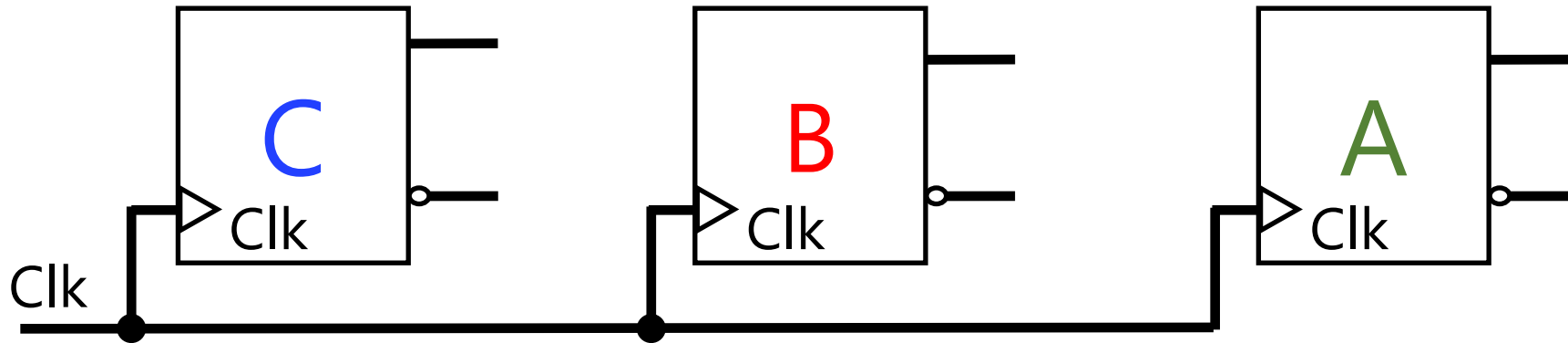


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1			
1	1	0			
1	1	1			

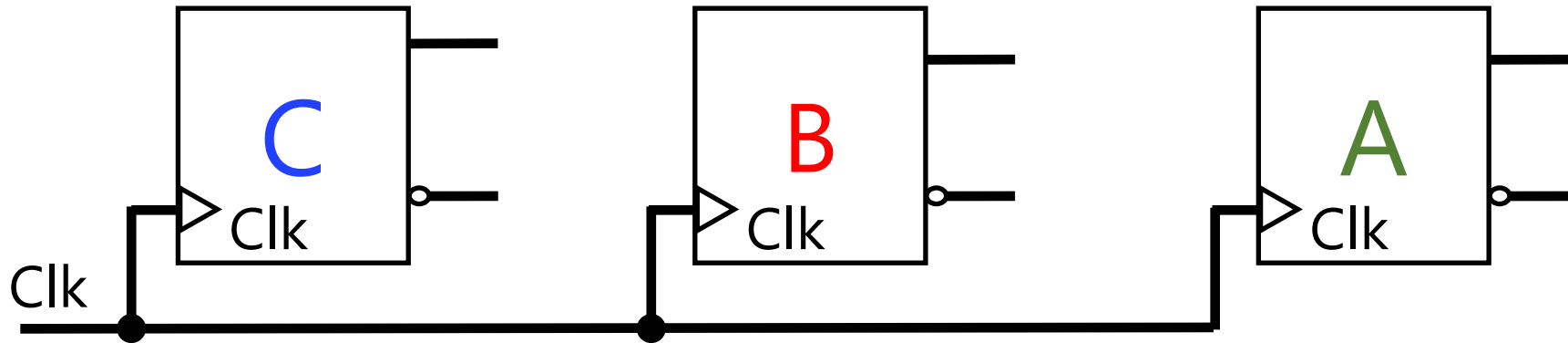


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0			
1	1	1			

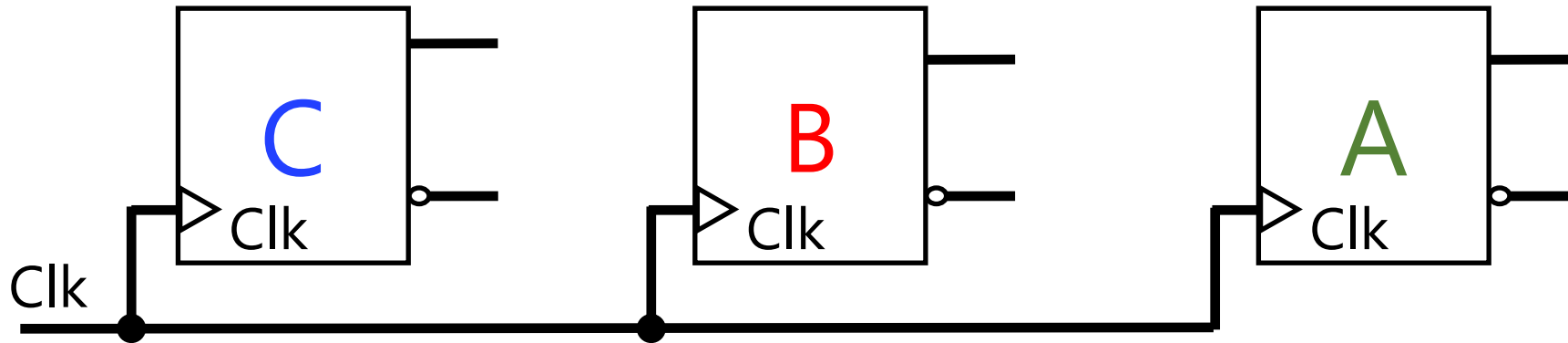


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1			

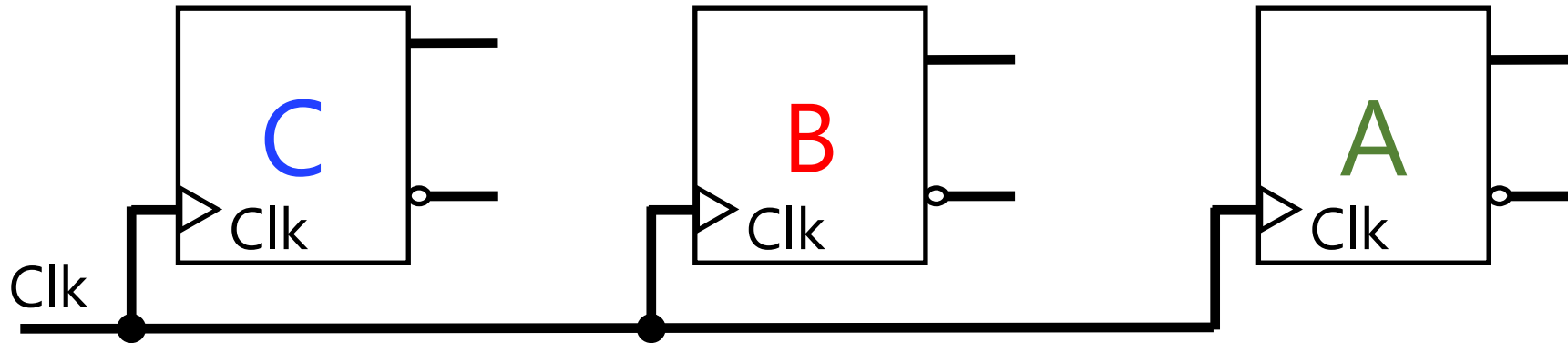


Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	?	?	?

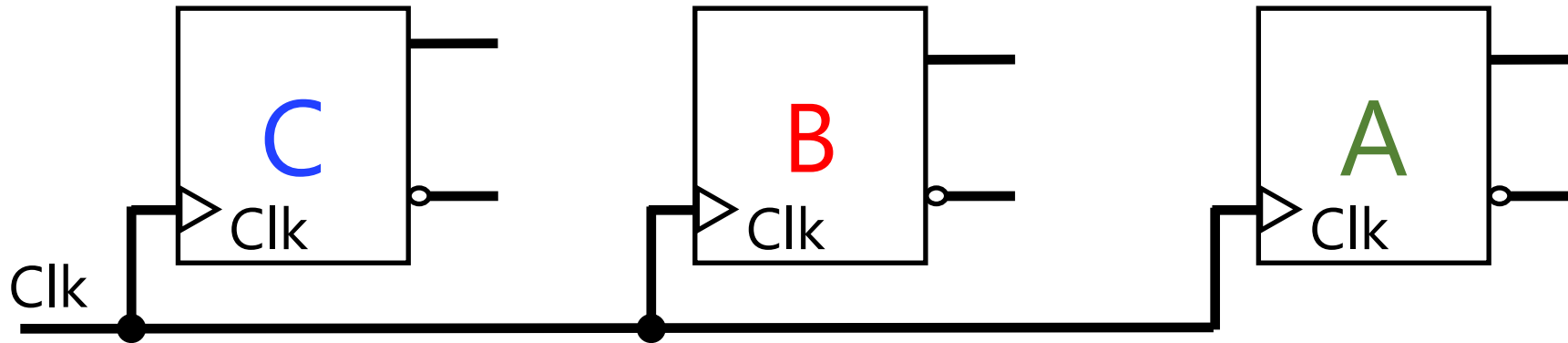

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	Loop to the beginning!	1
1	0	1	1		0
1	1	0	1		1
1	1	1	0	0	0

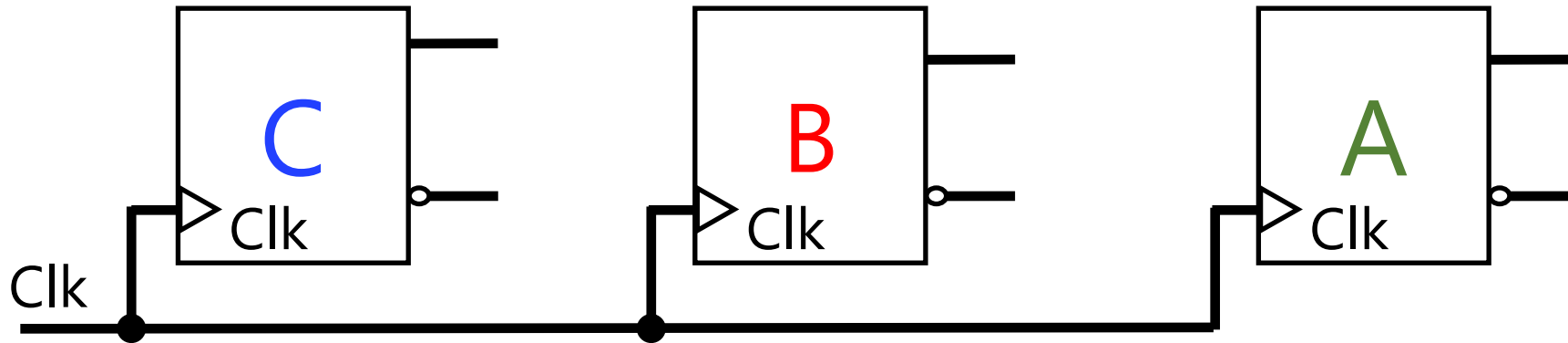

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	Stuck in 7 Just one time counter!	1
1	0	1	1		0
1	1	0	1		1
1	1	1	1		1

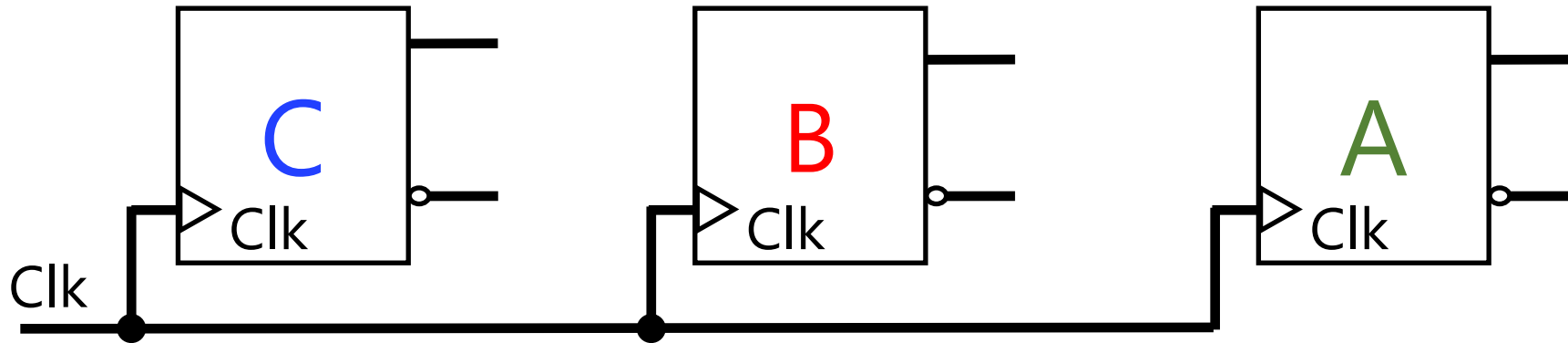

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	Our Design Choice!	1
1	0	1	1		0
1	1	0	1		1
1	1	1	0	0	0

Design

5. What type of storage (flip-flop)?

RS, D, T, JK, or Mixed

Design

5. What type of storage (flip-flop)?

RS, D, T, JK, or Mixed



In terms of design, does not matter.

In terms of **efficiency**, matters!

Counter

Count from 0 to $N=7$

Let's select **JK**, the complete FF.

  

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Design

6. Boolean expression for the flip-flops' input?
input equations, aka, *excitation* equations

Counter


Count from 0 to N=7

A	$J_A =$	$K_A =$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$


Counter

Count from 0 to $N=7$


A	$J_A =$	$K_A =$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

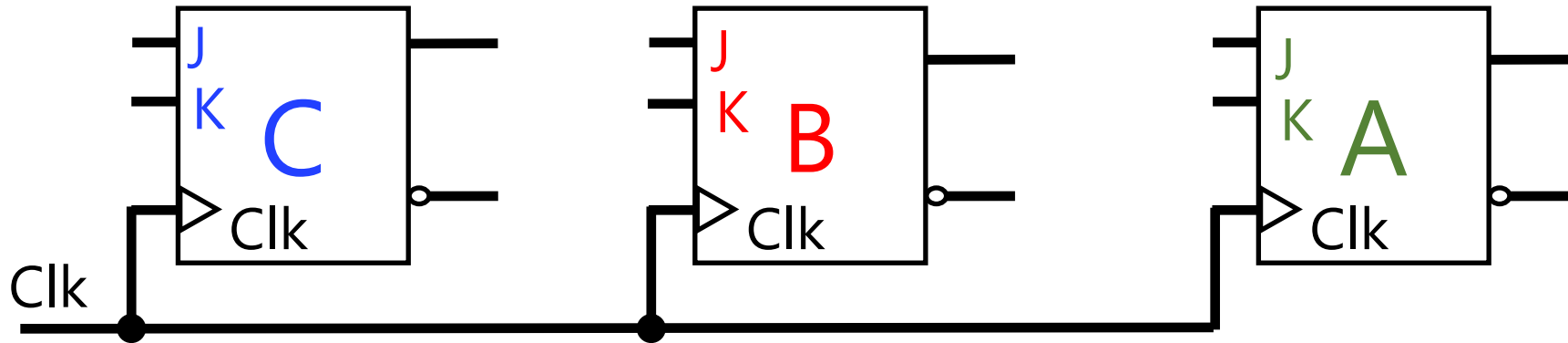

Q(T)			Q(T+1)		
C	B	A	C	B	A
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

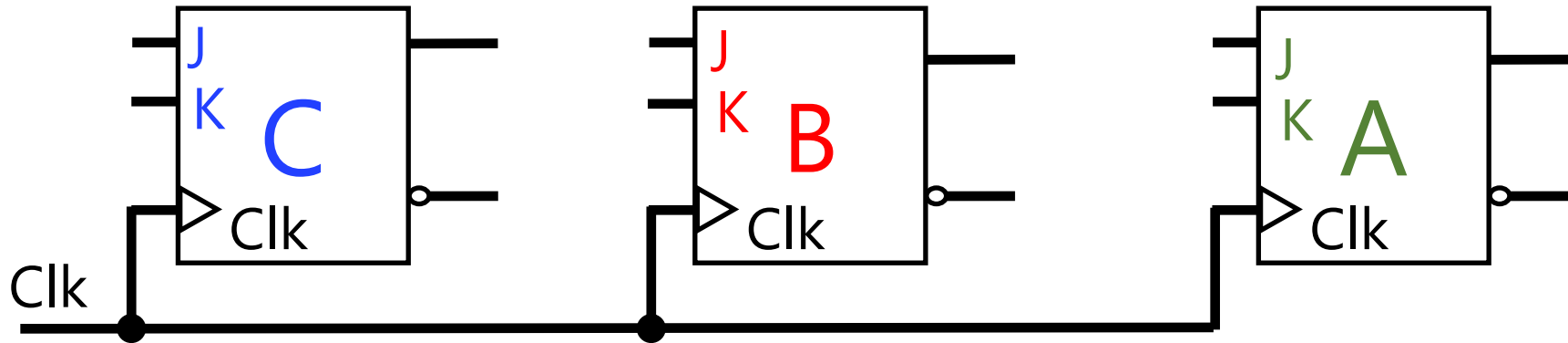


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1			
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

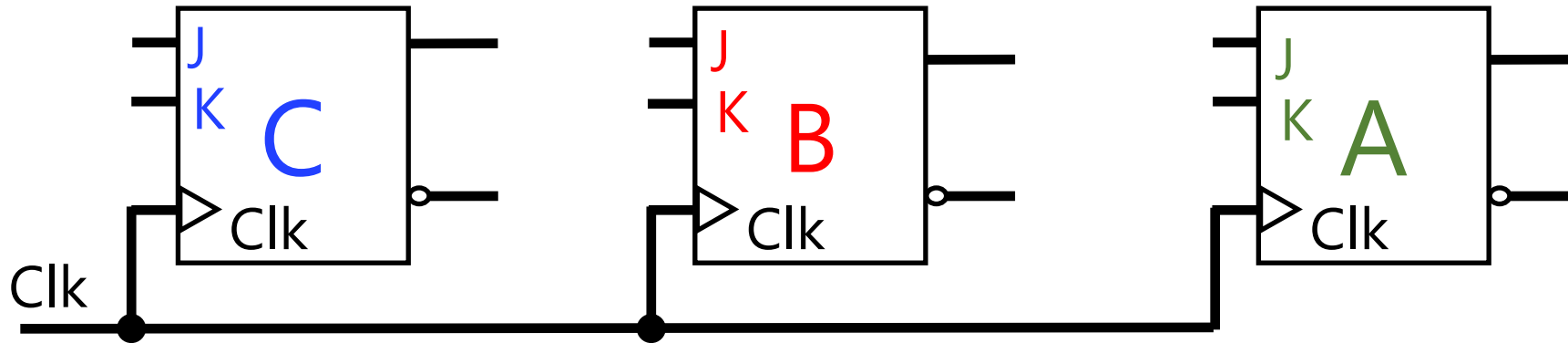


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set	1	0
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			


OR

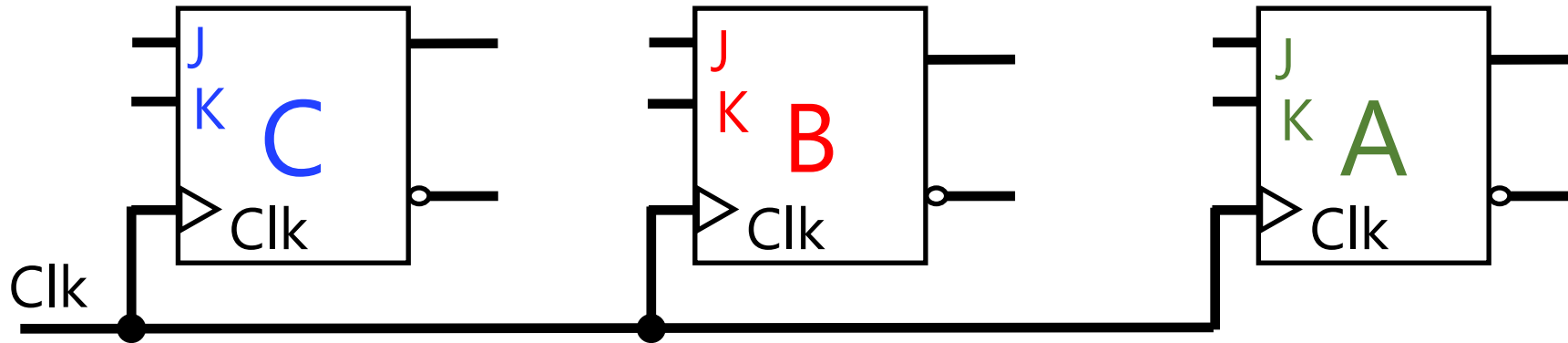

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Comp	1	1
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

 


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	0/1 → ∞
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

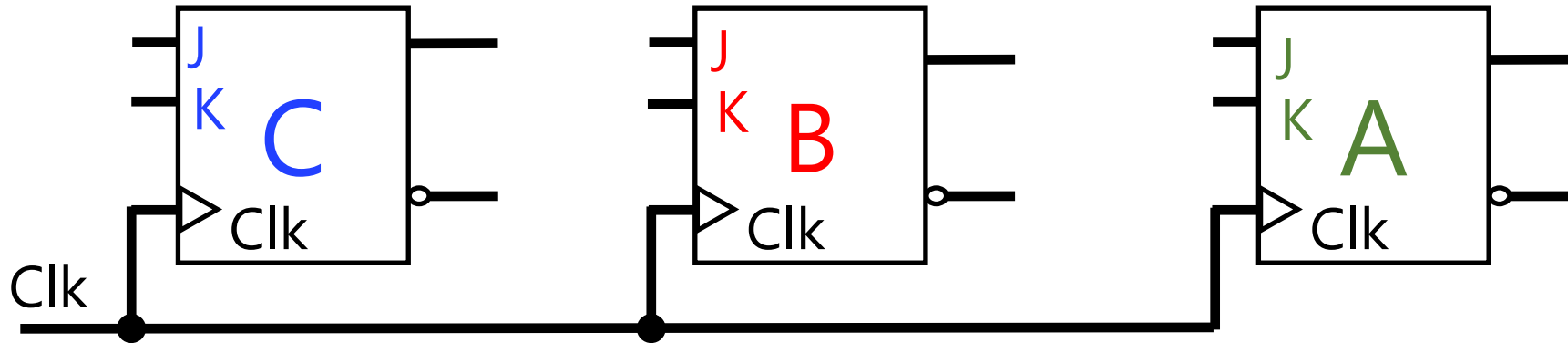


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset	0	1
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			


OR

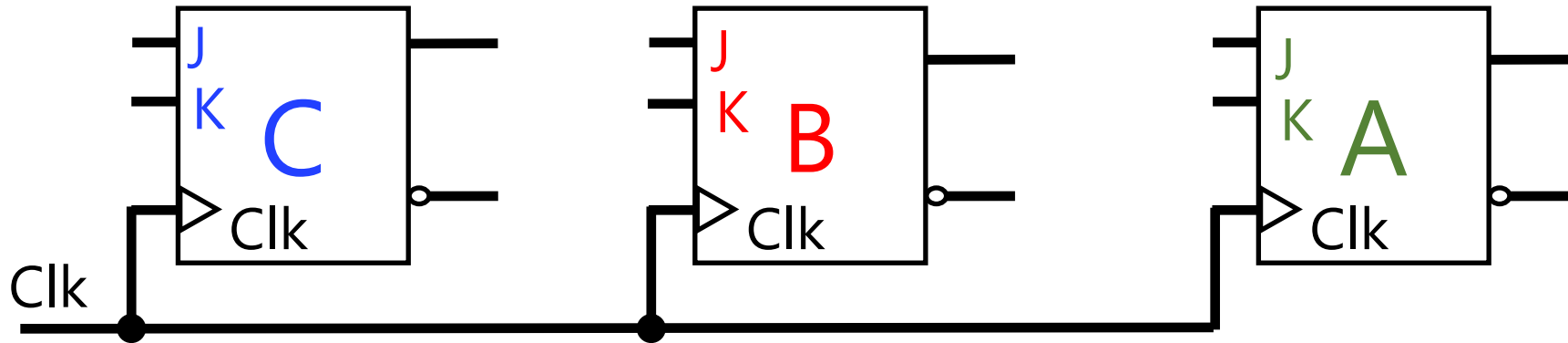


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Comp.	1	1
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

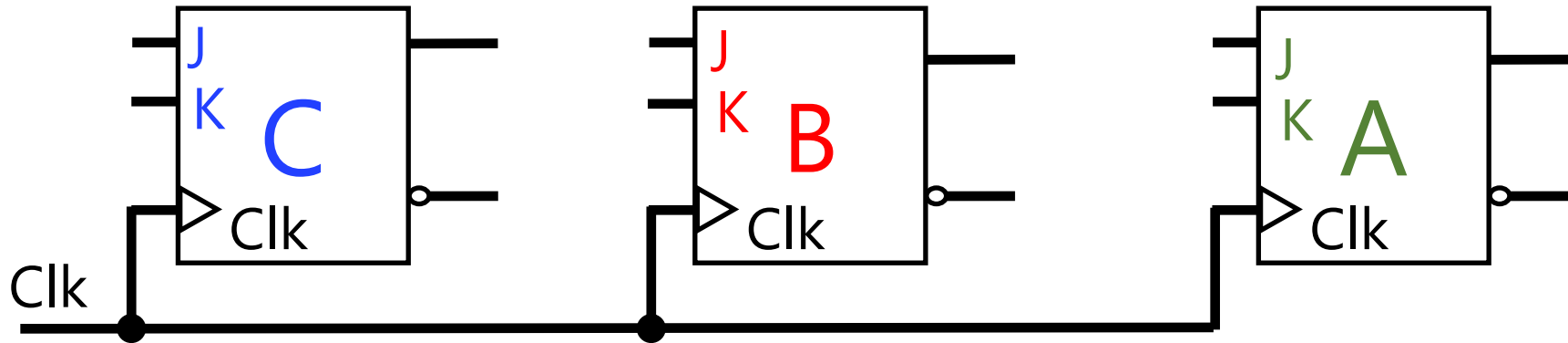


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset/Comp	\times	1
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

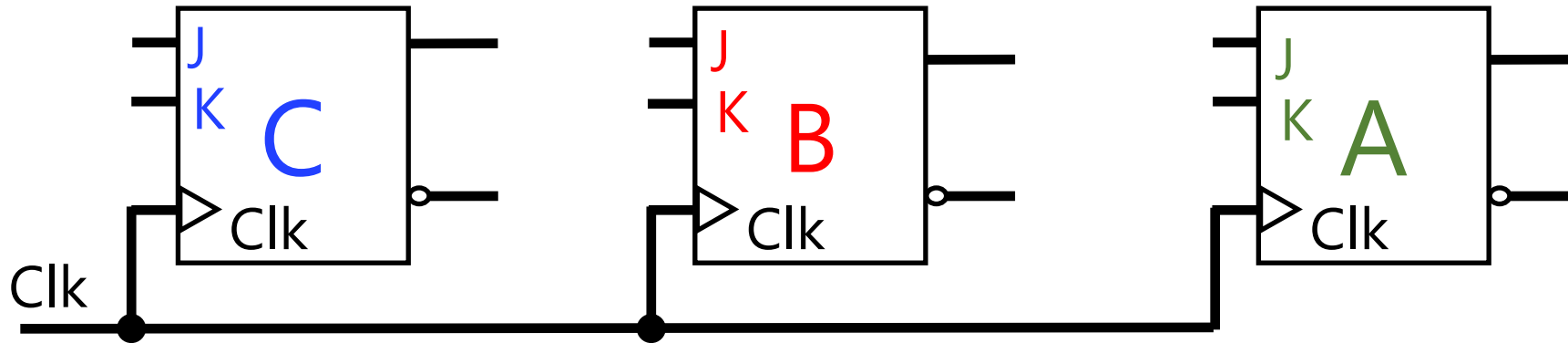

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	\times
0	0	1	0	1	0	Reset/Comp	\times	1
0	1	0	0	1	1	Set/Comp	1	\times
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

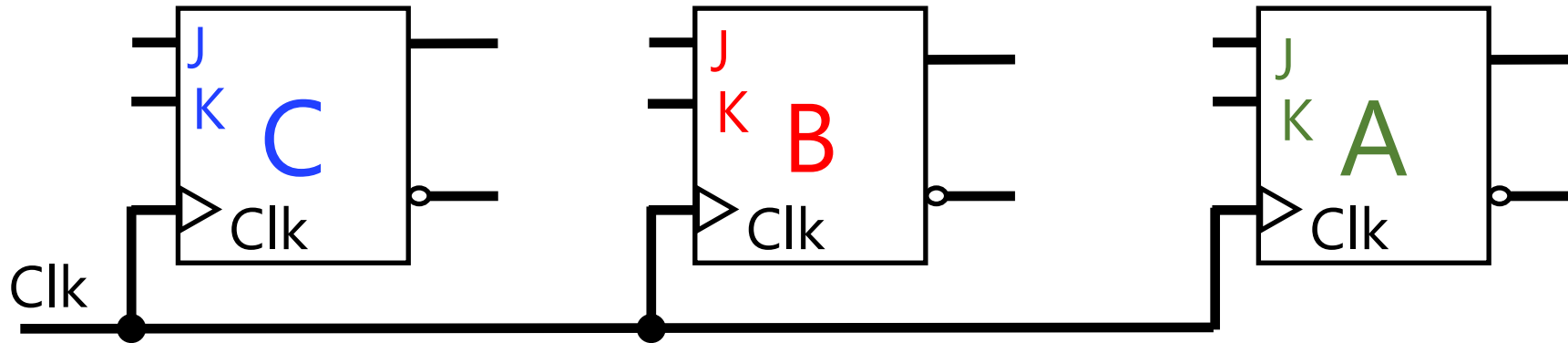

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_A	K_A
0	0	0	0	0	1	Set/Comp	1	×
0	0	1	0	1	0	Reset/Comp	×	1
0	1	0	0	1	1	Set/Comp	1	×
0	1	1	1	0	0	Reset/Comp	×	1
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

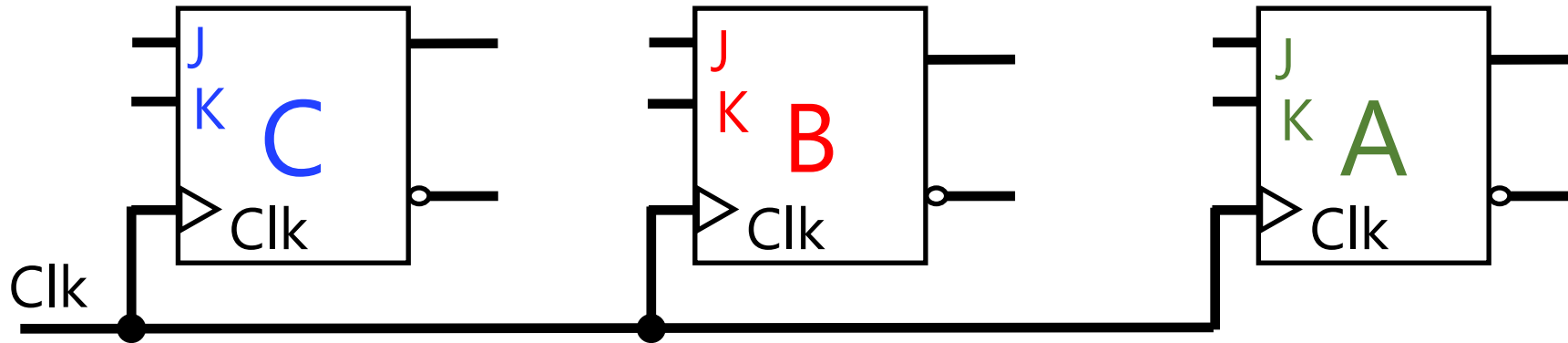


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _A	K _A
0	0	0	0	0	1	Set/Comp	1	×
0	0	1	0	1	0	Reset/Comp	×	1
0	1	0	0	1	1	Set/Comp	1	×
0	1	1	1	0	0	Reset/Comp	×	1
1	0	0	1	0	1	Set/Comp	1	×
1	0	1	1	1	0	Reset/Comp	×	1
1	1	0	1	1	1	Set/Comp	1	×
1	1	1	0	0	0	Reset/Comp	×	1

Counter

Count from 0 to N=7

Flip-Flops

 


A	$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$	$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

Counter


Count from 0 to N=7

A	$J_A = F(C, B, A) = \sum(0, 2, 4, 6) + d(1, 3, 5, 7)$	$K_A = F(C, B, A) = \sum(1, 3, 5, 7) + d(0, 2, 4, 6)$
B	$J_B =$	$K_B =$
C	$J_C =$	$K_C =$

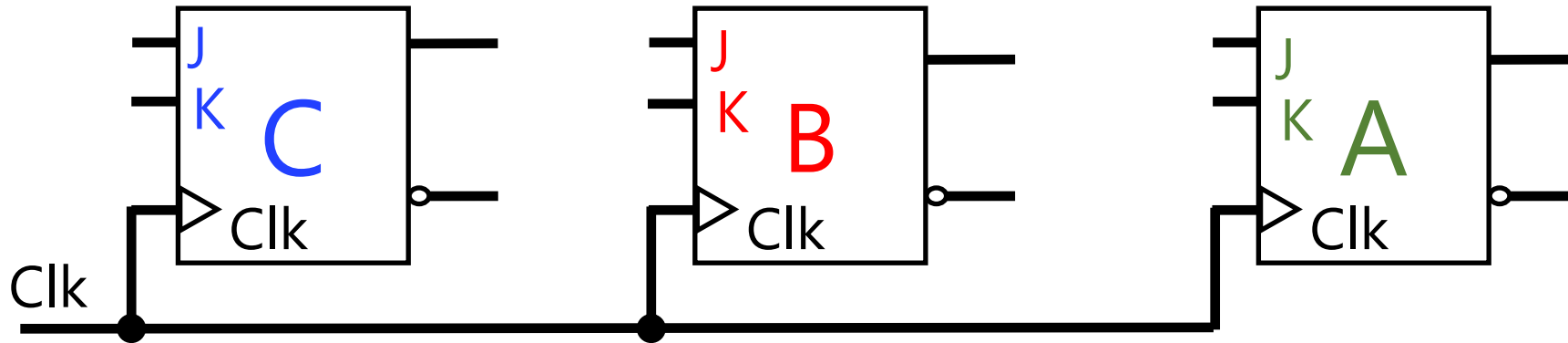


Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_B	K_B
0	0	0	0	0	1	Store	0	0
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

OR

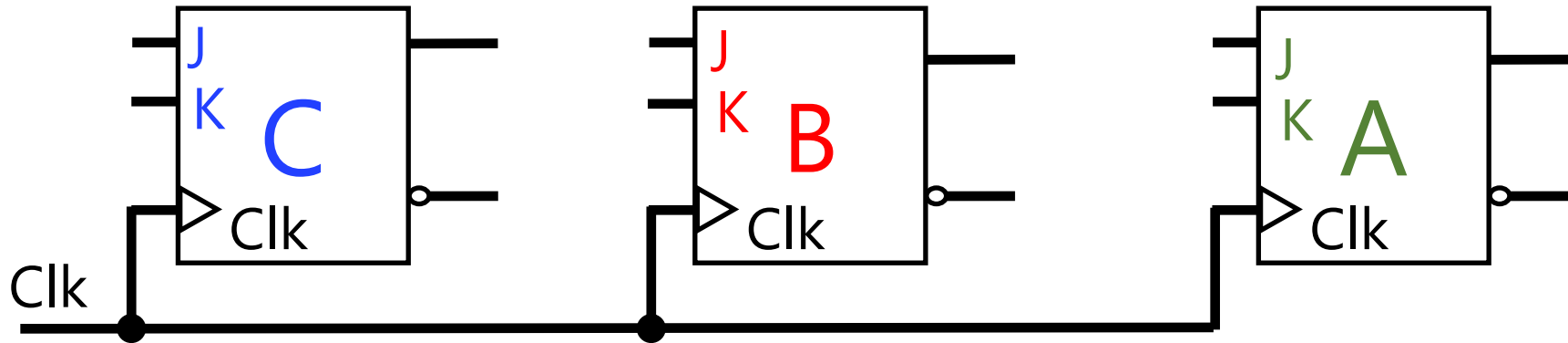

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_B	K_B
0	0	0	0	0	1	Reset	0	1
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

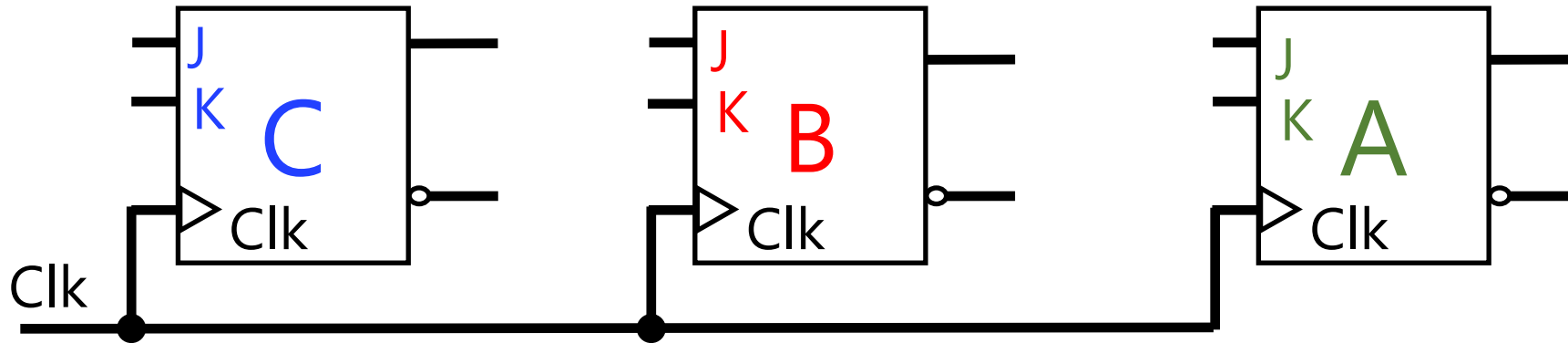

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J _B	K _B
0	0	0	0	0	1	Store/Reset	0	×
0	0	1	0	1	0	Set/Comp	1	×
0	1	0	0	1	1	Store/Set	×	0
0	1	1	1	0	0	Reset/Comp	×	1
1	0	0	1	0	1	Store/Reset	0	×
1	0	1	1	1	0	Set/Comp	1	×
1	1	0	1	1	1	Store/Set	×	0
1	1	1	0	0	0	Reset/Comp	×	1

Counter


Count from 0 to N=7

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C =$	$K_C =$

Counter

Count from 0 to N=7

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C =$	$K_C =$

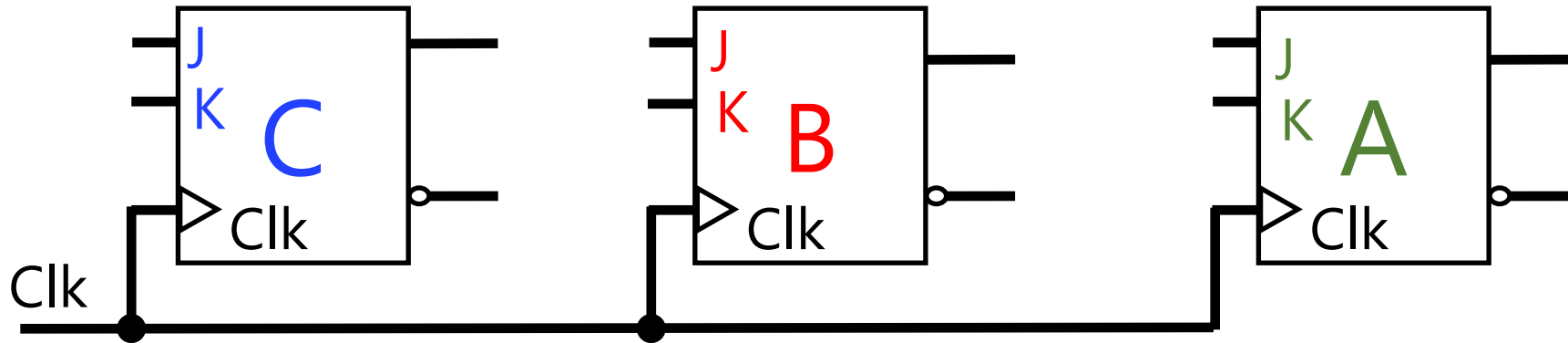

Q(T)			Q(T+1)			Not part of state table!		
C	B	A	C	B	A	Action	J_C	K_C
0	0	0	0	0	1	Store/Reset	0	×
0	0	1	0	1	0	Store/Reset	0	×
0	1	0	0	1	1	Store/Reset	0	×
0	1	1	1	0	0	Comp/Set	1	×
1	0	0	1	0	1	Store/Set	×	0
1	0	1	1	1	0	Store/Set	×	0
1	1	0	1	1	1	Store/Set	×	0
1	1	1	0	0	0	Comp/Reset	×	1

Counter

Count from 0 to N=7

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C = F(C,B,A) = \sum(3) + d(4,5,6,7)$	$K_C = F(C,B,A) = \sum(7) + d(0,1,2,3)$

Design

7. Minimization of input (*excitation*) equations

Counter

Count from 0 to N=7

3-Variable K-Map

A	$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$	$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$
B	$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$	$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$
C	$J_C = F(C,B,A) = \sum(3) + d(4,5,6,7)$	$K_C = F(C,B,A) = \sum(7) + d(0,1,2,3)$

		BA			
		00	01	11	10
C	0	0 m_0	0 m_1	1 m_3	0 m_2
	1	X m_4	X m_5	X m_7	X m_6

$$J_C = F(C,B,A) = \sum(3) + d(4,5,6,7)$$

$$J_C = BA$$

		BA			
		00	01	11	10
C	0	0 m_0	1 m_1	X m_3	X m_2
	1	0 m_4	1 m_5	X m_7	X m_6

$$J_B = F(C,B,A) = \sum(1,5) + d(2,3,6,7)$$

$$J_B = A$$

		BA			
		00	01	11	10
C	0	1 m_0	X m_1	X m_3	1 m_2
	1	1 m_4	X m_5	X m_7	1 m_6

$$J_A = F(C,B,A) = \sum(0,2,4,6) + d(1,3,5,7)$$

$$J_A = 1$$

		BA			
		00	01	11	10
C	0	X m_0	X m_1	X m_3	X m_2
	1	0 m_4	0 m_5	1 m_7	0 m_6

$$K_C = F(C,B,A) = \sum(7) + d(0,1,2,3)$$

$$K_C = BA$$

		BA			
		00	01	11	10
C	0	X m_0	X m_1	0 m_3	1 m_2
	1	X m_4	X m_5	0 m_7	1 m_6

$$K_B = F(C,B,A) = \sum(3,7) + d(0,1,4,5)$$

$$K_B = A'$$


		BA			
		00	01	11	10
C	0	X m_0	1 m_1	1 m_3	X m_2
	1	X m_4	1 m_5	1 m_7	X m_6


$$K_A = F(C,B,A) = \sum(1,3,5,7) + d(0,2,4,6)$$

$$K_A = 1$$

Design


8. Draw/Sketch Logic Circuit

 

 


Design


9. (Optional) Test

 


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	?	?
5 → ?					

 


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	?	?
5 → ?					

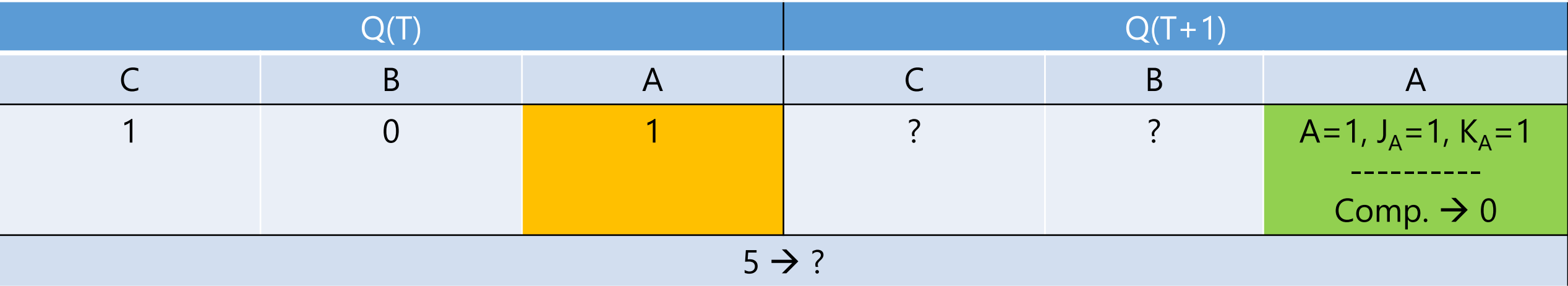

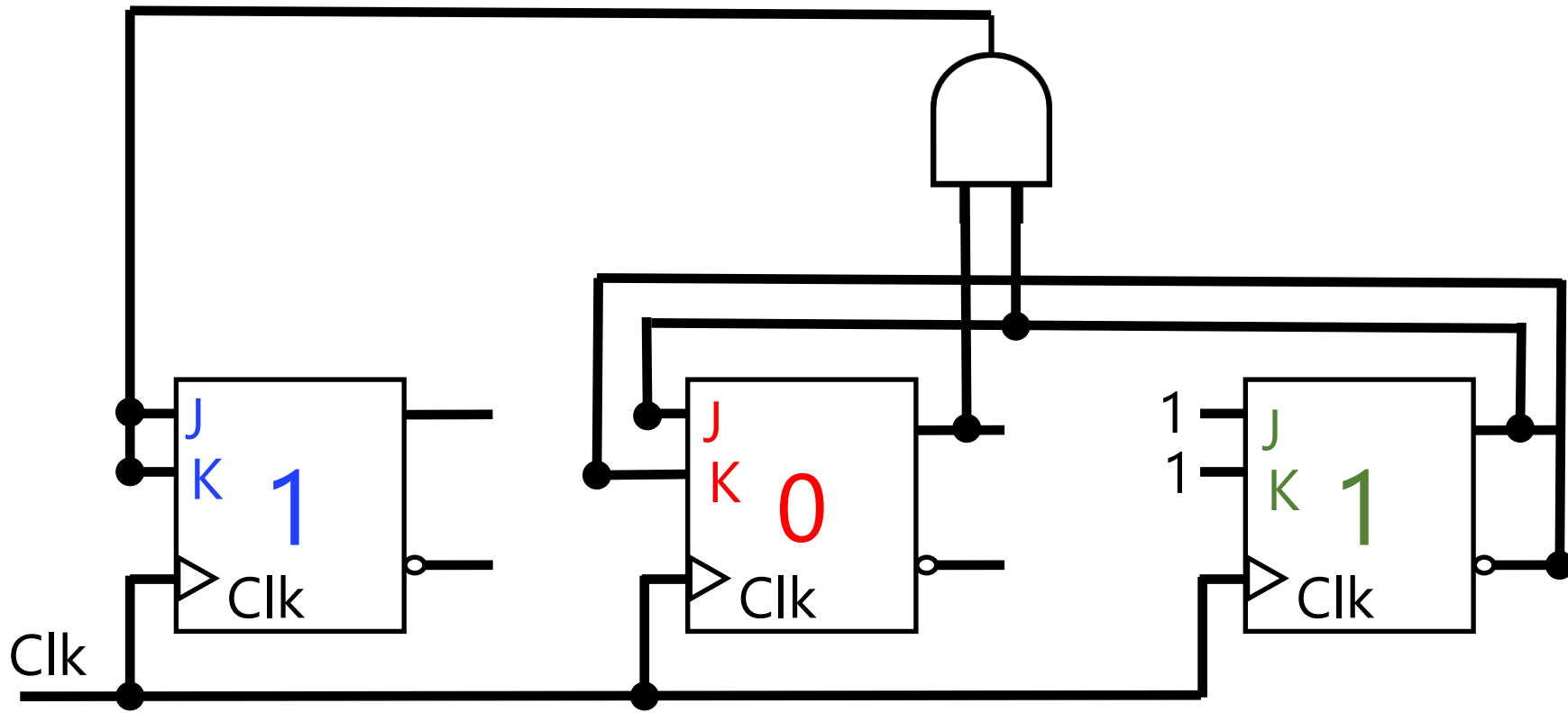



Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	?	0
5 → ?					

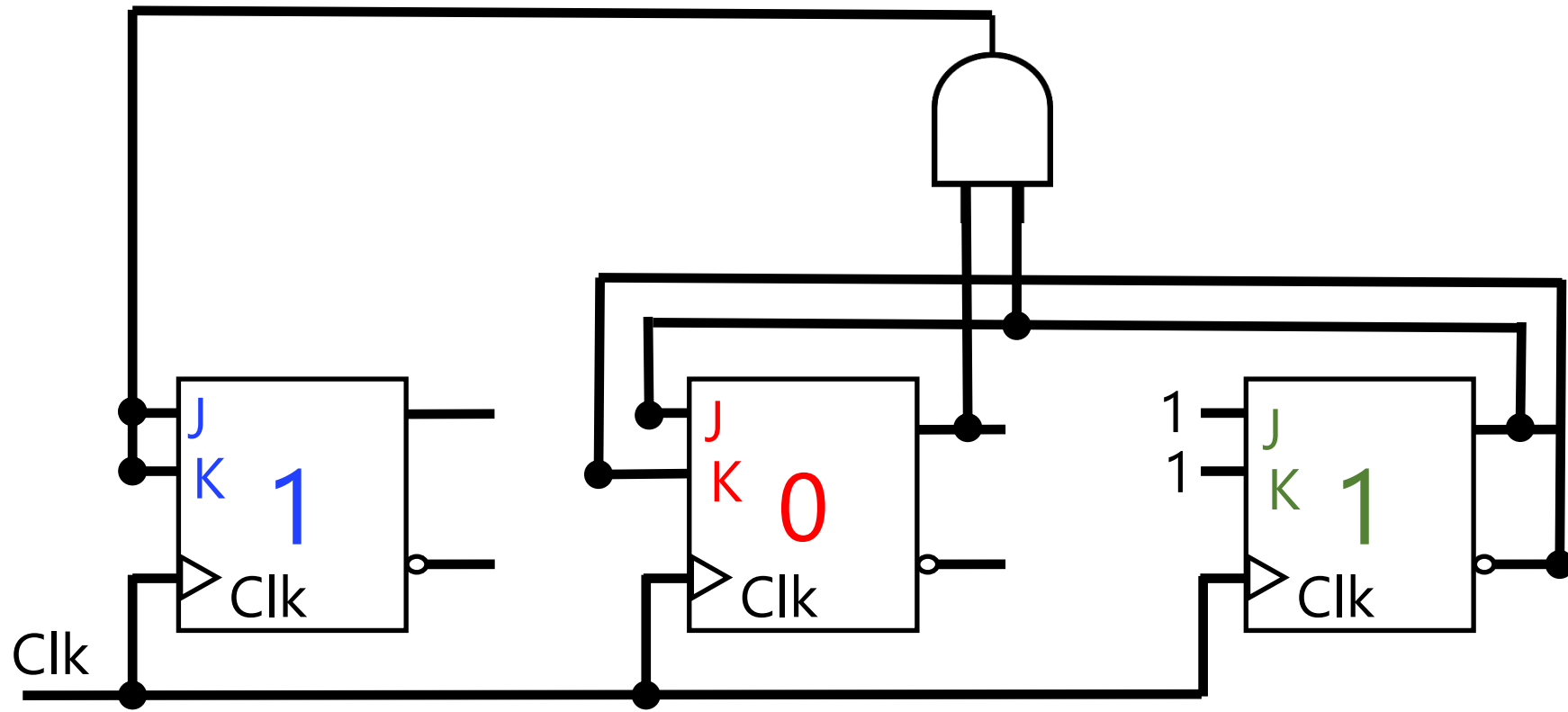


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	B=0, $J_B=A=1$, $K_B=A'=0$ ----- Set $\rightarrow 1$	0

5 \rightarrow ?

 

 


Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	?	1	0
5 → ?					

 

Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	$C=1, J_C=BA=01=0$ $K_C=BA=01=0$ ----- Store $\rightarrow 1$	1	0

5 \rightarrow ?

 

Q(T)			Q(T+1)		
C	B	A	C	B	A
1	0	1	1	1	0
5 → 6					



Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. Form the state (transition) diagram
 3. Form the state table
 4. Fill the state table
 5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 6. Input (*excitation*) equations for each FF
 7. Minimization of input (*excitation*) equations
 8. Draw/Sketch Logic Circuit
 9. (Optional) Test
-

Design (Recap)

0. Do we need combinational logic or sequential logic? Do we need memory?
 1. How many storage (flip-flops)? #FF
 2. Form the state (transition) diagram
 3. Form the state table
 4. Fill the state table
 5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed
 6. Input (*excitation*) equations for each FF
 7. Minimization of input (*excitation*) equations
 8. Draw/Sketch Logic Circuit
 9. (Optional) Test
-

Design (Advanced)

0. Do we need combinational logic or sequential logic? Do we need memory?

1. How many storage (flip-flops)? #FF

2. Form the state (transition) diagram

2.1. State Reduction

3. Form the state table

4. Fill the state table

5. What type of storage (flip-flop)? RS, D, T, JK, or Mixed

6. Input (*excitation*) equations for each FF

7. Minimization of input (*excitation*) equations

8. Draw/Sketch Logic Circuit

9. (Optional) Test

Theory of Automata

COMP-2140: Computer Languages, Grammars, and Translators

