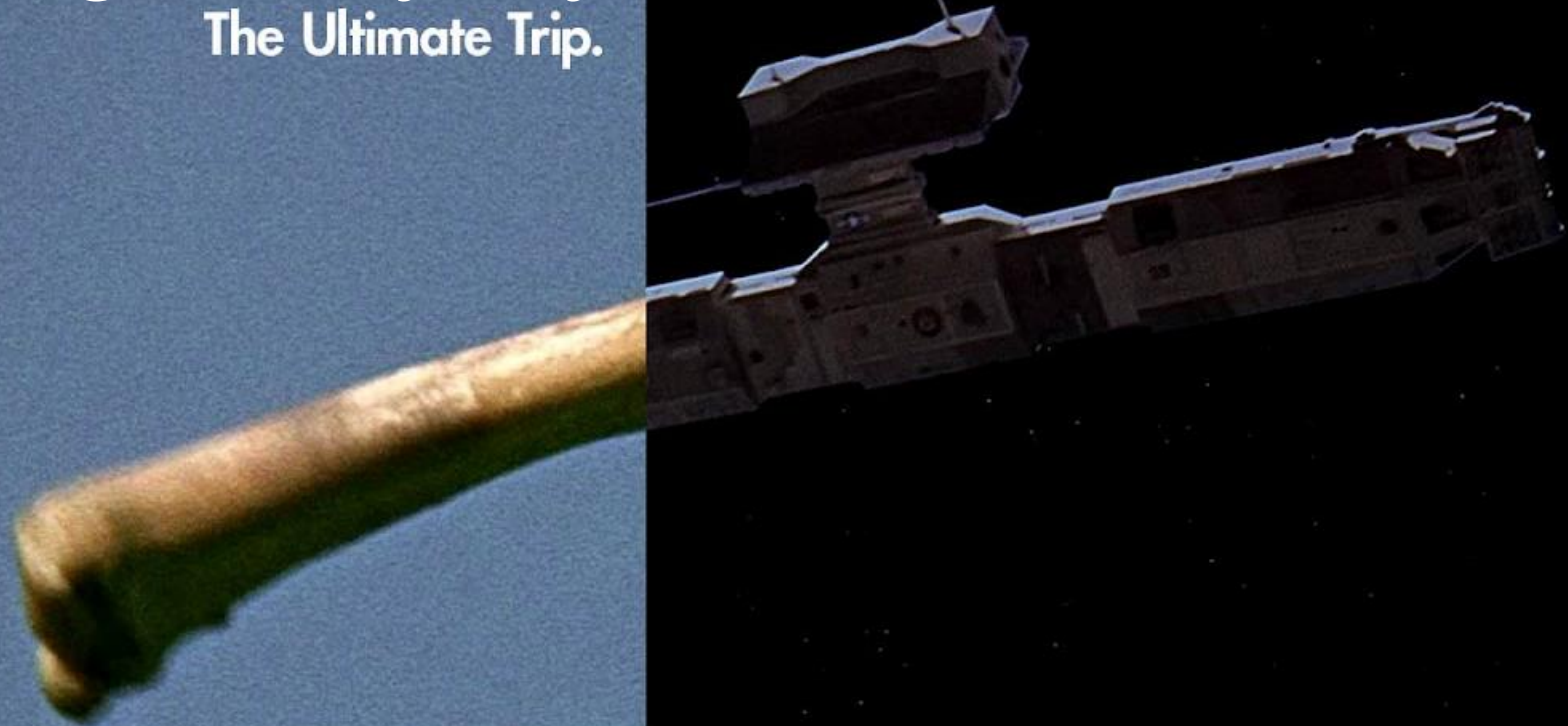


W2022: A Digital Odyssey

The Ultimate Trip.




Number Systems | $(12)_{10} \rightarrow (1100)_2$


Logic Gates |




Combinational Logic |

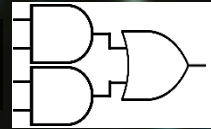


Flip-Flop |

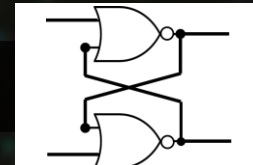

Sequential Logic |

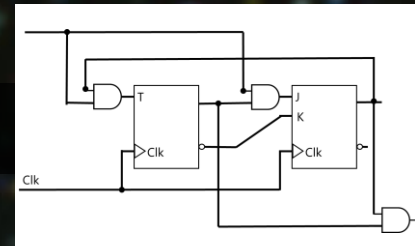

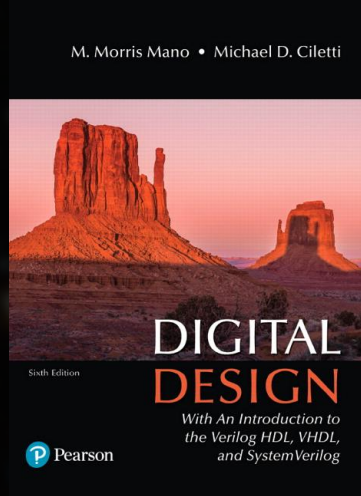


Chapter 2

Boolean Algebra and Logic Gates

ANALOG SYSTEMS

Continuous

Voltage

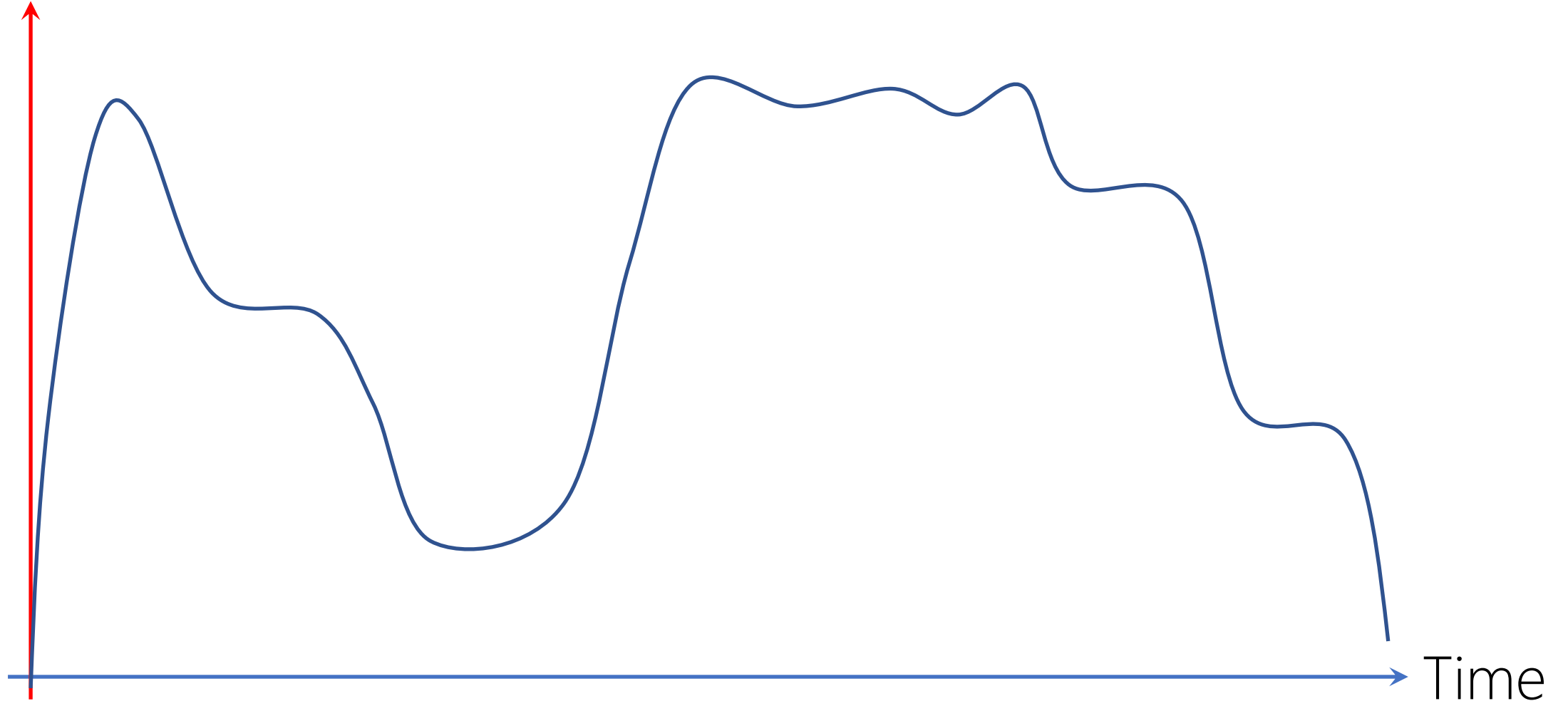

DIGITAL SYSTEMS

Discrete


ELECTRICITY NUMBER SYSTEM

BASE-?


BASE-10

Voltage

$+\infty \rightarrow 10$

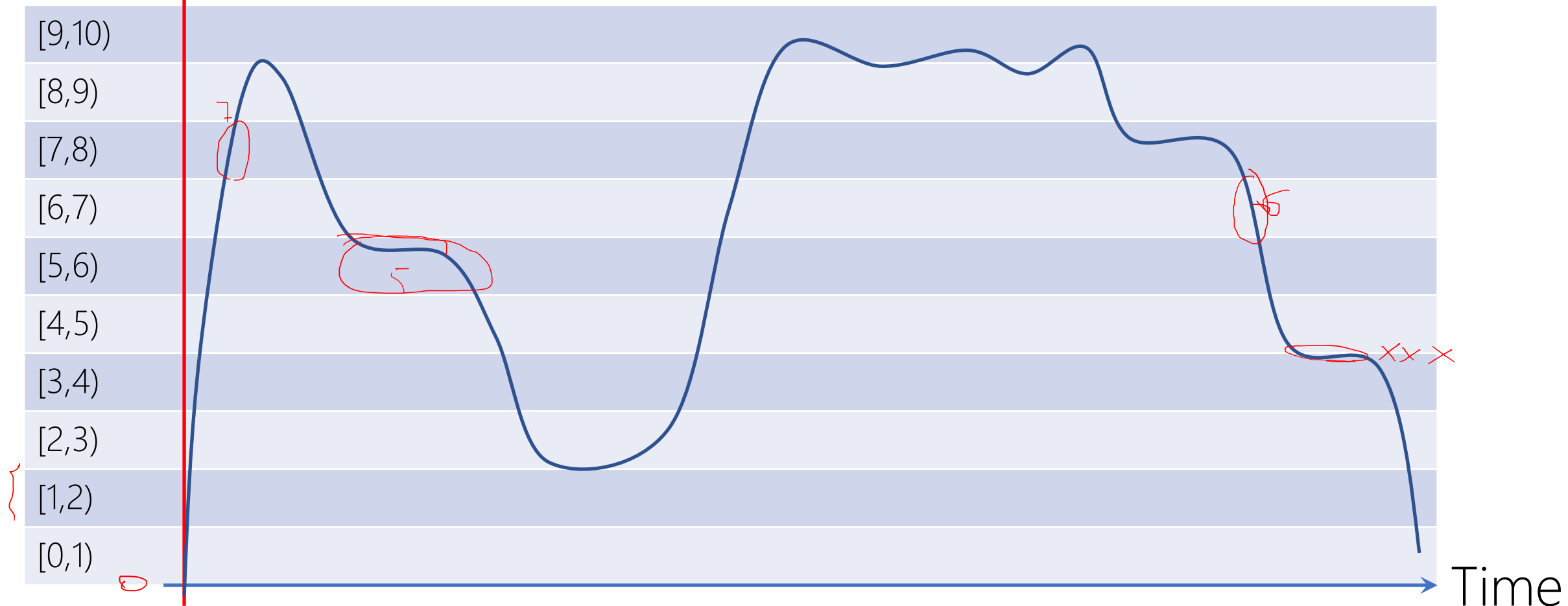


Voltage

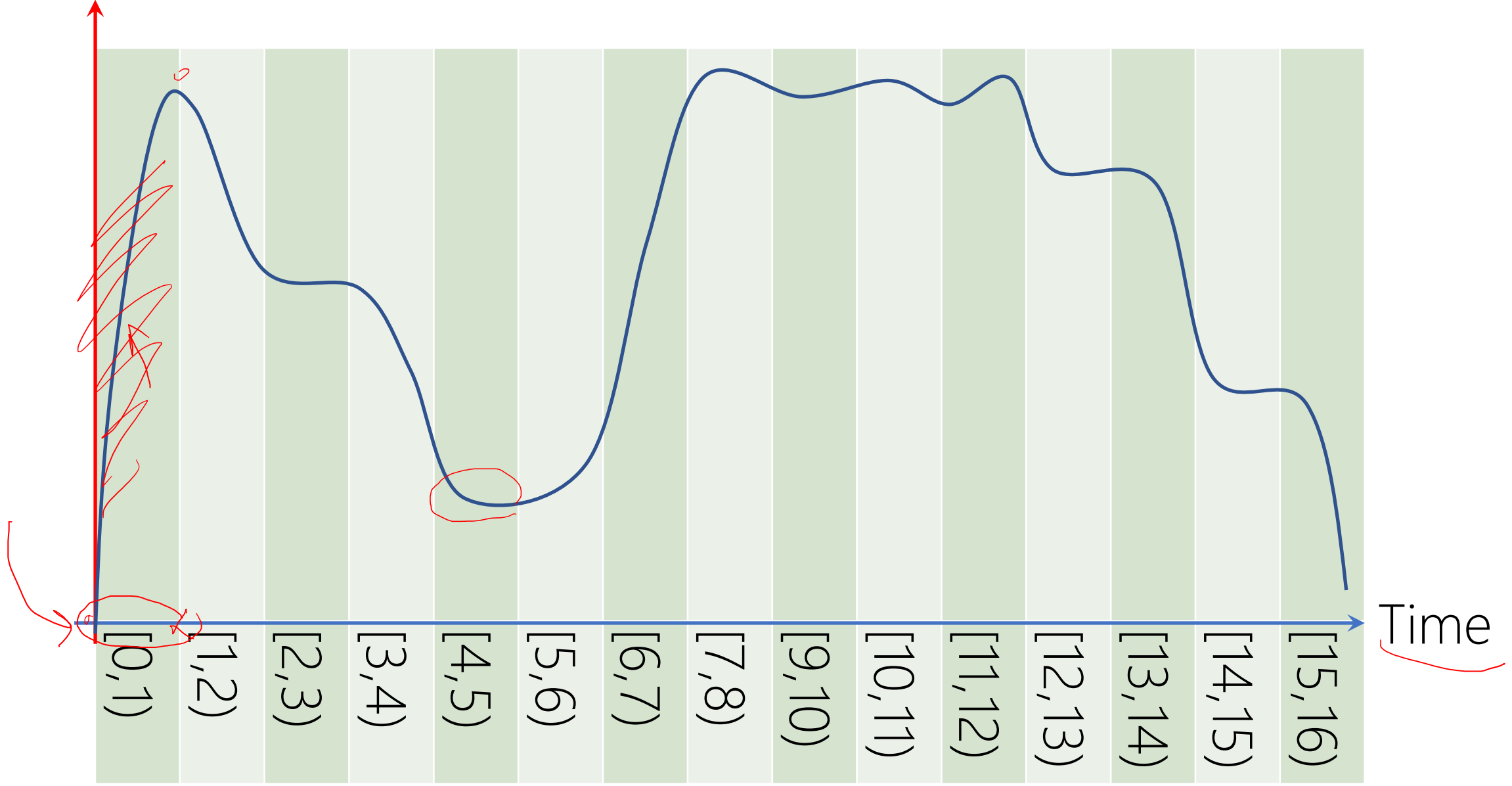


Time

Voltage

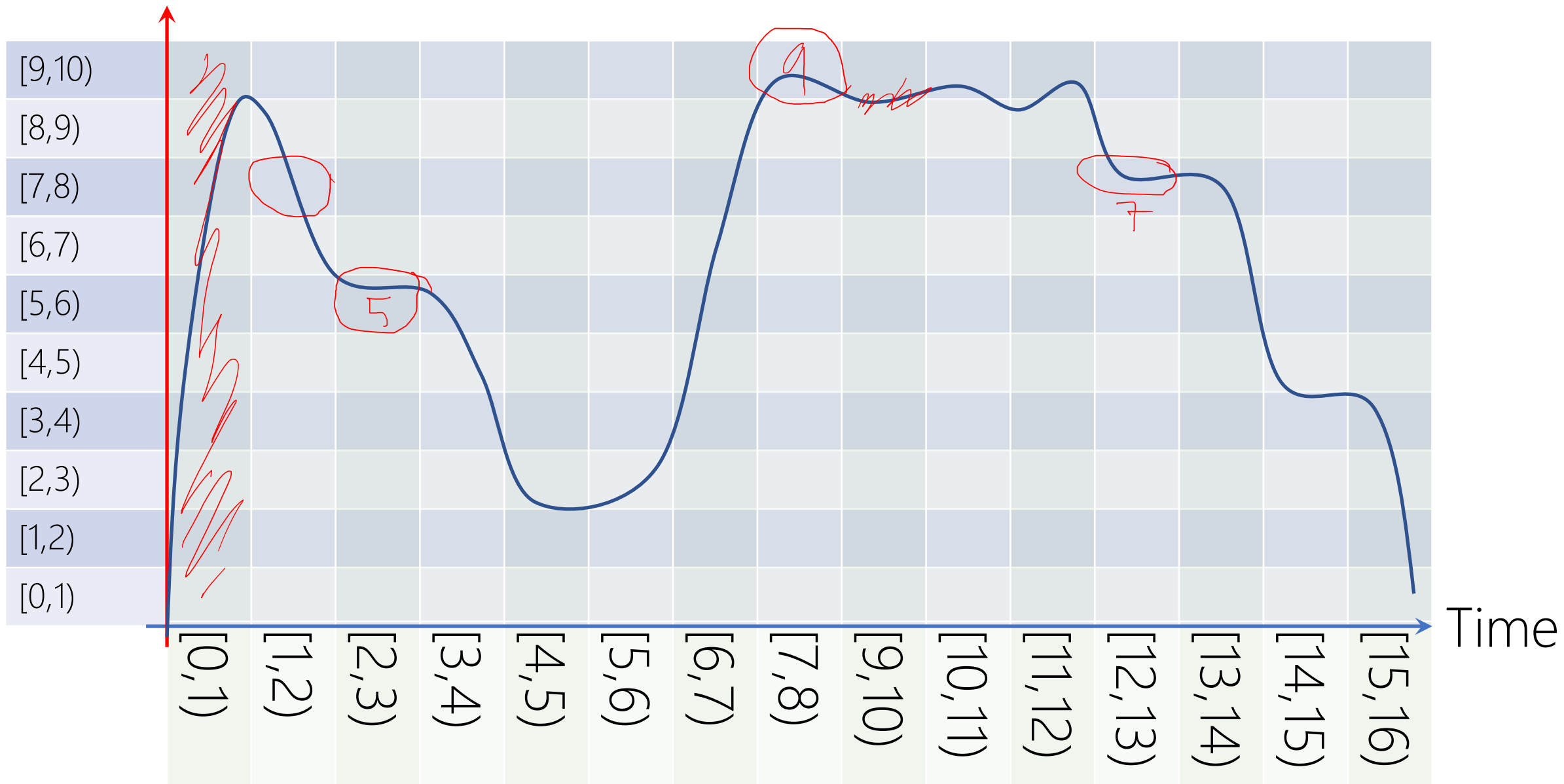


Voltage

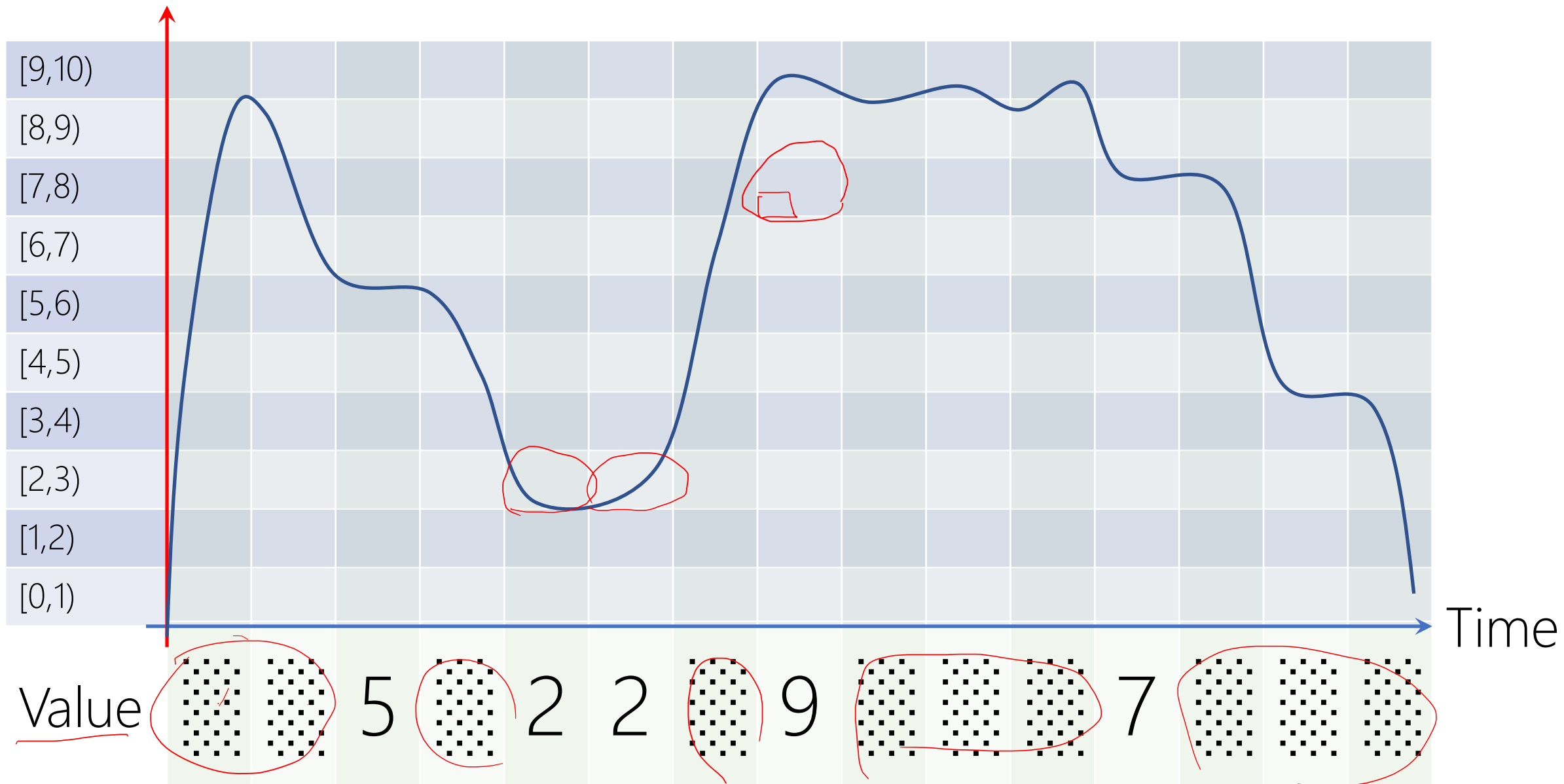


GRANULARITY

Voltage

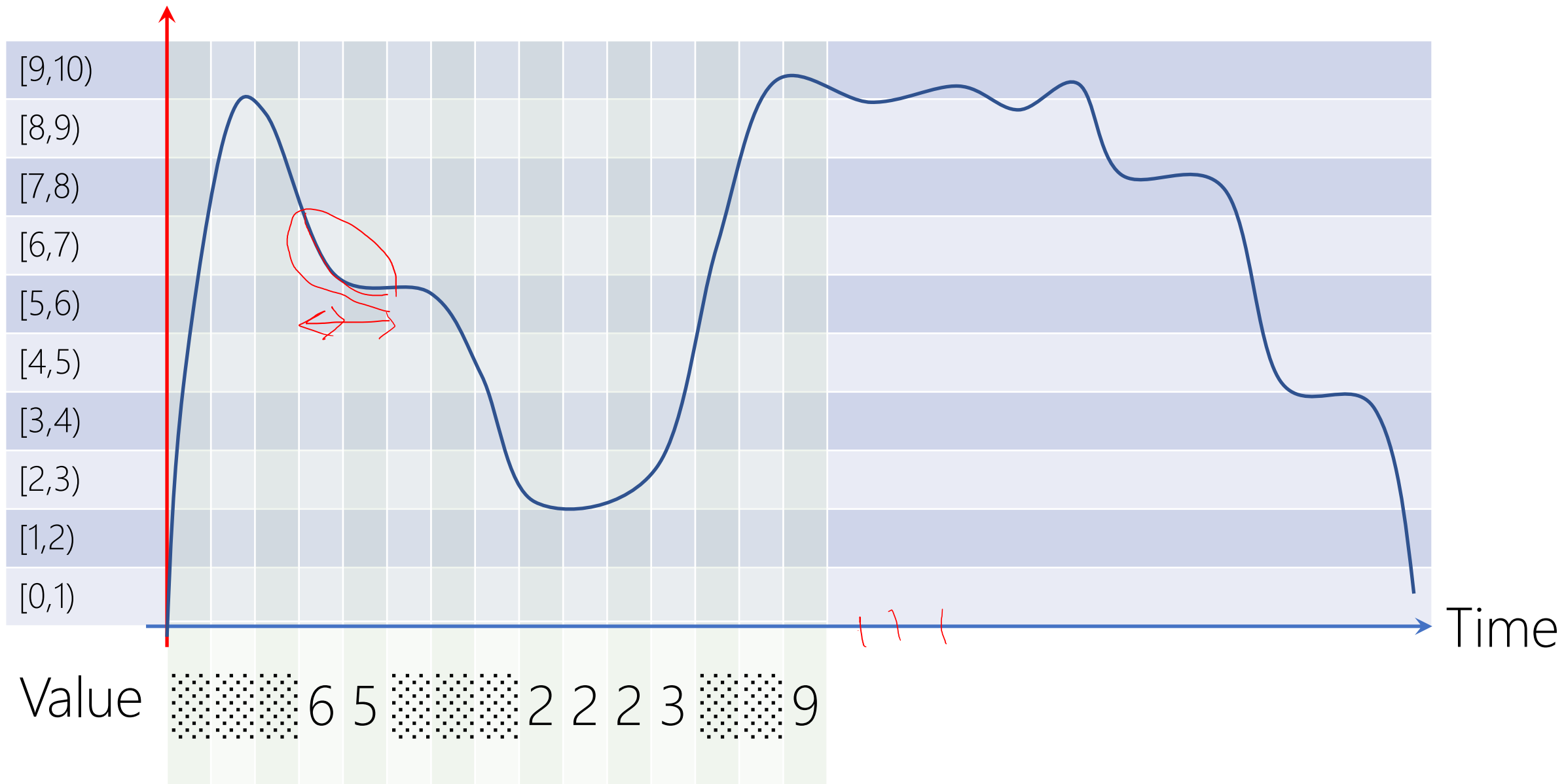


Voltage

Box e-10 → Base - 4

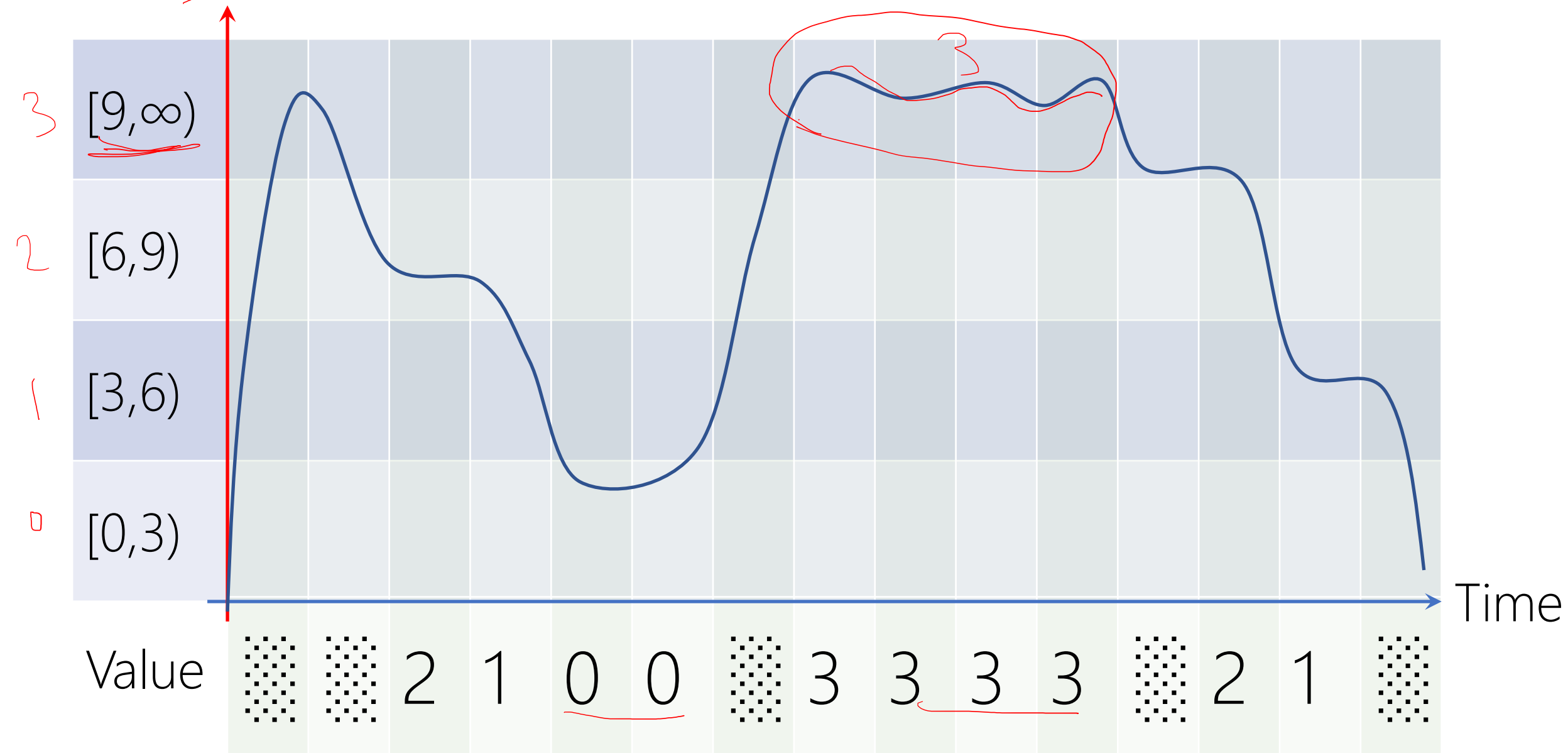

Voltage

Bn-2

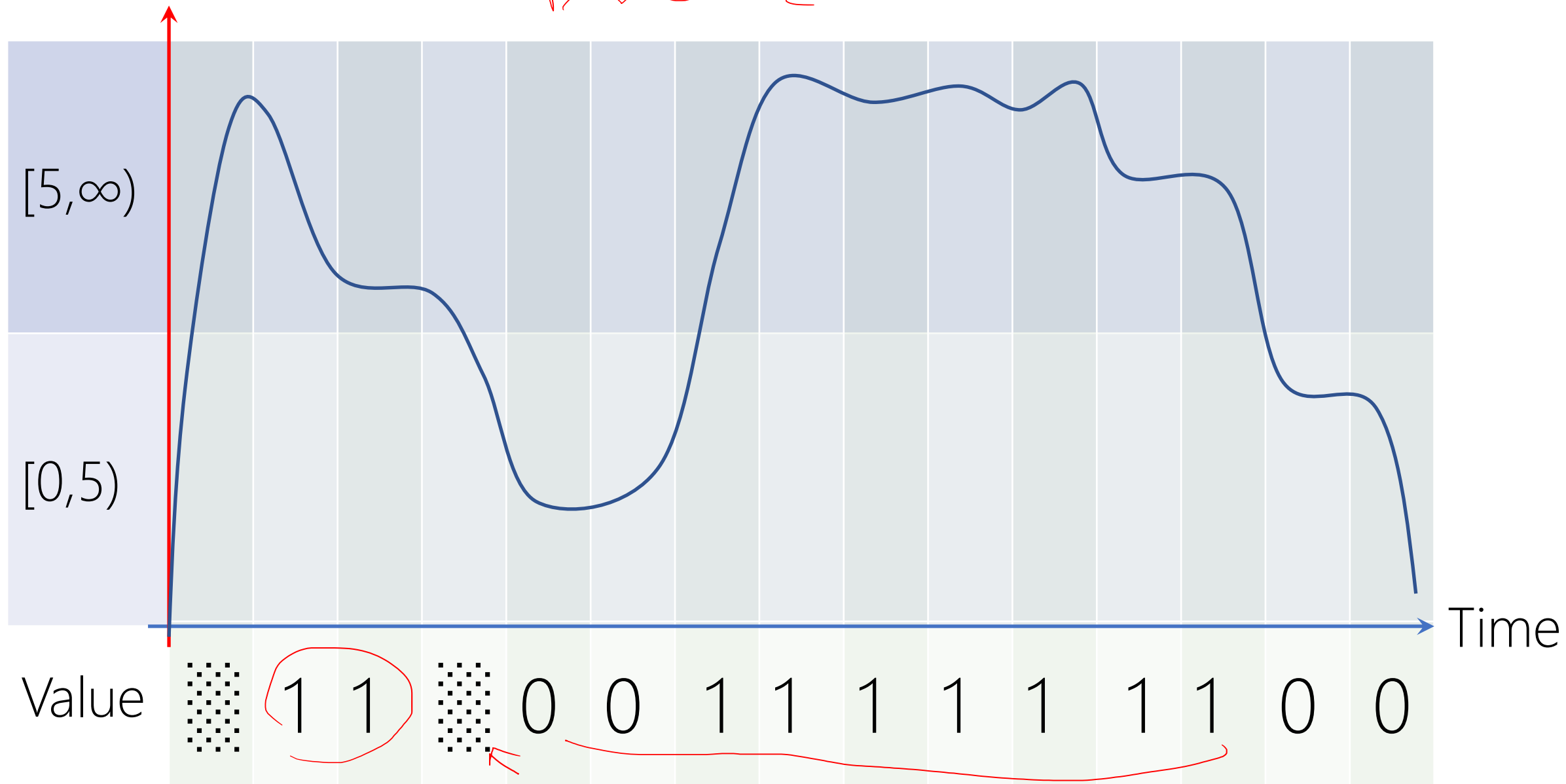

RELIABILITY

Robust to Noise

Fundamentally Hardware/Engineering Problem

TERNARY COMPUTER

https://en.wikipedia.org/wiki/Ternary_computer

Balanced Trinary $\{-1, 0, 1\}$

Entirely from Wood!

Thomas Fowler 1840

More History and Etymology → <https://en.wikipedia.org/wiki/Computer>


X X X X

DECIMAL COMPUTER

https://en.wikipedia.org/wiki/Decimal_computer

They are not actually base-10! We'll cover them later.

TRUE VS. FALSE

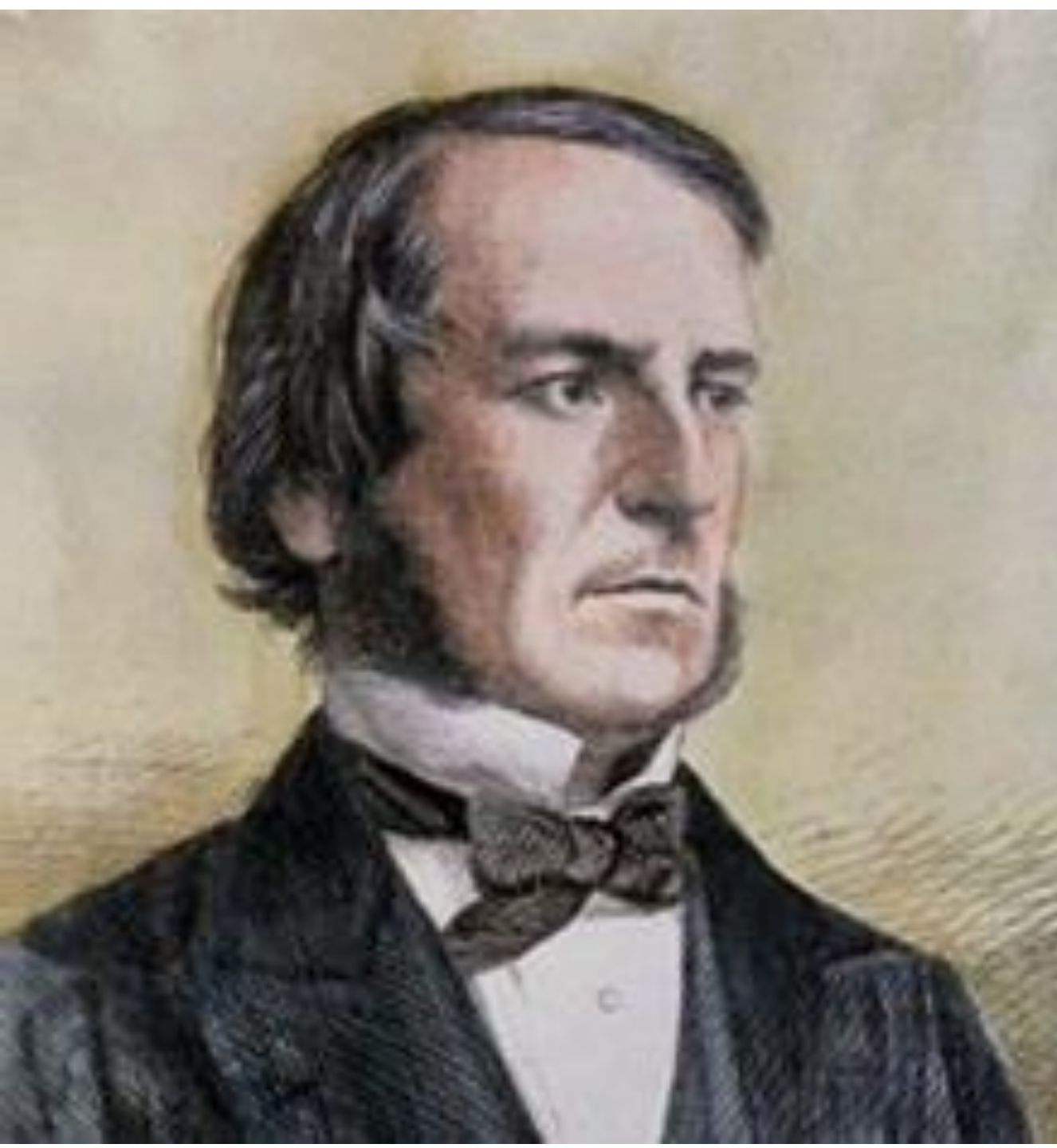

George Boole (/bu:l/)

Mathematician

Philosopher

Logician

The Laws of Thought (1854)

Boolean Algebra!

Claude Elwood Shannon

Mathematician
Electrical Engineer
Cryptographer

M.Sc. Thesis (1937)

A Symbolic Analysis of Relay and Switching Circuits
21 years old!

Switching Algebra!



BINARY COMPUTER


Base-2
More Reliability in Engineering
Deep Logic Foundation







Monolith ↑


2001: A Space Odyssey (1968), Stanley Kubrick, Arthur C. Clarke

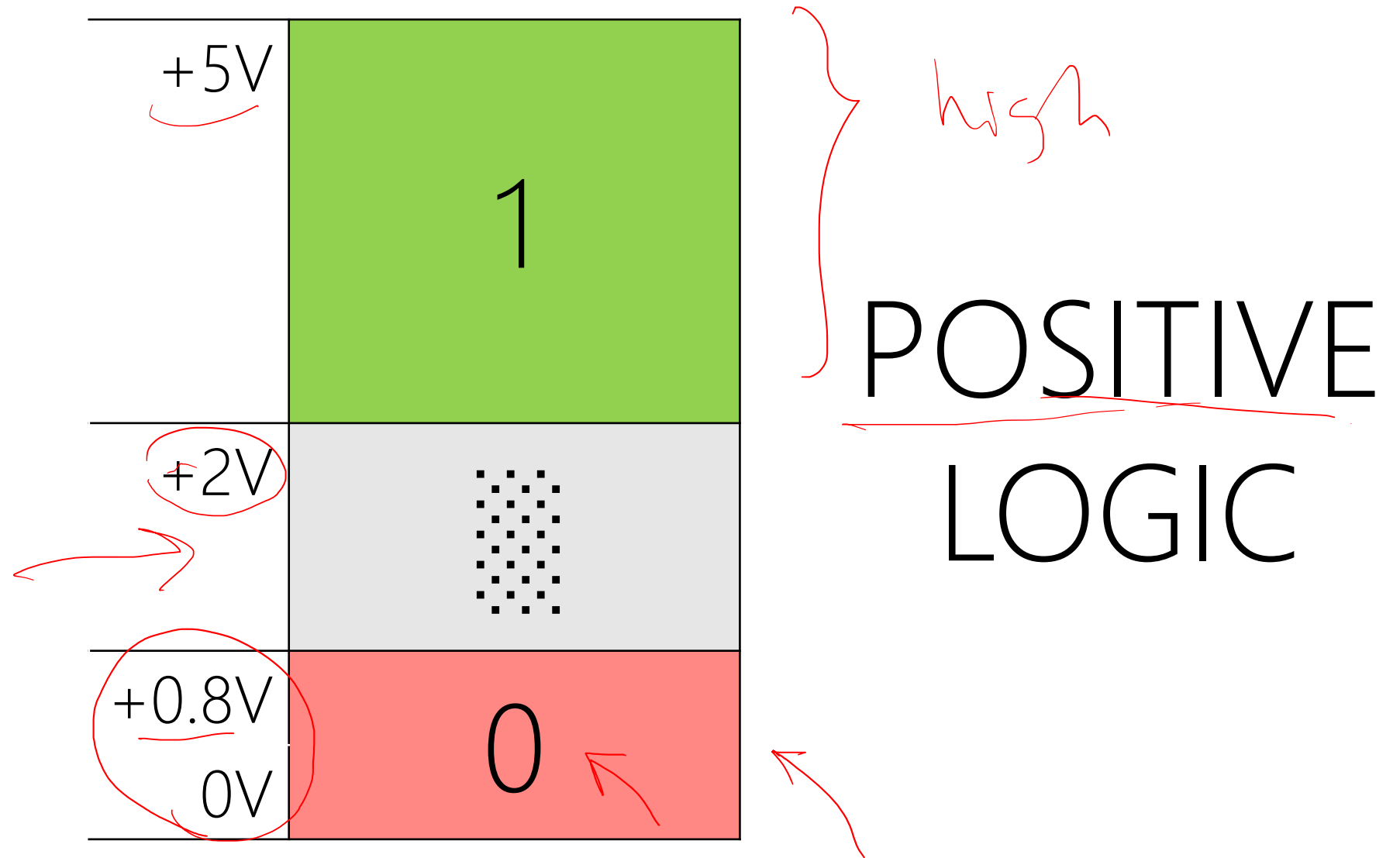{ Ape Learning Scene: https://www.youtube.com/watch?v=VABNA_an2A0
Bone/Satellite Match Cut: <https://www.youtube.com/watch?v=avjdKTqiVvQ>



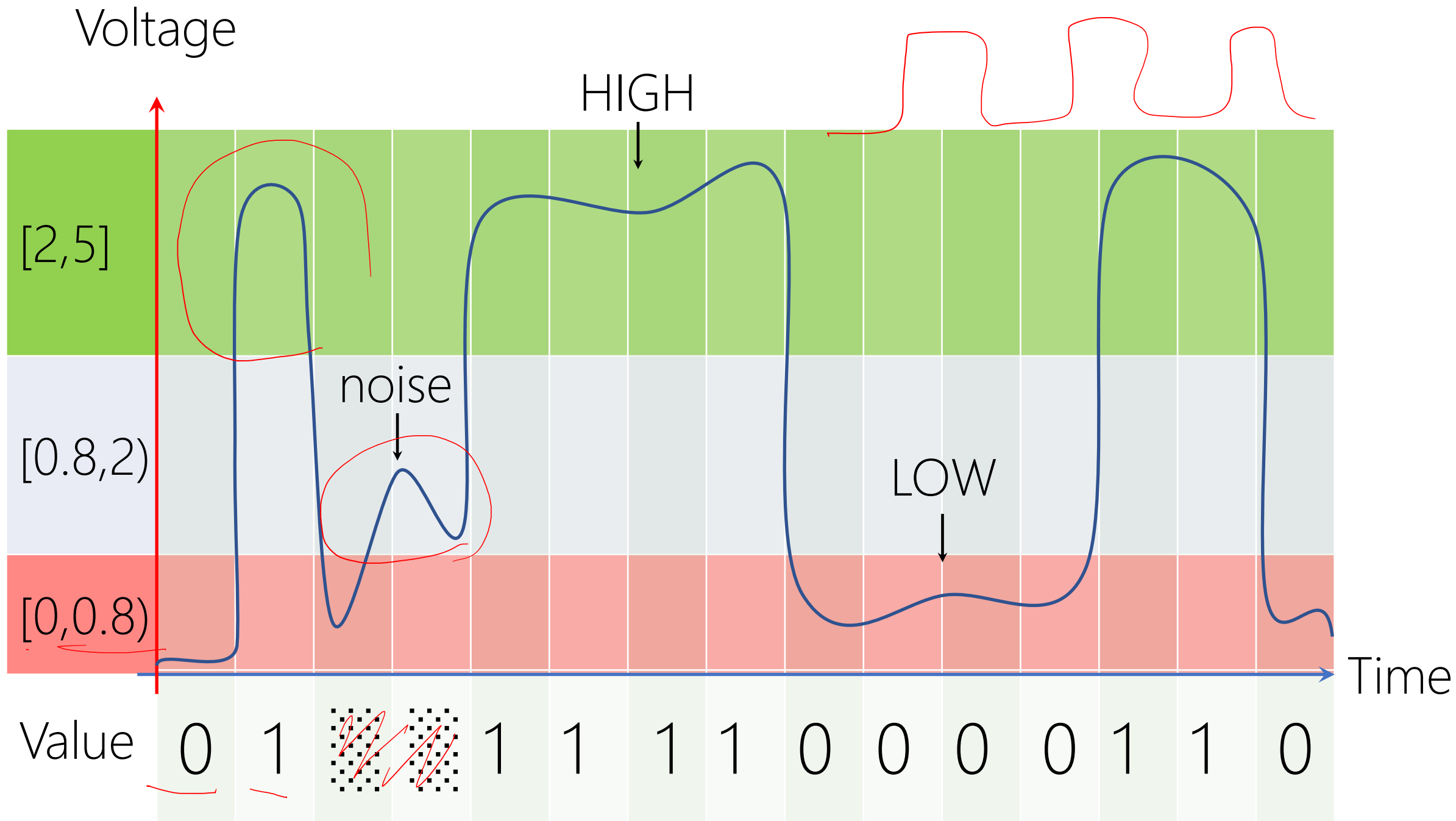

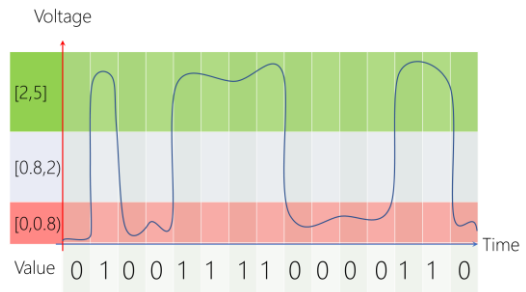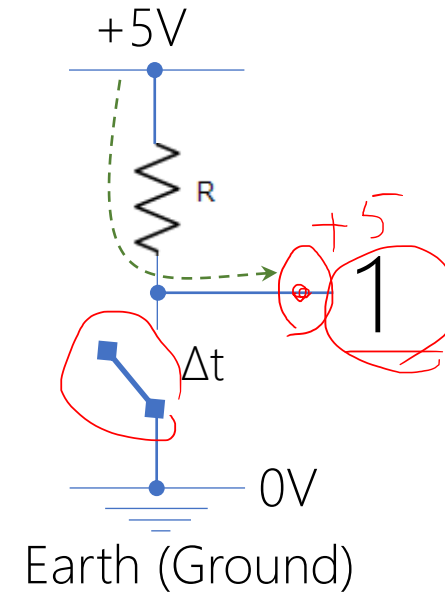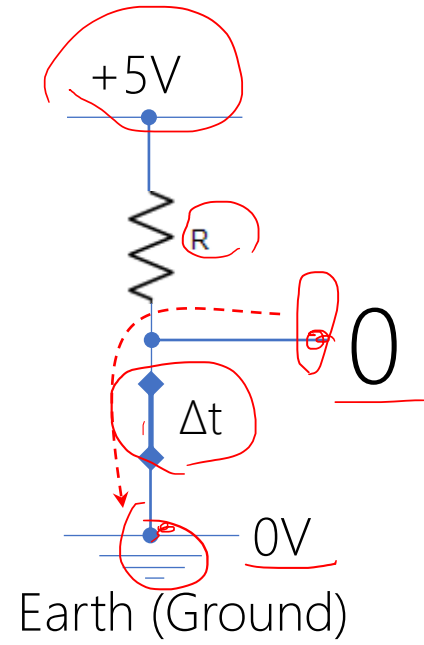

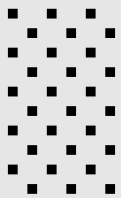+5V	0
+2V	
+0.8V 0V	1

NEGATIVE LOGIC

Voltage

HIGH

 $[2, 5]$

noise

LOW

 $[0, 0.8)$

Time

Value

1

0

0

0

0

0

1

1




1

1

0

0

1

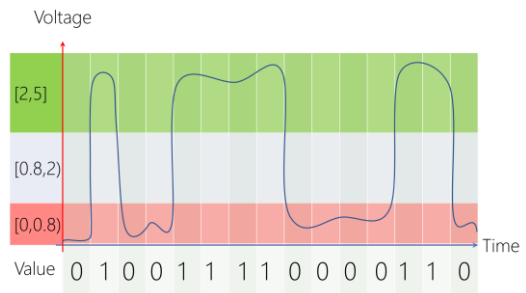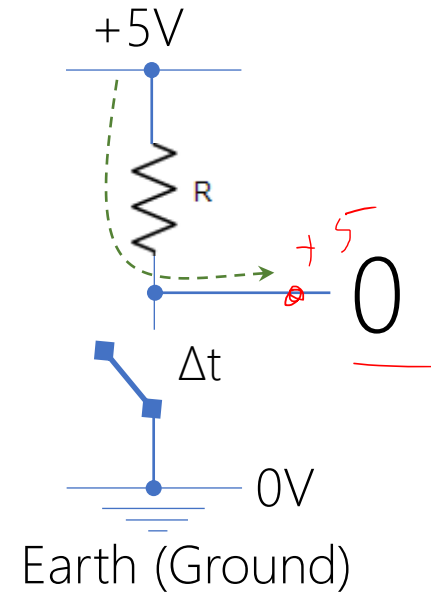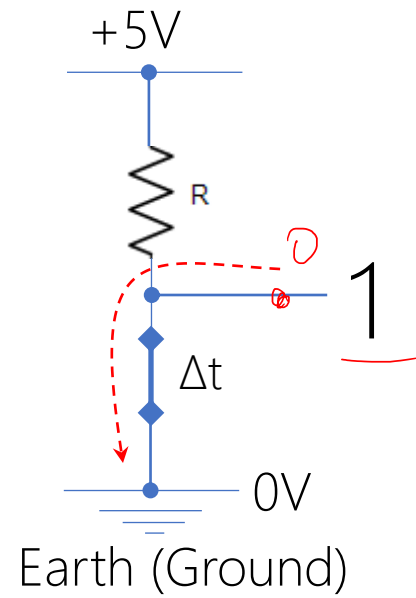

DESIGN COMPUTER

Positive Logic
Button-Up Approach

DESIGN COMPUTER

Positive Logic
Button-Up Approach

Finding simpler, but equivalent, computers reduces the overall cost!
Rely primarily on mathematical methods in Boolean algebra!


BUILD COMPUTER

Electrical and Computer Engineering




LOGIC GATES

BOOLEAN GATES

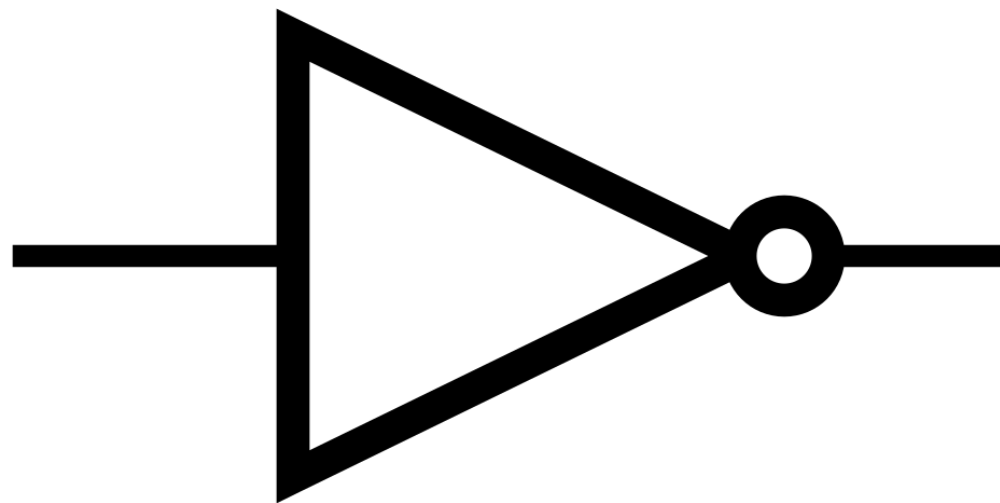


Truth Table

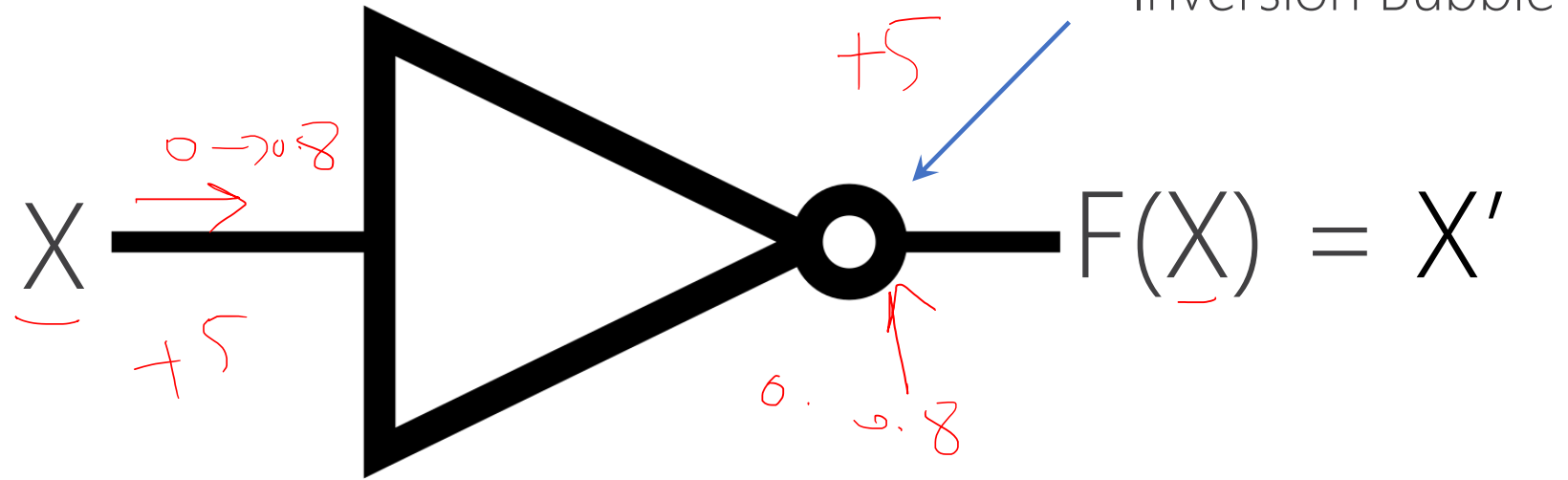


X	<u>NOT X</u>	<u>Invertor X</u>	X'	\bar{X}
0		1		
1		0		

Boolean Expression/Function: $F(X) = X'$

> *inverse of X gives F* <

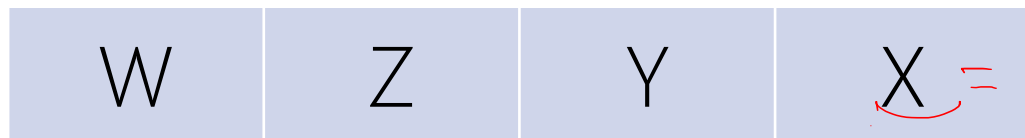

0, 1

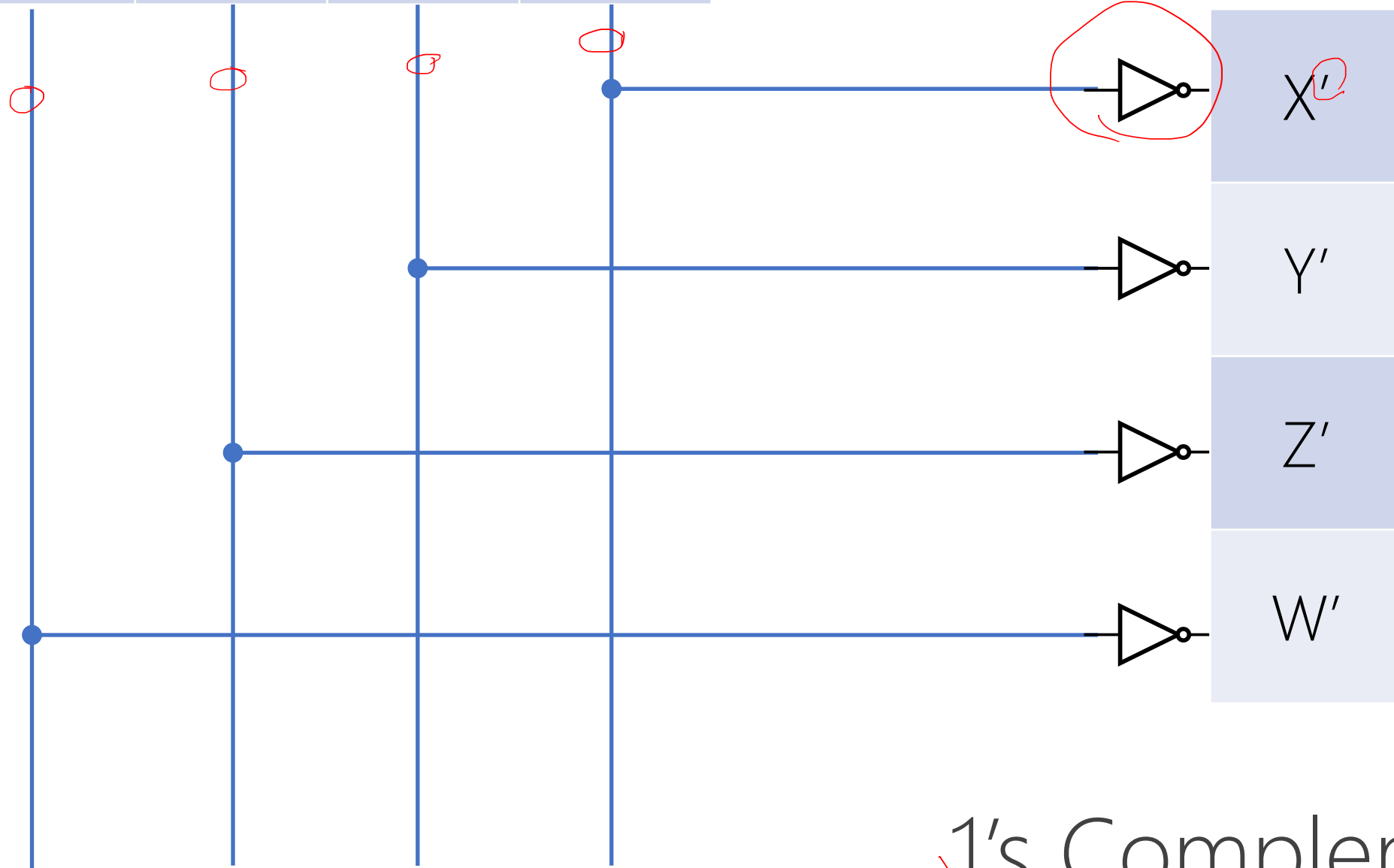

$$F_1 = X'$$

$$F_2 = Y'$$

$$F_3 = Z'$$

$$F_4 = W'$$

1's Complement

BINARY VARIABLE

aka. Boolean variable


A variable that can have a value in $\{0,1\}$

→ X, Y, Z, W, ...


BOOLEAN FUNCTION

aka. Boolean Expression

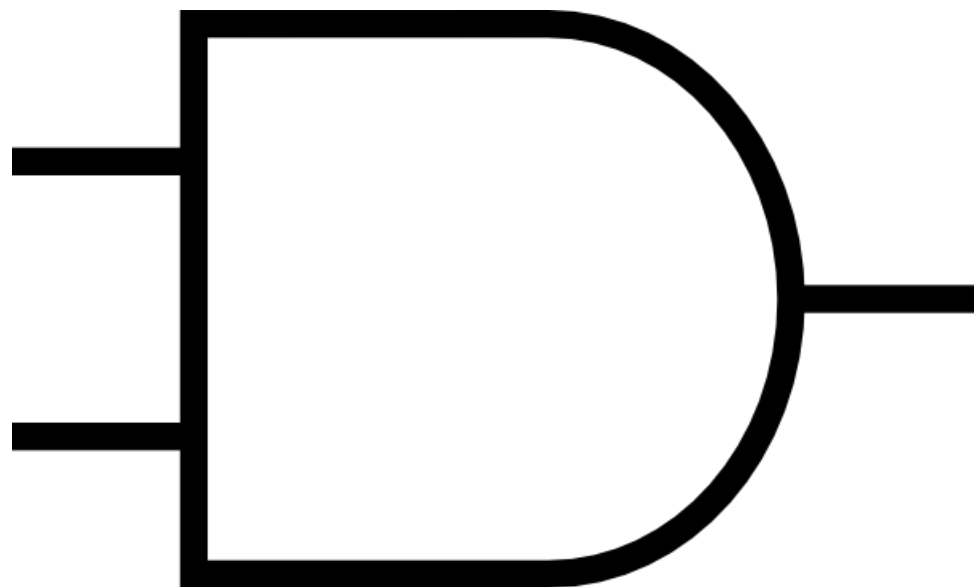
A function that accept Boolean variable(s) and output a value in $\{0,1\}$, e.g., $F(X) = X'$



Truth Table

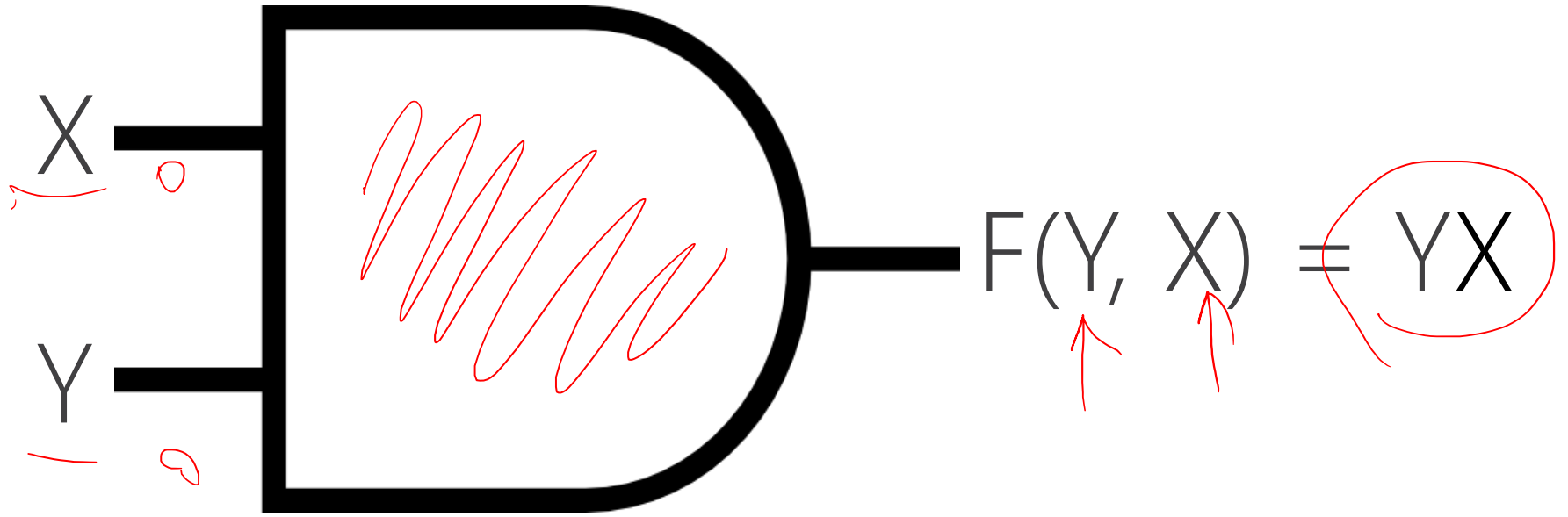

Y	X	X AND Y	$Y \cdot X$	$Y * X$
<u>0</u>	<u>0</u>		<u>0</u>	
0	1		0	
<u>1</u>	0		0	
1	1		1	

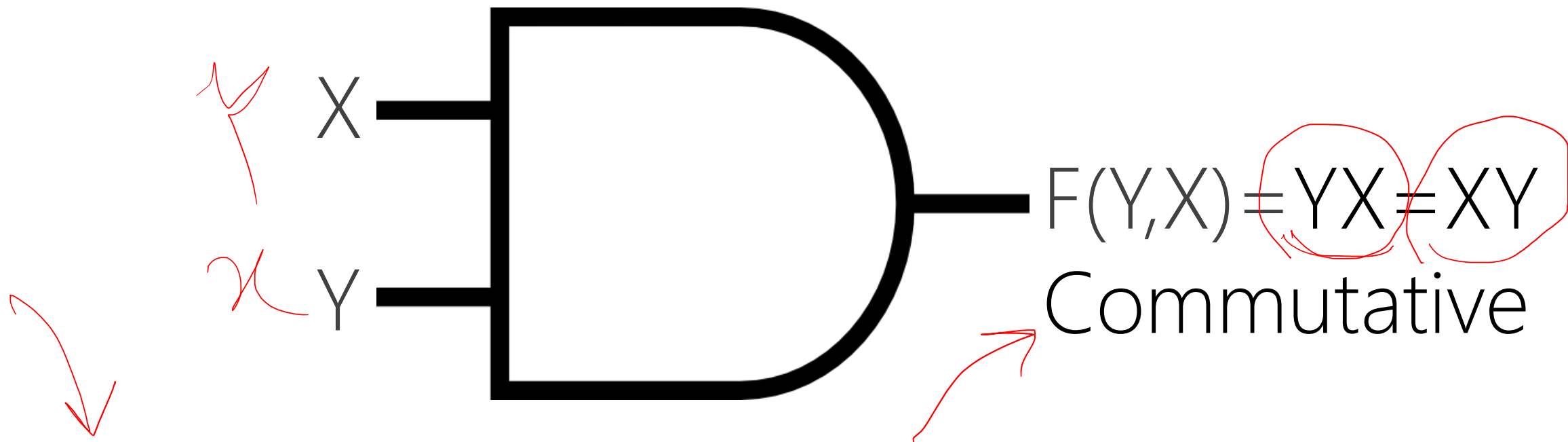


X	Y	Y AND X	$X \cdot Y$	$X * Y$
0	0		0	
0	1		0	
1	0		0	
1	1		1	

BOOLEAN FUNCTION


Equality $F1 = F2$

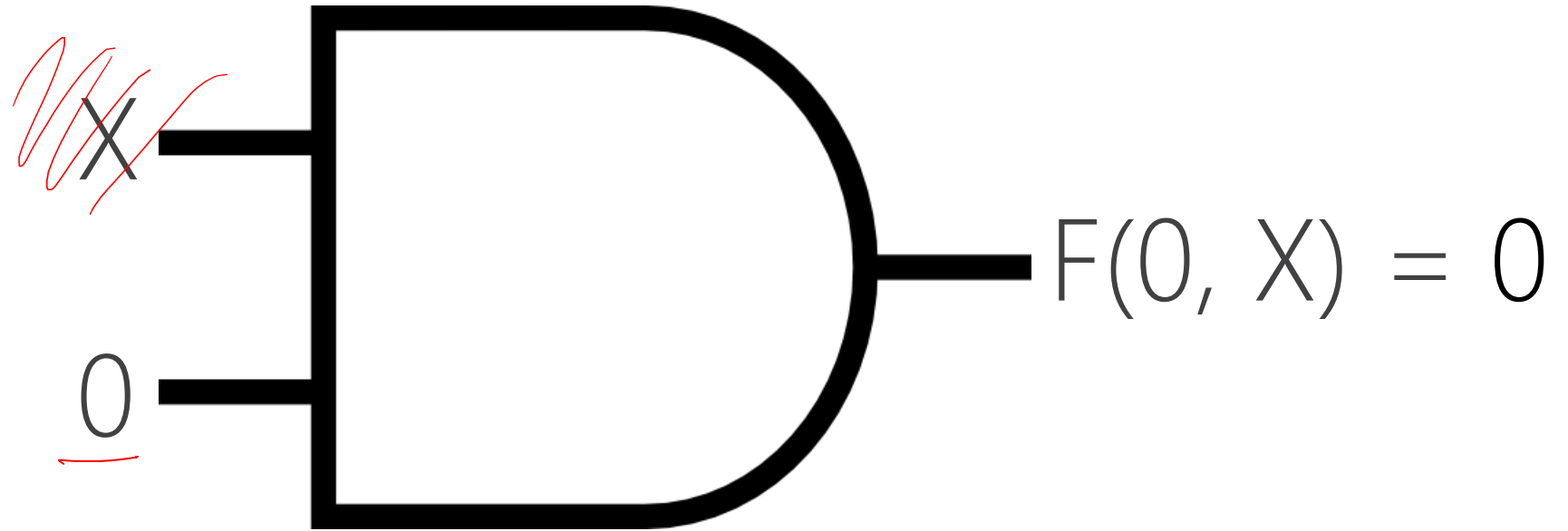For the same input(s), F1 and F2 result in same output




Y	X	YX
0	1	0
0	0	0
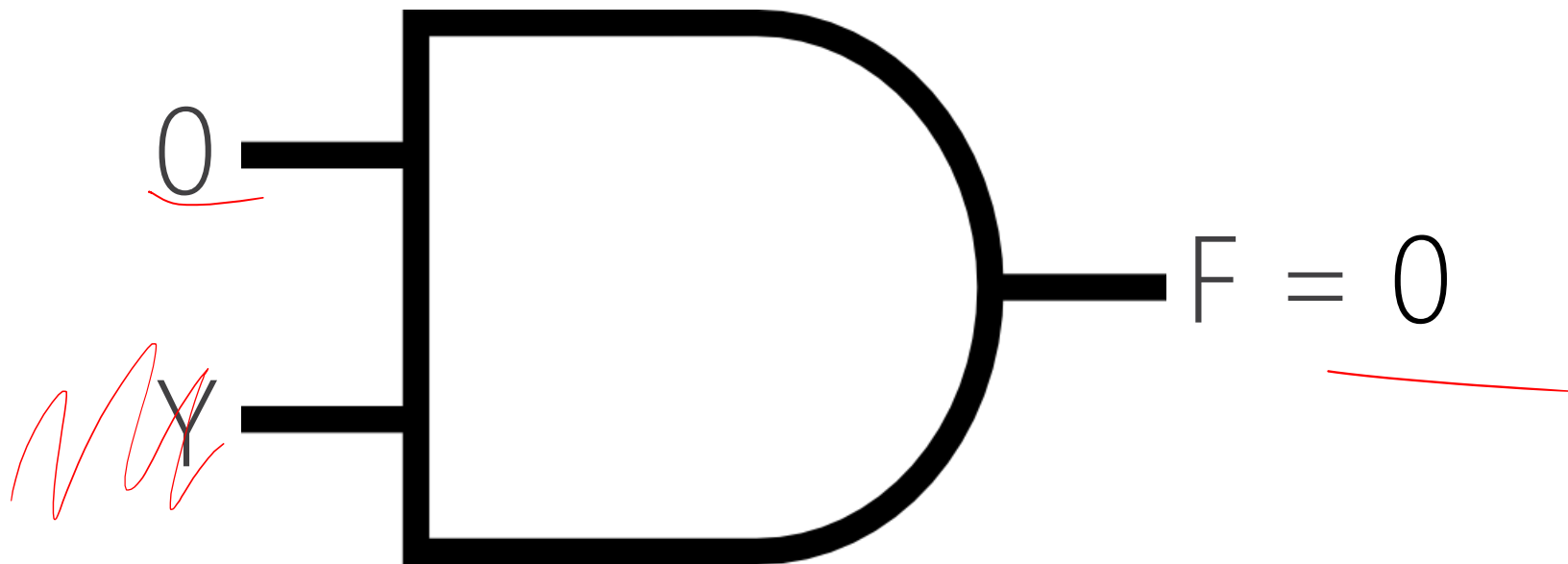
$$\leftarrow F(X, 0) = X0 = \underline{0}$$



Y	X	YX
0	0	0
1	0	0


$$F = 0Y = 0$$

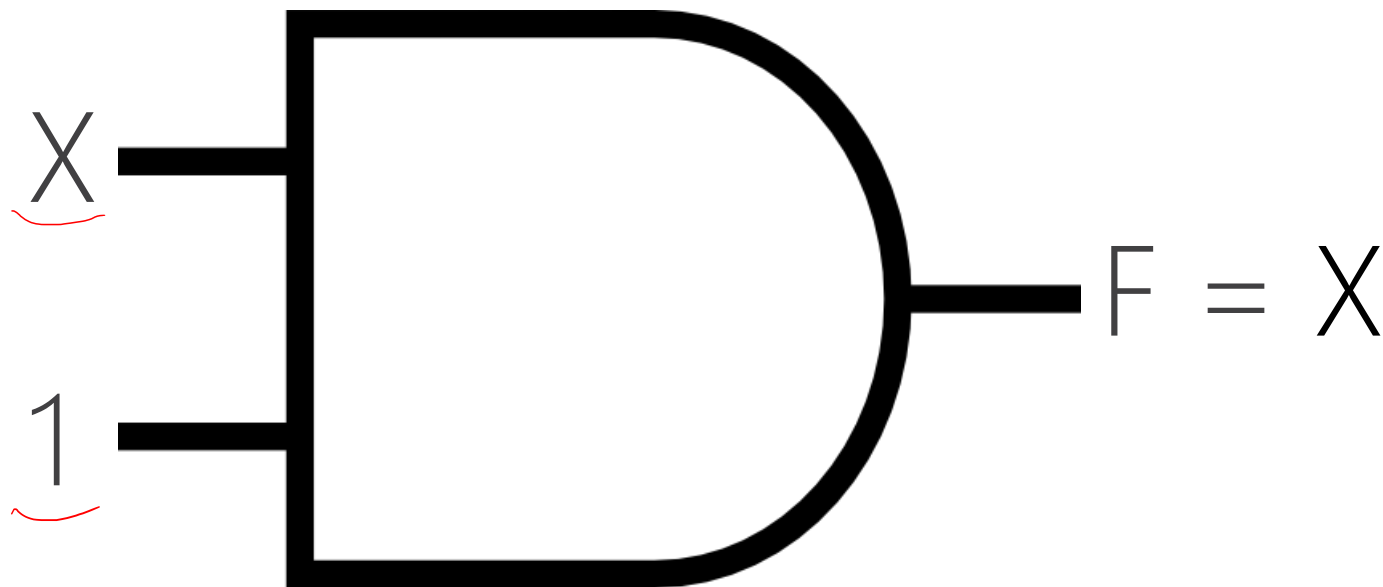


Y	X	YX
1	0	0
1	1	1

$$F = \underline{X}1 = 1111\underline{X}1111 = X$$

X	X	XX
0	0	0
1	1	1

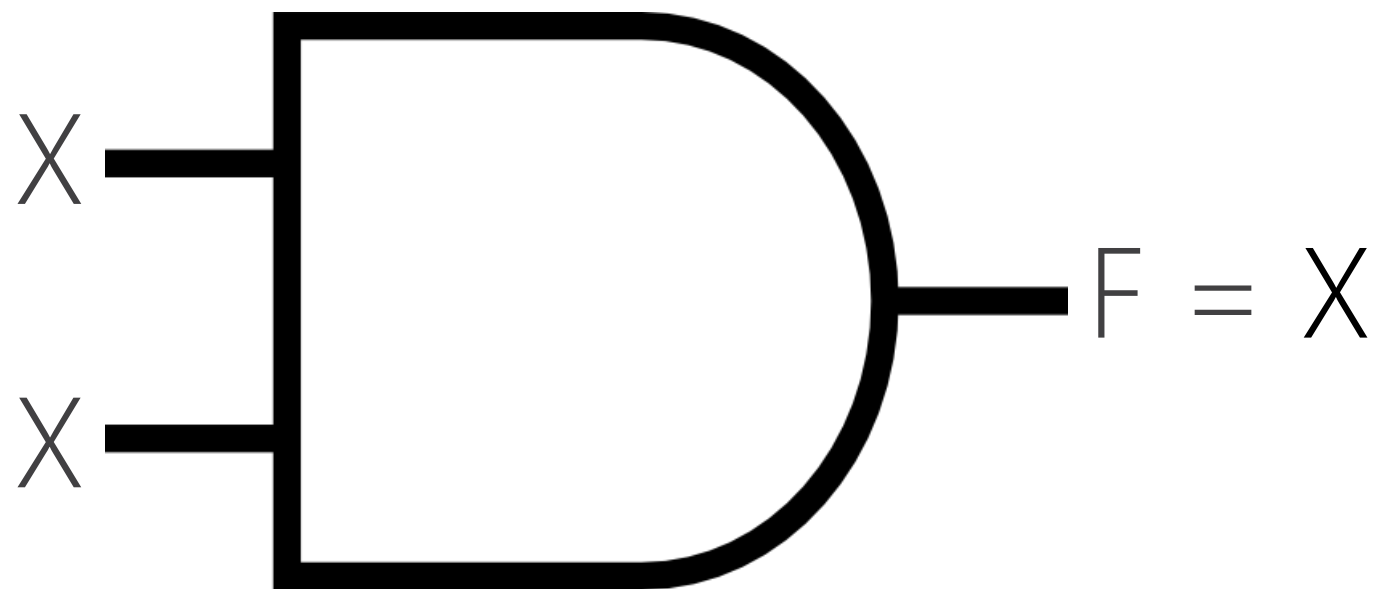


$$F = \underline{XX} = X$$

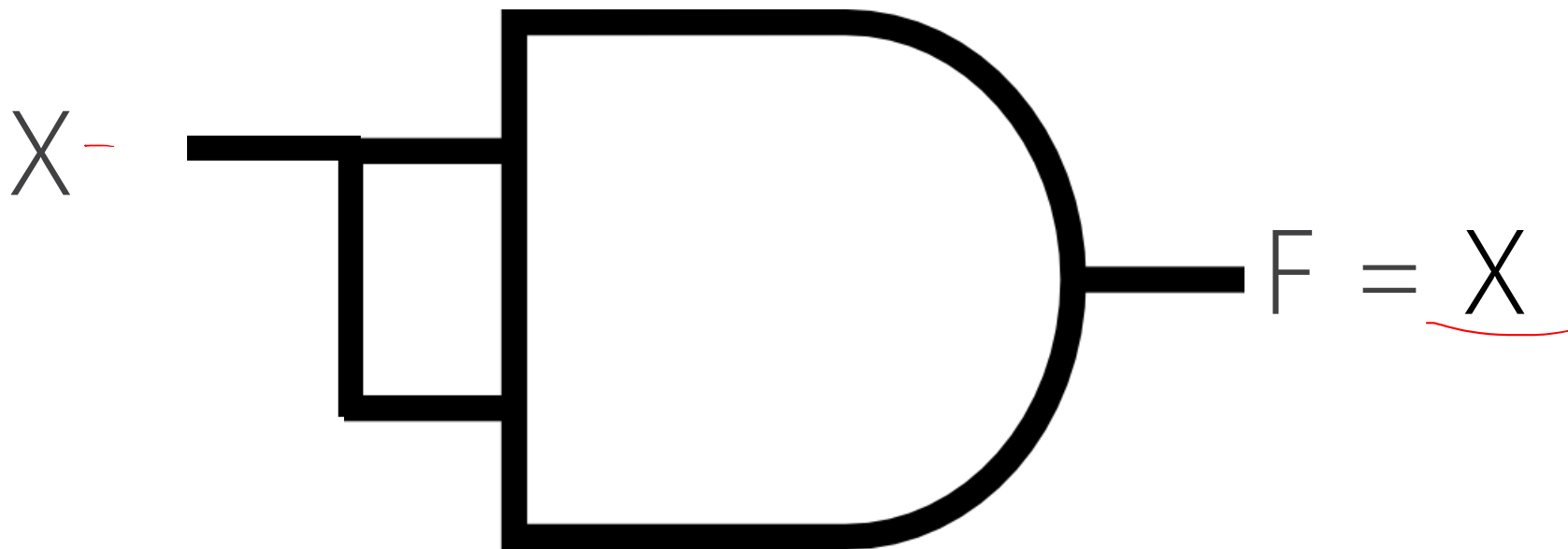


X	X	XX
0	0	0
1	1	1

$$F = XX = X$$

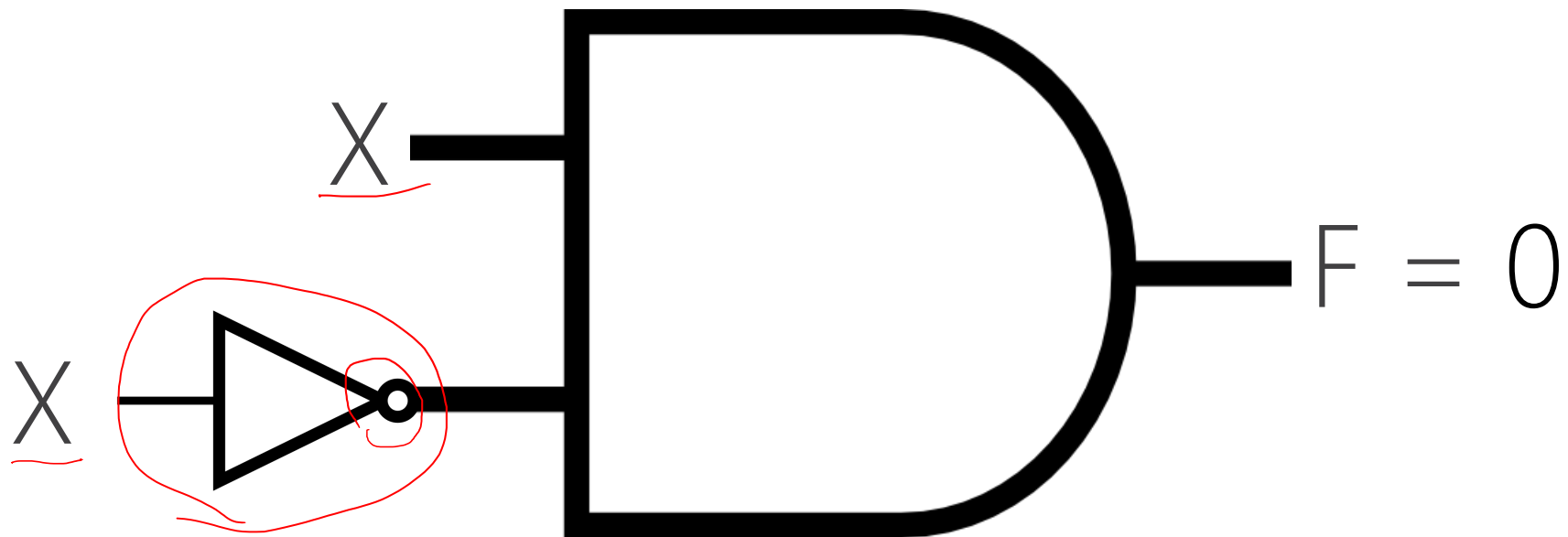


X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

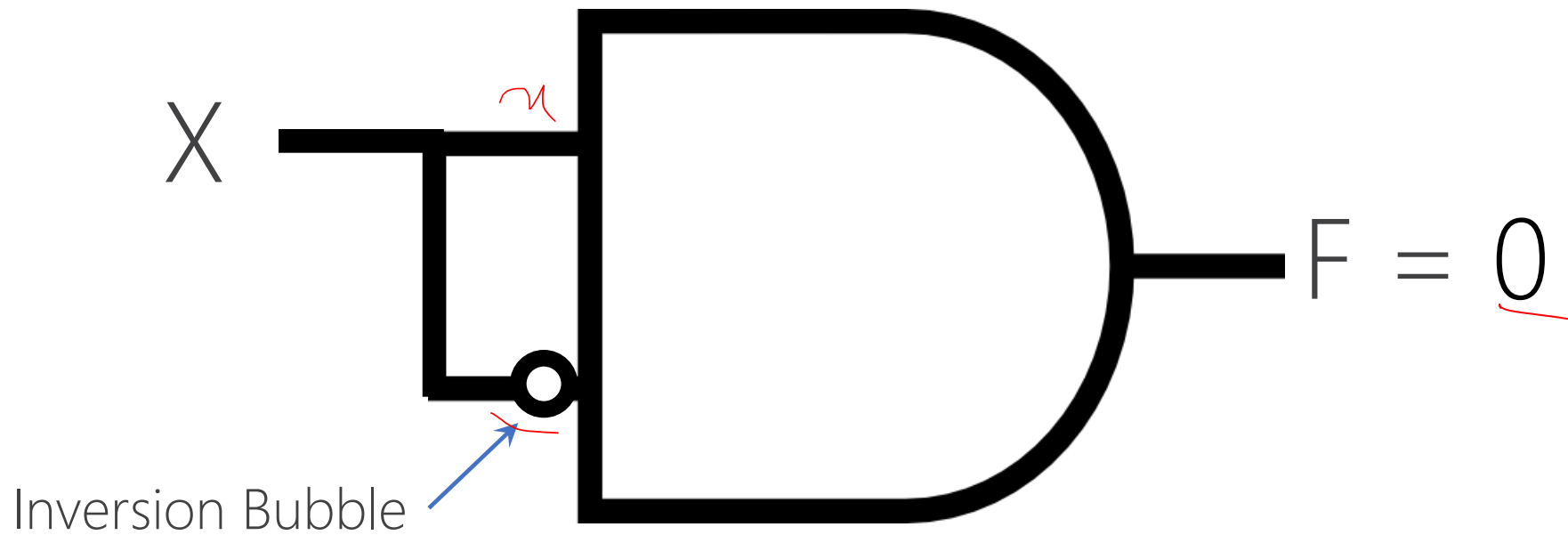

$$F = XX' = 0$$

X'	X	$X'X$
1	0	0
0	1	0

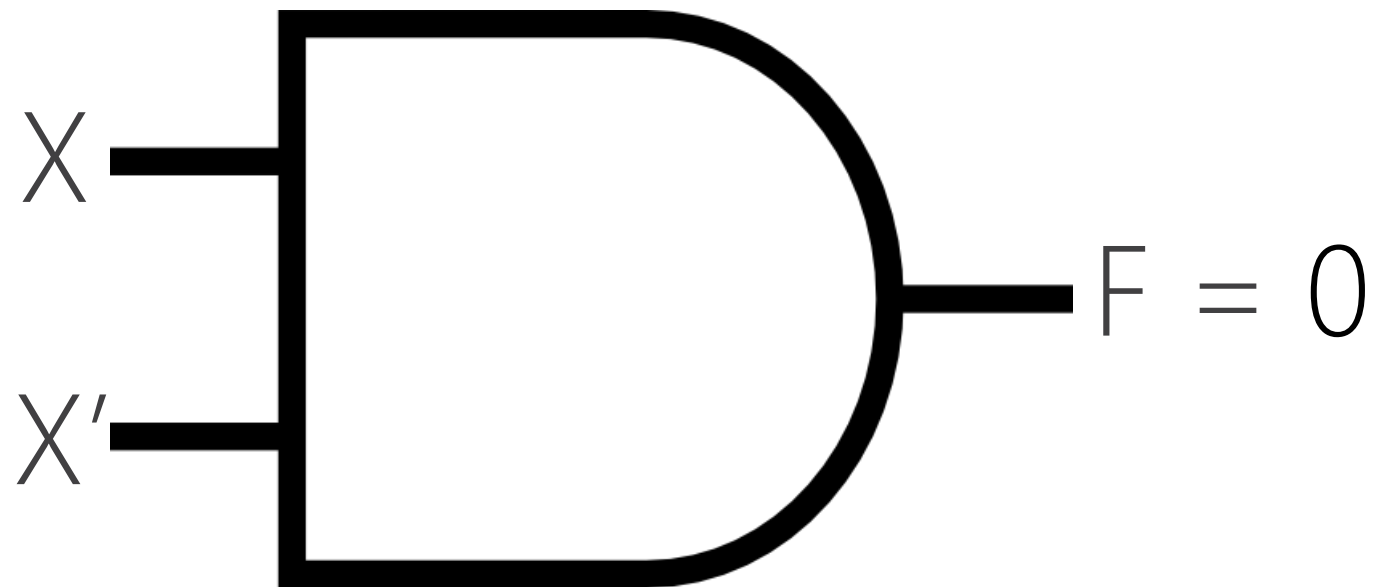

X'	X	$X'X$
1	0	0
0	1	0

$$F = XX' = 0$$

DESIGN

given the **functionality**, design the structure of a system


—Do—
—D—

3-INPUT AND


TRUTH TABLE

3-INPUT AND

Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

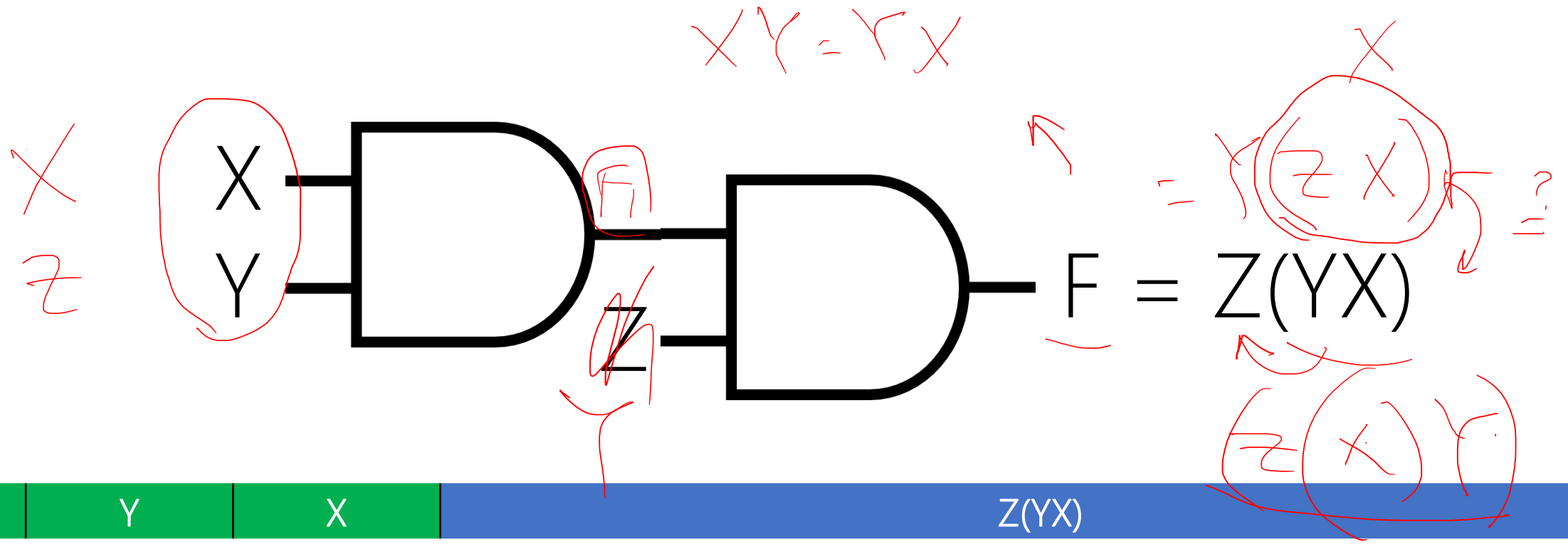


Z	Y	X	Z(YX)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

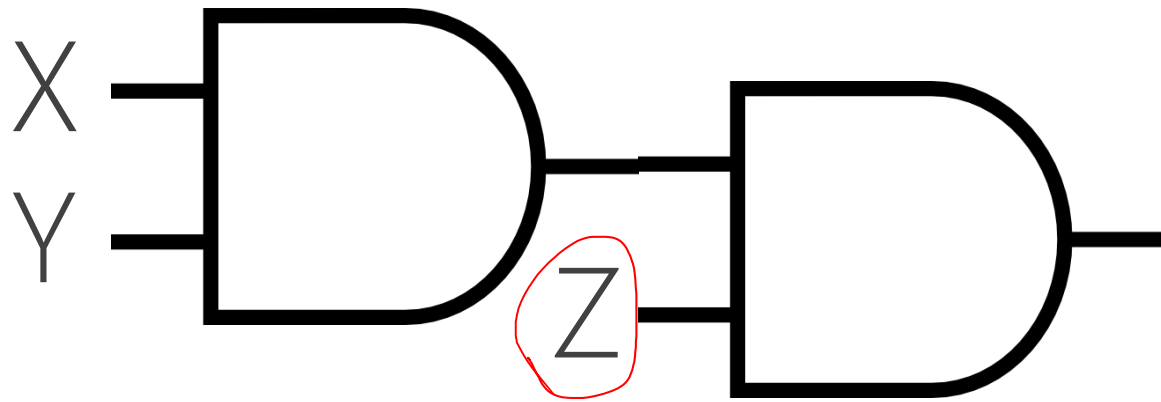

$$F = Z(YX) = Z(XY) = (ZX)Y = (XZ)Y = XZY$$

Associative

<u>Z</u>	<u>Y</u>	<u>X</u>	<u>Z(YX)</u>	<u>Z(XY)</u>	<u>(ZX)Y</u>	<u>XZY</u>
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	1	1	1	1

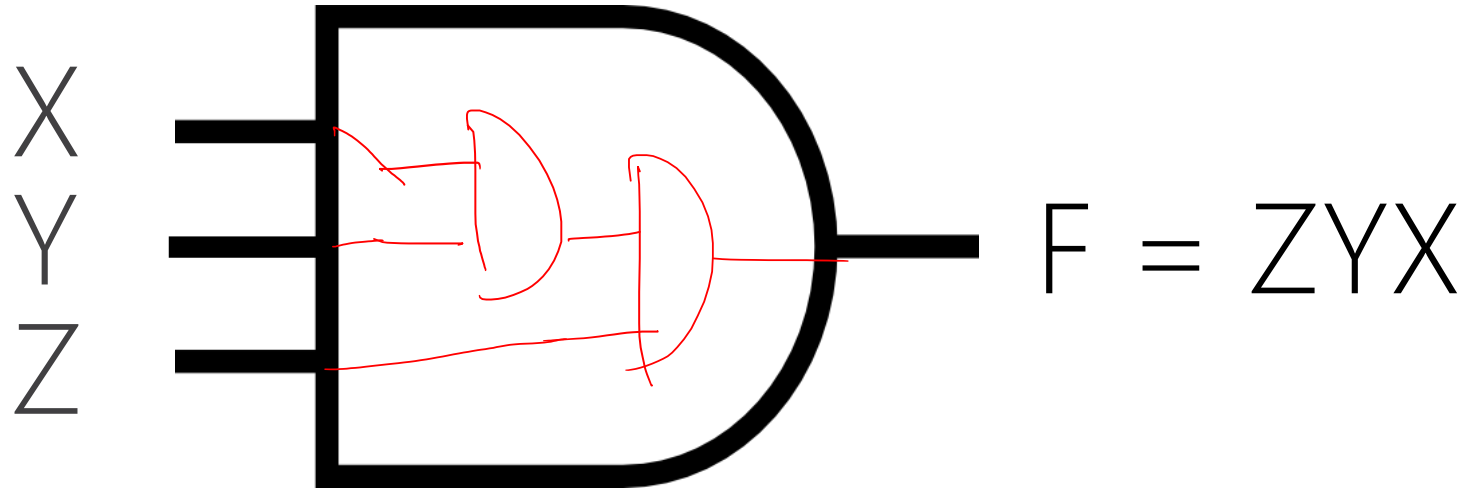

Z	Y	X	ZYX
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

DESIGN




given the **functionality**, design the structure of a system

4-INPUT AND

DESIGN PATTERNS

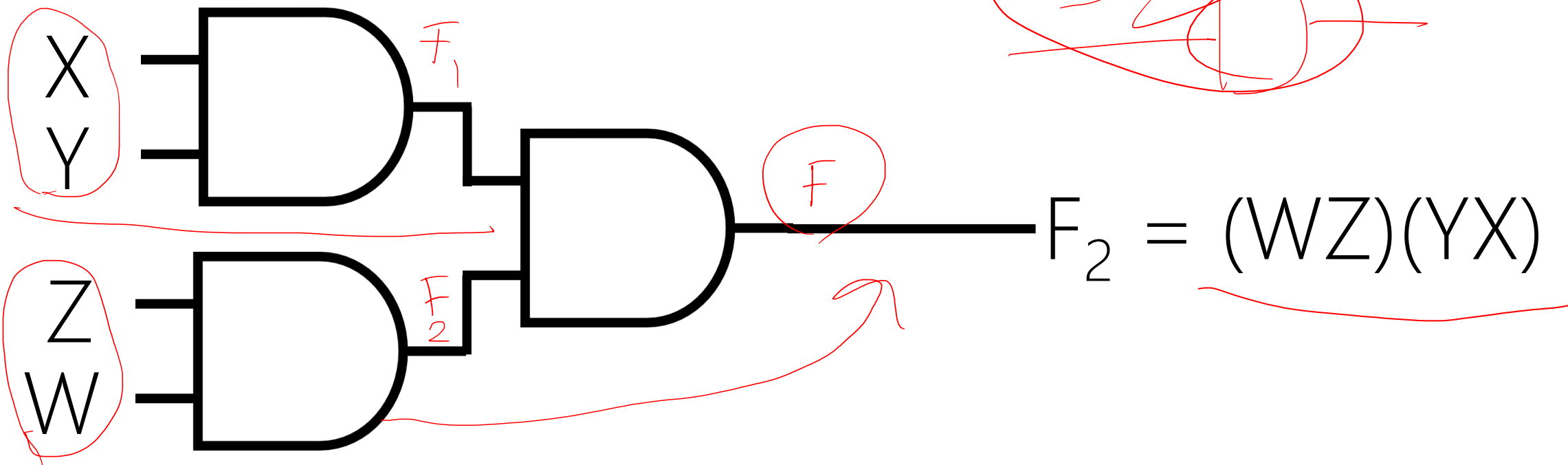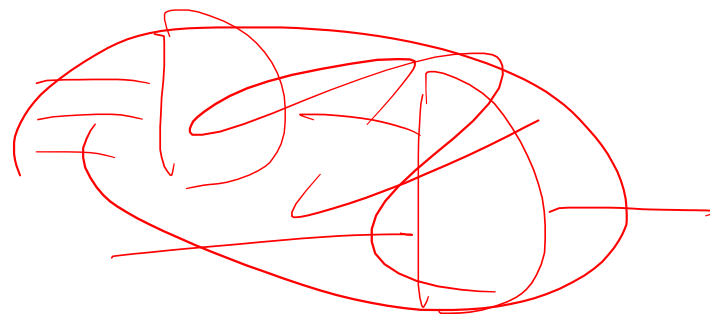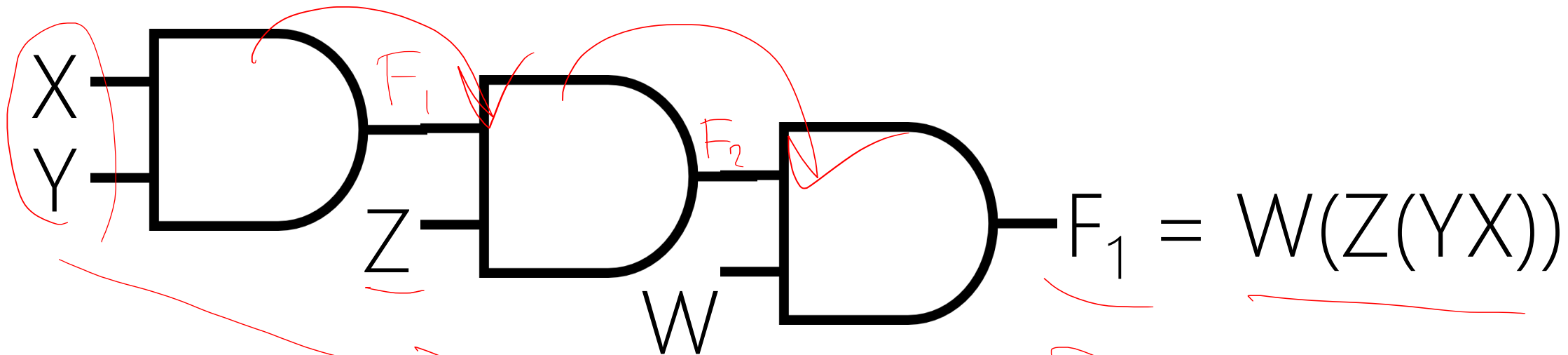Using Same or Similar Previous Designs for New Designs





ANALYSIS



given the structure of a system, find its functionality.

determine the functionality exhibited by a structure.



EVALUATION


Correct vs. Wrong

Nice vs. Poor

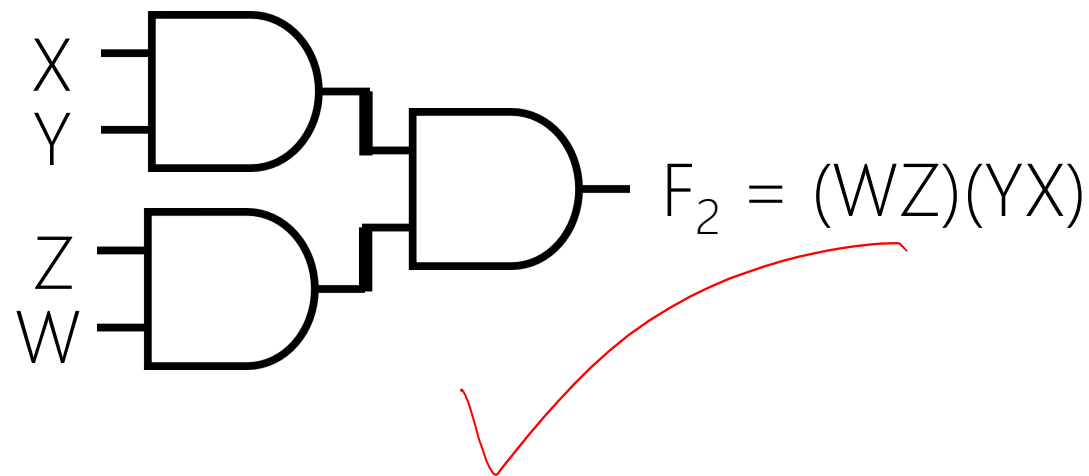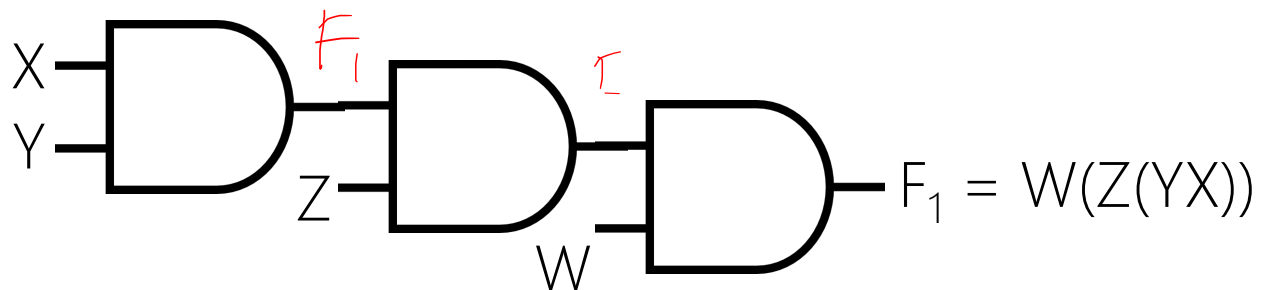

$F = WZYX$	F_1	F_2
Effective (True)	Yes	Yes
Efficient (Fast)	Hmm, 3 levels, No!	Yes! 2 levels
Min. Cost	3 gates, Yes	3 gates, Yes

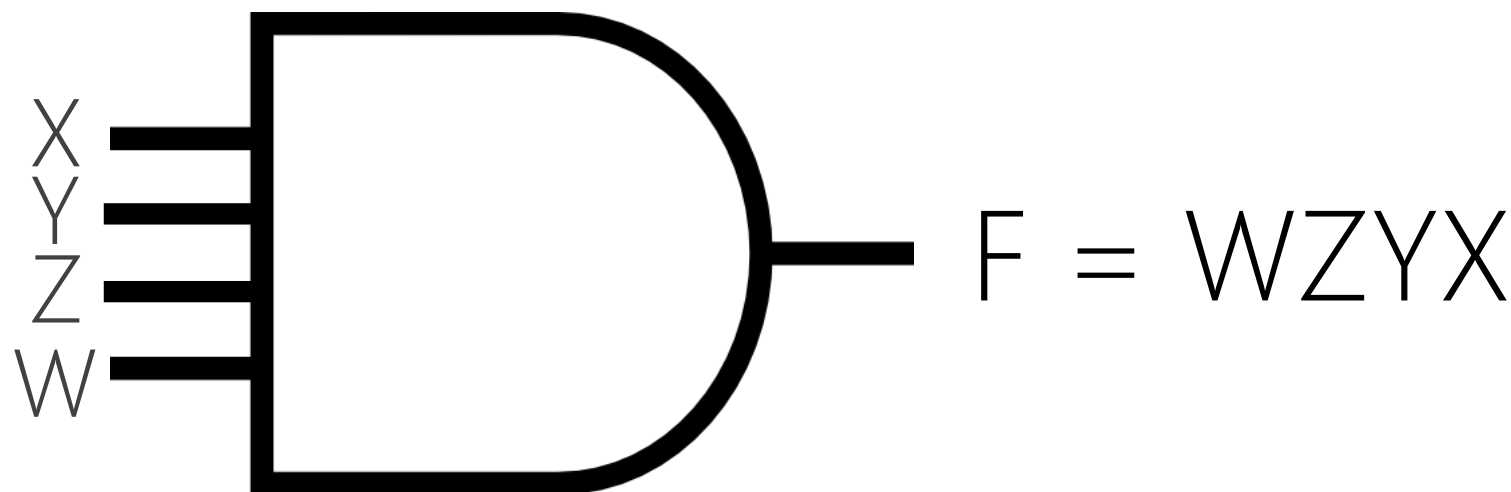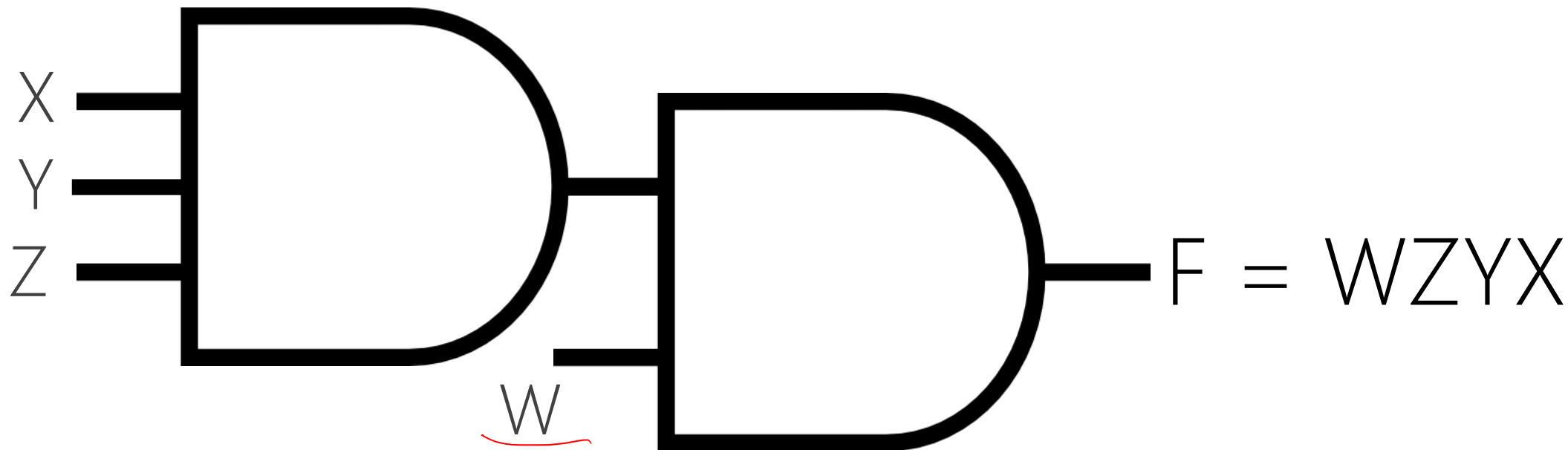

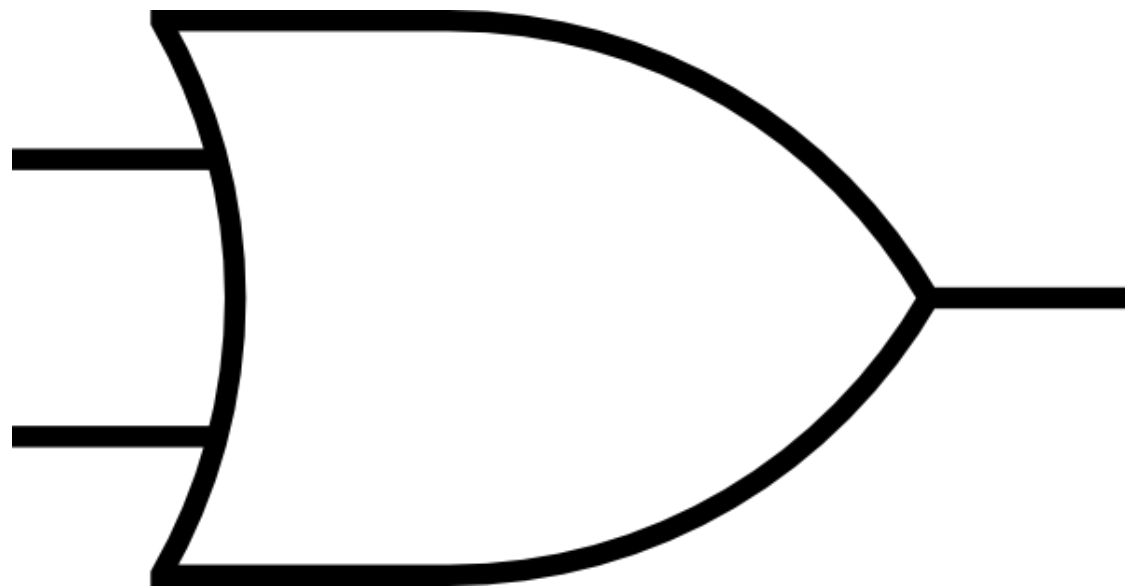

OR